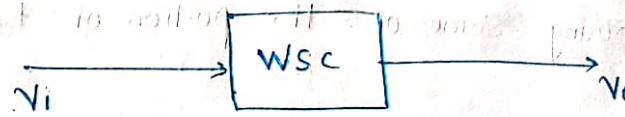


Diode Circuits

* Wave shaping Circuits

of basic waveforms obtained from simple supply
differentiation and integration process is called as wave shaping









- It is used for changing the shape of waveforms.

WSC


Linear WSC
based on linear element
 R, L, C
eg: RC HPF LPF

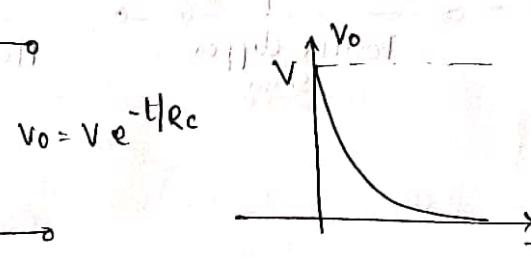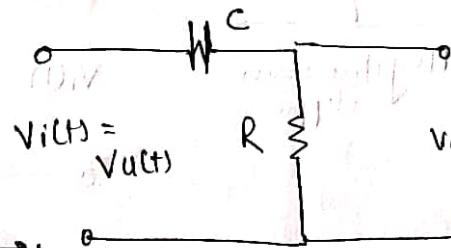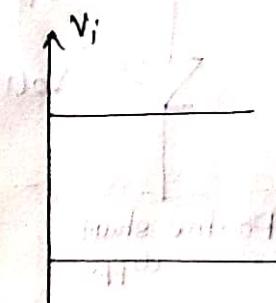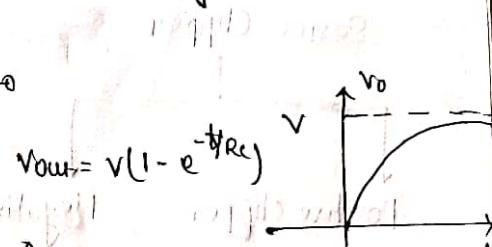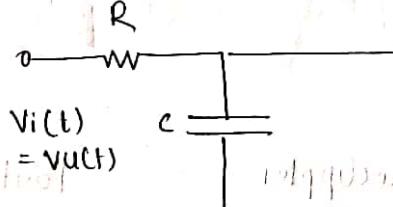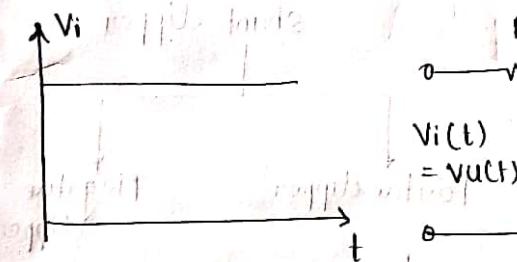Non-linear WSC
Based on Nonlinear element
like diode
eg Half wave Rectifier




* Clipper Circuits


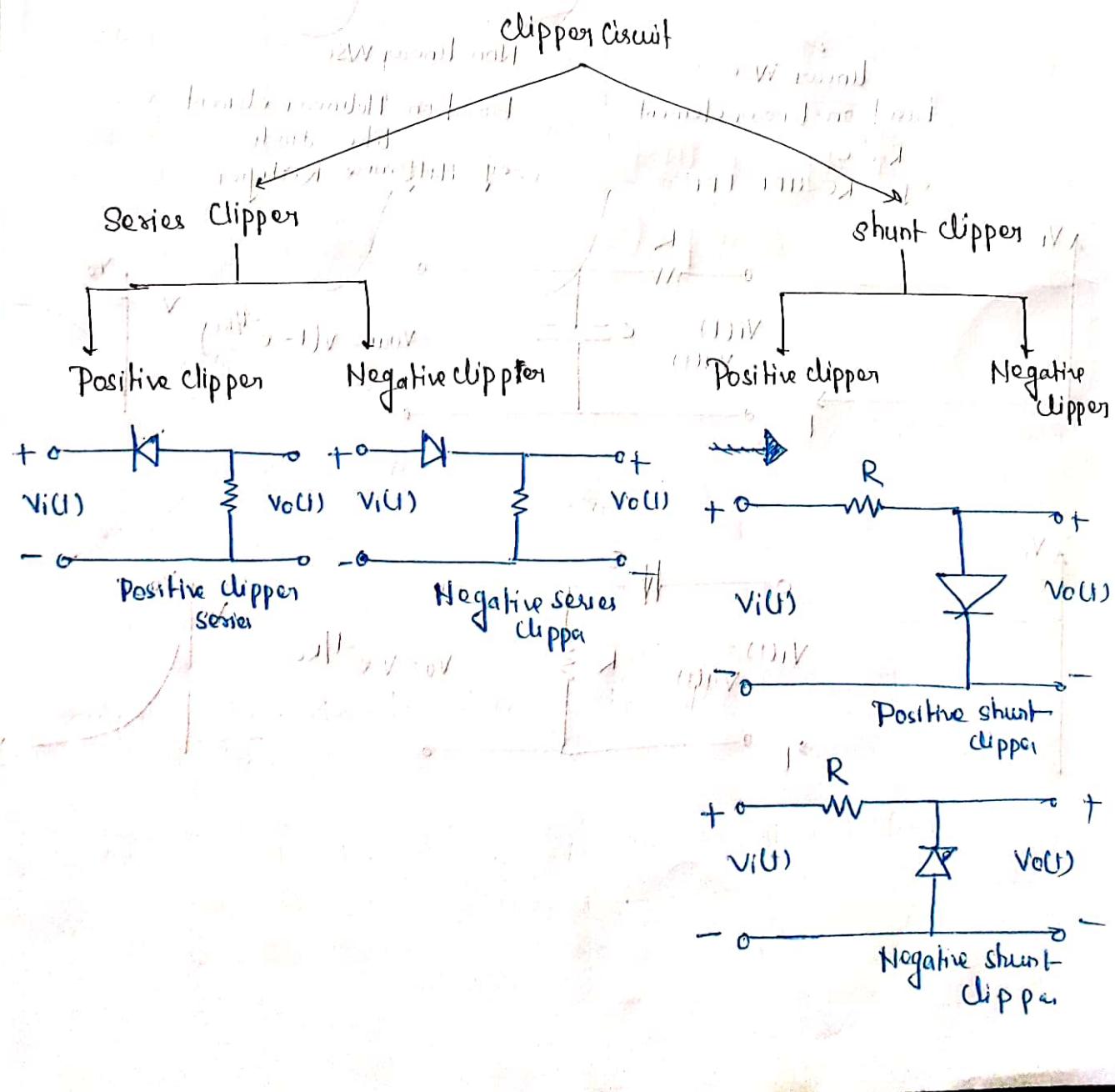
- Clipper Circuit is a non linear WSC which is used for clipping or removing some of the portion of transmitted waveform.
- The Main Circuit element is diode
- Clipper circuit is also referred as amplitude limiter or amplitude selector circuit.
- Classification of clipper circuit



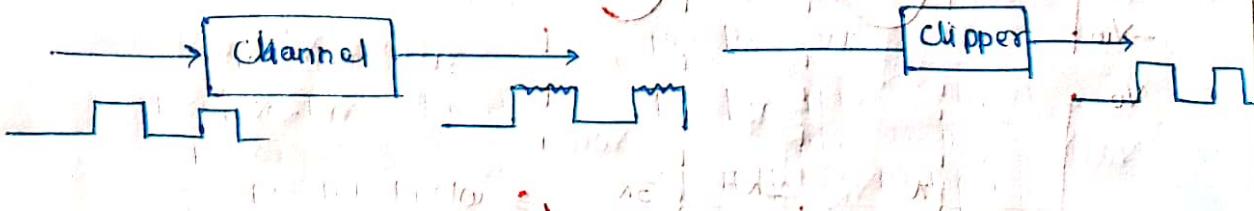
- In Series clipper Circuit diode is connected in series and in shunt clipper circuit diode is connected in parallel (structure wise)
- Positive clipper circuit removes maximum portion of x mitted wave form.
- Negative clipper circuit removes maximum portion of x mitted wave form.
- clipper circuit can be used for eliminating the effect of noise from waveform in digital communication.




* Positive Series Clipper Circuit

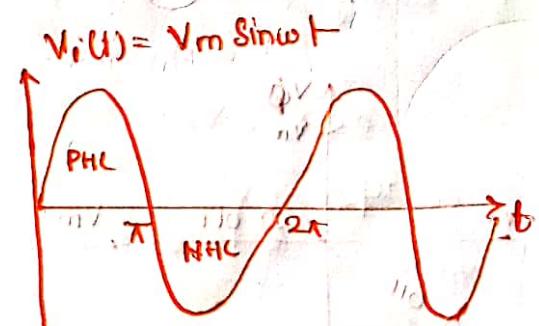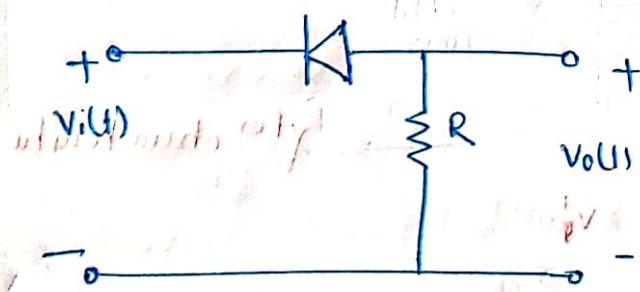

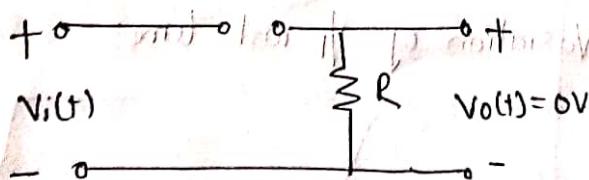- During positive half cycle (PHC) ($0 < \omega t < \pi$)
Diode = Reverse Bias (RB)




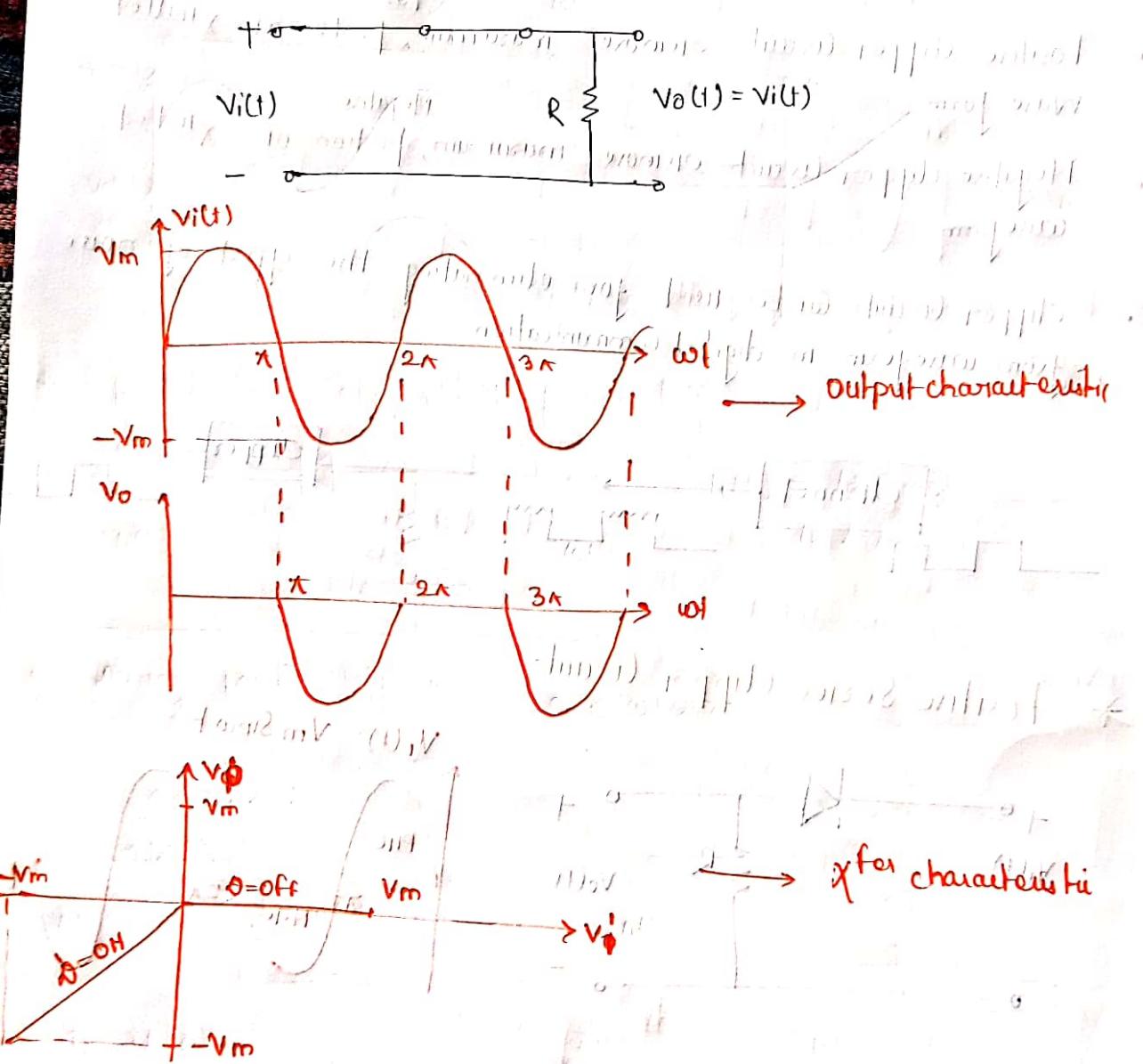- During Negative Half cycle Diode = forward biased (FB) $\pi < \omega t < 2\pi$




- output characteristic describe the variation of o/p wrt time
- x for characteristic describe variation of i/p wrt time

* Negative Series clipper

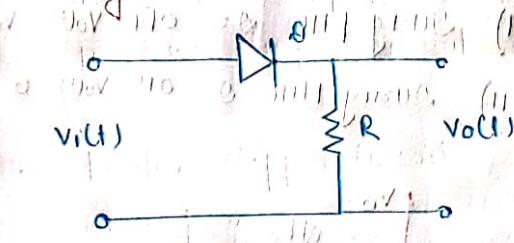


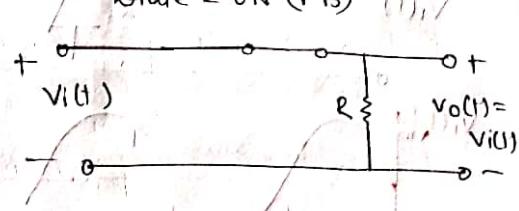i) During positive half cycle $0 < \omega t < \pi$
State = ON (FB)




ii) During Negative half cycle $\pi < \omega t < 2\pi$

D = OFF

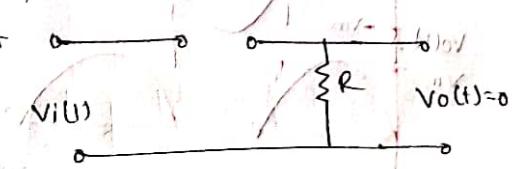


$V_{i(t)}$

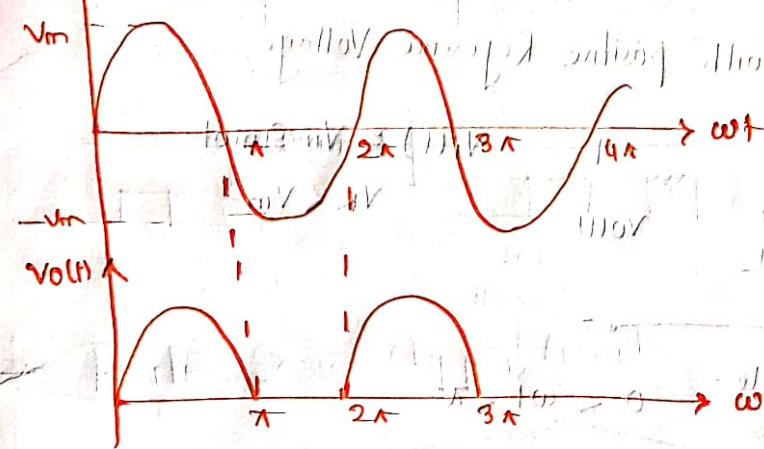

Output charac.

* Positive shunt clipper circuit

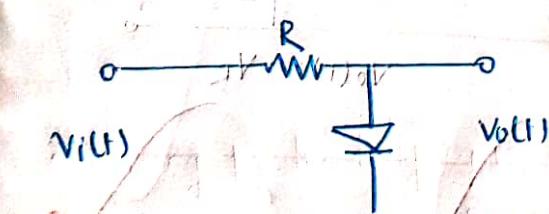

i) PHC


D → ON

$$V_o(t) = \cancel{V_i(t)} 0$$


ii) NHC

(D → off)

$$V_o(t) = V_i(t)$$

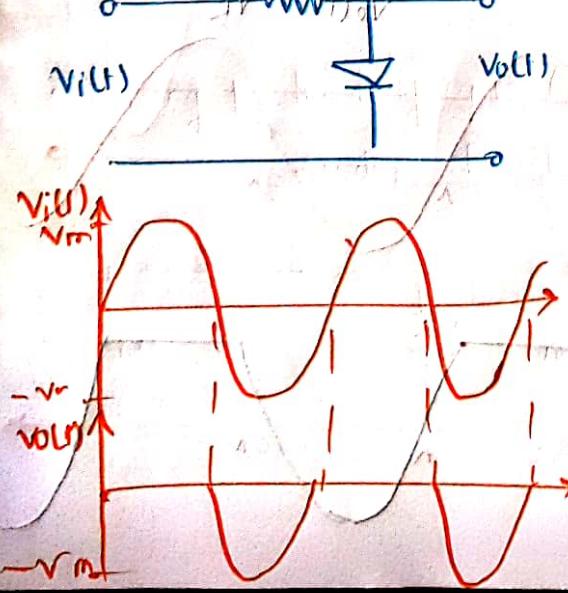


* Negative shunt clipper circuit

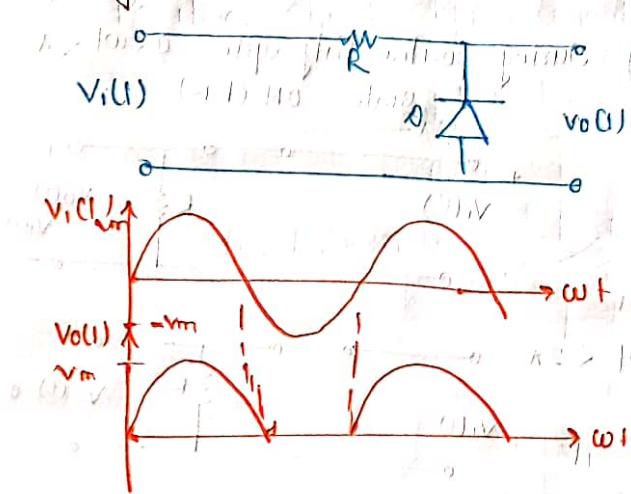


i) During PHC, $\theta = \text{OFF}$ $V_o(t) = V_i(t)$


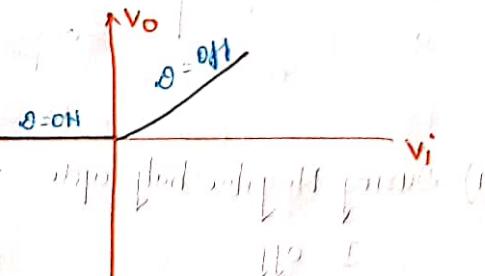
ii) During NHC, $\theta = \text{ON}$ $V_o(t) = 0$



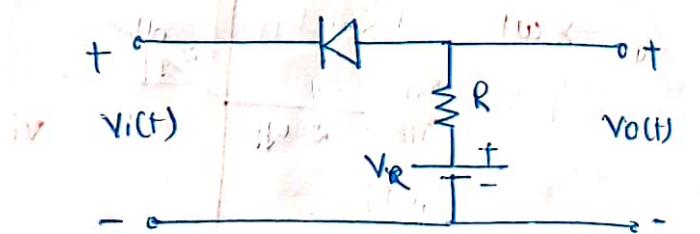* Positive Series clipper with positive Reference Voltage




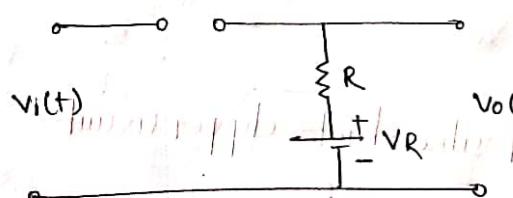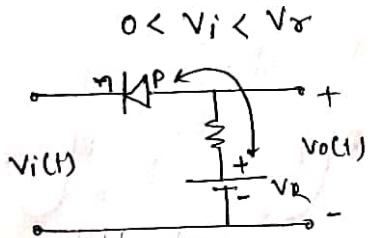i) During positive Half cycle $0 < \omega t < \pi$



$$I_D = f(V_R)$$


$$\theta = \text{ON}$$

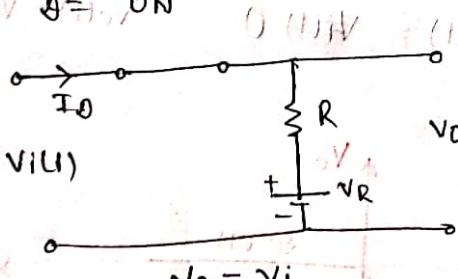

$$-Vi + 0 + I_\theta R + VR = 0$$


$$I_\theta = \frac{Vi - VR}{R}$$

$$V_o = I_\theta R + VR = Vi$$

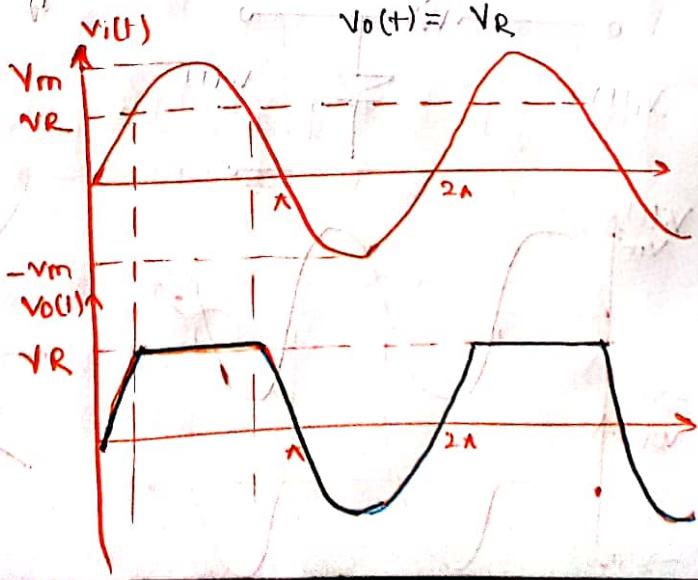

2) During Negative half Cycle :


$$\pi < \omega t < 2\pi$$

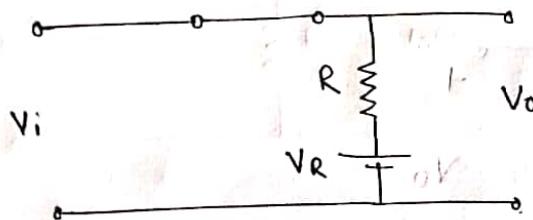


$$\theta = f(V_i) \text{ or } \theta = f(V_R)$$

$$V_o(t) = V_i(t)$$

$$V_R = 1V$$

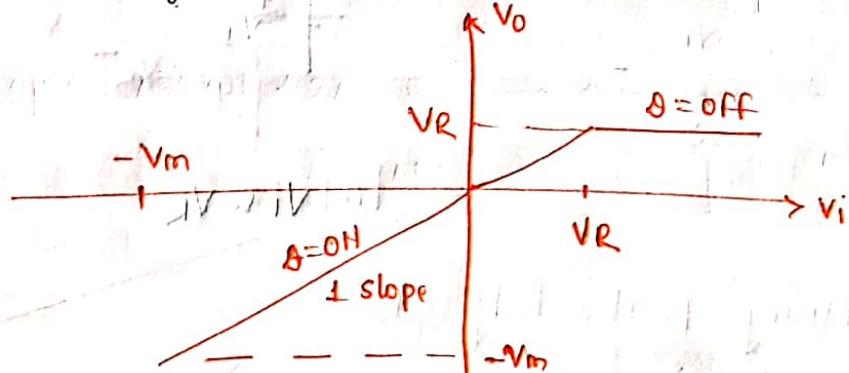

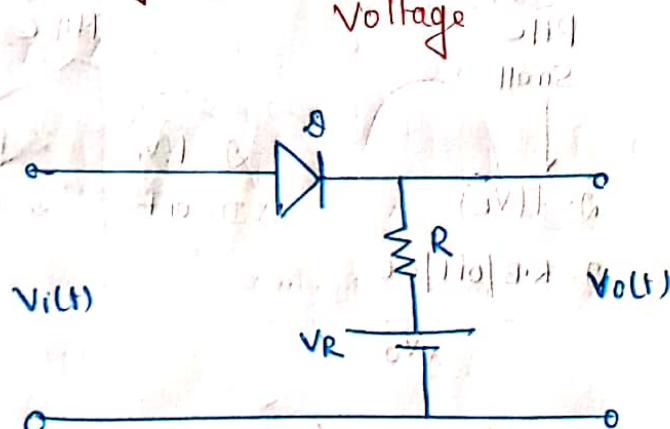* Negative Series clipper Circuit with Positive Reference Voltage



$$V_R < V_m$$



i) $V_i > V_R$
 $\theta = f(V_i) \rightarrow \theta \rightarrow \text{ON}$
 $V_o = V_i$

ii) $V_i < V_R$


PMC
 $\theta \rightarrow f(V_R)$
 $\theta \rightarrow \text{OFF}$

NHC
 $\theta \rightarrow f(V_i)$
 or
 $\theta \rightarrow f(V_R)$
 $\theta \rightarrow \text{OFF}$

$$V_o = V_R$$

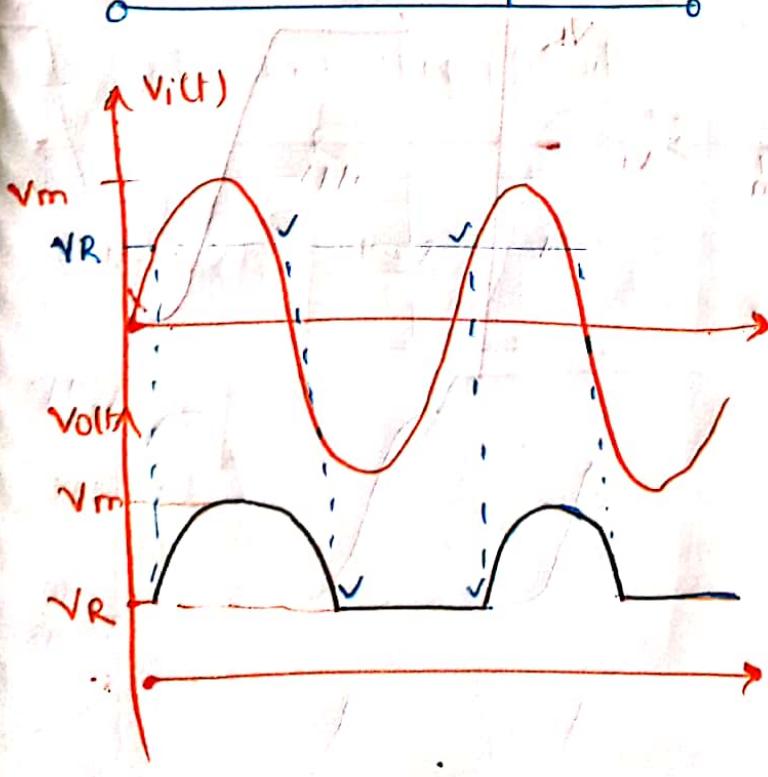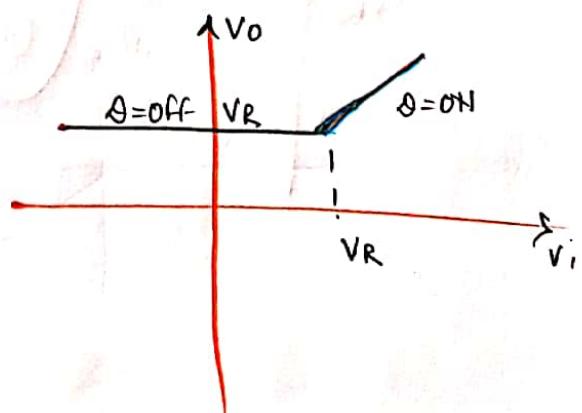

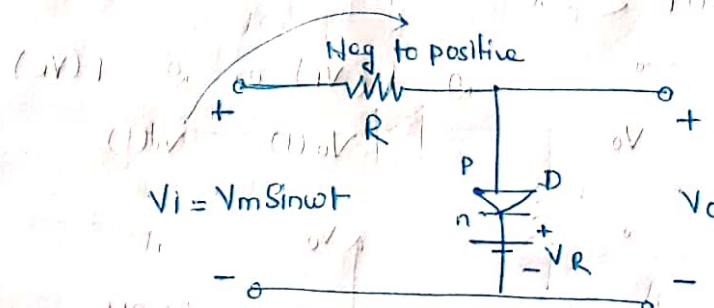* Positive shunt clipper Circuit with Positive Reference Voltage



Positive Half Cycle
(PHC)

$$D = f(V_i) \quad mV > dV$$

$$D = \alpha N / f_B / s.c.$$

$$V_o = V_R$$

$$dV = dV$$

PHC
Small

$$D = f(V_R)$$

$$D = R \cdot B / \text{off} / \text{on}$$



Neg C

$$D = f(V_i)$$


$$D = \text{off}$$

$$D = f(V_R)$$



$$D = \text{off}$$

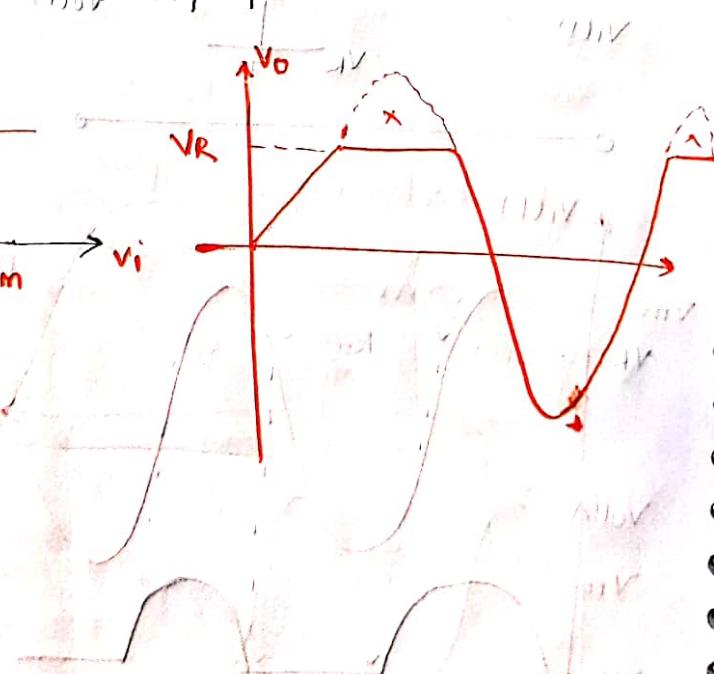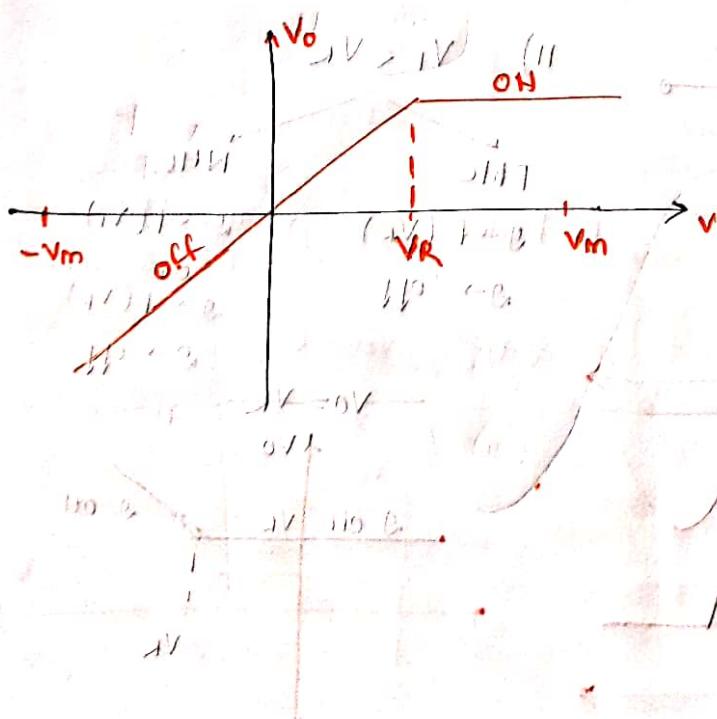

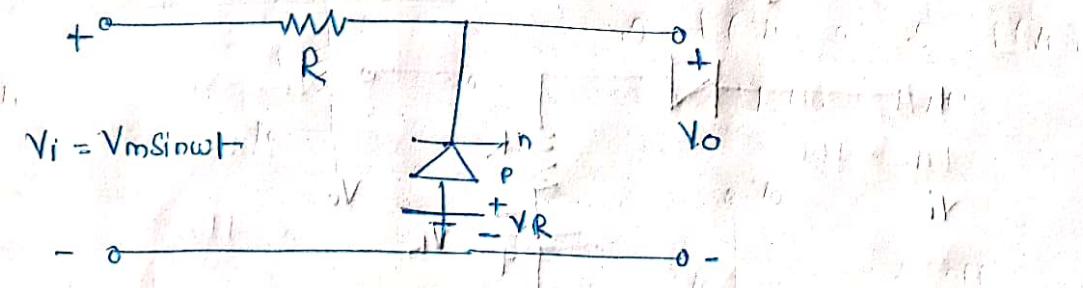
* Negative shunt clipper circuit with positive Ref. Voltage



$$V_i & V_R \text{ Inv. Inv}$$

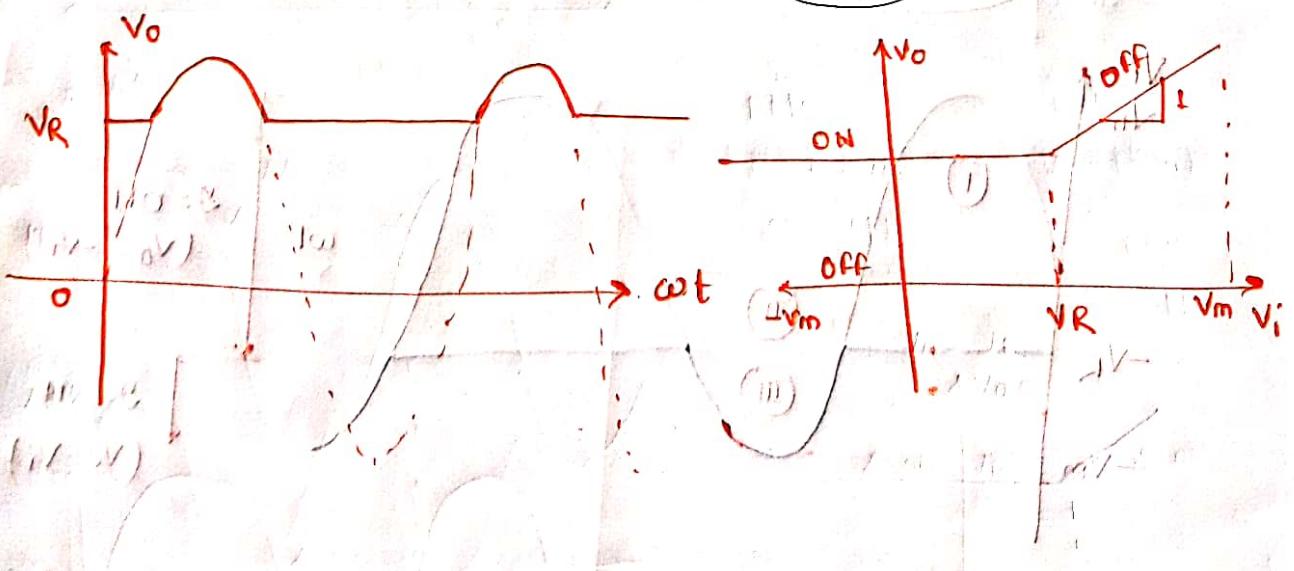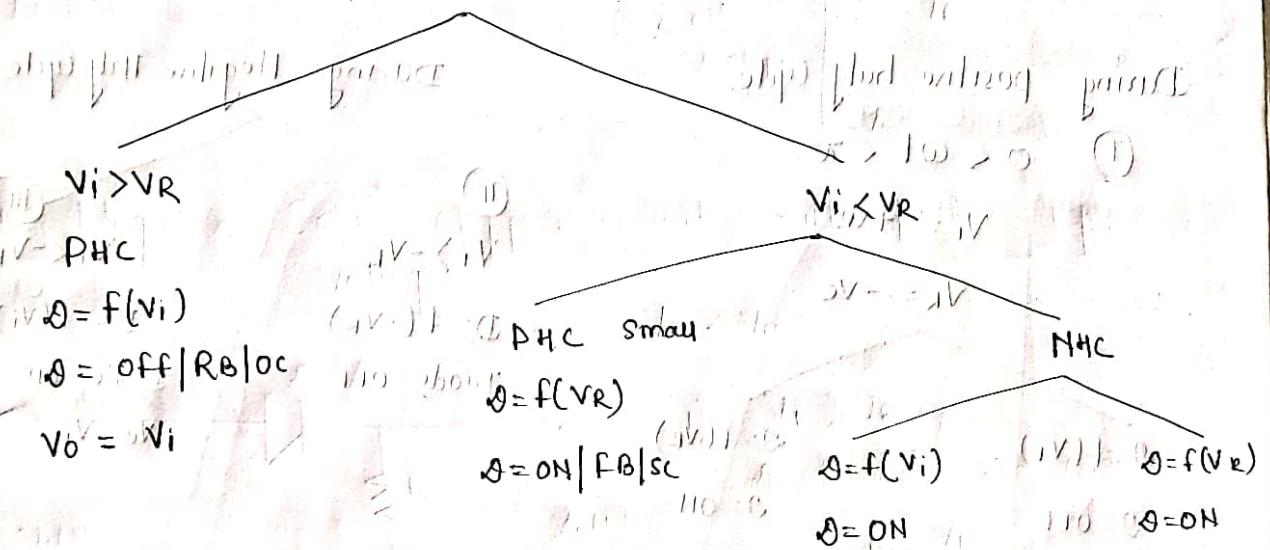

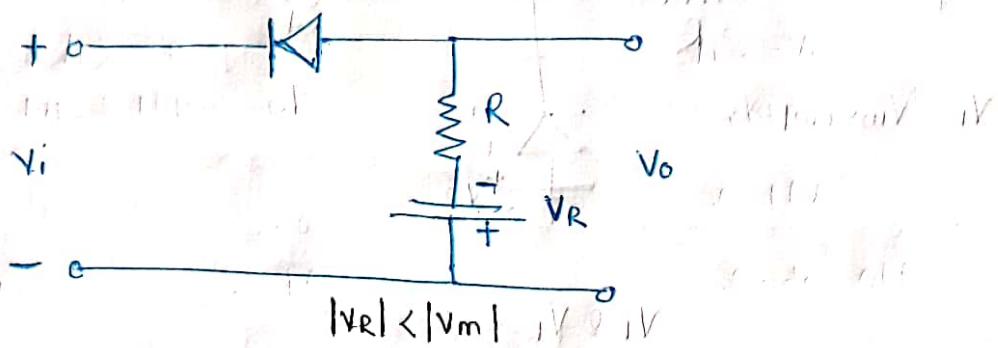* Positive Series Clipper Circuit with negative reference voltage



During positive half cycle

$$\textcircled{I} \quad 0 < \omega t < \pi$$

$$V_i = +ve$$

$$V_R = -ve$$

$$D = f(V_i)$$

$$D = \text{OFF}$$

$$V_o = -V_R$$

During Negative Half Cycle

$$\textcircled{II}$$

$$V_i > -V_R$$

$$D = f(-V_R)$$

$$\text{Diode = OFF}$$


$$\textcircled{III}$$


$$V_i < -V_R$$

$$D = f(V_i)$$

$$\text{Diode = ON}$$

$$V_o = V_i$$

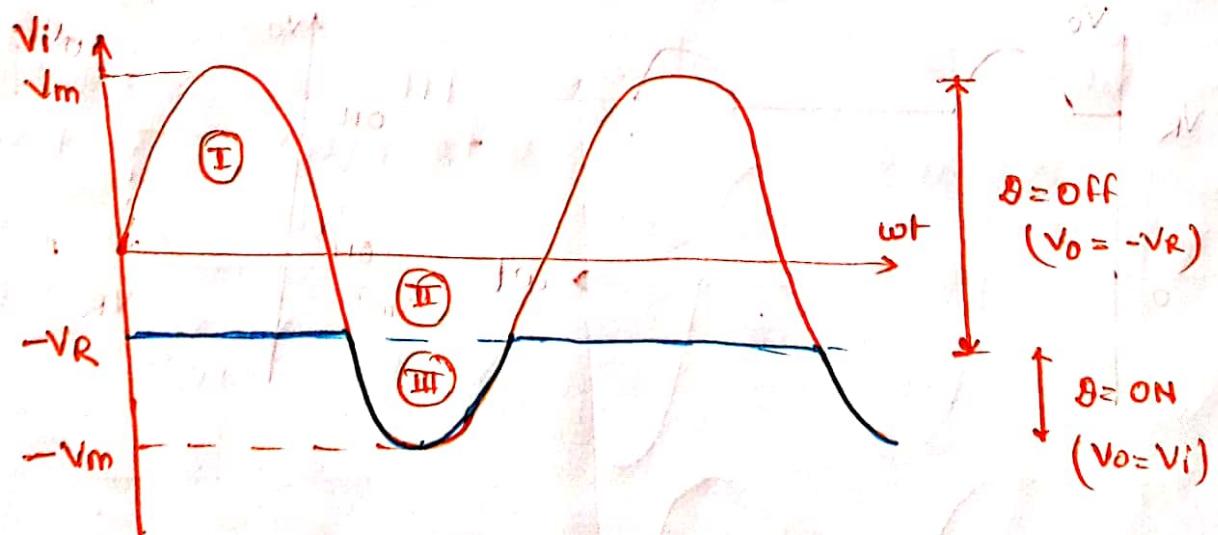

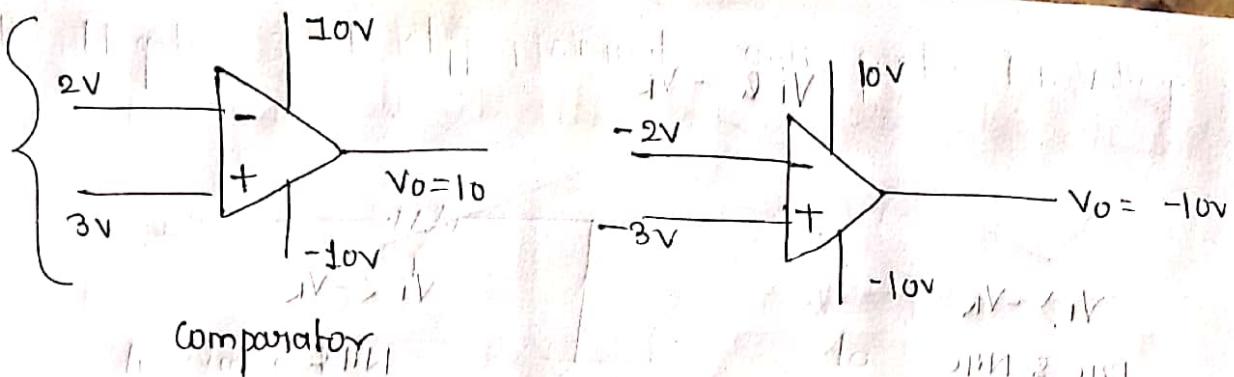


i) non Inverting > Inverting

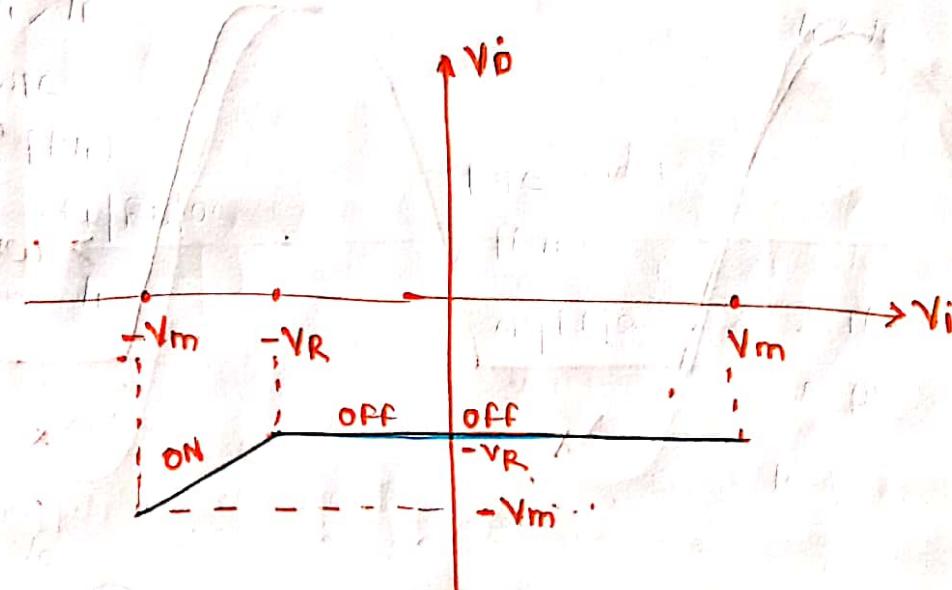
ii) Non Inverting < Inverting




In Comparators, numbers decide the output

In Case of diode, potential decides the output





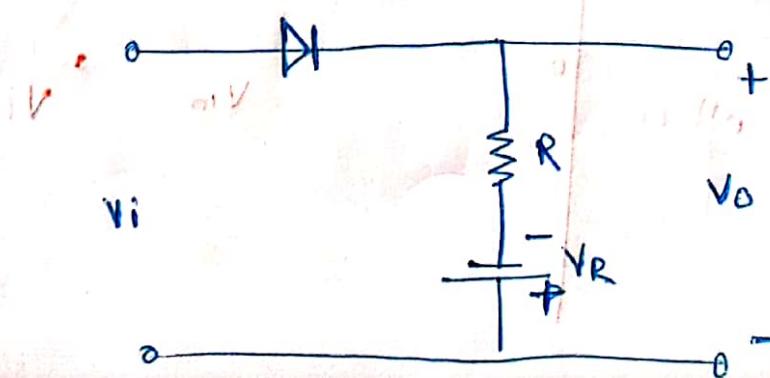* Negative Series Clipper Circuit with Negative Reference Voltage




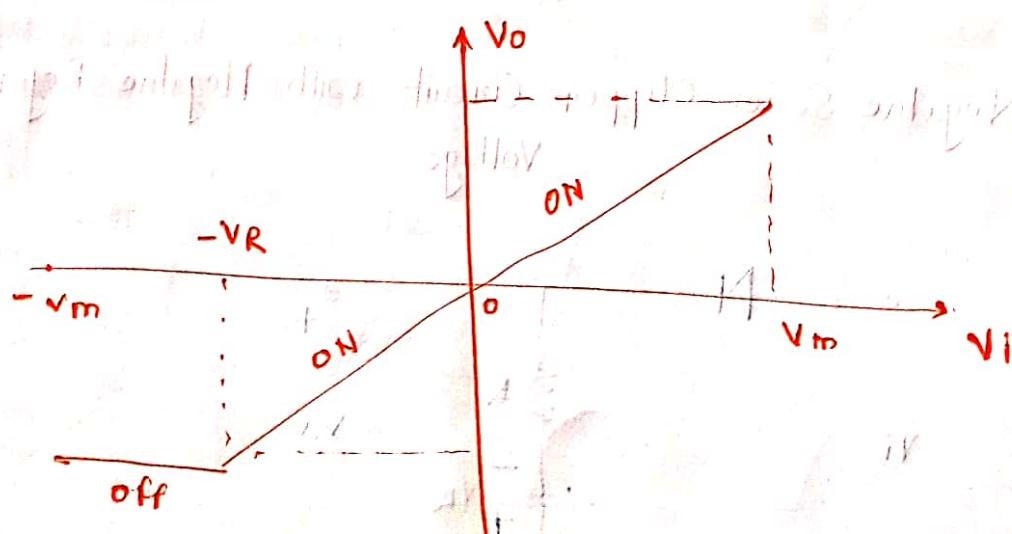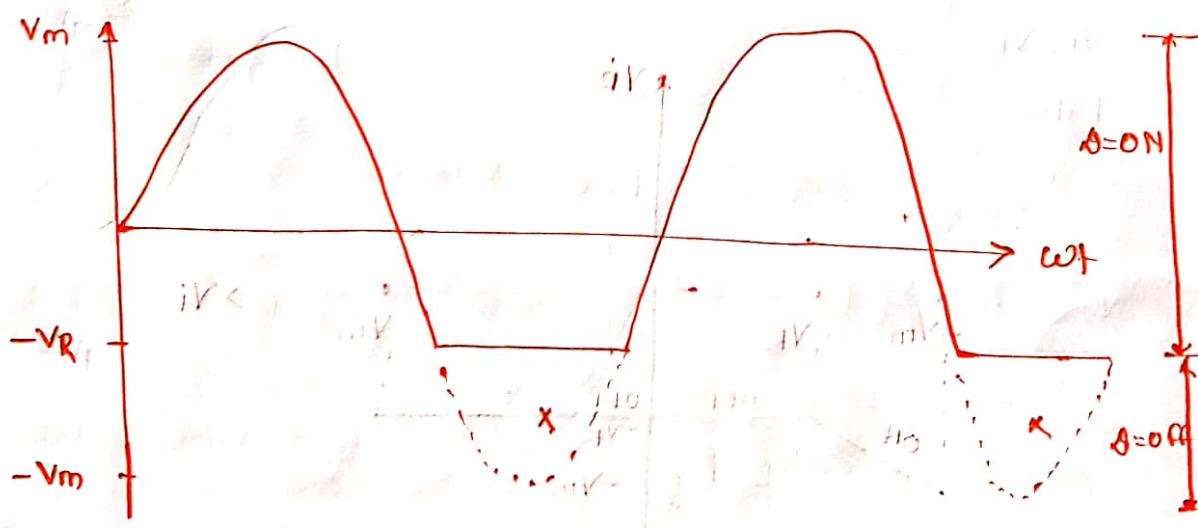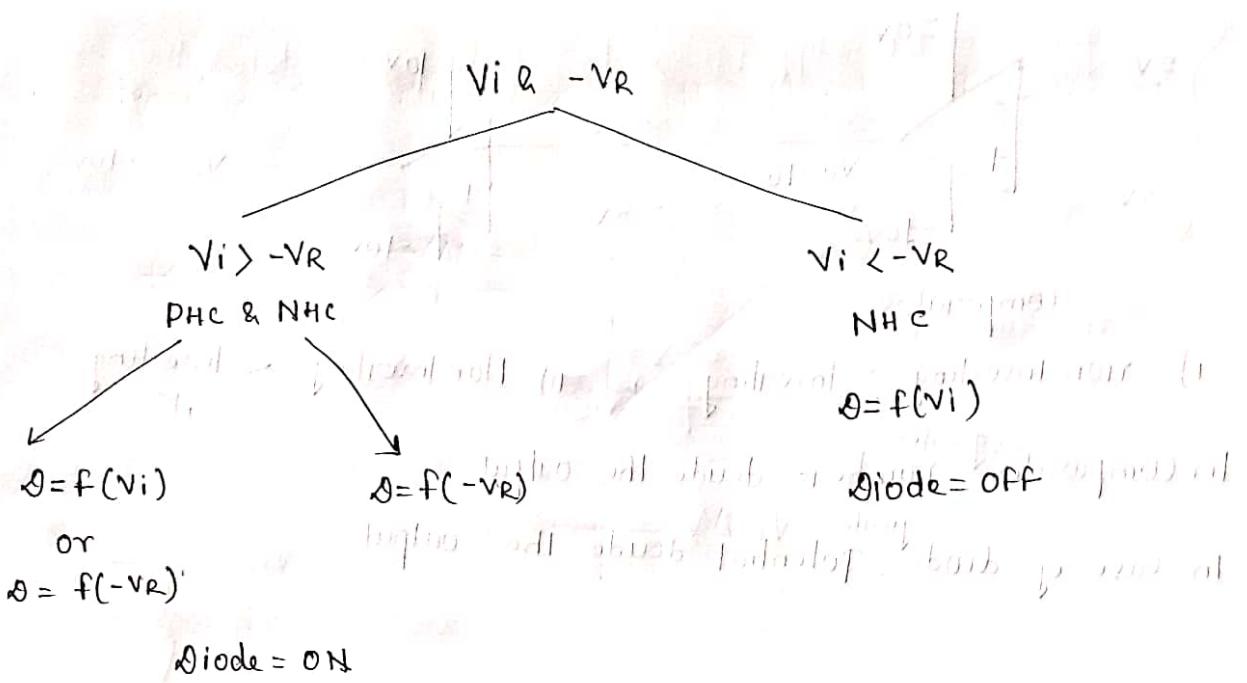


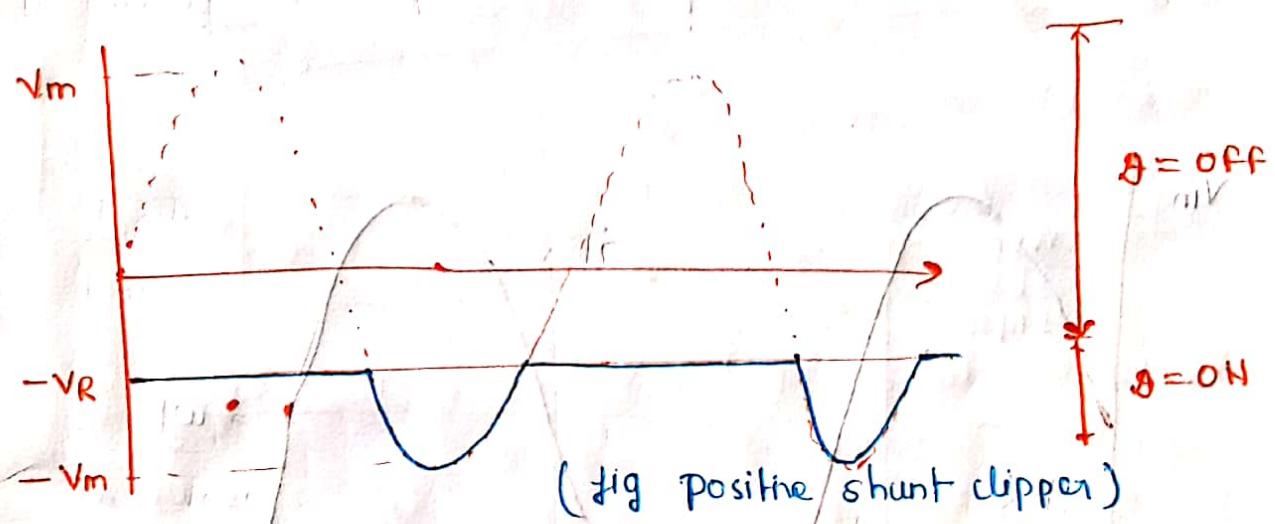
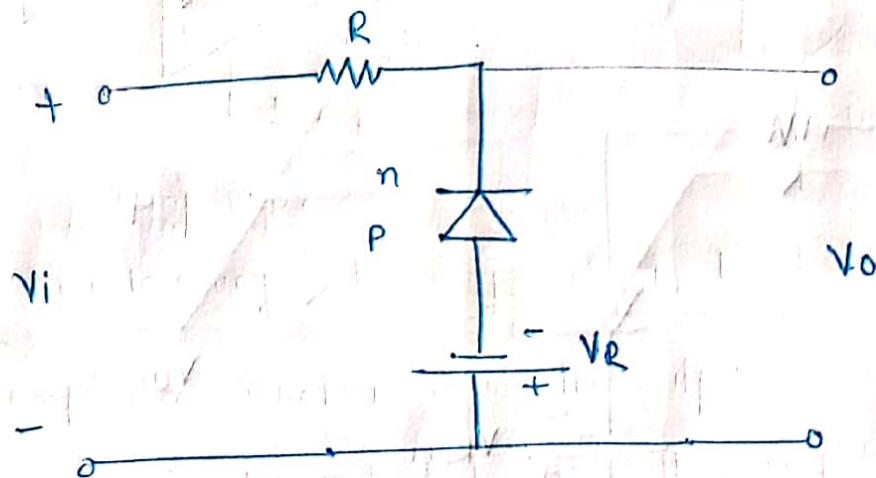
* Negative shunt clipper circuit with Negative Reg. Voltage




(fig positive shunt clipper)

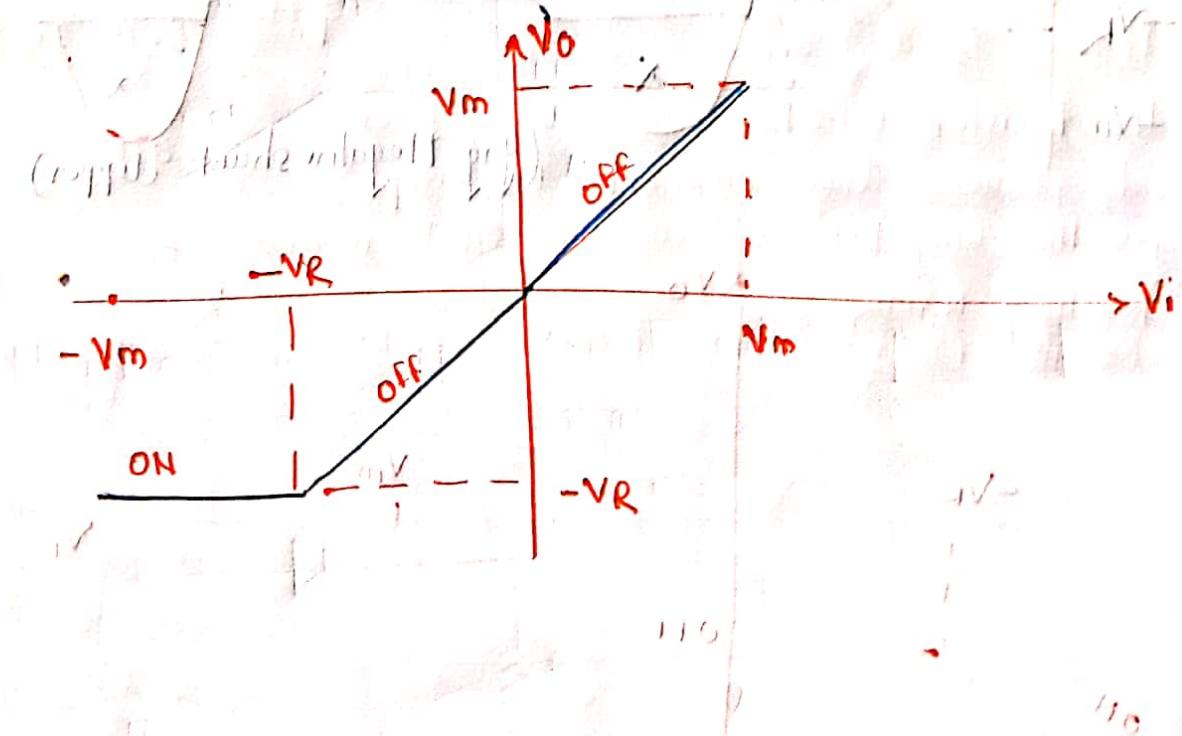


* Positive shunt clipper ckt with Negative Reg. Voltage

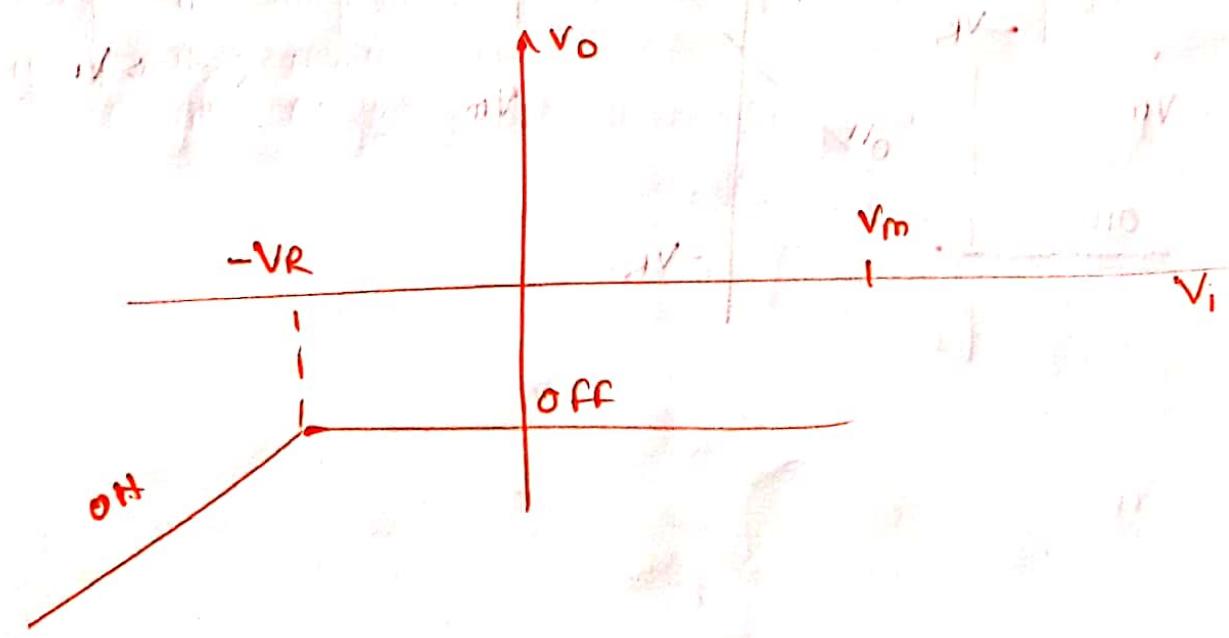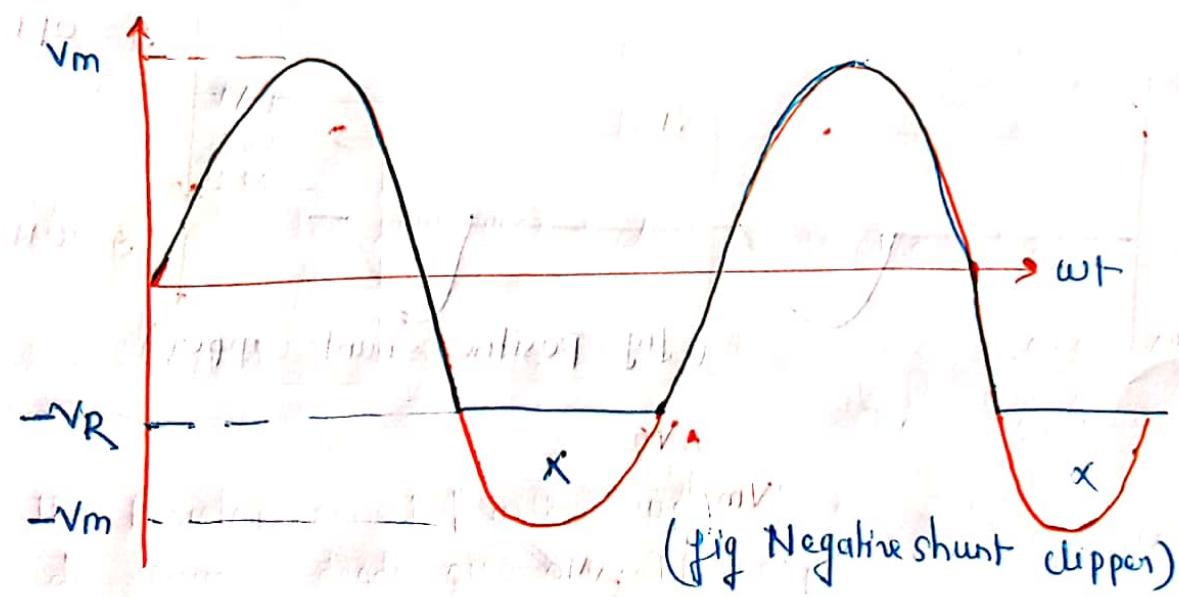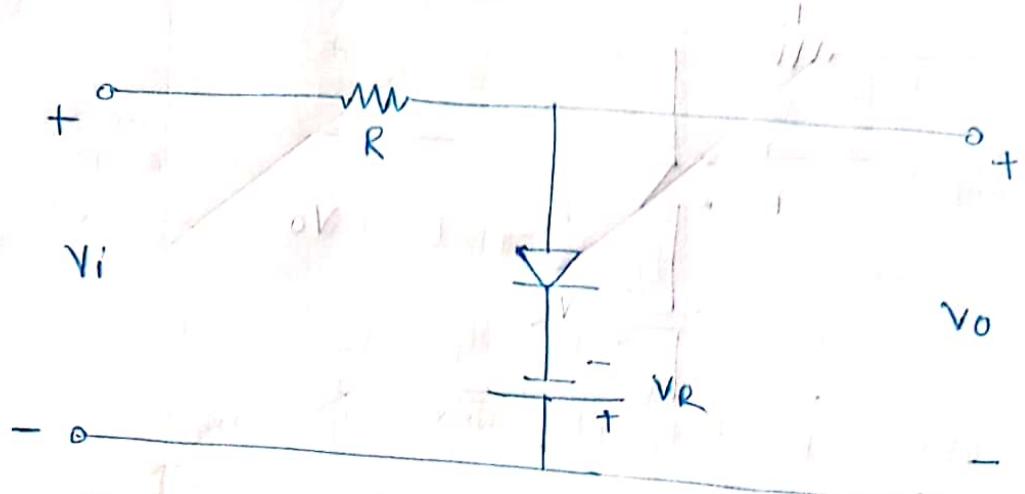


Ques1

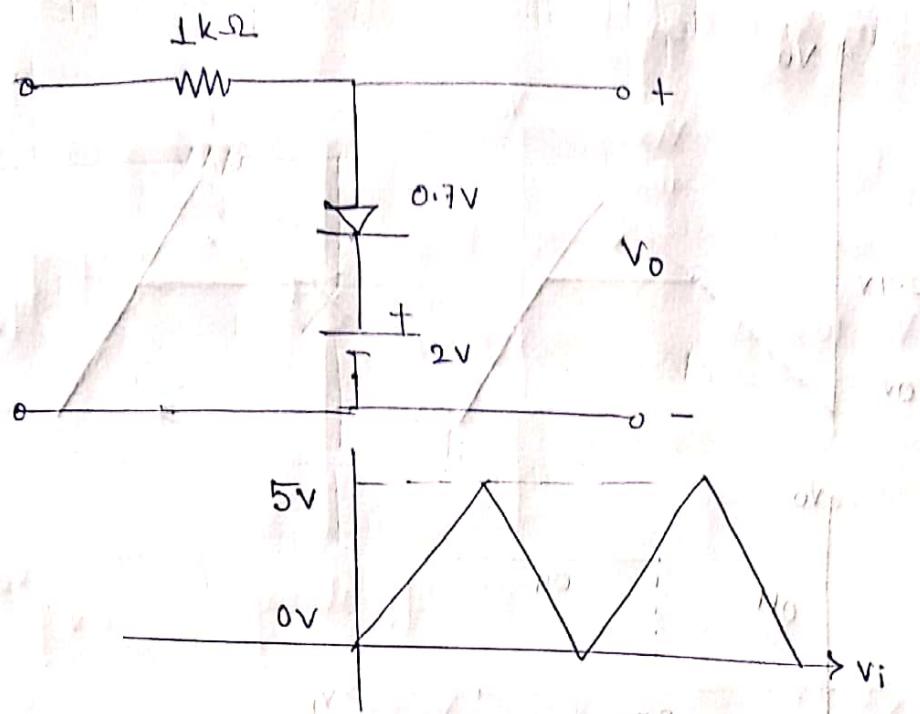

Sol

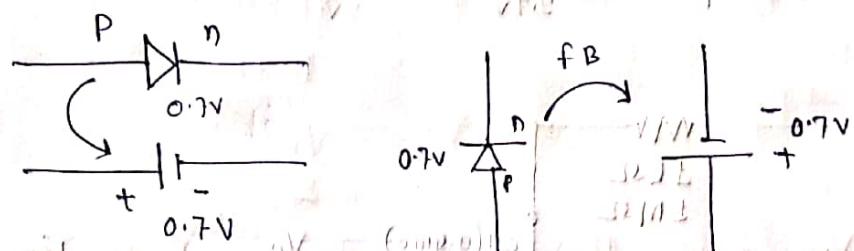

Assume diode as ideal

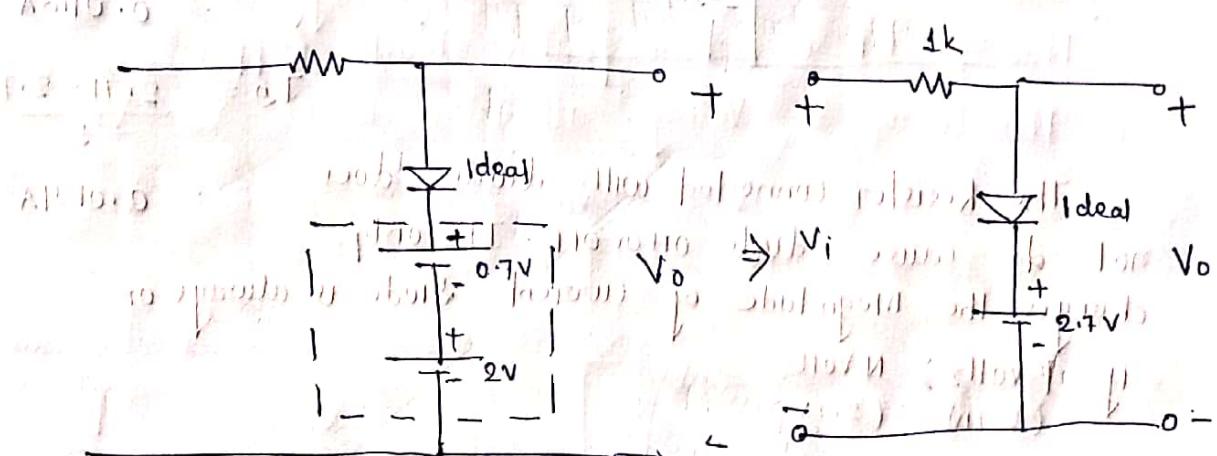

$V_i \& 2.7V$

$V_i > 2.7V$

$$D = f(V_i)$$

$$D = ON | S$$




$$V_o = 2.7V$$

$V_i < 2.7V$

$$D = f(2.7V)$$

$$D = OFF$$

$$V_o = V_i$$

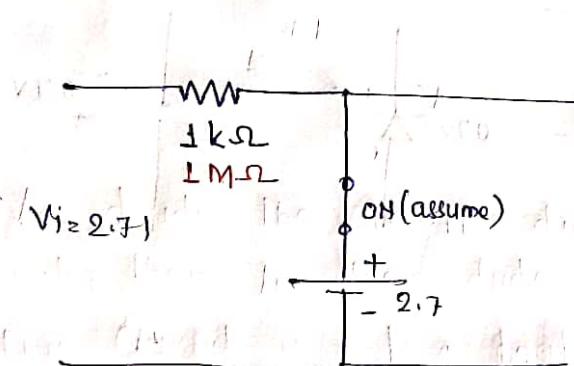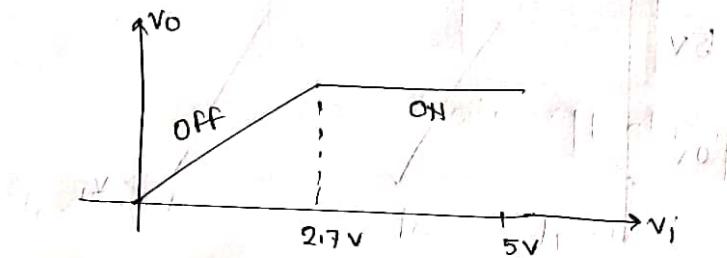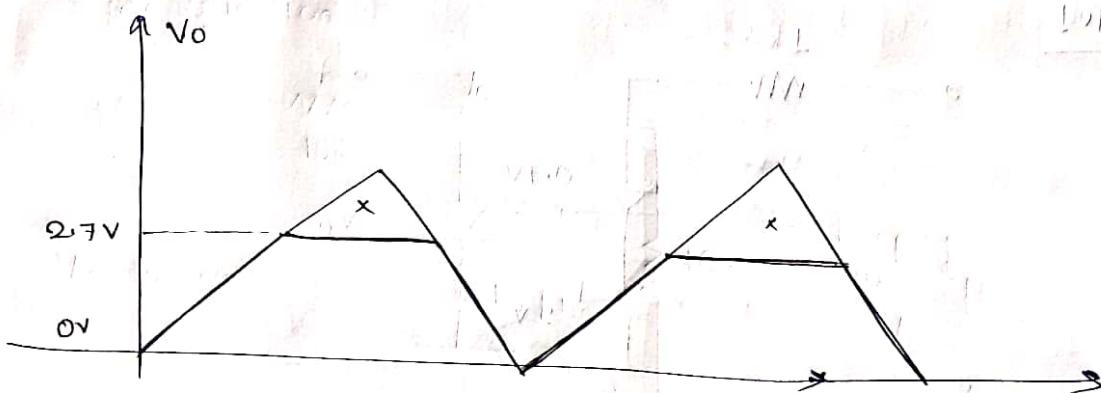

$$I_d = \frac{2.71 - 2.7}{1M\Omega} \approx 0.01mA$$

$$I_d = \frac{2.71 - 2.7}{1M\Omega} = 0.01mA$$



The Resistor Connected with diode does not do cause diode ON or OFF. It only changes the Magnitude of current. Diode is always on

If $P_{vout2} > N_{vout1}$

$$(2.71V) > (2.7V)$$

Que 2

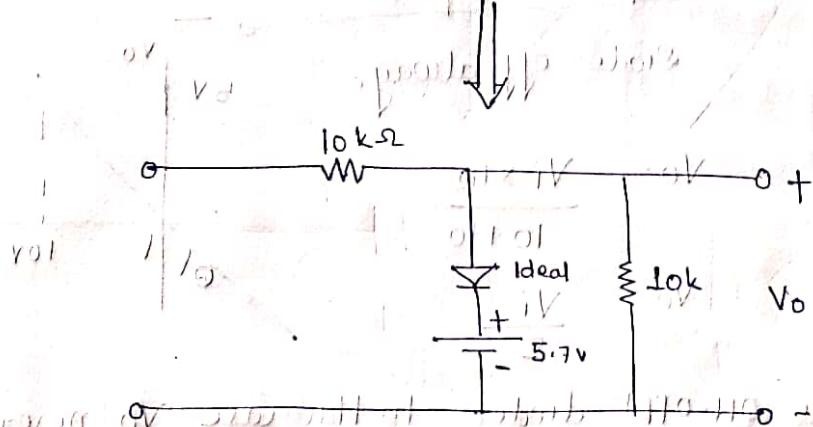
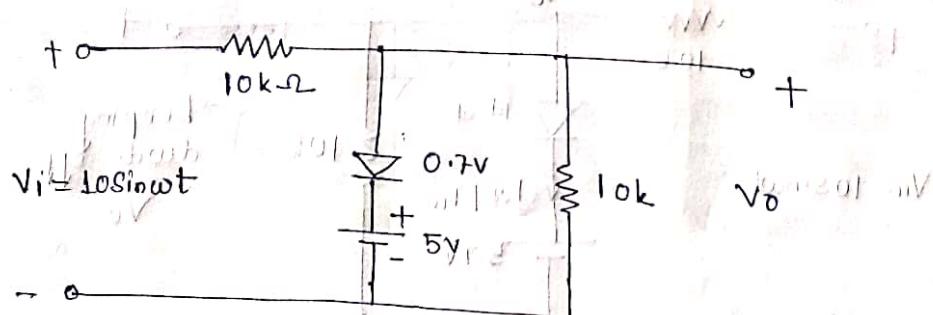
Draw xfer and output characteristic for a given below figure.



Wrong solution


In actual diode
is not comparable
with V_i

i) $V_i > 5.7V$ diode ON $V_o = V_i - 0.7V$ $V_i < 5.7V$ diode off $V_o = 5.7V$

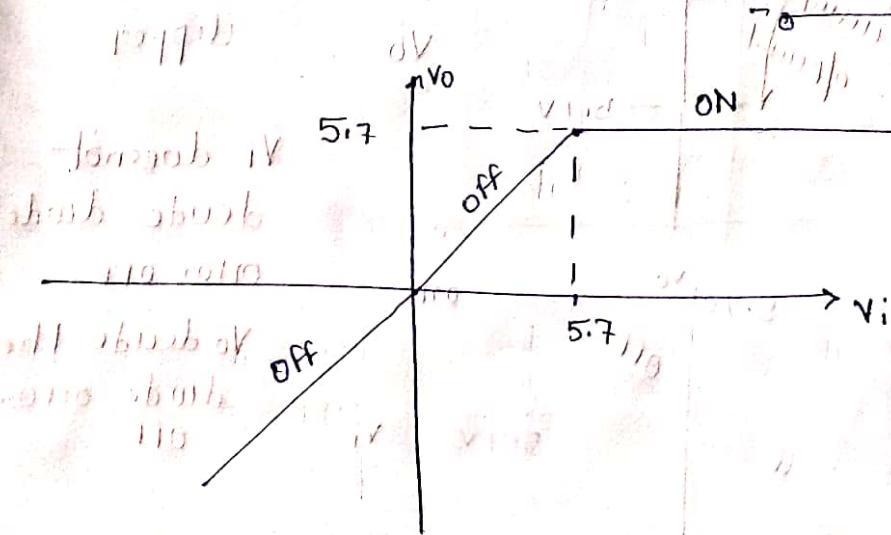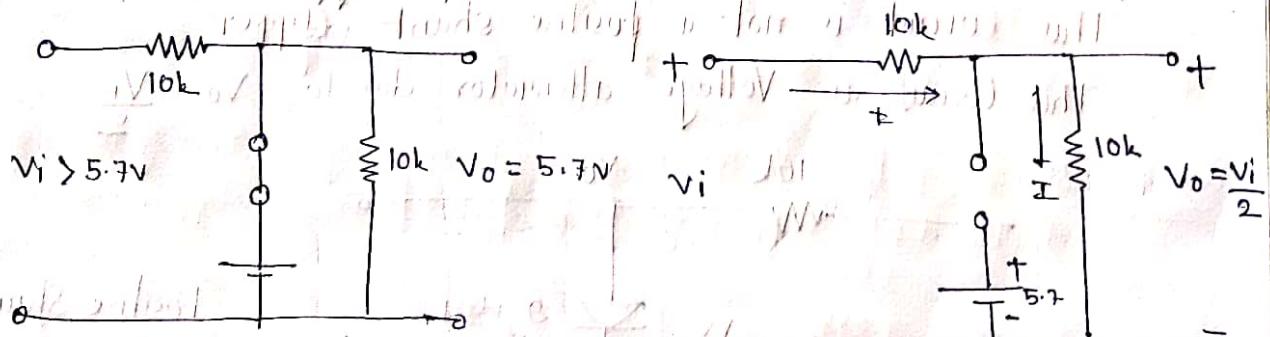

Que 3

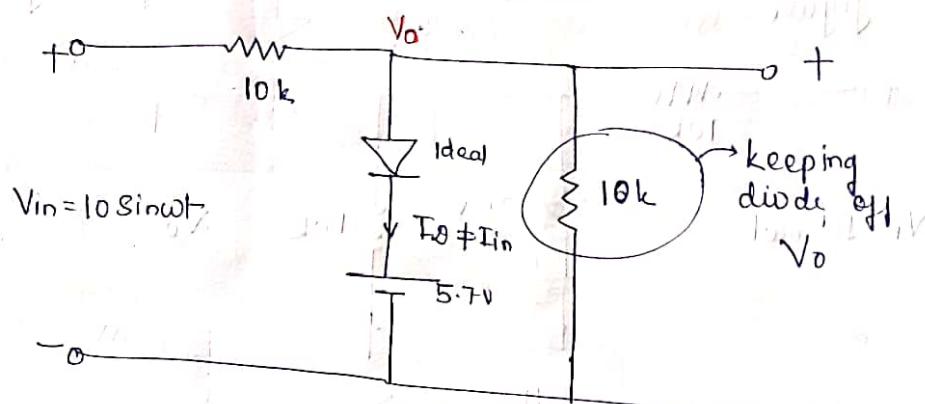
Same question is asked in the last PPT & part 1 is solved



$V_i < 5.7V$

$$V_o = \frac{V_i \times 10}{10 + 10}$$


$$V_o = \frac{V_i}{2}$$

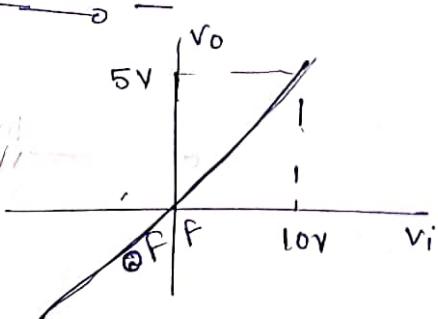

Diode off always
start from $V_i = 5.7V$
if the V_o decide the (ON-OFF) diode. In this case V_o never greater than V_i . Hence diode always off.

This circuit is not a positive shunt clipper.

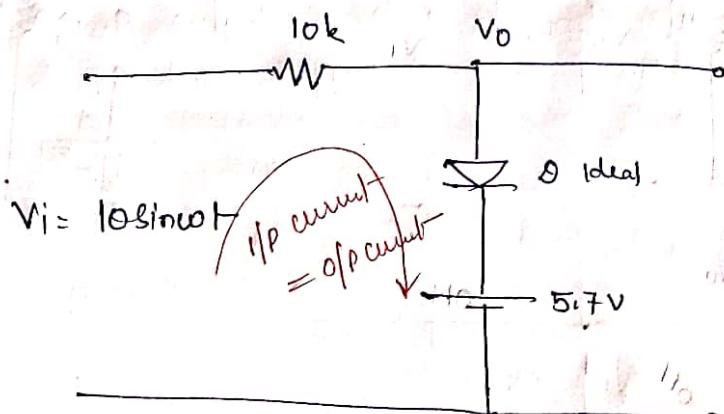
This circuit is Voltage attenuator due to $V_o = \frac{V_i}{2}$



Positive Shunt
Clipper

V_i does not
decide diode
ON or OFF

V_o decide the
diode ON or
OFF

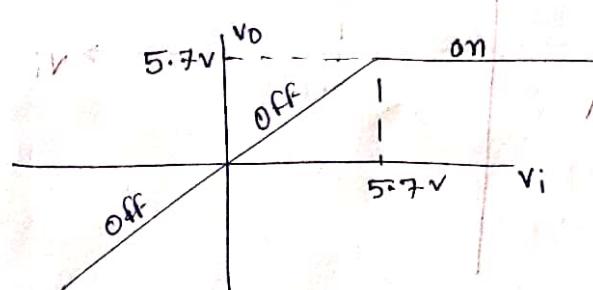

Ques 3 $V_i = 20\sin\omega t$

$$V_i = 11.4$$

$$V_i > 11.4 \text{ V}$$


Diode ON

$$V_o = 5.7$$


on

off

Ques.

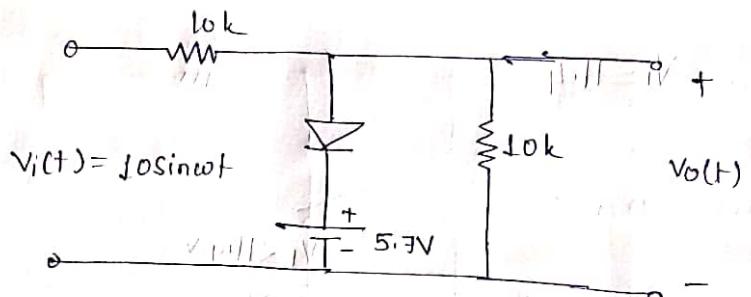

How to check diode -

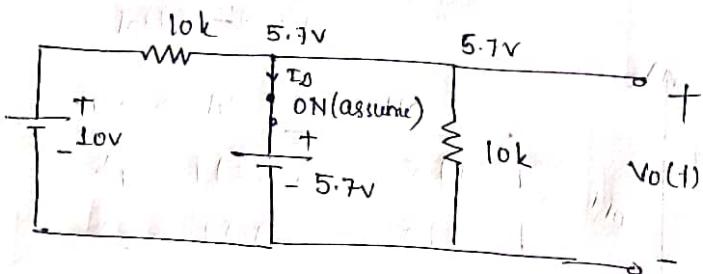

$$\frac{5.7}{10} + \frac{5.7 - 10}{10} + I_D = 0$$

$$I_D = -0.57 + 0.43$$

$$I_D = -0.14$$


} Diode current never negative
 Hence assumption was wrong

$$I_D = 0A$$


Negative value of diode current i.e. diode is open circuited



Ques 4: Draw output & Xfer characteristic for the following double diode clipper circuit (parallel diode clipper ckt).

(i)


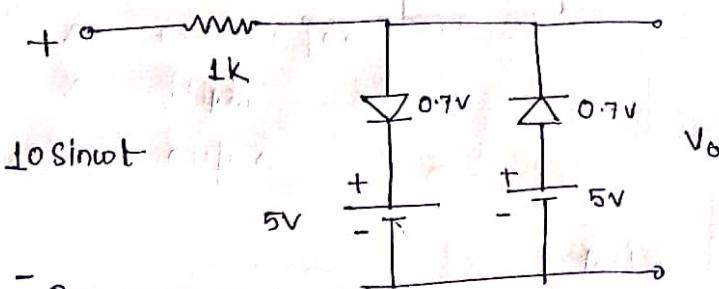


(ii)

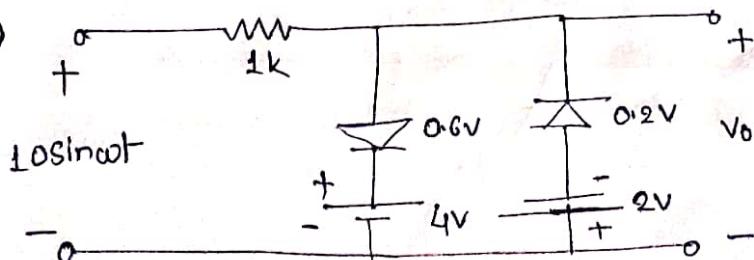


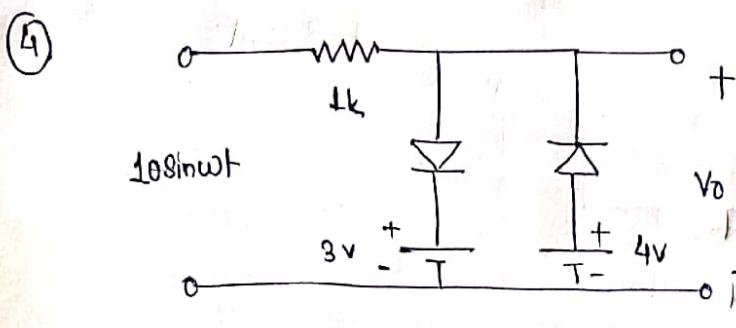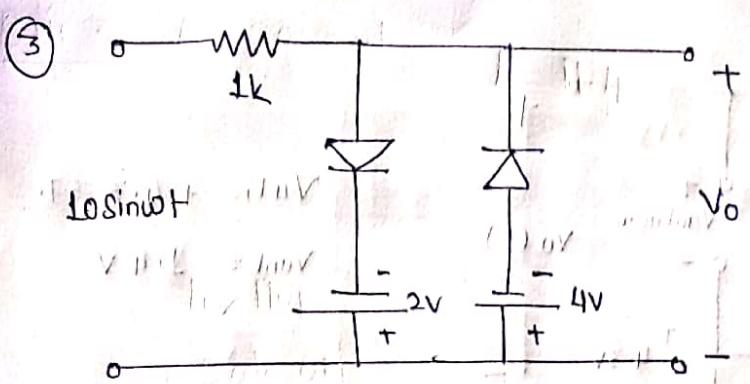

If there is no information of diode, that means Ideal or practical
Then we assume Ideal diode.

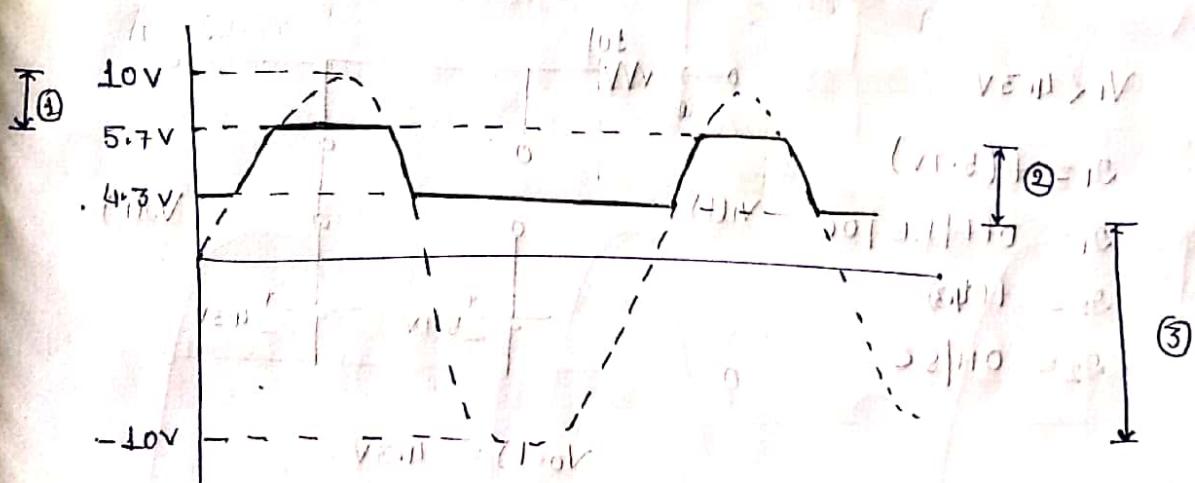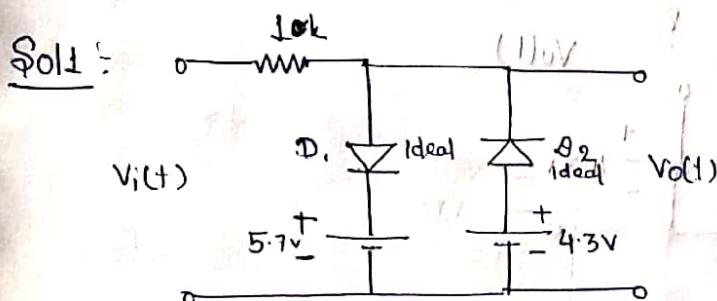

Case I:- $V_i > 5.7$ $D_1 = f(V_i)$ $D_1 = ON | SC | fB$
 $D_2 = f(V_i)$ $D_2 = OFF | OC | RB$

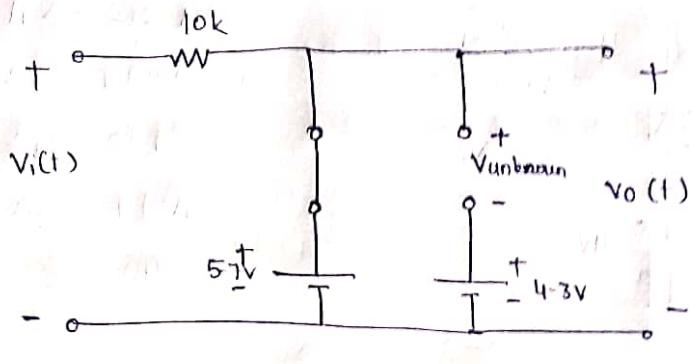

$$V_{unkn} + 4.3 = 5.7$$


$$V_{unk} = 1.4 \text{ V}$$

$$V_o(t) = 5.7 \text{ V}$$

Case II $4.3 < V_i(t) < 5.7$

$$D_1 = f(5.7 \text{ V}) = \text{off}$$

$$D_2 = f(V_i) = \text{off}$$

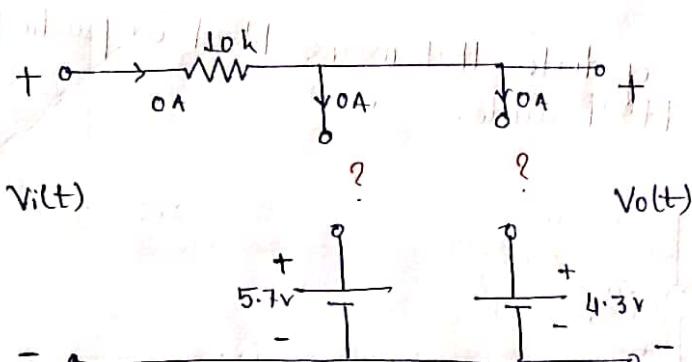

$$V_o(t) = V_i(t)$$

Case III


$$V_i < 4.3 \text{ V}$$

$$D_1 = f(5.7 \text{ V})$$


$$D_1 = \text{off} | R_B | 0 \text{ C}$$

$$D_2 = f(4.3)$$



$$D_2 = \text{ON} | S.C.$$

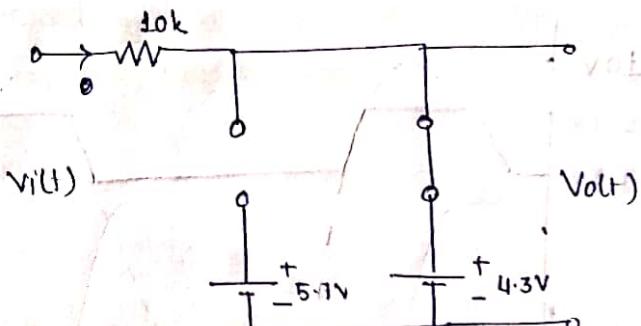

$$V_o(t) = 4.3 \text{ V}$$

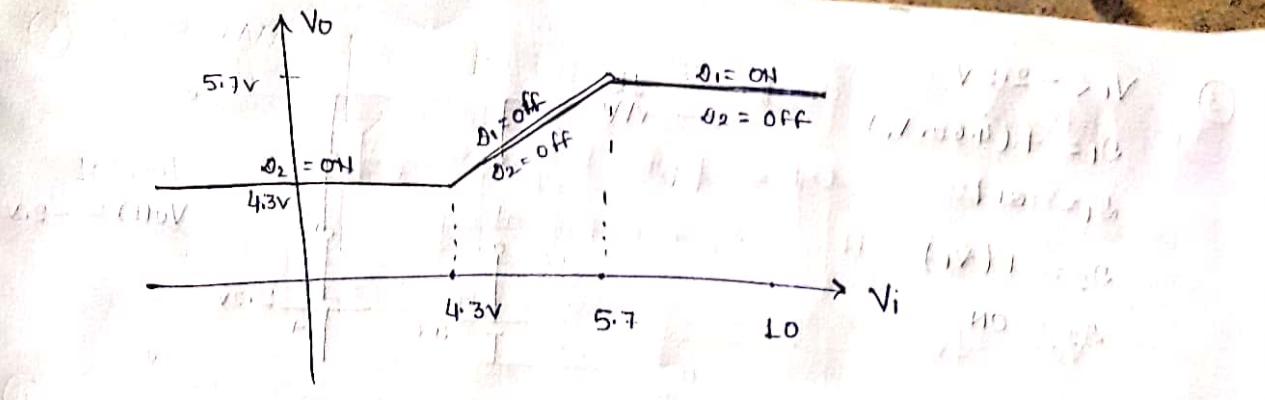

Sol 2:

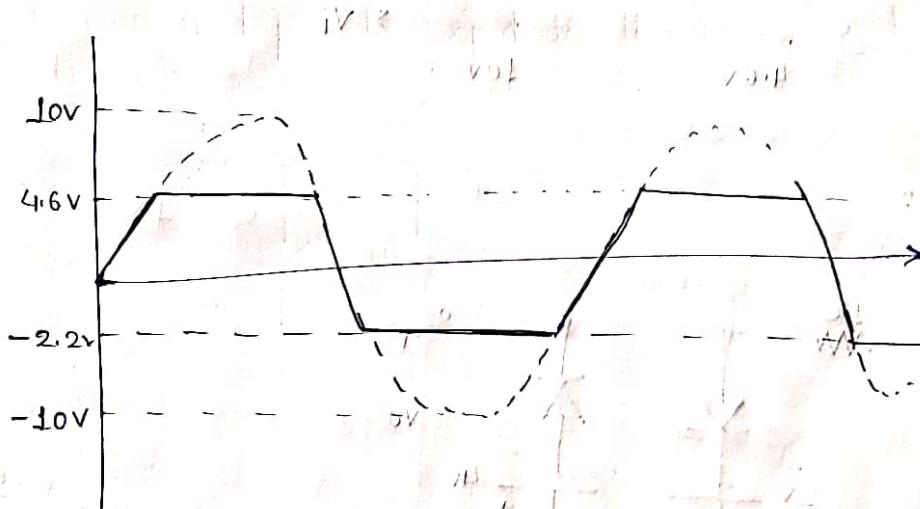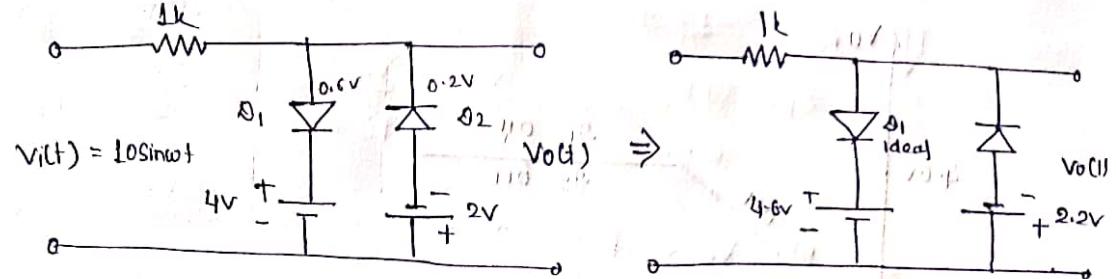

(i) $V_i > 4.6V$


$$D_1 = f(V_i)$$

$$D_1 = \text{ON} | f_B | S_C$$

$$D_2 = \text{OFF} | R_B | O_C$$

$$D_2 = f(V_i \text{ or } -2.2V)$$

$$V_o = 4.6V$$

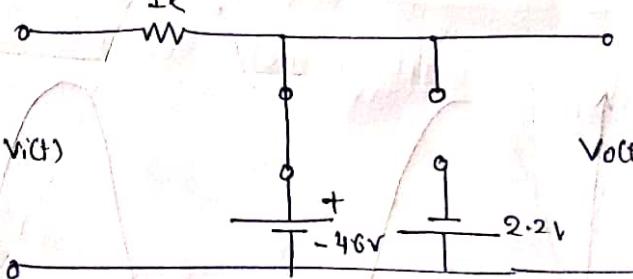

(ii)


$$-2.2 < V_i < 4.6$$

$$D_1 = \text{Off} = f(4.6V)$$

$$D_2 = f(V_i \text{ or } -2.2V)$$

$$D_2 = \text{Off}$$

$$V_o(t) = V_i$$

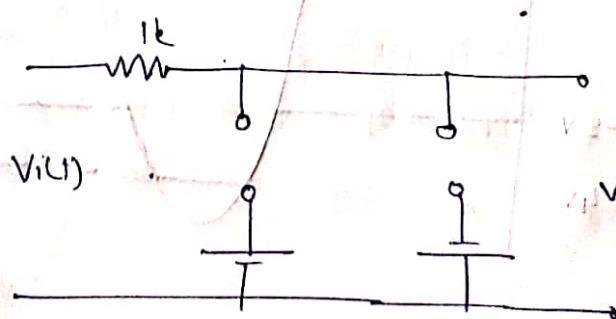



$$\textcircled{3} \quad V_i < -2.2V$$

$$D_1 = f(4.6 \text{ or } V_i)$$



$D_1 = \text{OFF}$


$$D_2 = f(V_i)$$

$D_2 = \text{ON}$

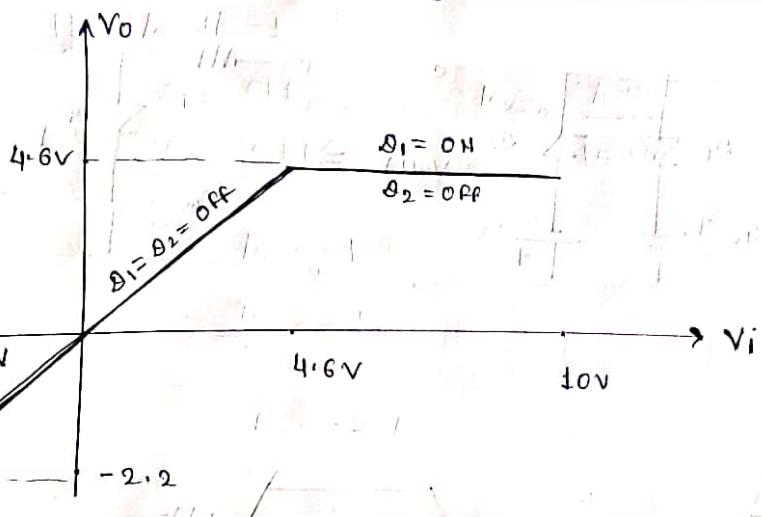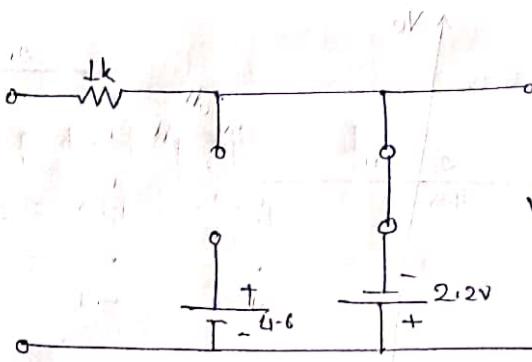


Sol 3

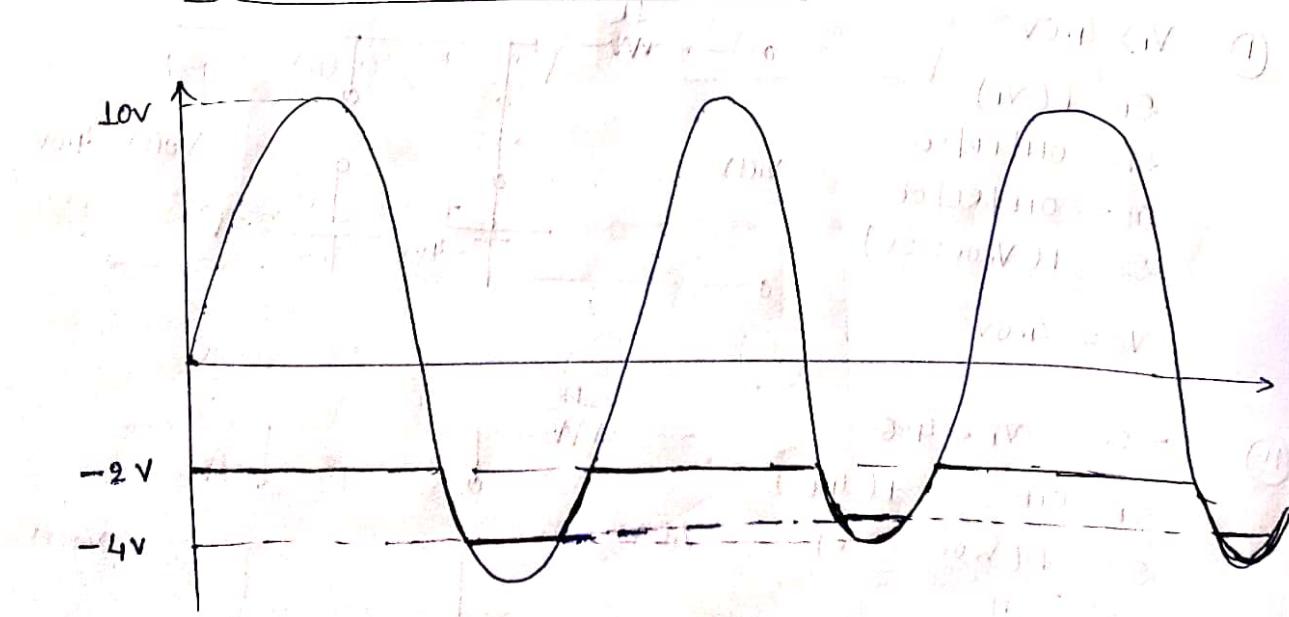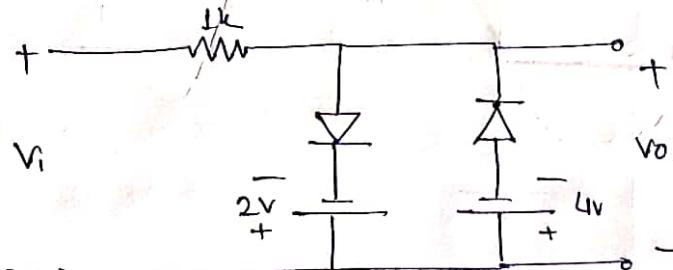


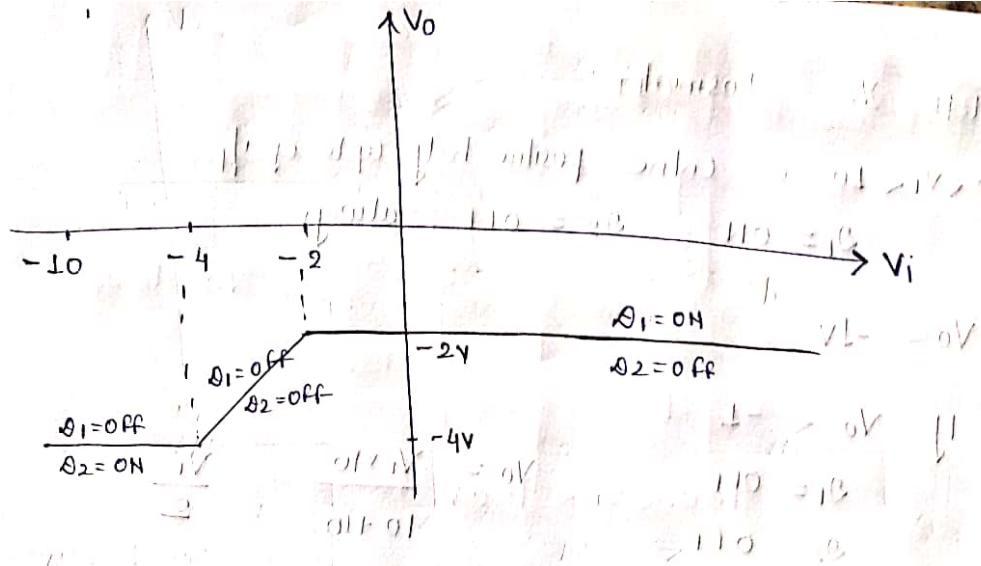


Sol 14:

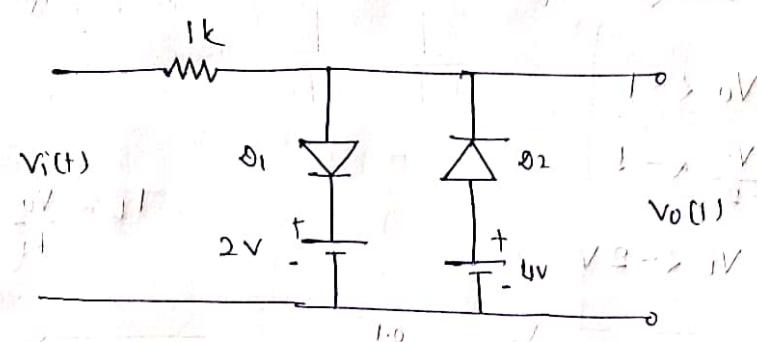

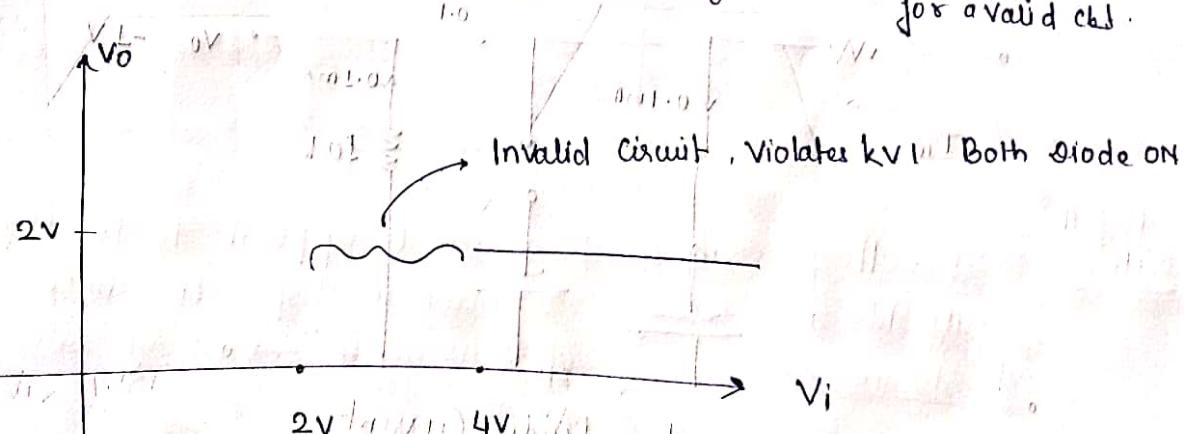Reference Volt
of P \rightarrow N diode
should always be
at higher potential
for a valid cl. .



Q16.

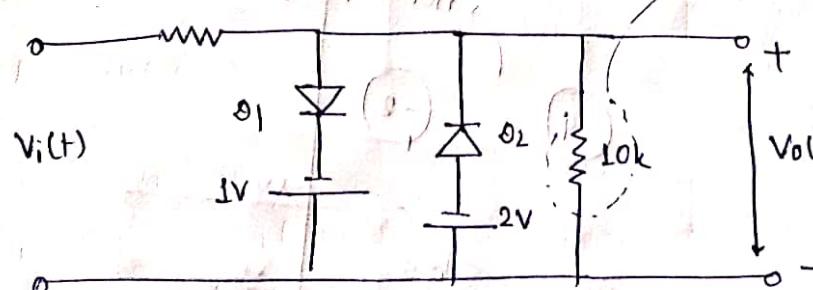

Assuming diode to be ideal, for op to be clipped the 1/p Volt V_i must be outside range.

Sol When $v_i = 0$

$0 < v_i < 10$ or entire positive half cycle of v_i

$\theta_1 = \text{ON}$ $\theta_2 = \text{OFF}$ always

$$V_o = -1V$$

now, if $V_o < -1$

$\theta_1 = \text{OFF}$

$\theta_2 = \text{OFF}$

$$V_o = \frac{V_i \times 10}{10 + 10} = \frac{V_i}{2}$$


$$V_o < -1$$

$$\frac{V_i}{2} < -1$$

$$V_i < -2V$$


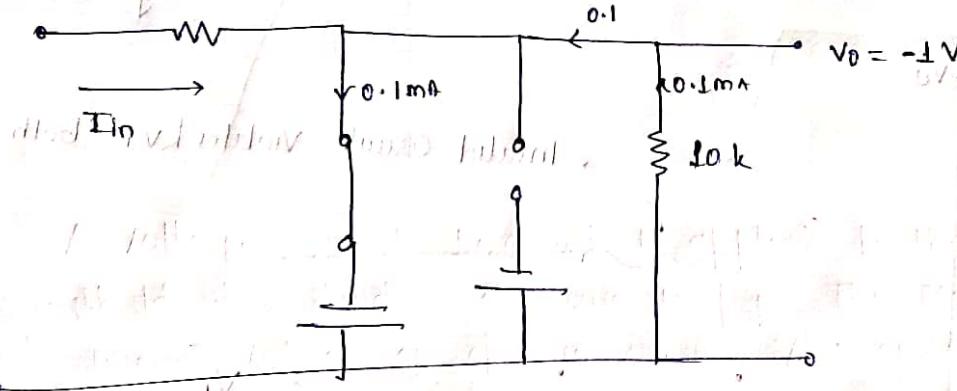
$$I_L = \frac{V_o}{R_L} = \frac{-1}{10} = -0.1 \text{ mA}$$



Input current is not diode current

If

$$V_o < -2V$$

$\theta_2 = \text{ON}$

$$\frac{V_i}{2} < -2$$


$$V_i < -4V$$

not clipping

(-2 to -4)

attenuation happening (not clipping)

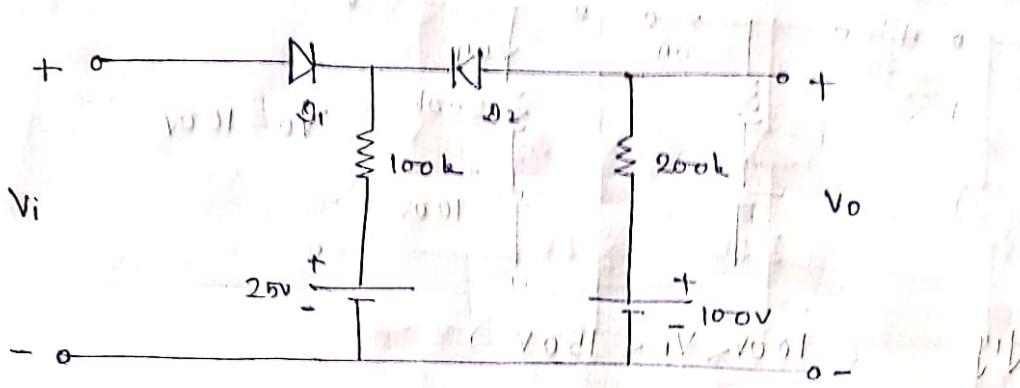Ques. Derive the x for characteristics of clipper circuit where input Voltage vary linearly from (0 to 150V) V_i



Sol:-

$$V_i > 100V \quad X$$


$$V_i < 25V \quad X$$

$$25V < V_i < 100V \quad X$$

$$V_i = 0.1V \quad [\text{Initially}]$$

$$Q_2 = \text{ON} \quad [\text{due to } 100V]$$
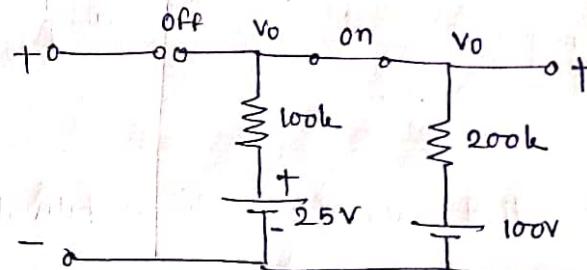
$$Q_1 = \text{off} \quad [\text{due to } 25\text{Vbar}]$$



Condition of half loop is formed


$$\frac{V_o - 100}{200} + \frac{V_o - 25}{100} = 0$$

$$0 < V_o < 50V$$

$$V_o = 50V$$

$$\text{If } V_i > 50V$$
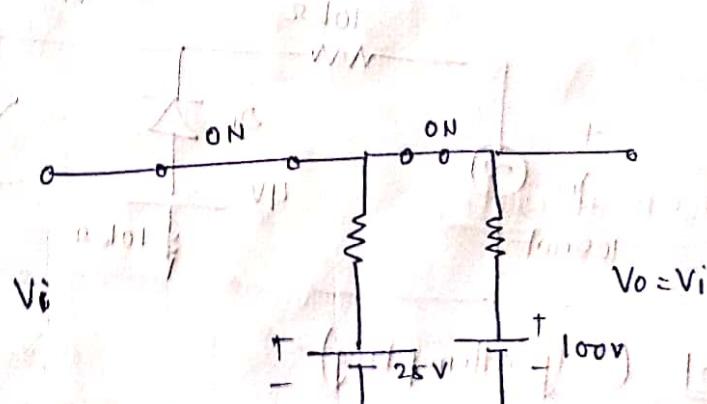
$$Q_1 = \text{ON} \quad Q_2 = \text{ON}$$



$$50 < V_i < 100$$

If $V_i > 100V$, $D_2 = \text{off}$


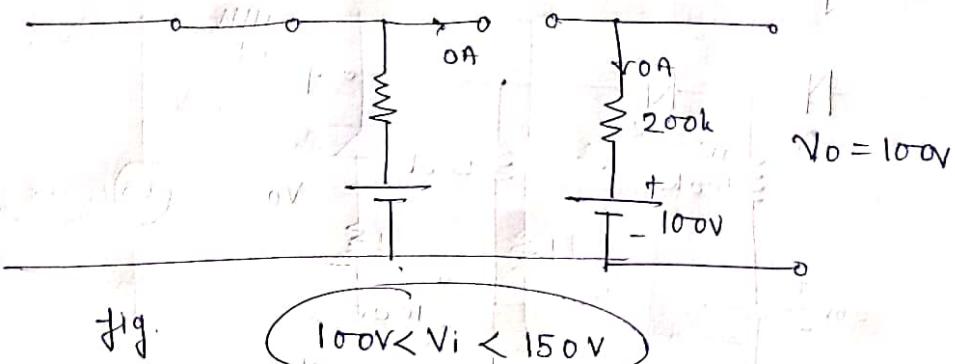



Fig.

$$100V < V_i < 150V$$

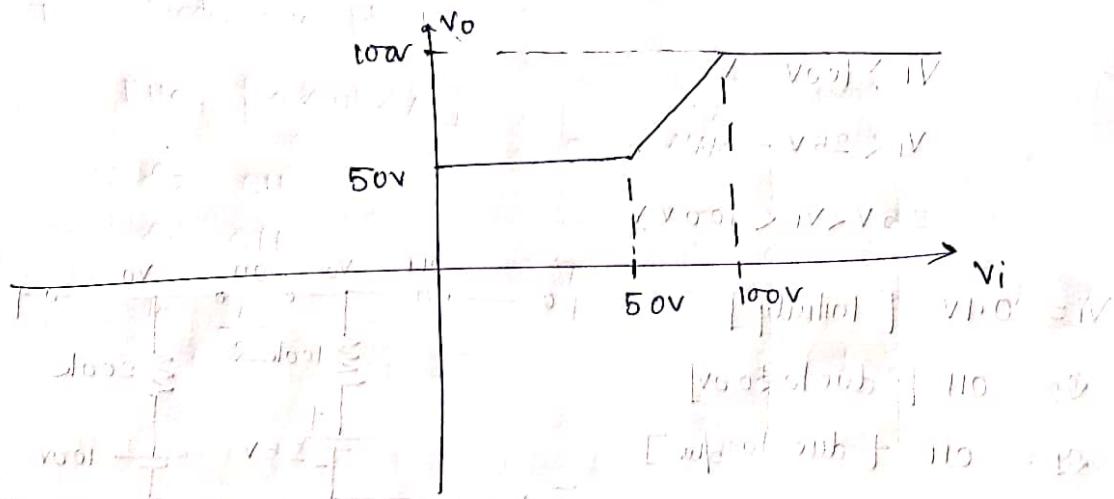

Pg 11

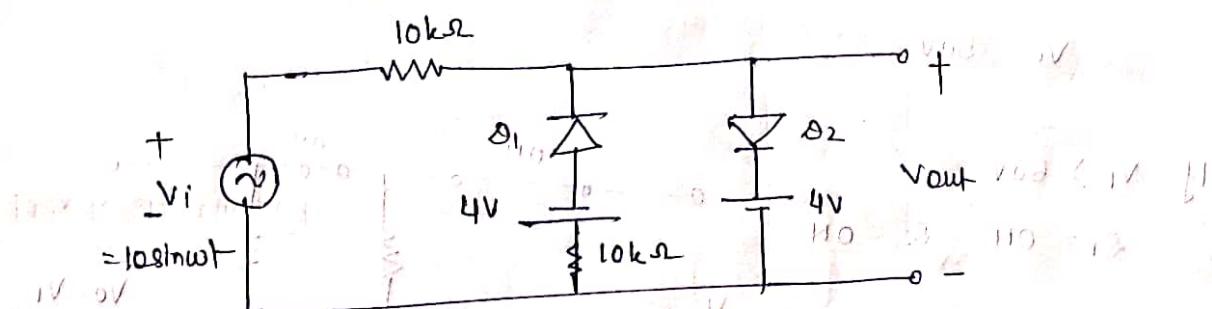Ques 7. A voltage signal $10\sin\omega t$ is applied to the circuit with ideal diodes as shown in fig. The Maxm and Minim value of o/p waveform V_{out} by cbt are



Sol (Self attempting) :-

$$\text{i)} V_i = 0.1 \quad D_2 \text{ off} \quad D_1 = \text{on} \quad V_o = V_i$$

$$\text{ii)} V_i < -4 \quad D_1 \text{ on} \quad D_2 \text{ off} \quad V_o = \frac{V_i}{10}$$

$$\frac{V_o + 4}{10} + \frac{V_o - V_i}{10} = 0$$

$$2V_o = V_i + 4$$

$$V_o = \frac{V_{in} + 4}{2}$$


$V_{min} =$

actual Solution

$$V_i = 10V (\text{max})$$

$D_2 = \text{ON}$

$D_1 = \text{OFF}$

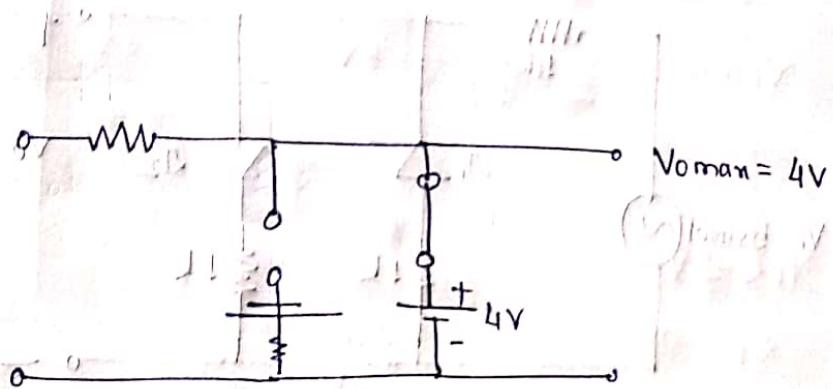


$$\text{if } V_i = -10V (\text{min})$$

$D_1 = \text{ON}$

$D_2 = \text{OFF}$

$$\frac{V_o + 4}{10} + \frac{V_o - V_{in}}{10} = 0$$

$$V_o = \frac{V_{in} - 2}{2}$$

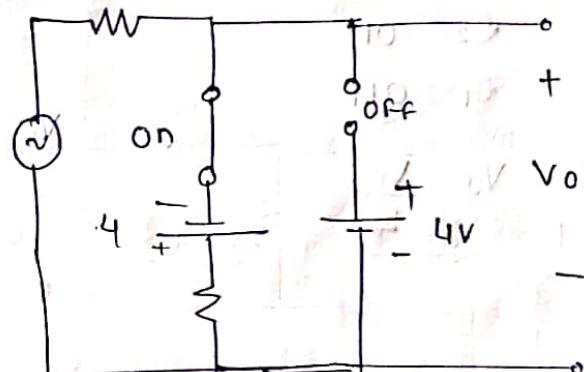


$$V_{o \min} = \frac{-10}{2} - 2$$


$$= -7 \text{ Volts}$$

$$\left\{ \begin{array}{l} V_o + 4 = -7 - V_i \\ -10 + 4 = V_o \end{array} \right.$$

$$V_o = -7 - V_i$$

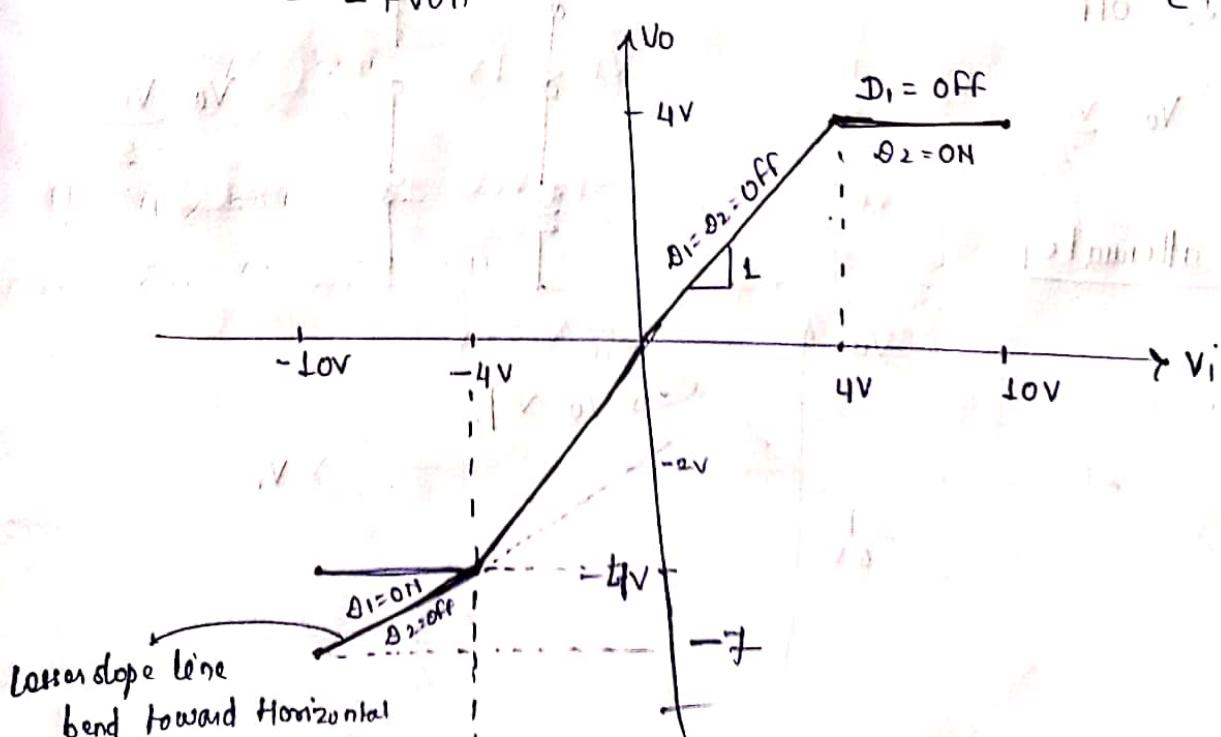

Que. Draw the Xfer characteristic for a given below figure
 i) Diode are ideal ii) If offset voltage of diode is 1V.

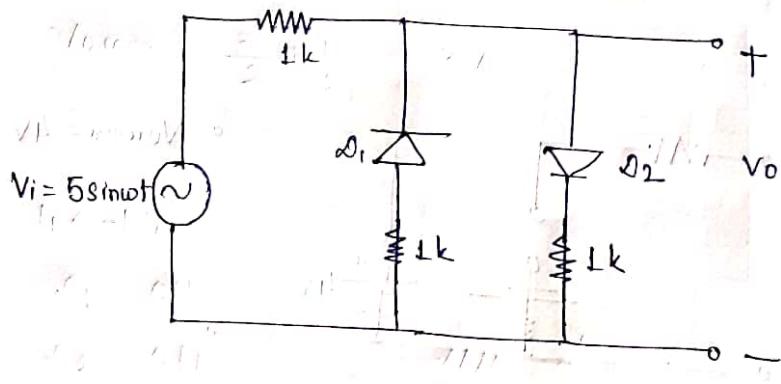


Sol I. Diode are Ideal

PHC [$0 < \omega t < \pi$]

$D_2 = \text{ON}$

$D_1 = \text{OFF}$

$$V_o = \frac{Vi}{2}$$

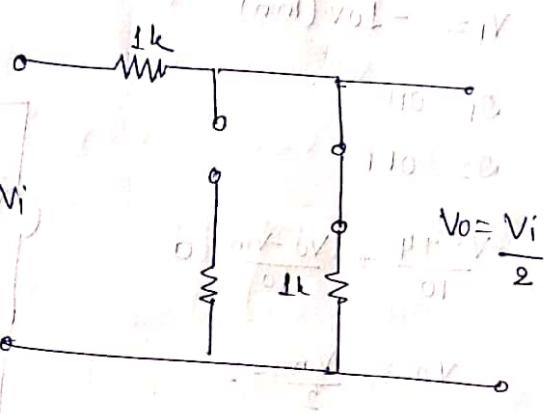


NHC [$\pi < \omega t < 2\pi$]


$D_1 = \text{ON}$

$D_2 = \text{OFF}$


$$V_o = \frac{Vi}{2}$$

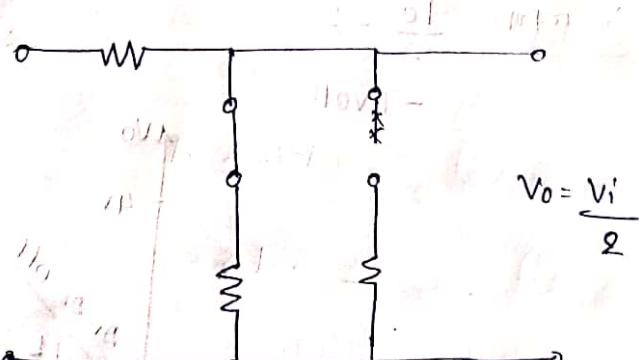

This is attenuator

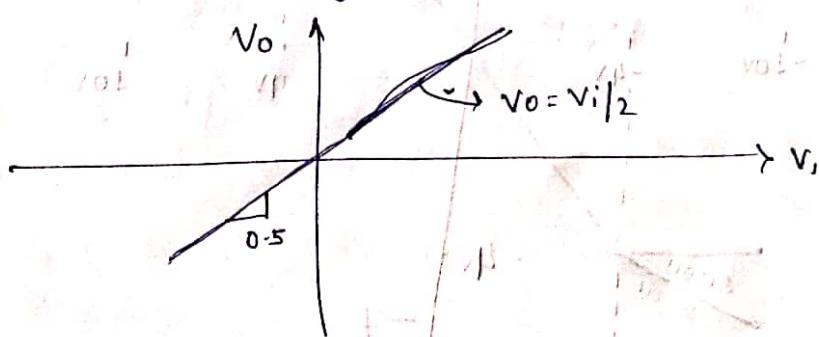

ii) Offset Voltage $\pm V$

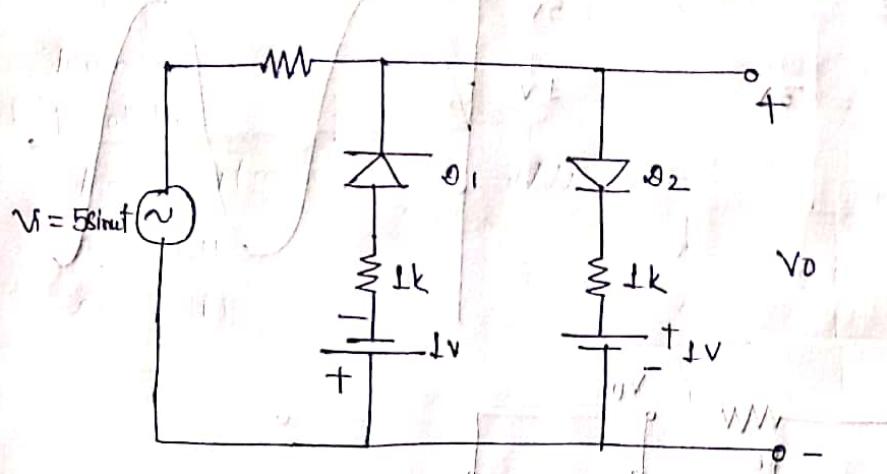

Initially, $V_S = 0.1V$

$$D_2 = f(\pm V)$$

$$D_2 = \text{off}$$

$$D_1 = f(-\pm V)$$


$$D_1 = \text{off}$$

$$V_O = V_I$$

$\left. \begin{array}{l} V_O \text{ always } V_I \\ \text{when reference} \end{array} \right\}$

Voltage is equal
to opposite
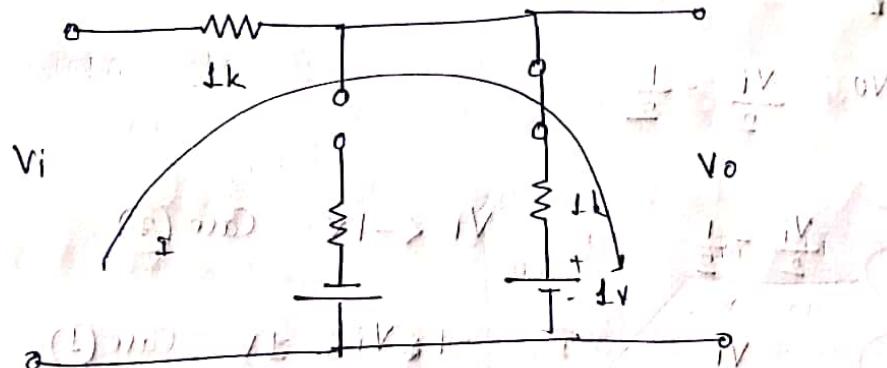
$$V_I > \pm V \quad D_2 = \text{ON} \quad D_1 = \text{OFF}$$



$$V_I - I \cdot \frac{1}{2} \cdot 1 = 0$$

$$V_I - 2 \cdot \frac{1}{2} = 1$$

$$I = \frac{V_I - 1}{2}$$

$$\begin{aligned} V_O &= I \times 1 + 1 \\ &= \frac{V_I - 1}{2} + 1 \end{aligned}$$


$$V_o = \frac{V_i}{2} + \frac{L}{2}$$

$$V_{o\max} = \frac{5}{2} + \frac{1}{2} = 3V$$

$$V_i < -1V$$

$$\theta_1 = ON$$

$$\theta_2 = OFF$$

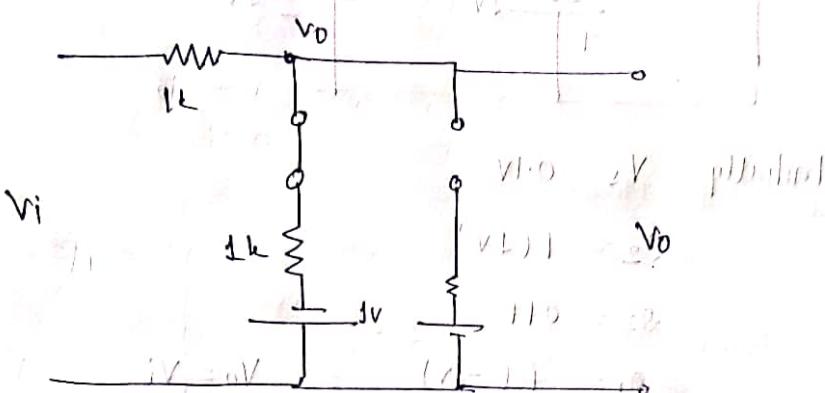

$$\text{By KVL, } \frac{V_o - V_i}{\frac{1}{L}} + \frac{V_o + L}{L} = 0$$

$$\Rightarrow 2\frac{V_o}{L} - V_i + 1 = 0$$

$$V_o = \frac{V_i}{2} - \frac{1}{2}$$


$$V_o =$$


$$\frac{V_i}{2} - \frac{1}{2} \quad ; \quad V_i < -1V \quad \text{Case ③}$$

$$V_i \quad ; \quad -1 \leq V_i < 1V \quad \text{Case ①}$$


$$\frac{V_i}{2} + \frac{1}{2} \quad ; \quad V_i \geq 1V \quad \text{Case ②}$$

$$1 + 1 + 1 = 3V$$

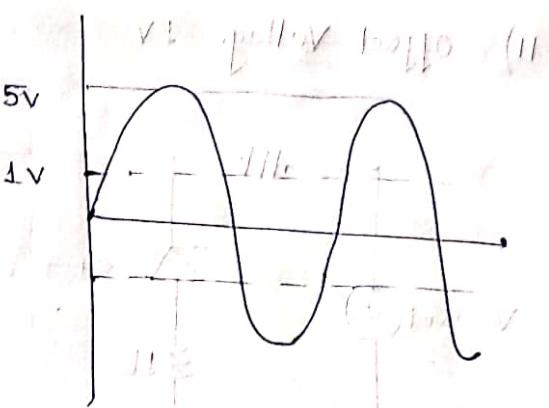

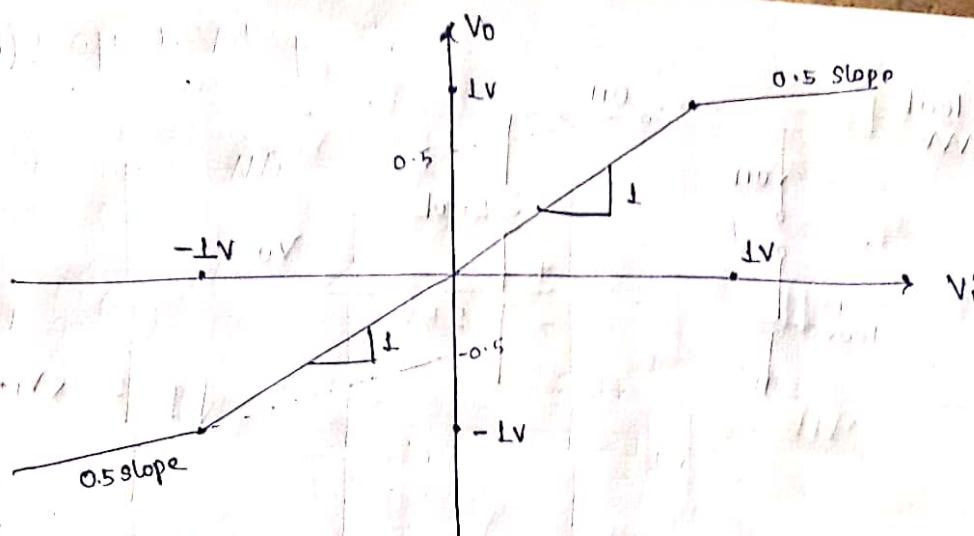

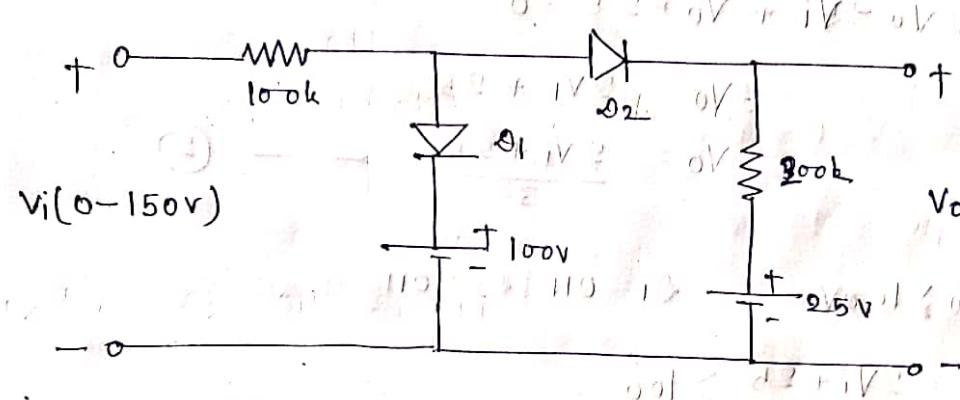H-W Que. Draw xfer characteristic for a given below figure




Sol: When $V_i = 0 \text{ V}$

$$D_1 = \text{off}, D_2 = \text{off}$$

$$V_o = 25 \text{ V} \quad \left. \begin{array}{l} \text{Series Resistance does not} \\ \text{affect Diode ON OFF} \end{array} \right\}$$

That is, when $0 < V_i < 25$

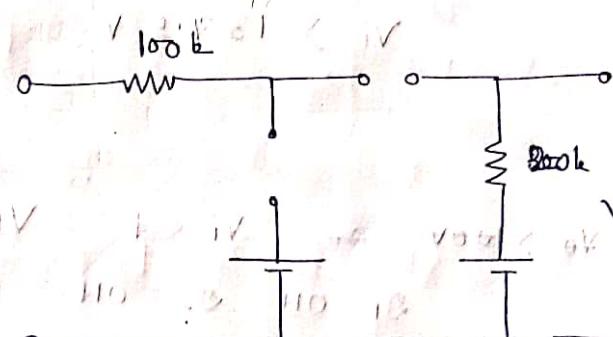

when $V_i > 25 \text{ V}$ $D_2 \text{ ON}, D_1 = \text{off}$

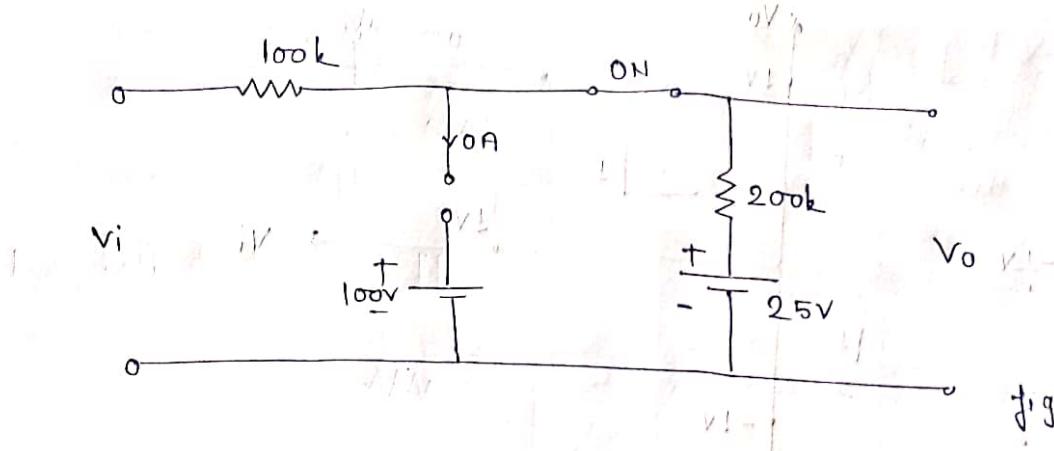


fig. $25 < V_1 < 137.5$

$$\frac{V_0 - 25}{200} + \frac{V_0 - V_1}{100} + 0 = 0$$

$$2V_0 - 25 + V_0 - V_1 = 0$$

$$3V_0 = 2V_1 + 25$$

$$V_0 = \frac{2V_1 + 25}{3} \quad (2)$$

(2) When $V_0 > 100V$ $\theta_1 = ON$ $\theta_2 = ON$

$$\frac{2V_1 + 25}{3} > 100$$

$$V_1 > \frac{275}{2}$$

$$V_1 > 137.5V$$


Hence fig (2)

$$25 < V_1 < 137.5V$$

(3) $V_0 > 100V$ or $V_1 < \pm 137.5$


$\theta_1 = ON$ $\theta_2 = ON$

$$V_0 = 100V$$

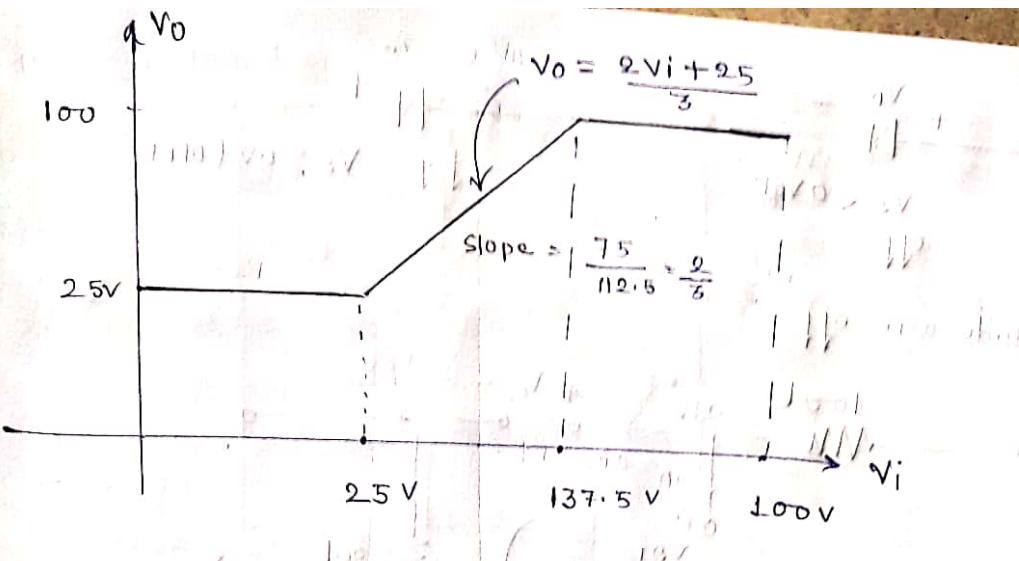

Concept of Diode

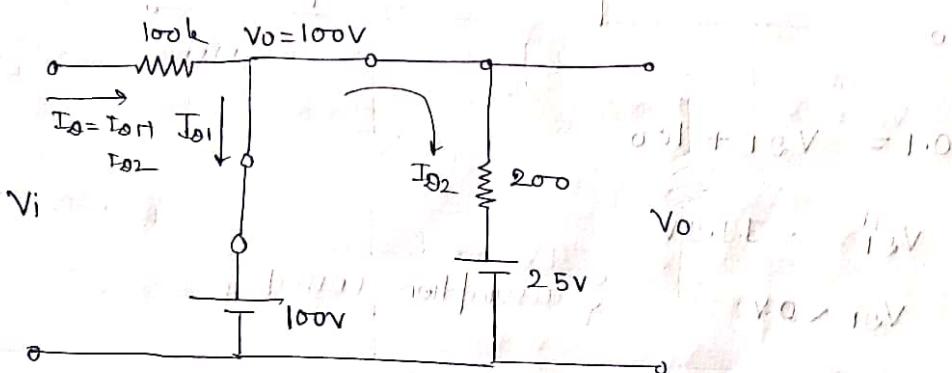Initially both diodes are ON $\Rightarrow \{$ Diode Current greater than 0A from plot?



$$200 I_{D2} = 75$$

$$I_{D2} = \frac{75}{200} = 0.375$$


$$I_{D1} + I_{D2} = \frac{V_o - V_i}{100} + \frac{V_o - 25}{200} = 0$$

If $V_i = 0.1$

$$I_{D1} + I_{D2} = -\frac{100 + 0.1}{100} + \frac{100 - 25}{200}$$

$$= -0.99 \text{ mA}$$
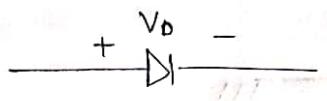
$$I_{D1} = -1.374 \text{ mA} \quad \{ \text{Invalid date assumption} \}$$



$V_d < 0 \text{ volt}$
off


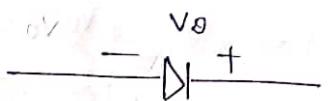


fig. $V_d > 0 \text{ v} (\text{off})$

Let both diode are off.

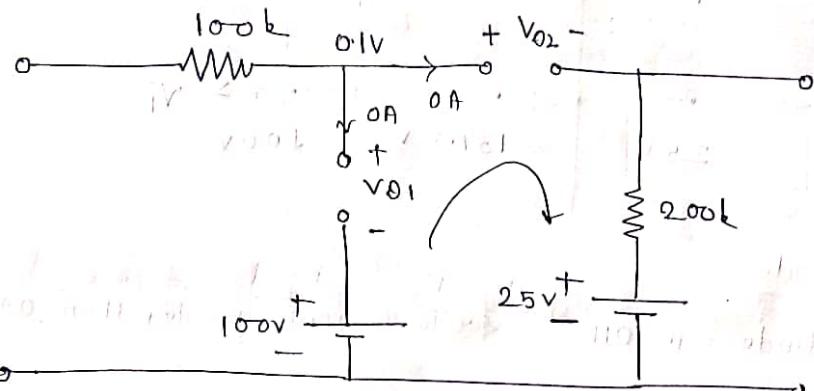

$$0.1 = V_{d1} + 100$$

$$V_{d1} = -99.9 \text{ V}$$

$V_{d1} < 0 \text{ v}$ { assumption correct }

also,


$$0.1 = V_{d2} + 25$$

$$V_{d2} = -24.9 \text{ V}$$

$V_{d2} < 0$ { assumption is correct }

Both diode are off for $V_i = 0.1 \text{ v}$

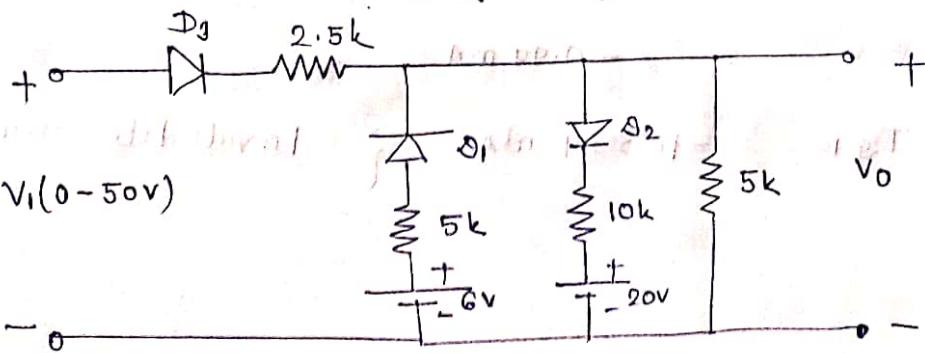Ques. Draw Xfer characteristic for a given below figure.



{ HW D₂ off assume

D₁ on
D₃ off

V_i(0-50V)

I_{D1}>0 V_{D3}<0V

Sol:

D₂ off due to 20V

D₁ ON due to 6V

D₃ off due to 6V & Small Value of V_i

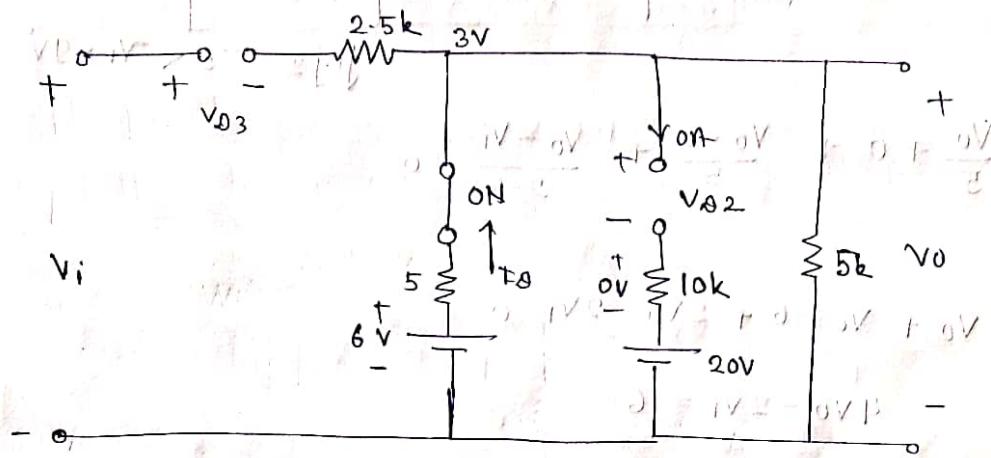


fig 1 0 < V_i < 3V

By Voltage division

$$V_O = \frac{6 \times 5}{5+5} = 3V \quad \text{Hence } 3 + V_{D2} + 20 = 0$$

$$V_{D2} = -17V$$

$$D_2 = \text{off}$$

$$V_i = V_{D3} + 8V$$

$$V_{D3} = V_i - 3$$

$$= 0.1 - 3$$

$$V_{D3} = -2.9V \quad \{ D_3 = \text{off} \}$$

D₃ will change (ON) first due to 3V in right of D₃

Case: V_i > 3V D₃ = ON Hence fig 4: 0 < V_i < 3V

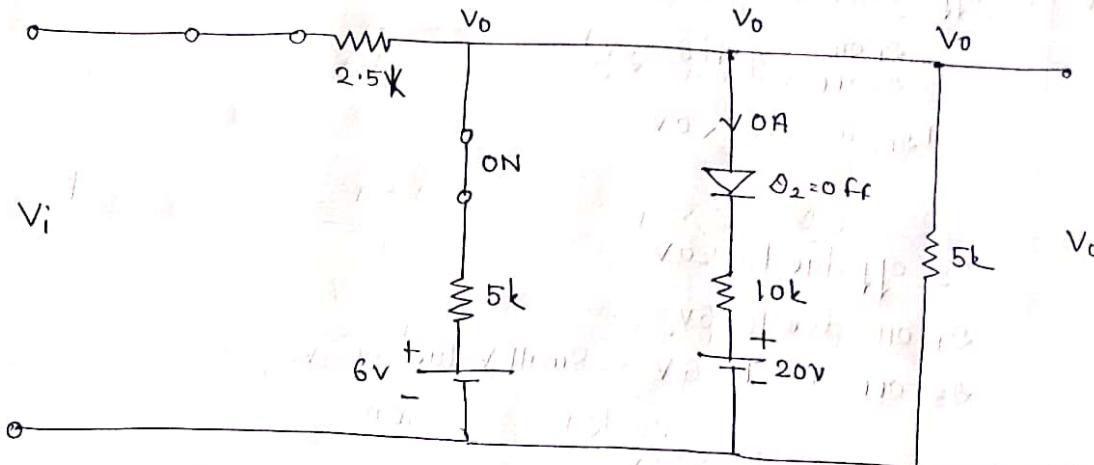


Fig 2 $3 < V_i < 9V$

$$\frac{V_0}{5} + 0 + \frac{V_0 - 6}{5} + \frac{V_0 - V_i}{2.5} = 0$$

$$\Rightarrow V_0 + V_0 - 6 + 2V_0 - 2V_i = 0$$

$$\Rightarrow 4V_0 - 2V_i = 6$$

$$2V_i = 4V_0 - 6$$

$$V_0 = \frac{2V_i + 6}{4}$$

Now D_1 to be off

$$V_0 > 6V$$

$$D_2 = \text{off}$$


D_3 ON

D_1 OFF

$$\frac{2V_i + 6}{4} > 6$$

$$2V_i > 24 - 6$$
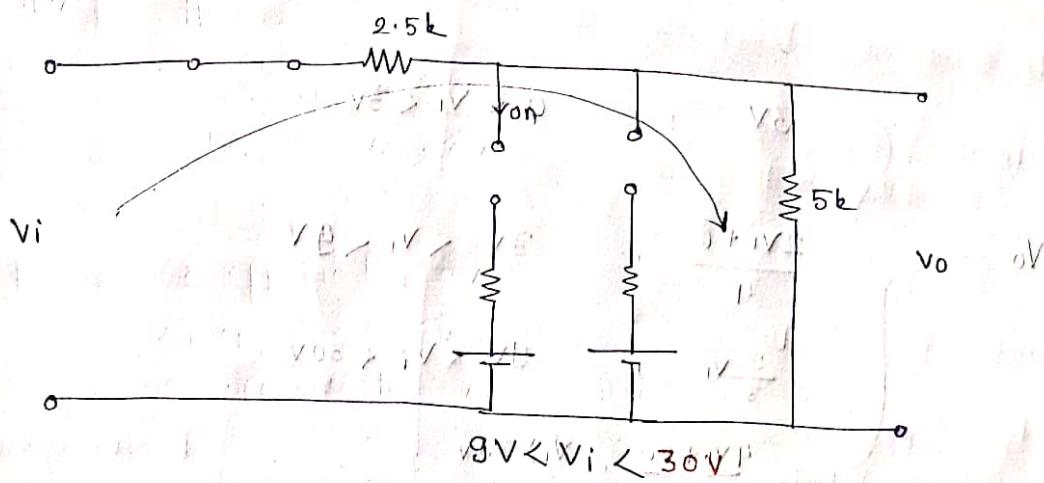
$$V_i > 9V \quad \text{Hence Fig 2 since } 3 < V_i < 9V$$




$$Vo = \frac{Vi \times 5}{7.5}$$

$$Vo = \frac{2}{3} Vi$$

Case 1 $Vo > 20\text{ volt}$ to ON Q2

$$\frac{2}{3} Vi \geq 20$$
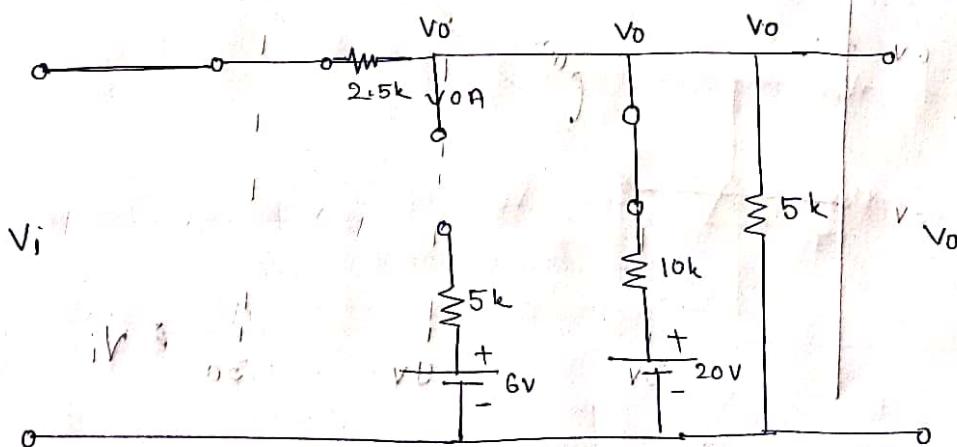
$$Vi > 30V \text{ Hence fig 3 } 9V < Vi < 30V$$



$$\frac{Vo}{5} + \frac{Vo - 20}{10} + \frac{Vo - Vi}{2.5} = 0$$

$$\Rightarrow 2Vo + Vo - 20 + 4Vo - 4Vi = 0$$

$$7Vo = 4Vi + 20$$

$$Vo = (4Vi + 20)/7$$


$$V_o = \begin{cases} 3V & ; 0 < V_i < 3V \\ \frac{2V_i + 6}{4} & ; 3V < V_i < 9V \\ \frac{2}{3}V_i & ; 9V < V_i < 30V \\ \frac{4V_i + 20}{7} & ; V_i > 30V \end{cases}$$

$$V_{o(\text{max})} = \frac{4 \times 50 + 20}{7} = 31.42V$$

$$V_i = 9V$$


$$V_o = \frac{2 \times 9 + 6}{4} = 6V$$

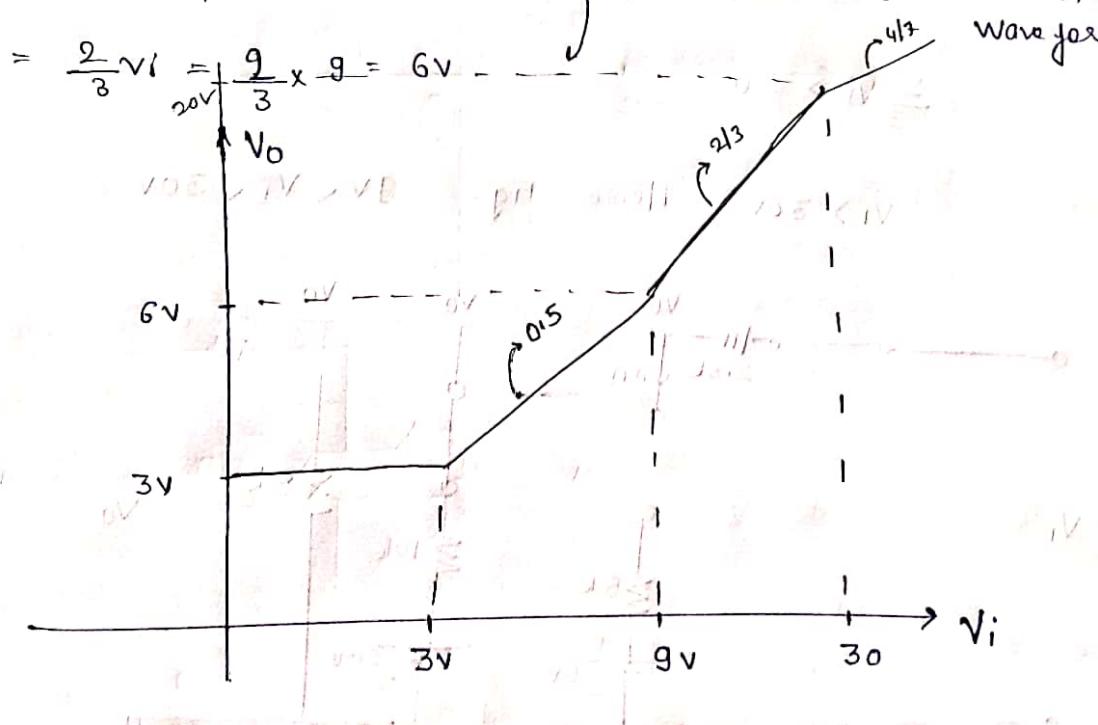also $V_o = \frac{2}{3}V_i = \frac{9}{3} \times 9 = 6V$



* Clipper Circuit (Using Zener diode)

①

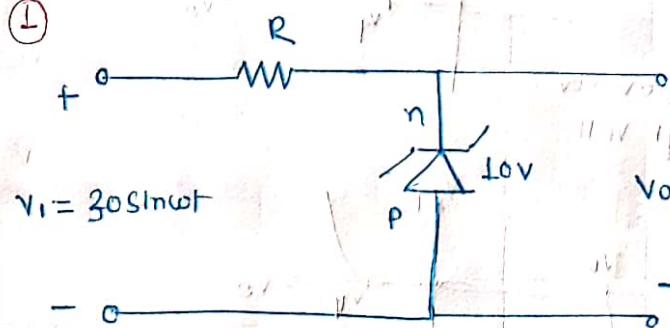

Reverse Bias Breakdown Voltage = 10V

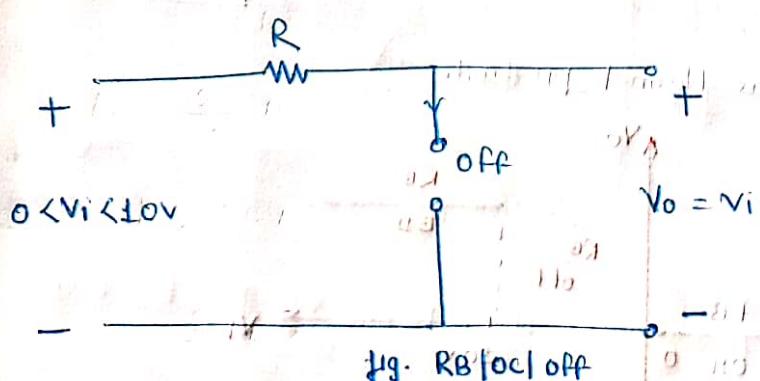


fig. RB | off

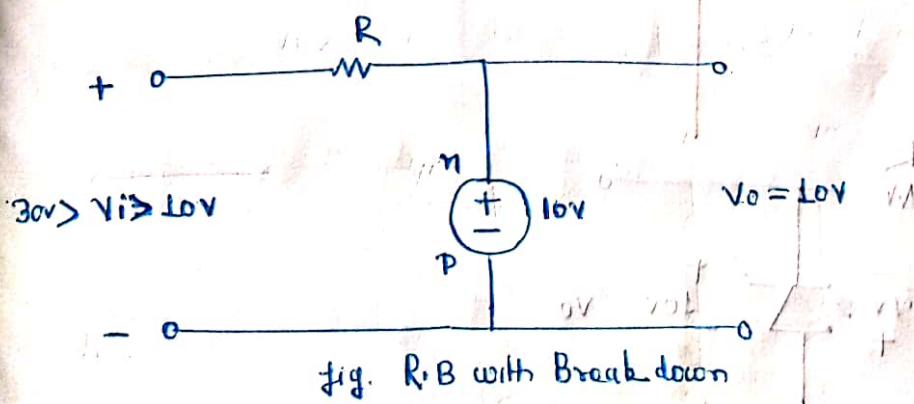


fig. R.B with Breakdown


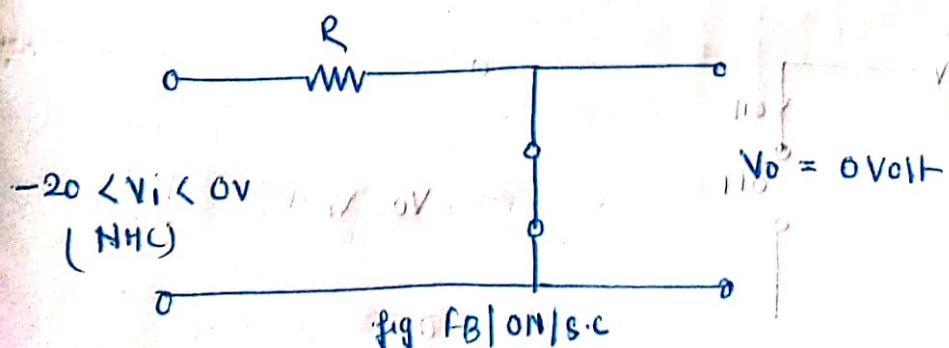


fig. FB | on / s.c

Normal p-n diode characteristics

Low Level doping

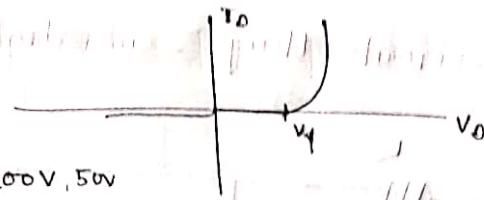
Breakdown Voltage 100V, 50V
Very High Volt-






Zener diode characteristics





High Level doping

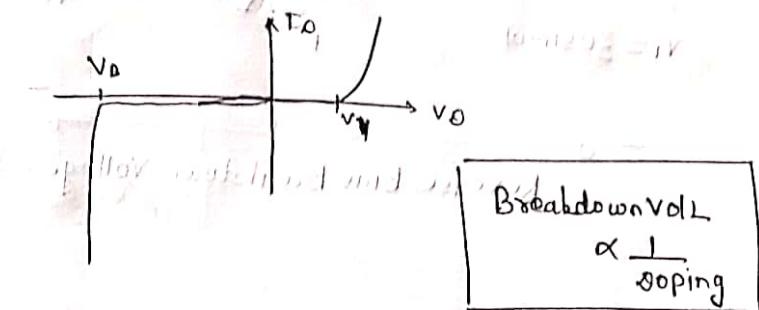Breakdown Voltage
5V, 6V, 10V
low voltage




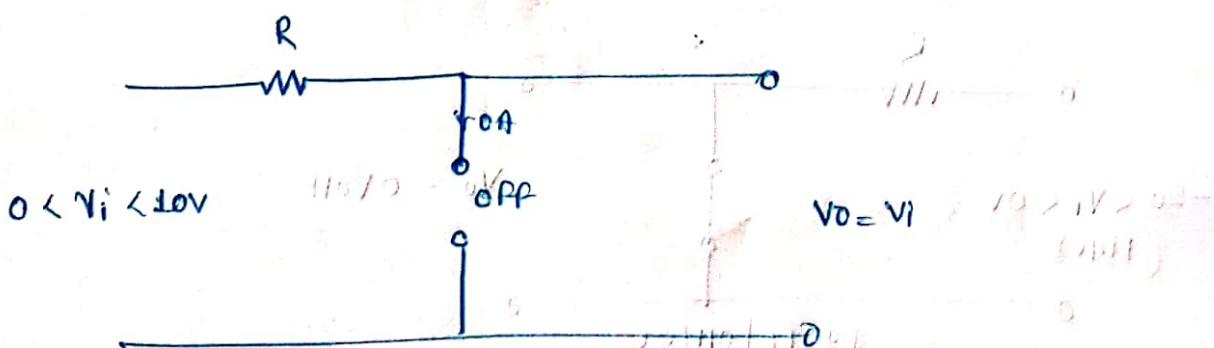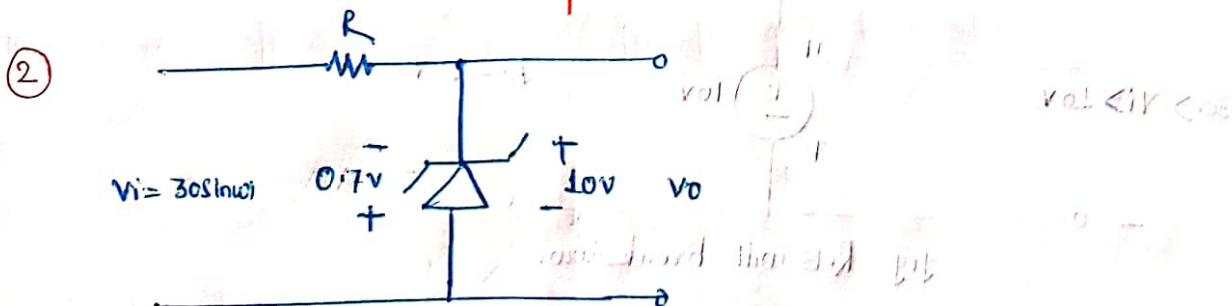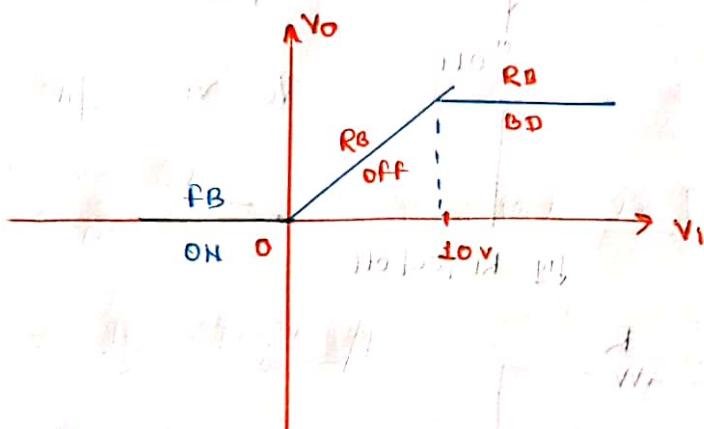- Zener diode can work as Normal p-n diode



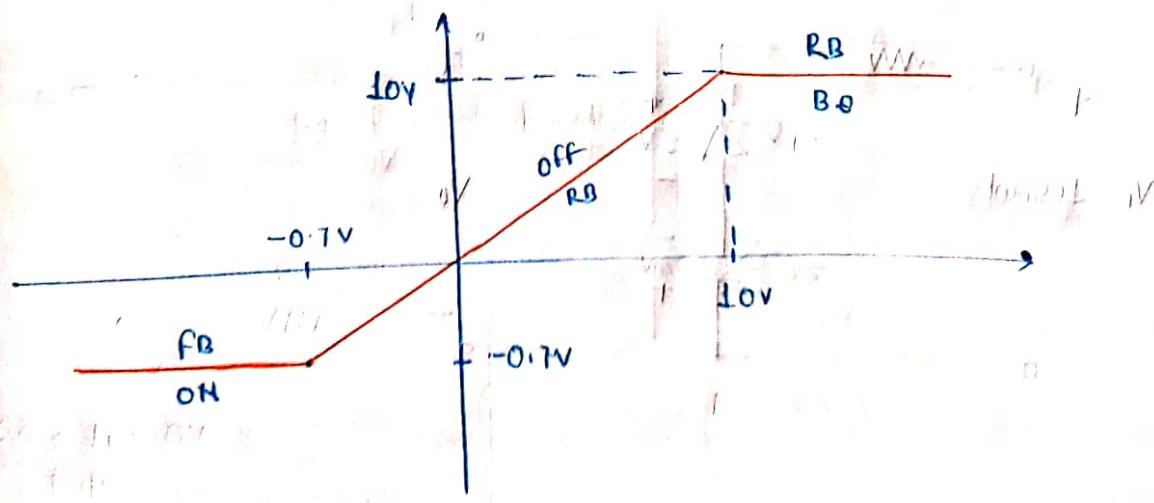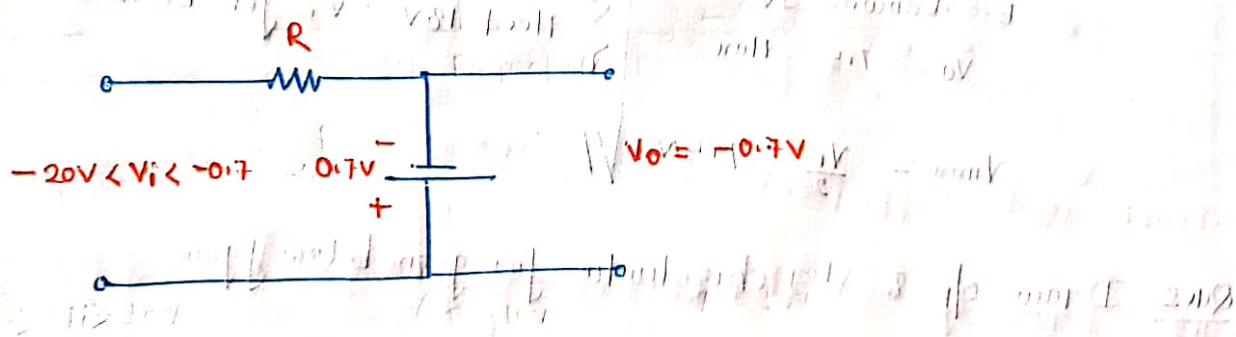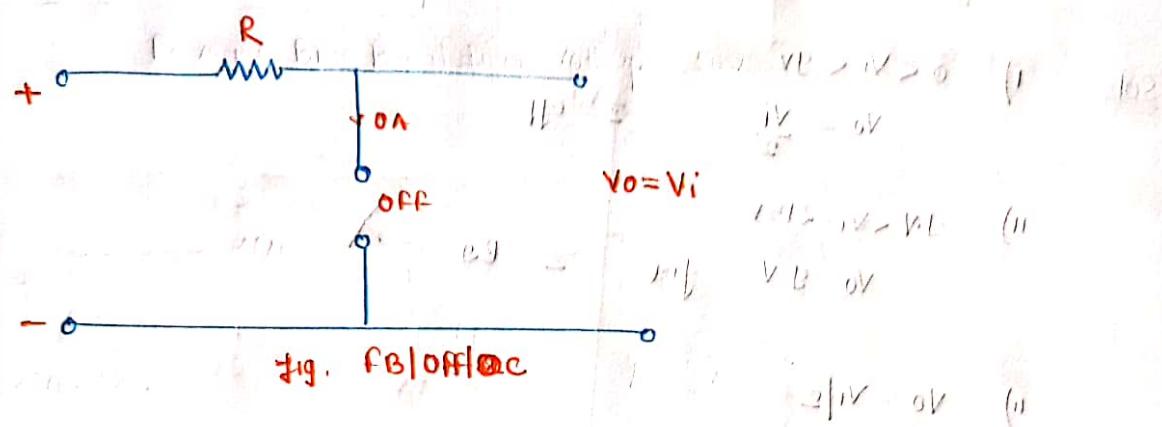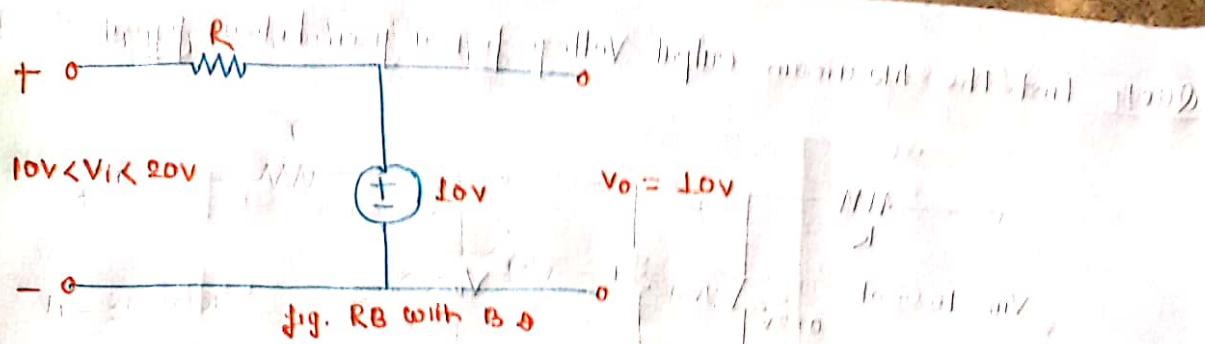

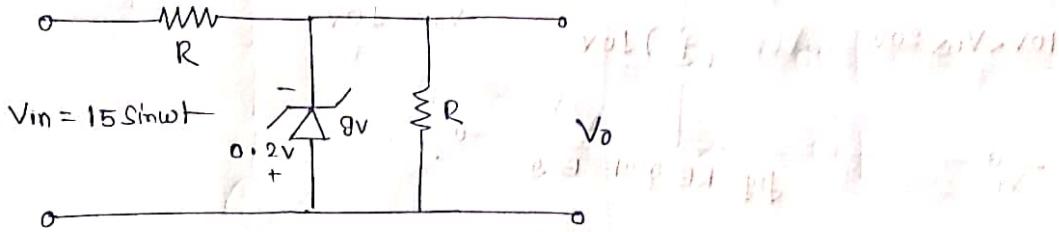Ques1 find the Maximum Output Voltage for a given below figure.



Sol

$$i) \quad 0 < Vi < 9V$$

$$Vo = \frac{Vi}{2} \quad Z = \text{off}$$

$$ii) \quad 9V < Vi < 15V$$

$$Vo = 9V \quad \text{for } Z = BZ \quad X$$

$$iii) \quad Vo = Vi/2$$


Breakdown = 9V


$$Vo = 7.5 \text{ Max}$$

Need 18V = Vi for breakdown

$$V_{max} = \frac{Vi}{2} = 7.5V //$$

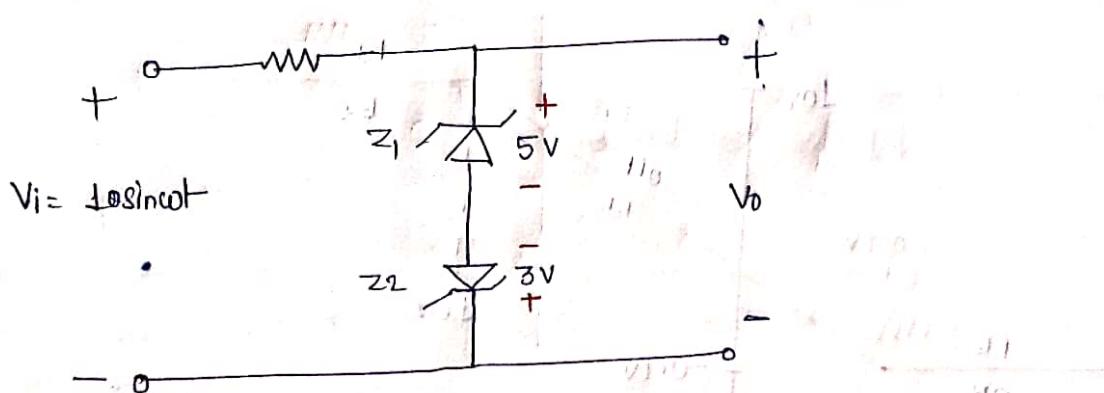Ques2 Draw o/p & x for characteristic for given below figure



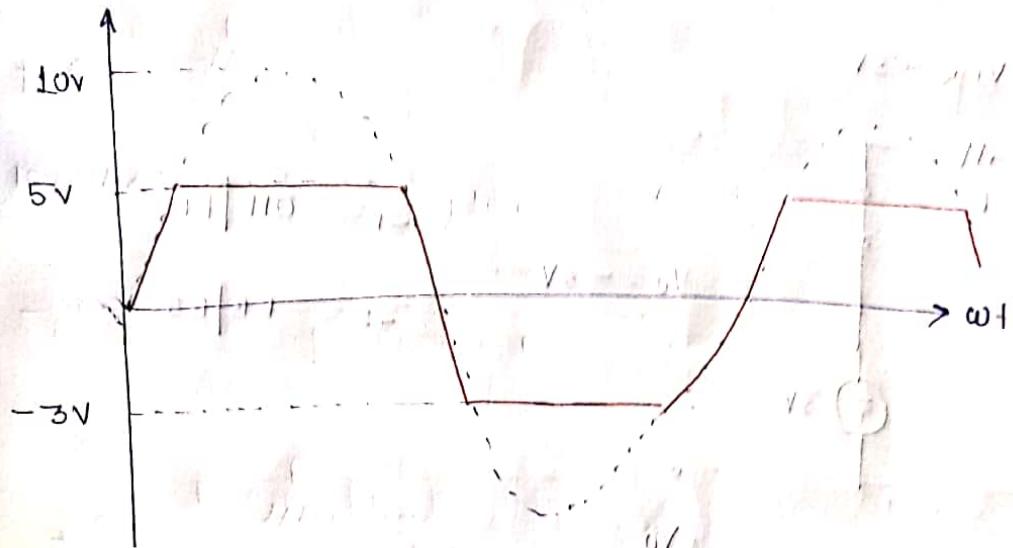


Ideal Zener diode (No cut-in Voltage given)

- i) $f_B | ON | S.C$
- ii) $R_B | OFF | S.C$
- iii) $R_B | B.O$

Case I $0 < V_i < 5V$ (PHC)

$Z_1 = OFF$ $R_B | OFF$


$Z_2 = ON$ $f_B | ON$

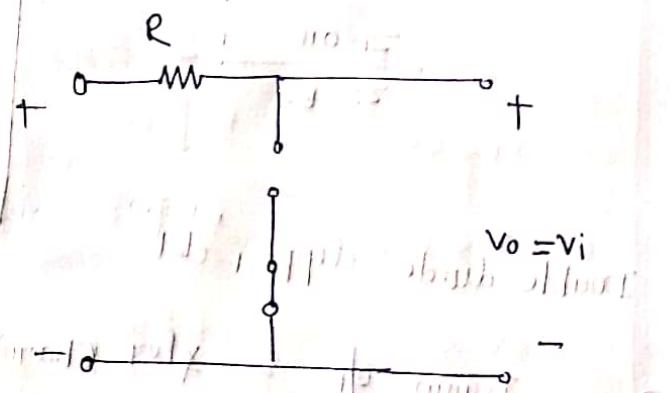

Case II $5 < V_i < 10V$ (PHC)

$Z_1 = R_B (B.O)$


$Z_2 = ON (f_B)$

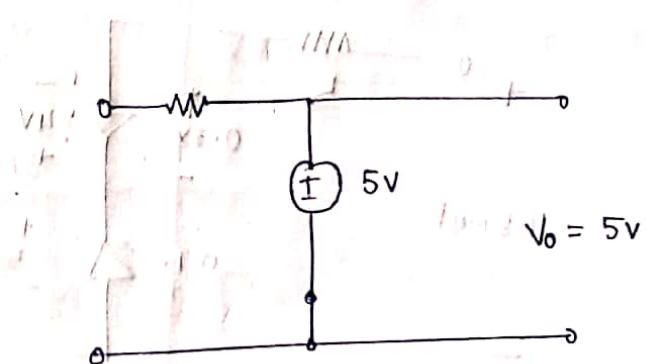


Case III $-3V < V_i < 0V$ (NHC)

$Z_1 = f_B | ON$

$Z_2 = R_B | OFF$

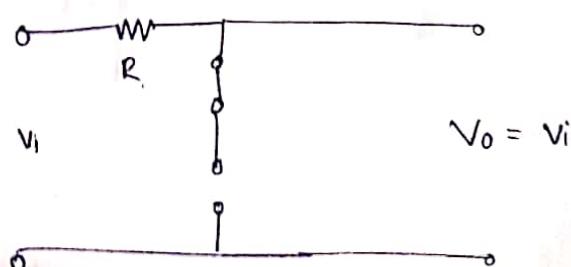


Casey $-10 < v_i < -3V$

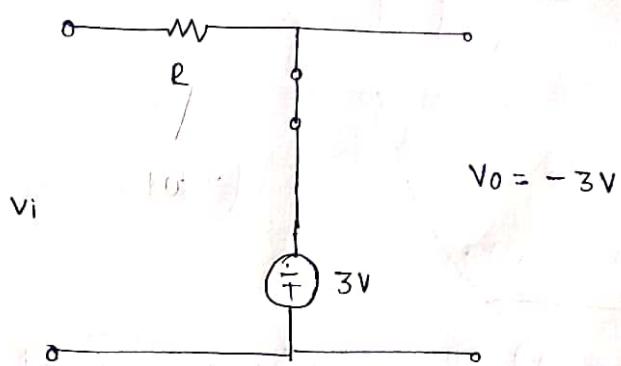


$$Z_1 = \text{ON} | f_B$$


$$Z_2 = R_B | B_D$$

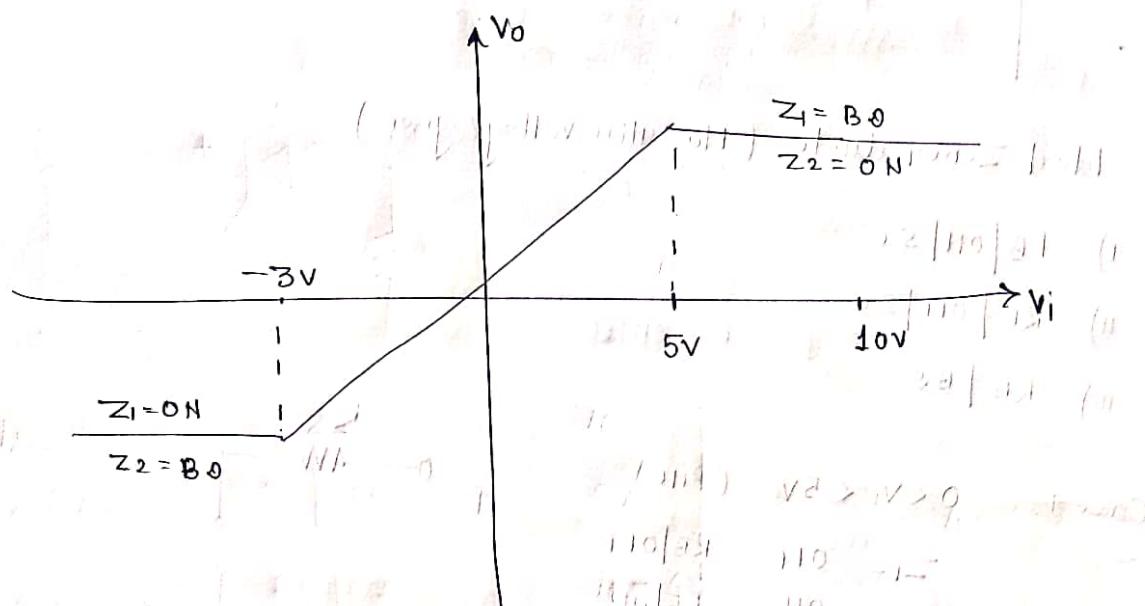


Double diode clipper circ


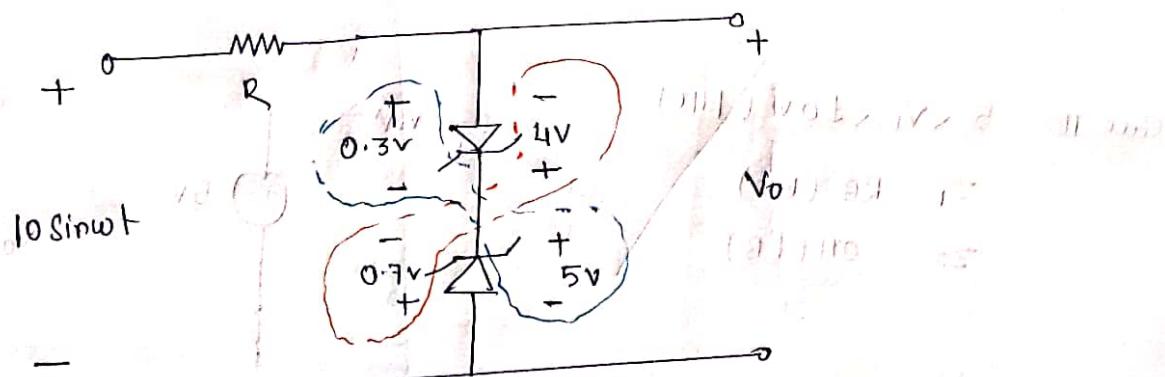
Ques Draw o/p vs x for characteristics for a given below figure.



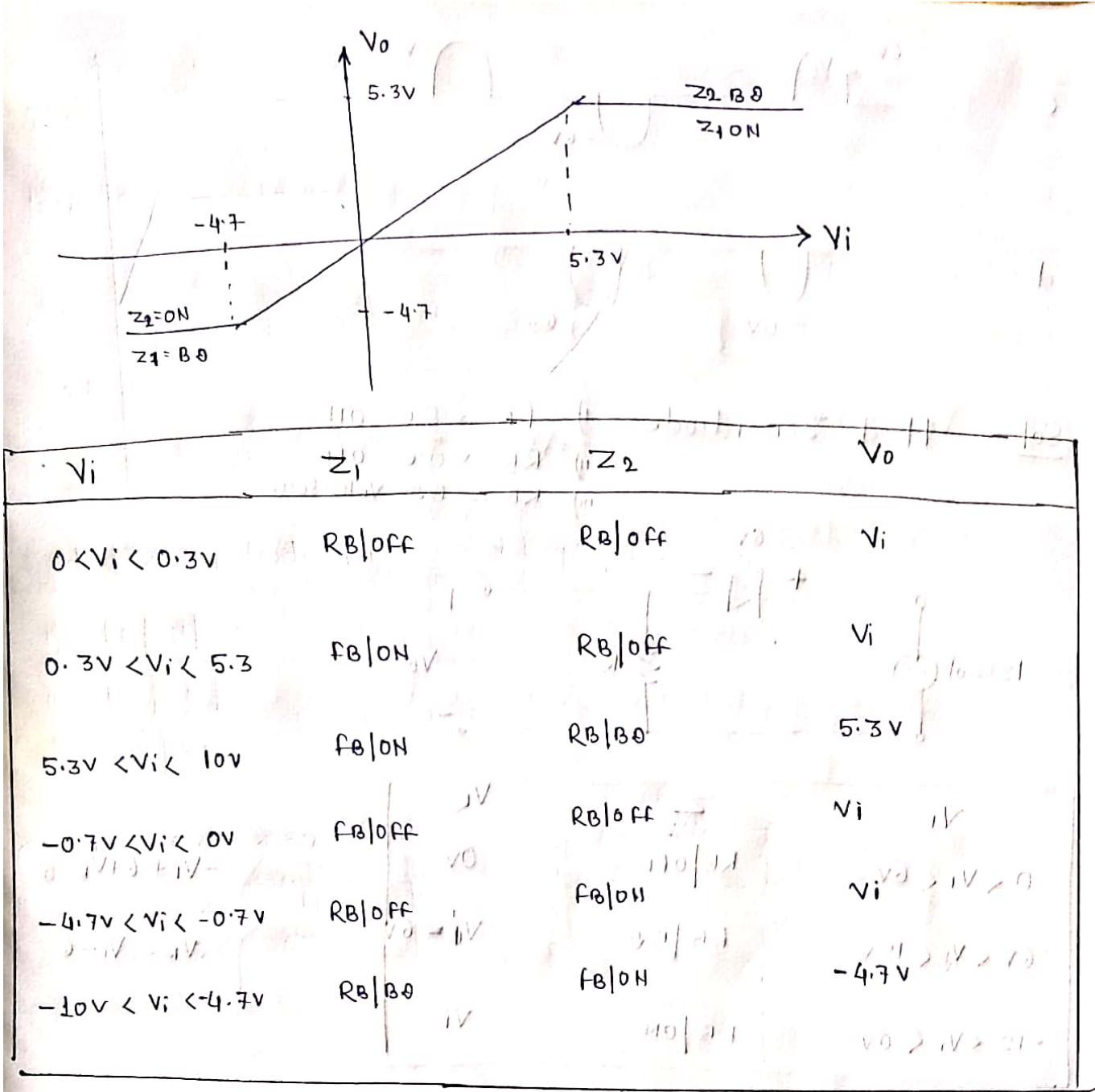

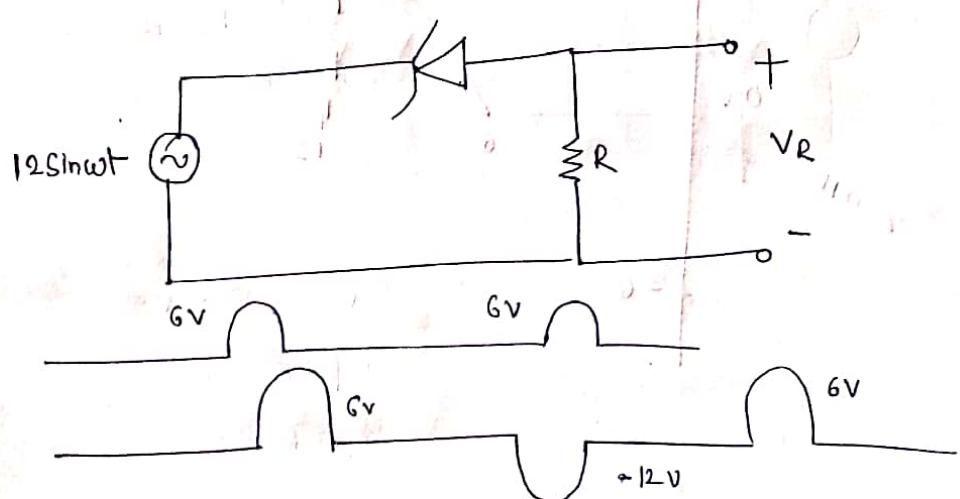
Que. for the Circuit shown in below fig., assume Zener diode is ideal with ZB voltage 6V. The waveform across R is



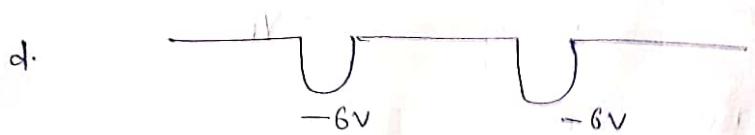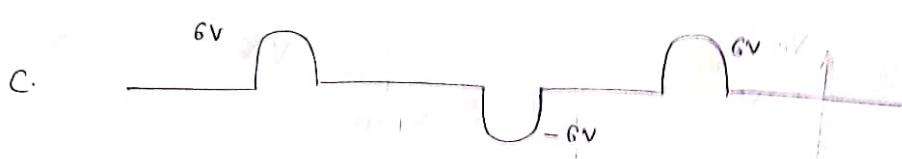


Sol: Ideal Zenerdiode

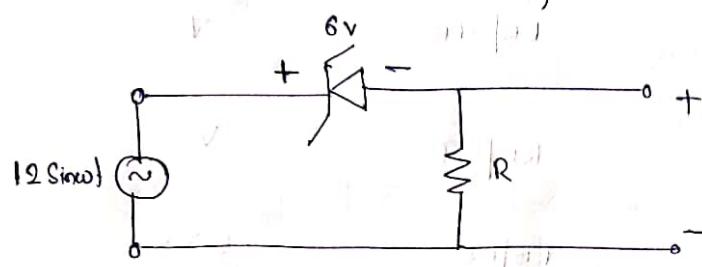
- $f_B \rightarrow B.C \text{ ON}$
- $R_B \rightarrow O.C \text{ OFF}$
- $R_B = B.D \text{ NOT SENSE}$




V_i	Z	V_R
$0 < V_i < 6V$	$R_B OFF$	$0V$
$6V < V_i < 12V$	$R_B B.D$	$V_R = 6V$
$-12 < V_i < 0V$	$R_B ON$	V_i
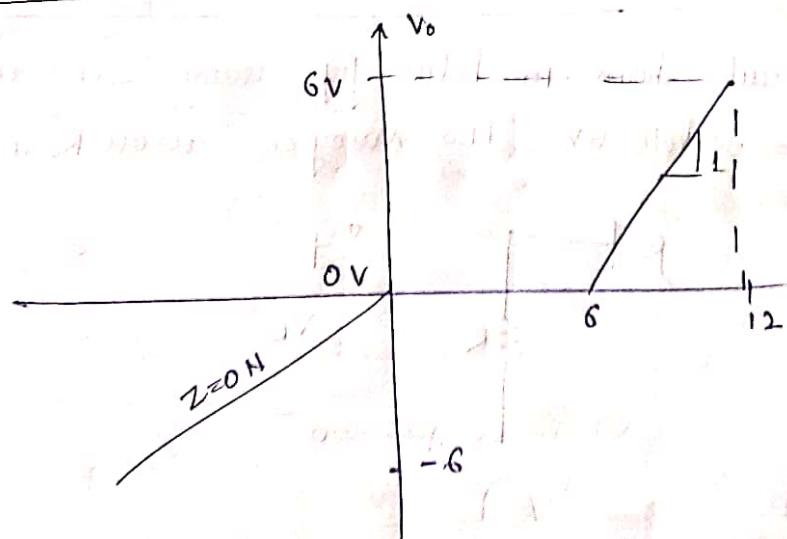
$$\begin{cases} -V_i + 6 + V_R = 0 \\ V_R = V_i - 6 \end{cases}$$



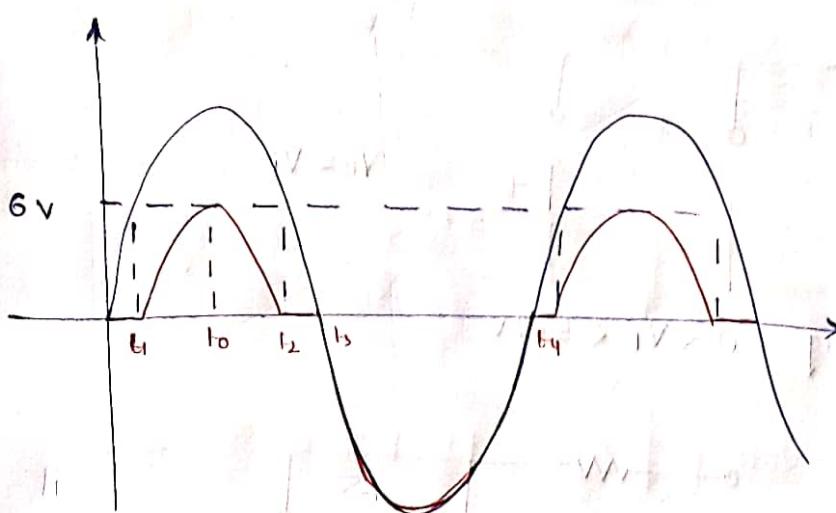

Q14. A clipper circuit shown below

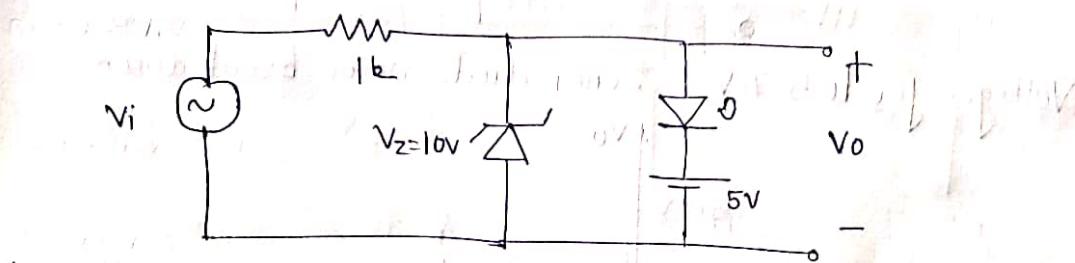


Assuming forward voltage drop of diode to be 0.7V.
Input o/p characteristic of cbt is

$$S_1 \quad V_{y(0)} = 0.7V$$

$$V_{y(z)} = 0.7V$$


$$V_{z}(z) = 10V$$

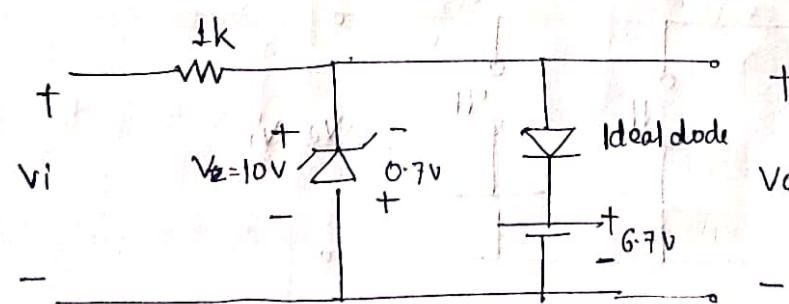

Initially. $V_i = 0.1V$

$D =$ open circuit / off due to 6.7V


$Z =$ off / 0V due to small V_i

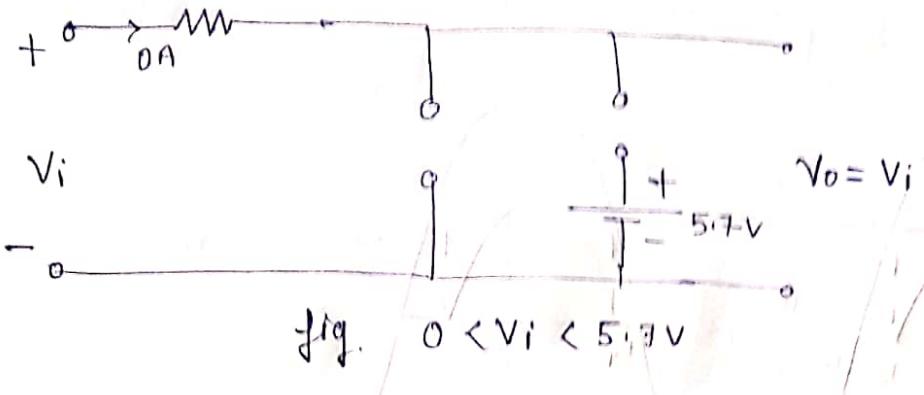


when $V_i > 5.7V$

$$\theta = \text{ON}$$


$$z = \text{OFF}$$

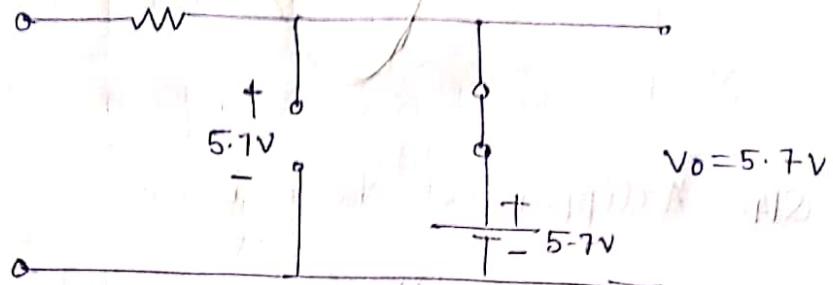

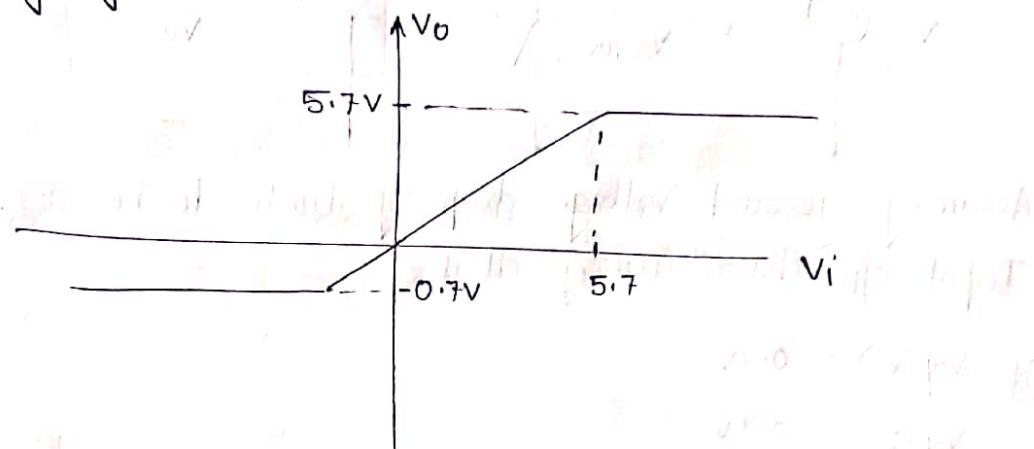
Voltage fix to 5.7V Zener diode never breakdown




when $-0.7V < V_i < 0V$

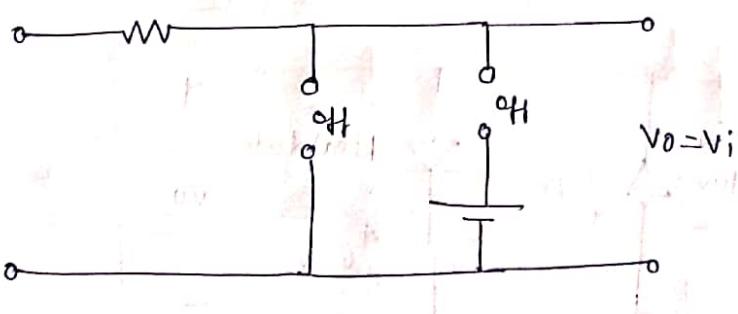

when $V_i < -0.7V$

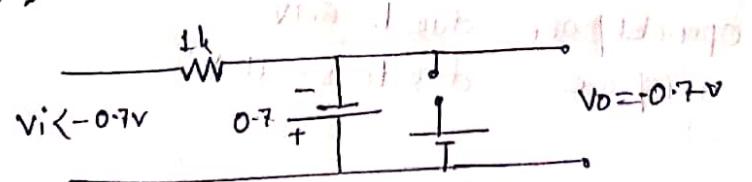

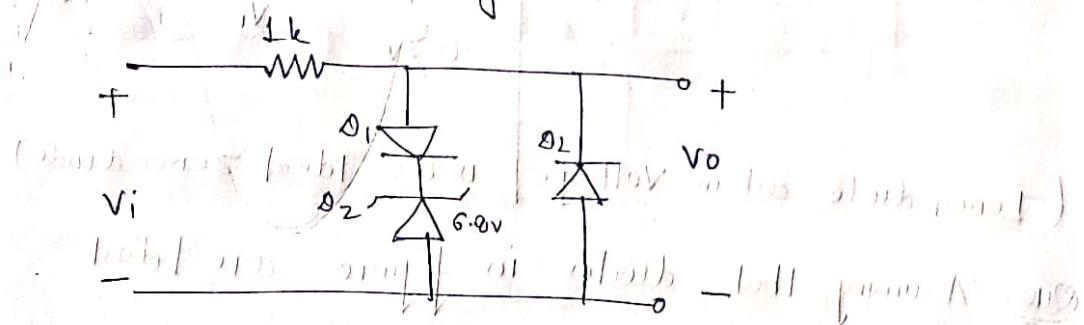Q12. In the following Limiter Circuit an Input Voltage $V_i = 10 \sin 100\pi t$ is applied. Assume that diode drop is 0.7V when it is forward biased. The Zener breakdown voltage is 6.8V.



Sol When $V_i = 0.7V$

$$V_o = V_i$$

when $V_i > 0.7V$

$$V_o = V_i$$

when $0.7V < V_i < 7.5V$

$$V_i = V_o$$

when $V_i > 7.5V$ ($V_{min} = 10V$)

$Z = \text{breakdown}$

$$V_o = 7.5V$$




$-0.7V < V_i < 0V$


$$V_o = V_i$$

$V_i > -0.7V$ ($V_{min} = -10V$)

$D_2 = \text{ON}$


$$V_o = -0.7V$$

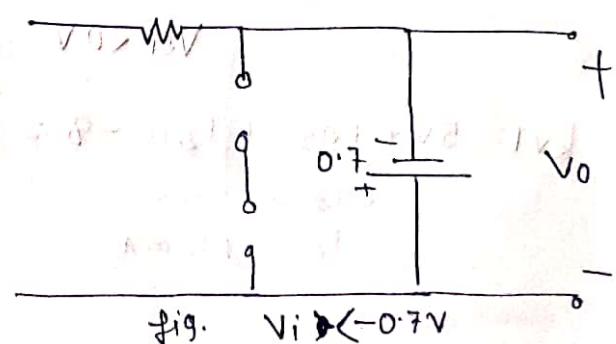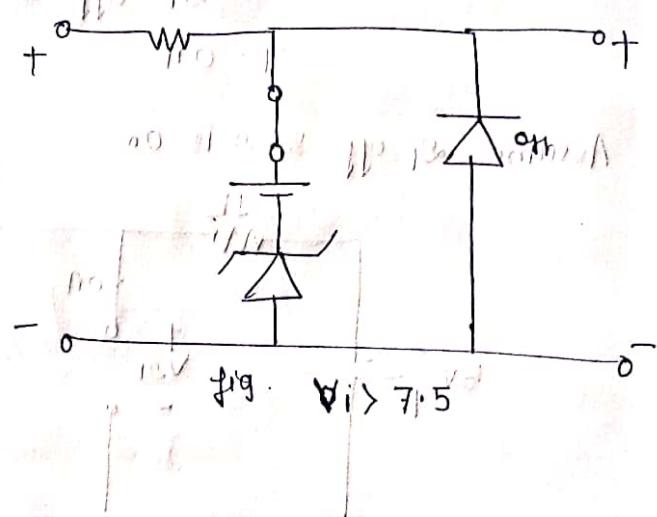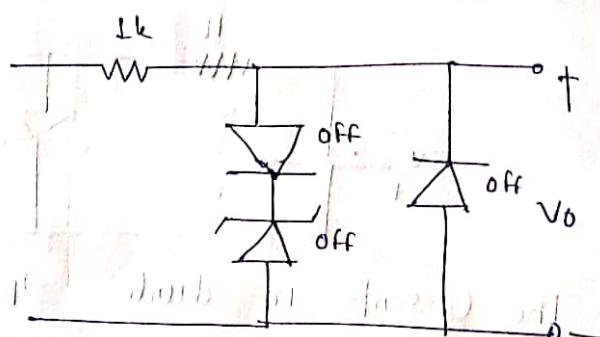

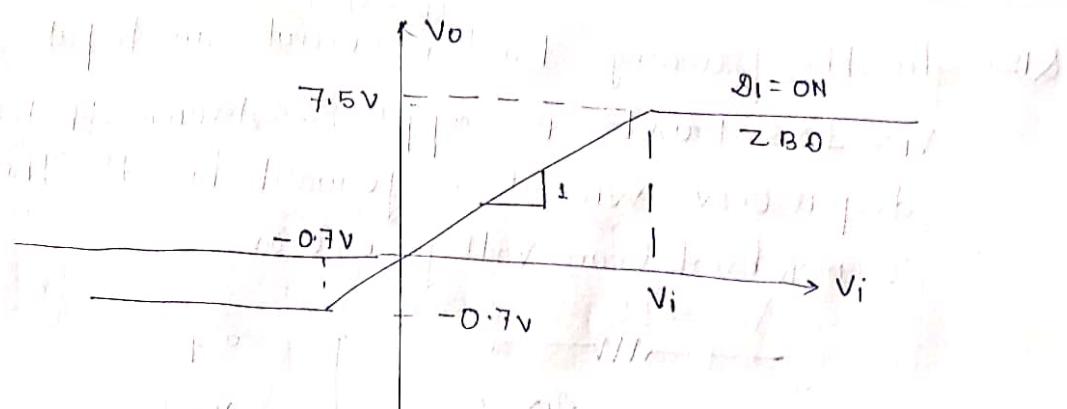

(-Zener diode cut-in Voltage is 0V Ideal zener diode)

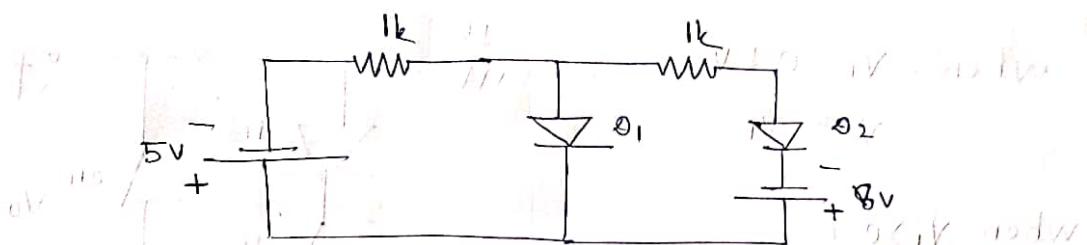Que. Assuming that diodes in figure are ideal




The Current in diode D_1 in (mA) is _____

Sol. Prediction: D_2 on due to -8V

D_1 off due to $-8V < -5V$

$$I = 0A$$

Assume D_1 off & D_2 is on

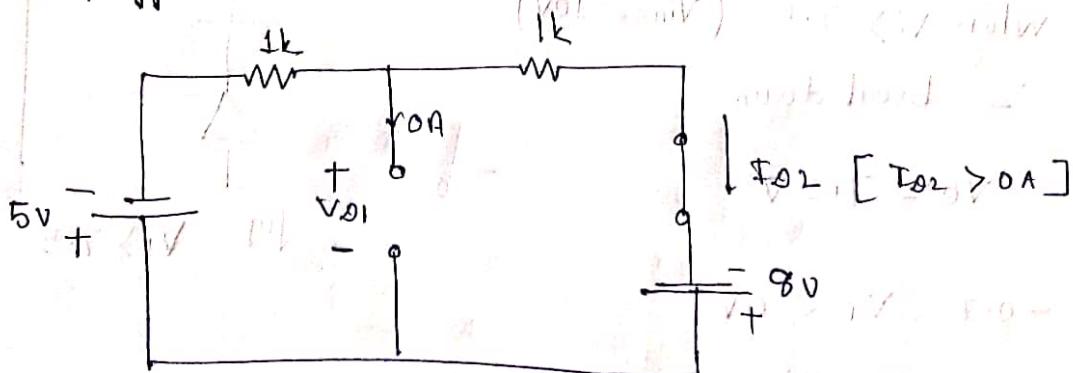

$$V_{o1} < 0V$$

$$kv1: 5V + I_{D2} + I_{D2} - 8 = 0$$

$$2I_{D2} = 3$$

$$I_{D2} = 1.5 \text{ mA}$$


$$V_{01} \neq +5 + 1 \times I_{02} = 0$$

$$V_{01} = +6.5 \text{ V}$$

$V_{01} < 0$ Hence prediction false

Note :- If prediction correct & another is wrong then whole prediction false.

Que.

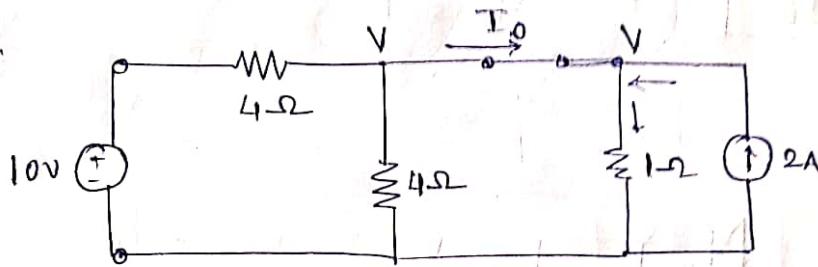

nodeal

$$\frac{V-10}{4} + \frac{V}{4} + \frac{V}{1} - 2 = 0 \quad \text{---(1)}$$

$$\frac{V}{2} + V = 2 + \frac{10}{4}$$

$$\Rightarrow 3V = 18/2$$

$$V = 6 \text{ Volt}$$

OR

$$\frac{V-10}{4} + \frac{V}{4} + I_0 = 0 \quad \text{---(2)}$$

$$\frac{V}{1} - 2 - I_0 = 0 \quad \text{---(3)}$$


All three eqn are correct

$$I_0 = \frac{V-2}{1\Omega} = 3A - 2A \\ = 1A$$



Q -
I ≠ 0
I = unknown
between
short terminals

OR

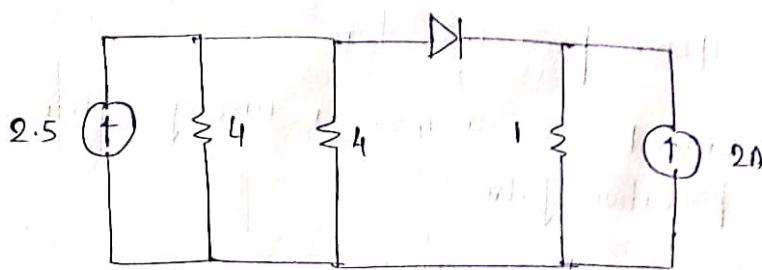By using Source Transformation in left & Right side.



Again Source Transformation

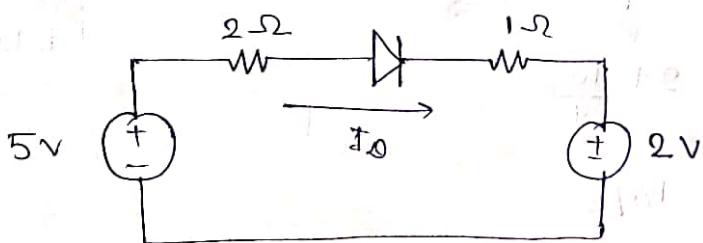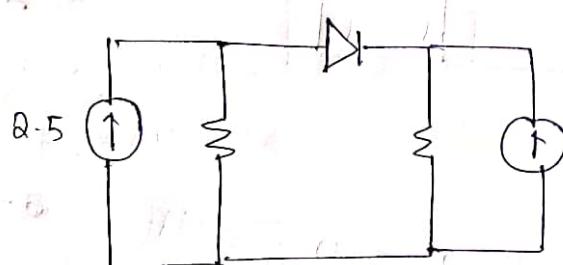


$$-5 + 3I_0 + 2 = 0$$


$$3I_0 = 3$$

$$I_0 = 1 \text{ A} \parallel$$

OR


By Thevenin

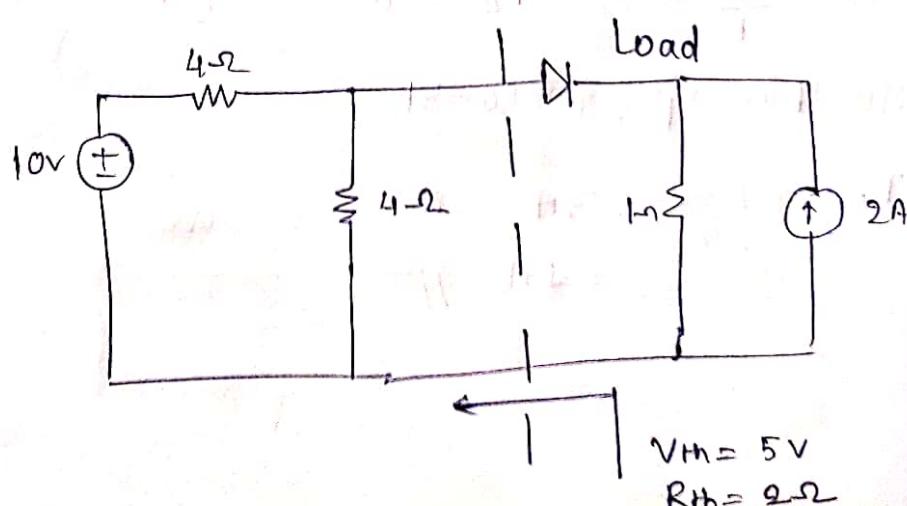

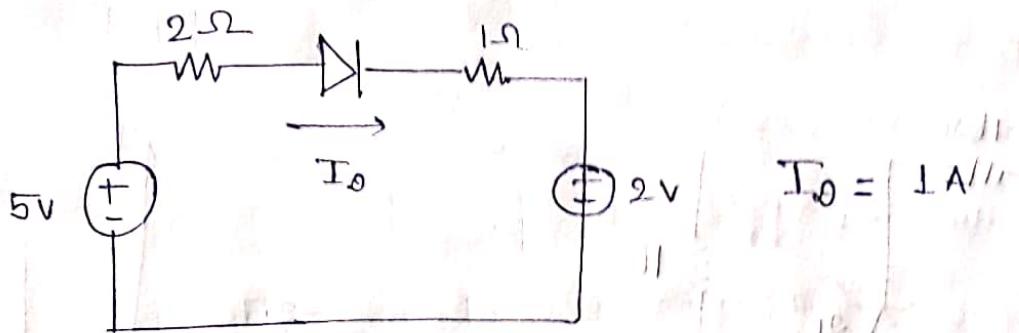


$$I_D = 1A/1\Omega$$

2.13
Ques 20

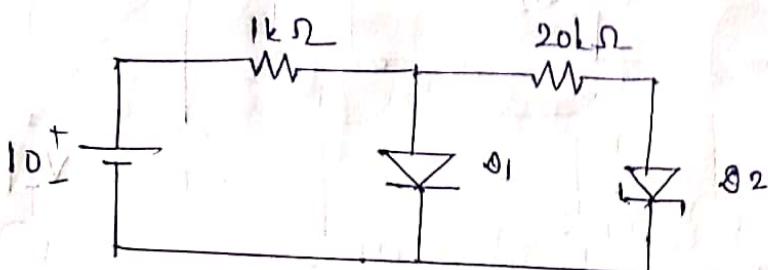

Prediction:

If both D1 and D2

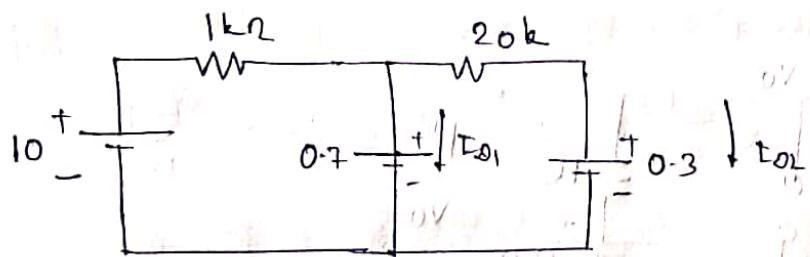

$$I_{D1} + \frac{0.7 - 10}{1k\Omega} + \frac{20 \cdot 0.7 - 0.3}{20k\Omega} = 0$$

$$I_{D2} = \frac{0.7 - 0.3}{20k\Omega} \leq +ve \quad \text{Hence } D2 \text{ on}$$

$$I_{D1} = +9.3 - \frac{0.4}{20k\Omega}$$

$$= +ve \quad (\text{D1 off})$$

Prediction Cound opt A

If D2 on D1 off

I_{D2} :-

$$-10 + 21I_{D2} + 0.3 = 0$$

$$21I_{D2} = 10 - 0.3$$

$$I_{D2} = +ve$$

V_{D1} :-

$$-10 + I_{D2} + V_{D1} = 0$$


$$V_{D1} = 10 - I_{D2}$$

= +ve

Wrong predn.

H. 40
Q 21, 24, 25, 23

Q17.
Sol

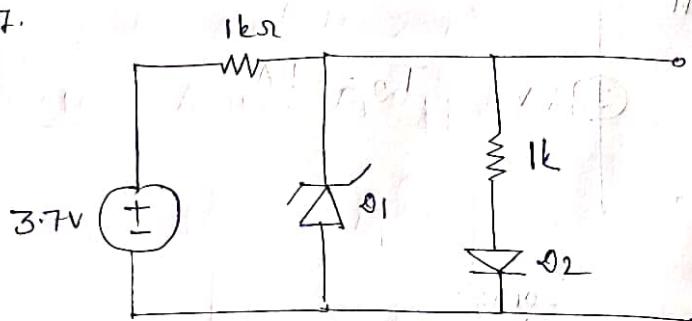



$$V_0 > 0.7V$$

OR

$$V_i > 0.7V$$

$$\theta_2 = ON$$

$$V_0 = V_i$$

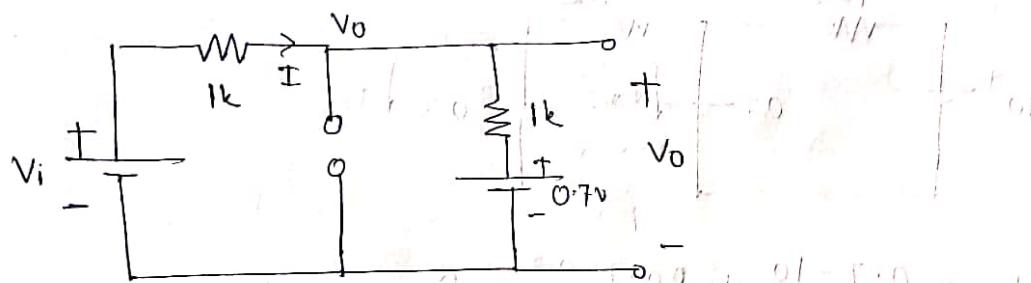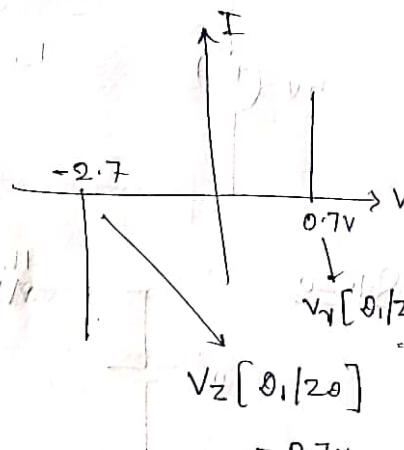

$$I = \frac{V_i - 0.7}{1k}$$

$$V_0 > 2.7V$$

$$\theta_1 = BO$$

$$V_0 = I \times 1 + 0.7$$

$$\frac{V_i + 0.7}{2} > 2.7$$

$$V_0 = \frac{V_i - 0.7}{2} + 0.7$$

$$V_i > 4.7V$$


$$\text{Help } V_0 = \frac{V_i + 0.7}{2} \quad \text{for } 0.7 < V_i < 4.7V$$

when $V_i = 3.7$


$$V_0 = \frac{3.7 + 0.7}{2}$$

$$= 2.2V$$

Q22.

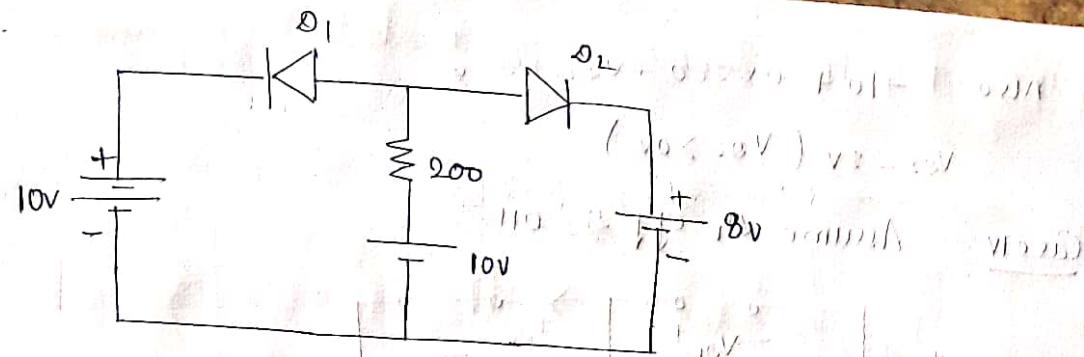


Sol :- Assume both ON.

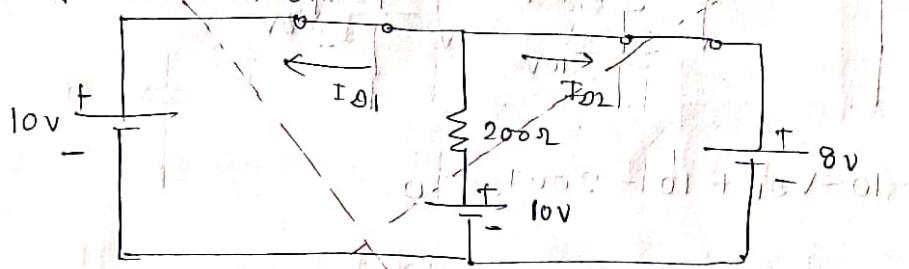

Thus it violates KVL. Voltage in branches are different (10v, 8v)

Case II :- Assume both diode are off

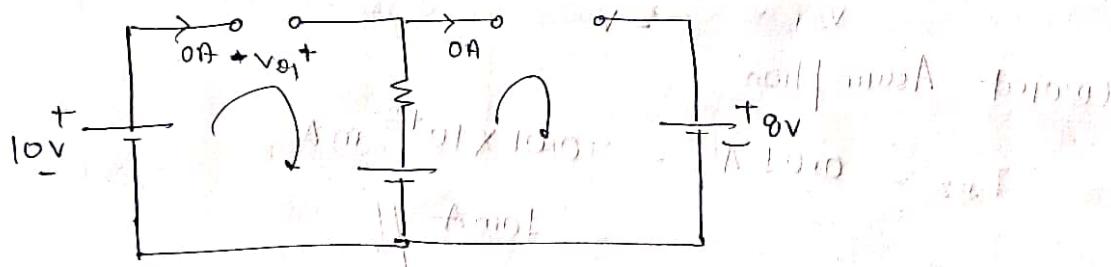


$$-10V - V_{D1} + 10 = 0$$

$$V_{D1} = 0V$$

$$V_{D2} + 8 - 10 = 0$$

$$V_{D2} = 2V \quad \{ V_{D2} > 0 \text{ wrong assumption}$$

Case III Assume D₁ is on & D₂ is off

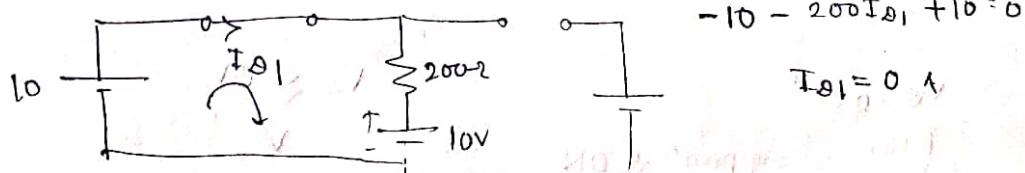


$$-10 - 200I_{D1} + 10 = 0$$

$$I_{D1} = 0A$$

$$\text{Also, } -10 + 0 \times 200 + V_{D2} + 8 = 0$$

$$V_{D2} = 2V \quad (V_{D2} > 0V)$$

Case IV Assume D_1 off, D_2 on

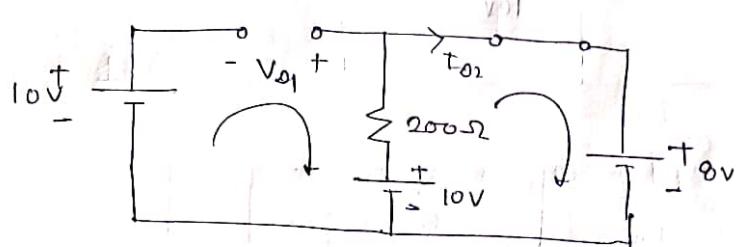

$$-10 - V_{D1} + 10 - 200 I_{D2} = 0$$

$$V_{D1} = -200 I_{D2}$$

$$\text{also, } -10 + 200 I_{D2} + 8 = 0$$

$$I_{D2} = \frac{2}{200}$$

$$I_{D2} = 0.01A$$


$$V_{D1} = -200 \times 0.01$$

$$V_{D1} = -2V$$



Correct Assumption

$$I_{D2} = 0.01A = 0.01 \times 10^3 \text{ mA}$$

$$= 10 \text{ mA} //$$

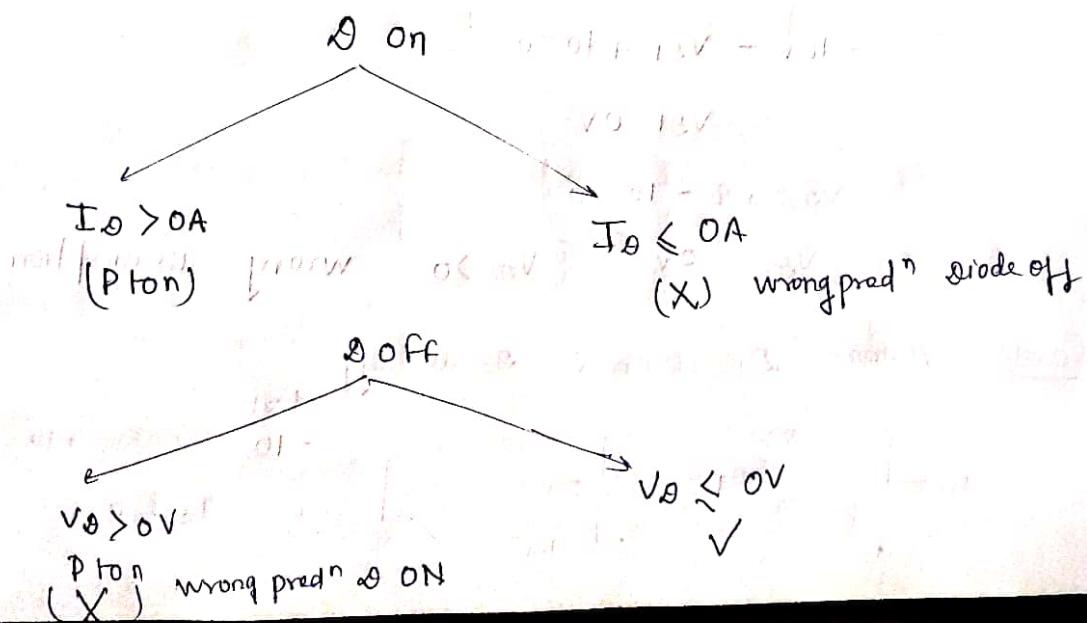

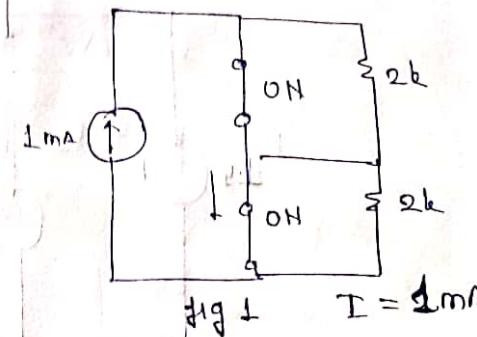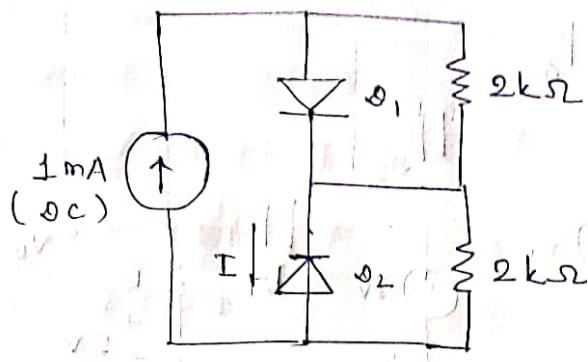Q9: Assume D_1, D_2 are ideal diodes. The value of I is



Sol: $D_1 = ON \quad D_2 = ON$

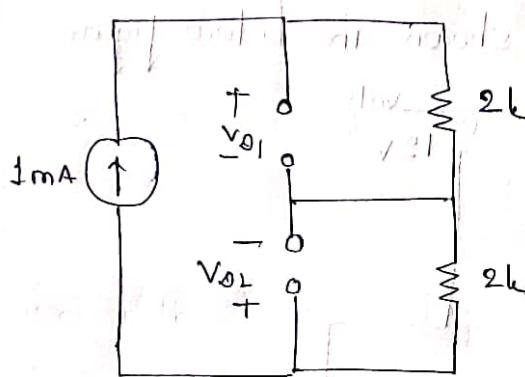


Fig. 2 $D_1 = OFF \quad D_2 = OFF$

$$V_{D1} = 2V \times$$

$$V_{D2} = -2V \checkmark$$

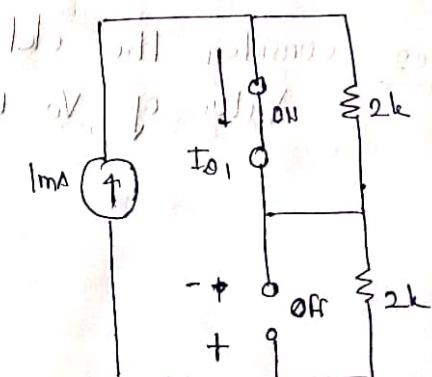



Fig. 3 $D_2 OFF$

$$D_1 ON$$

$$I_{D1} = 1mA \checkmark$$

$$V_{D2} = -2V \times \checkmark$$


$$I_D = 0A \quad II.$$

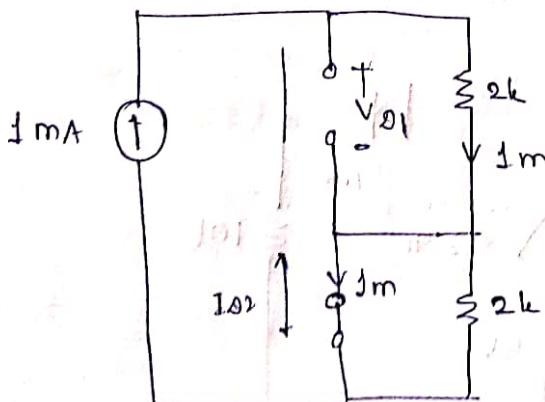

$$V_{D1} = 2V \times$$


$$I_{D2} = -1mA \times$$

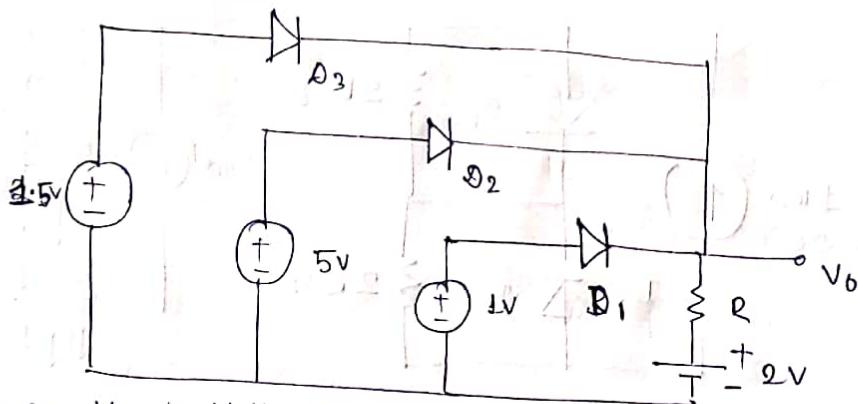Ques 1 For the circuit shown in below figure




The Value of V_o in Volt is —

Ques 2 Consider the ckt shown in below figure The Value of V_o is — volt

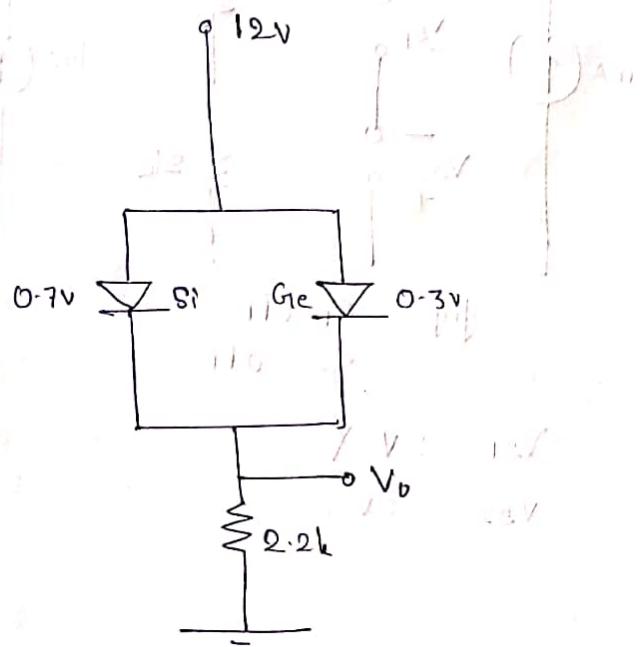


Ques 3

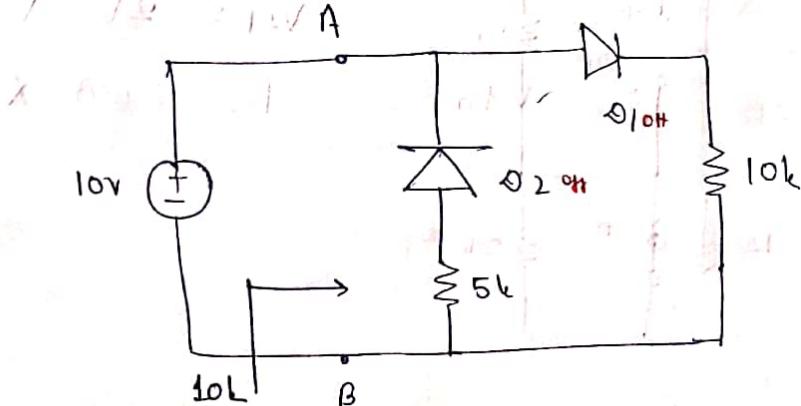

The Impedance across A-B is — $10k \Omega$.

Q4.

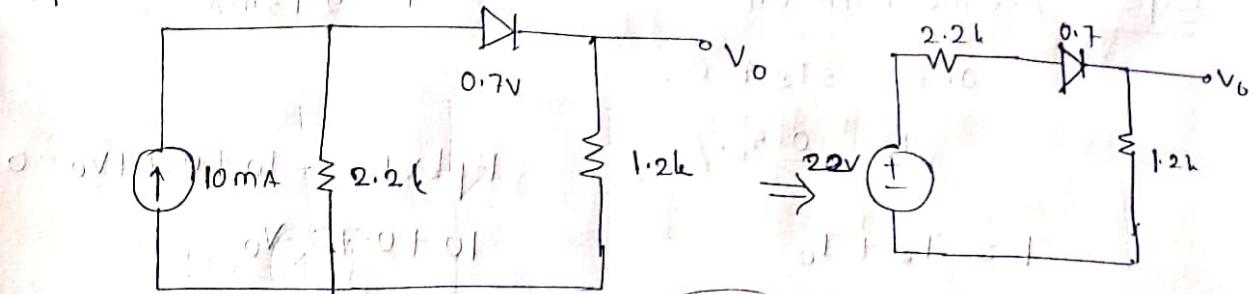


The Value of V_o is $7.51V$

$$\frac{V_o - 2.2}{2.2} + \frac{V_o}{1.2} = 0$$

$$V_o + 2.2 = V_o$$

$$V_o = \left[\frac{-10}{\frac{1}{2.2} + \frac{1}{1.2}} \right] =$$

Q5.

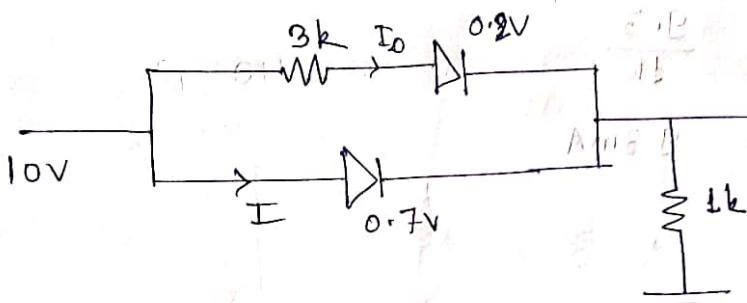

The Value

of I in mA is

Sol1

D_1 off due to 2V

D_2 ON


D_3 OFF

$$V_o = 5V$$

Sol2:

first Ge conduct and fix 0.3V across Si diode

Hence Si never conduct

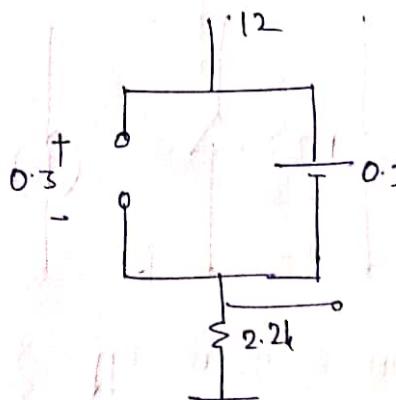

$$12 = 0.3 + V_o$$

$$V_o = 11.7V$$

Sol 5: Assume both on

$$0.7 = 3I_0 + 0.2$$

$$I_0 = \frac{0.5}{3} \text{ mA}$$

$$I = I_0 + I_0$$

$$I_0 = \frac{V_0}{1k}$$

$$\frac{10.7}{1k} \quad \frac{9.3}{1k}$$

$$I_{0,1} = 10.7 \text{ mA} \quad 9.3 \text{ mA}$$

$$I_0 = I + I_0$$

$$9.3 = I + \frac{0.5}{3}$$

$$I = 9.3 - \frac{0.5}{3}$$

$$I = 9.13 \text{ mA}$$

$$I = 9.13 \text{ mA}$$


$$\text{By KVL: } -10 + 0.7 + V_0 = 0$$

$$-10 + 0.7 = -V_0$$


$$V_0 = 9.3$$

$$V_0 = +9.3 \text{ V}$$

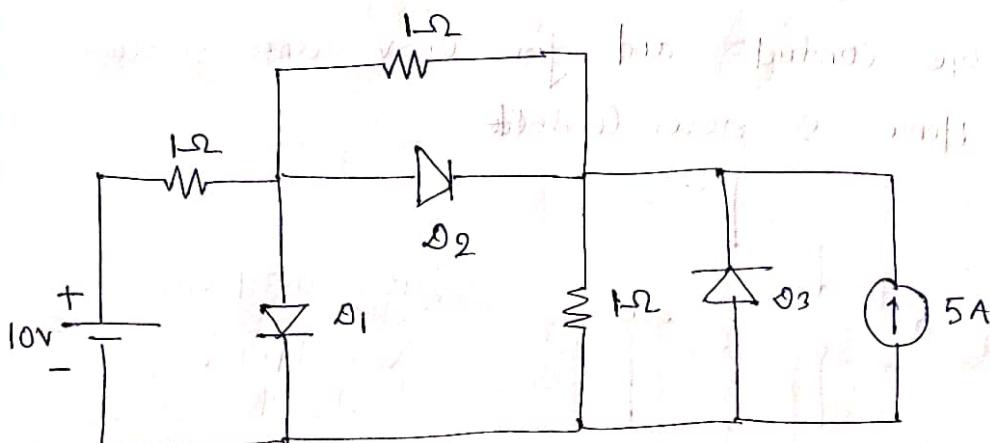Q10. What are the states of three ideal diodes?



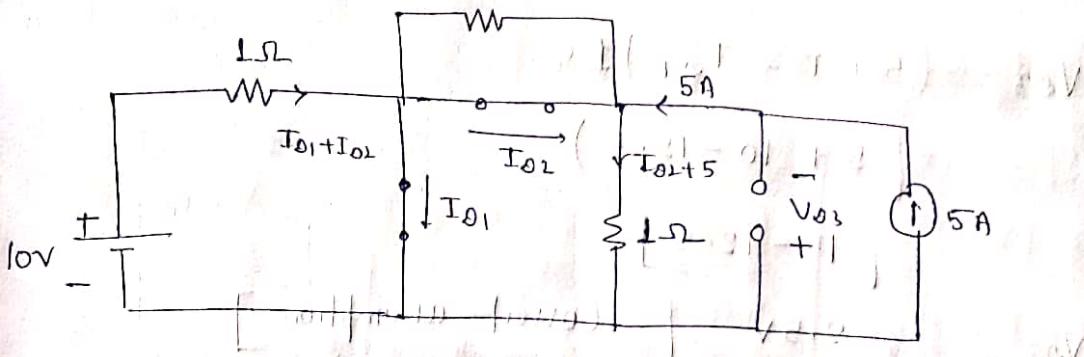Sol Assume D_1 & D_2 is on & D_3 is off { But its not in option }




$$kvl \quad (5 + I_{D2}) 1\Omega + 0 + 0 = 0$$

$$I_{D2} = -5A \quad (\text{Wrong Assumption})$$

No need of going further

Case:- Assume D₁ ON D₂ off D₃ off

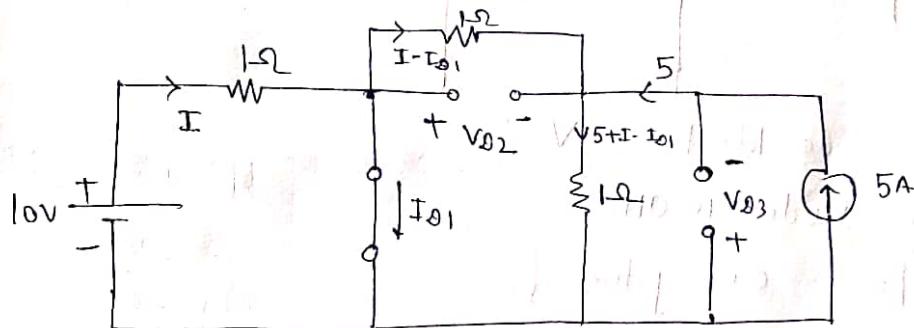

Apply kvl

$$V_{D2} + 5 + I - I_{D1} + 0 = 0$$

also,

$$-I_0 + I + 0 = 0$$

$$I = 10A$$

$$\text{also } (I - I_{D1}) 1 + 5 + I - I_{D1} + 0 = 0$$

$$10 - I_{D1} + 5 + I - I_{D1} = 0$$

$$\Rightarrow I_{D1} = \frac{25}{2} = 12.5 \quad [\text{Correct assumption}]$$

Check other.

$$V_{D2} = 12.5 - 10 - 5 \\ = -2.5 \quad \text{II. (Correct)}$$

$$\text{OR } (I - I_{D1}) 1\Omega = V_{D2} \\ 10 - 12.5 = V_{D2} \\ V_{D2} = -2.5$$

$$V_{D3} = -(5 + I - I_{D1}) \text{ } 1\Omega$$


$$= -[5 + 10 - 12.5]$$

$$= -[15 - 12.5]$$

$$V_{D3} = -2.5 \text{ V} \quad [\text{Correct assumption}]$$

Hence S_1 ON S_2 OFF S_3 OFF

Q12.

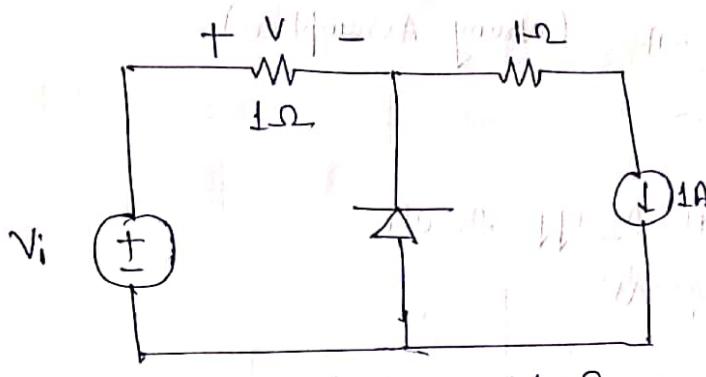


Diode-Ideal

$$V = ?$$

Sol Assume diode is ON

{ V_i can be positive or negative }

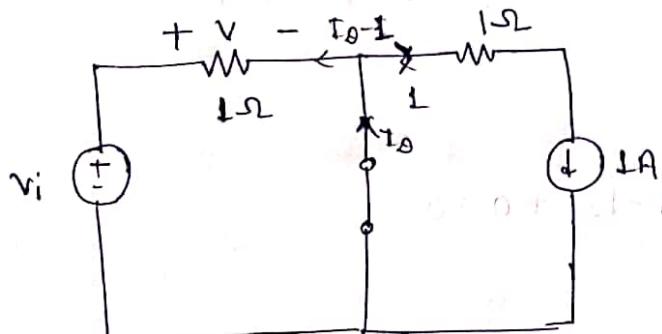

$$-V_i + V = 0$$

$$V = V_i \rightarrow \textcircled{1}$$

$$V = -(I_D - 1) \times 1$$

$$V = [1 - I_D] \rightarrow \textcircled{2}$$

Diode ON Condition :-

$$I_D > 0$$

$$I - V > 0$$

$$V < 1 \text{ Volt}$$

Options

$$\min(V_i, 1)$$

$$\min(0.5, 1) = 0.5 \text{ V}$$

State ✓

$$\max(V_i, 1)$$

$$\max(0.5, 1) = 1 \text{ V}$$

State ✗

$$\min(-V_i, 1)$$

$$\min(-0.5, 1) = -0.5 \text{ V}$$

State ✗

$$\max(-V_i, 1)$$


$$\max(-0.5, 1) = 1 \text{ V}$$

State ✗

Assume $V_i = 0.5 \text{ V}$

Option A

Assume diode is off

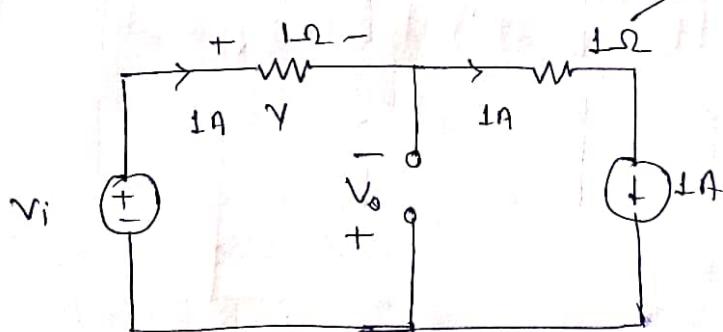

} no use of I_L
Ideal Current Source
Serial resistance
is of no use.

$$V = 1 \text{ V}$$

$$kVI - Vi + V - V_D = 0$$

$$V_D = V - Vi$$

for diode off

$$V_D < 0$$

$$V - Vi < 0$$

$$Vi > 1 \text{ Volt}$$

Assume $V_i = 2V$ $\left[V_i > \pm V \right]$

Option

$$\min(V_i, t)$$

$$\min(2, 1) = 1V$$

Statement



$$\max(V_i, t)$$

$$\max(+2, 1) = 2V$$

$$\min(-V_i, t)$$

$$\min(-2, 1) = -2V$$


$$\max(-V_i, t)$$

$$\max(-2, 1) = 1V$$

Now take $V_o = 0V$


Then only option A

* DC and AC Equivalent Circuit of Diode

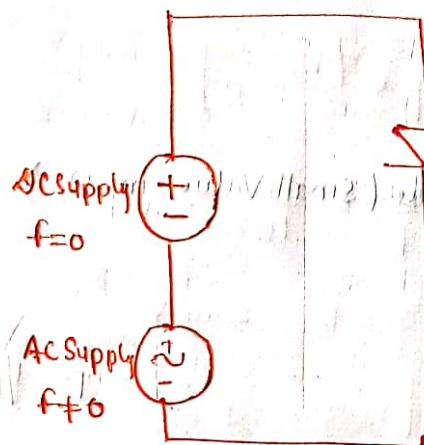


Apply Superposition theorem

Step 1 Consider DC Voltage Source V [$V_{AC}=0$]

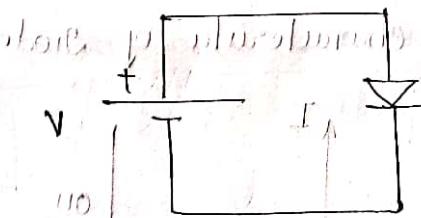

Case 1. $V > V_T$

$\theta =$ forward Biased ON

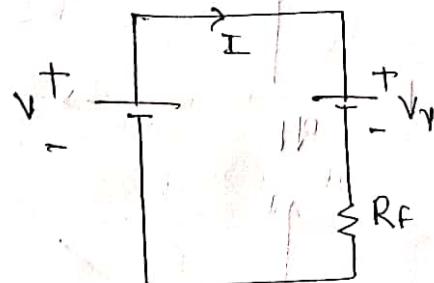

Where, V_T = Cut-in Voltage or offset Voltage

$$V_T = 0.6 \text{ to } 0.7 \text{ V [Si]}$$

$$V_T = 0.2 \text{ V to } 0.3 \text{ V [Ge]}$$

$$V_T [\text{Ge}] < V_T [\text{Si}]$$


Apply KVL in main path of diode A.B.C.E

$$-V + V_y + I R_f = 0$$

$$I = \frac{V - V_y}{R_f} \quad \text{--- (1)}$$

R_f = forward bias resistance of diode (small value in Ω)


$$y = mx + c$$

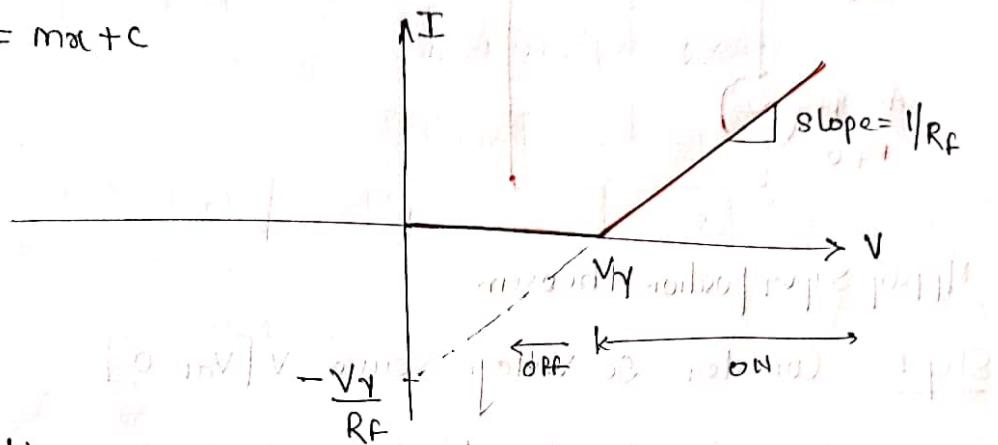


Piecewise linear forward biased characteristic of diode.

Case 1.1 $V_y \neq 0 \quad R_f = 0$

$$\text{Slope} = \infty$$

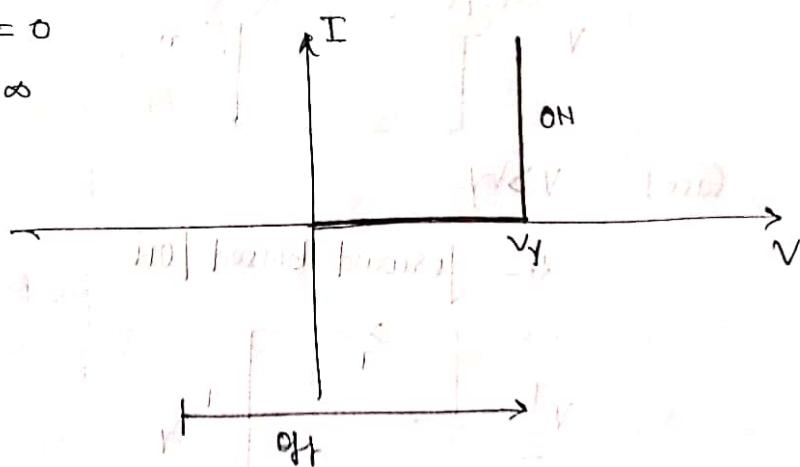


Case 1.2 $V_y = 0 \quad R_f \neq 0$

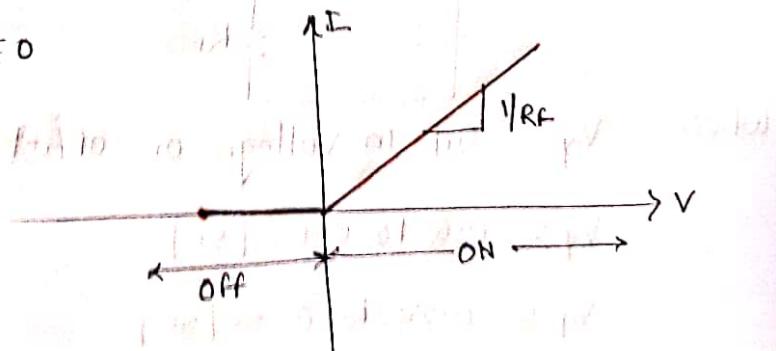

Case 1.3

$$V_y = 0V \quad R_F = 0$$

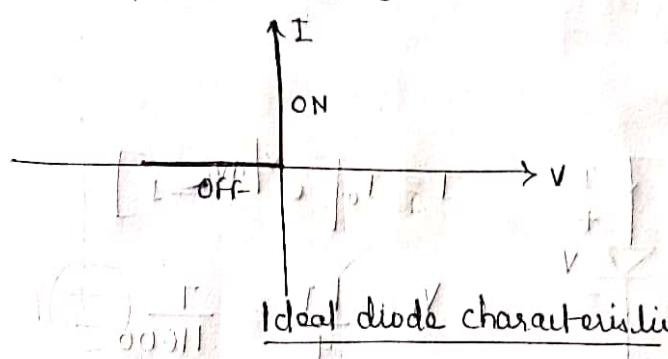


Ideal diode characteristic

Case 2

$$V < V_y$$

$$\theta = R_B F_{\text{ext}}$$

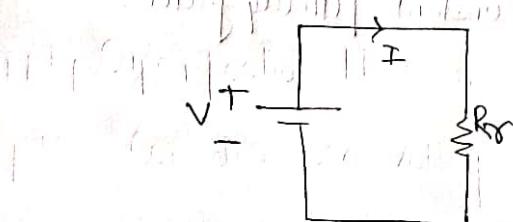

R_r = Reverse bias Resistance (Very High value)

Applying kvl

$$-V + R_r I = 0$$

$$I = \frac{V}{R_r}$$

$$R_r \rightarrow M\Omega$$

$$I \rightarrow 0A$$

Ideally $R_r \rightarrow \infty$

$$I = 0A \quad (\text{o.c.})$$


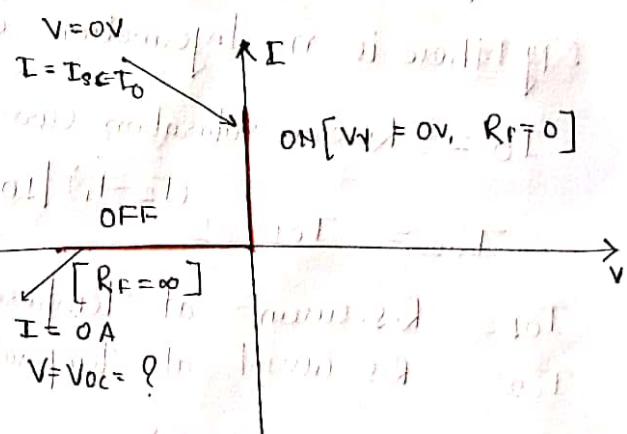


fig: Ideal charac. of diode

Step II Consider AC Source V_{AC}

$$V_{AC} = 0$$

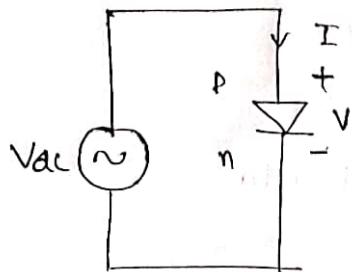

$$I = I_0 [e^{V/V_T - 1}]$$

$$V_T = \frac{kT}{q} = \frac{T}{11600}$$

$$V_T \text{ at } 300^\circ K = 26 \text{ mV}$$

$$\text{Exam } [V_T \text{ at } 300^\circ K] = 25 \text{ mV } (\text{Maxm Hm})$$

γ = Material Constant / Ideality Constant / Utility factor

$$\gamma = \begin{cases} 1 & \text{Ge} \\ 2 & \text{Si} \end{cases} \quad \text{old book}$$

$\gamma = 1$ for Ge & Si (new book)

If there is no information of γ then by default $\gamma = 1$

I_{01} = Reverse Saturation Current

$$I_{02} = I_{01} \left[\frac{(T_2 - T_1)}{2} \right] \frac{1}{I_0}$$

I_{01} = R.S. current at temperature T_1

I_{02} = R.S. current at temperature T_2

$$I_0 = f(T)$$

$$I_0 \uparrow \quad T \uparrow$$

$$I_0 \uparrow \quad 10^{\circ} \text{C} \uparrow$$

Dynamic Conductance of diode is given by.

$$g = \frac{dI}{dV}$$

$$g = I_0 e^{\frac{V}{nV_T}}$$

$$g = \frac{I + I_0}{nV_T}$$

$$\gamma_d = \gamma_{ac} \quad \gamma = \frac{1}{g} = \frac{nV_T}{I + I_0}$$

Dynamic Resistance

or

AC Resistance

Case 1 forward Bias $I \gg I_0$

$$\gamma_{ac} = \frac{nV_T}{I}$$

Case 2 Reverse Bias $I \ll I_0$ Comparable


$$\gamma_{ac} = \frac{nV_T}{I + I_0}$$

Pagoll

Q11

Sol

$$\gamma = 1$$

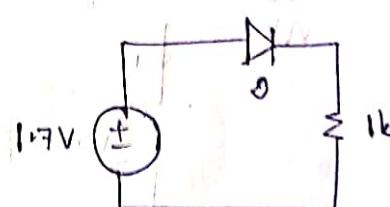


$$V_T = 0.7V$$

$$1.7V > V_T$$

$\theta = FB$

while, $I =$ forward bias
DC diode Current
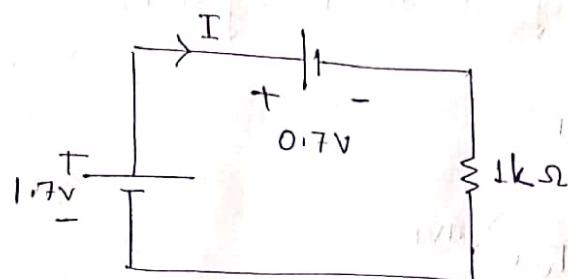
$$\gamma_d = \gamma_{ac} = \frac{nV_T}{I}$$



De equivalent circuit

$$-1.7 + 0.7 + I = 0$$

$$I = 1 \text{ mA}$$

$$\gamma_{ac} = \frac{1 \times 26}{1} \quad (\text{assume } 26 \text{ mV} = V_T)$$


$$\gamma_{ac} = 26 \Omega$$

OR assume $25 \text{ mV} = V_T$

$$\gamma_{ac} = 25 \Omega$$

Ques.

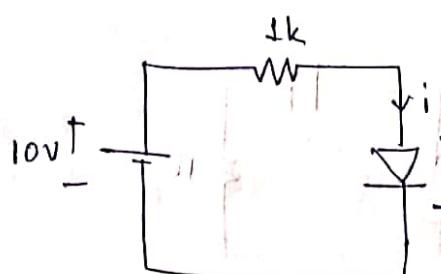
$$i = \begin{cases} \frac{V - 0.7}{500} & \text{if } V \geq 0.7 \text{ V} \\ 0 \text{ A} & \text{if } V < 0.7 \text{ V} \end{cases}$$



$$I = \frac{V - V_\gamma}{R_F}$$

forward biased Current
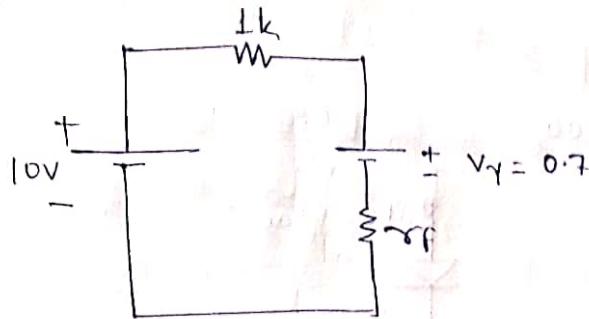
$$> V_\gamma = 0.7 \quad R_F = 500 \Omega \quad \left\{ \text{after Comparison} \right.$$



$$-10 + I + 0.7 + V_f I = 0$$

$$\frac{-9.3}{1k+500} = -I$$

$$I = + \frac{9.3}{1+0.5}$$

$$I = + \frac{9.3 \times 2}{3}$$

$$= + 3.1 \times 2$$

$$I = 6.2 \text{ mA}$$

OR

$$-10 + 1000i + V = 0$$

Diode Voltage across diode

$$-10 + 1000i + 500i + 0.7 = 0$$

from question

$$i = \frac{10 - 0.7}{1500}$$


$$= \frac{10 - 0.7}{1500} \times 10^3$$

$$\Rightarrow \frac{9.3}{15} \times 10$$

$$\Rightarrow \frac{9.3}{3} \times 2 = 6.2 \text{ mA}$$

Q.15,16


Sol $V_2 = 0.7V$

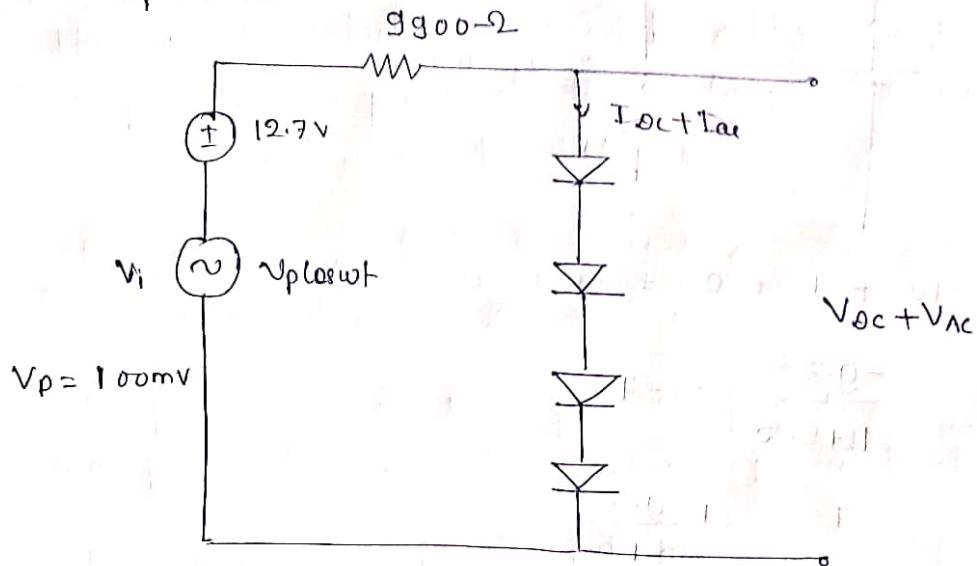

Sol Calculation of DC bias Current I_{dc}

DC Analysis

AC Signal = 0

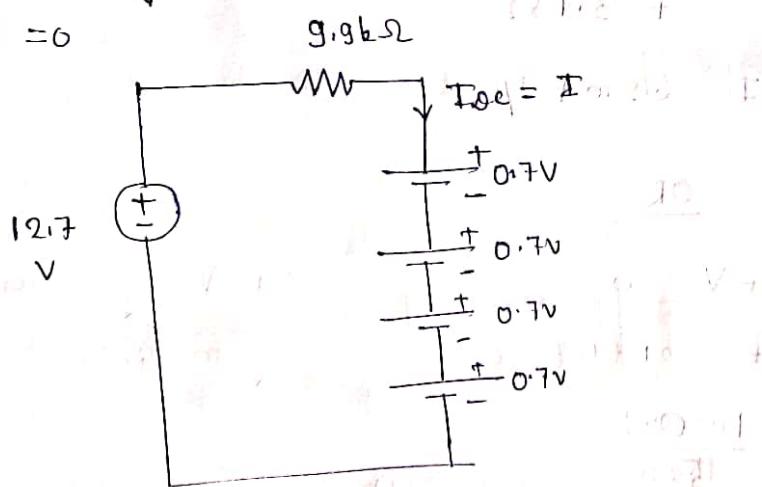


$$-12.7 + 9.9 \times I + 2.8 = 0$$

$$I = 1mA //$$

AC Analysis

DC Input = 0

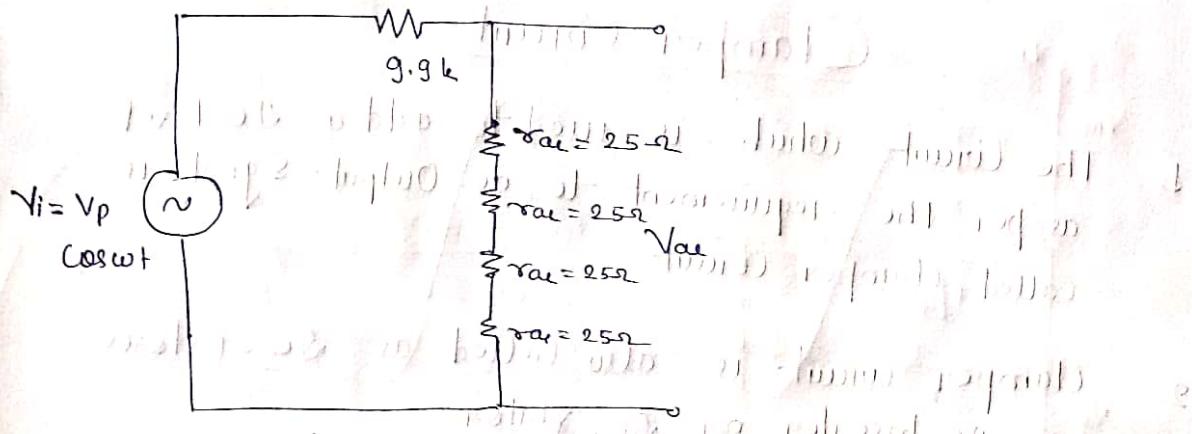

Ac equivalent circuit of Diode

$$\tau_{ae} = \frac{mV_T}{I_{ae}} \quad (\text{reverse voltage is fixed})$$

$$= \frac{1 \times 25}{1} \quad (\text{reverse voltage is fixed})$$

$$\tau_{ae} = 25 \Omega \quad (\text{fixed})$$

$$V_{ae} = \frac{100 \cos \omega t \times 100}{100 + 9.9 \text{ k}}$$

$$= \frac{100 \cos \omega t \times 100}{10000}$$

$$V_{ae} = 2 \cos \omega t \text{ mV} \quad (\text{without information})$$

$$\text{If } \gamma = 2$$

* $\gamma = 4$ without any information

$$\tau_{ae} = 50 \Omega$$


$$V_{ae} = \frac{100 \cos \omega t \times 200}{200 + 9900}$$

$$= \frac{100 \cos \omega t \times 2}{10100}$$

$$= \frac{2 \cos \omega t}{10100} \text{ mV}$$




Clamper Circuit

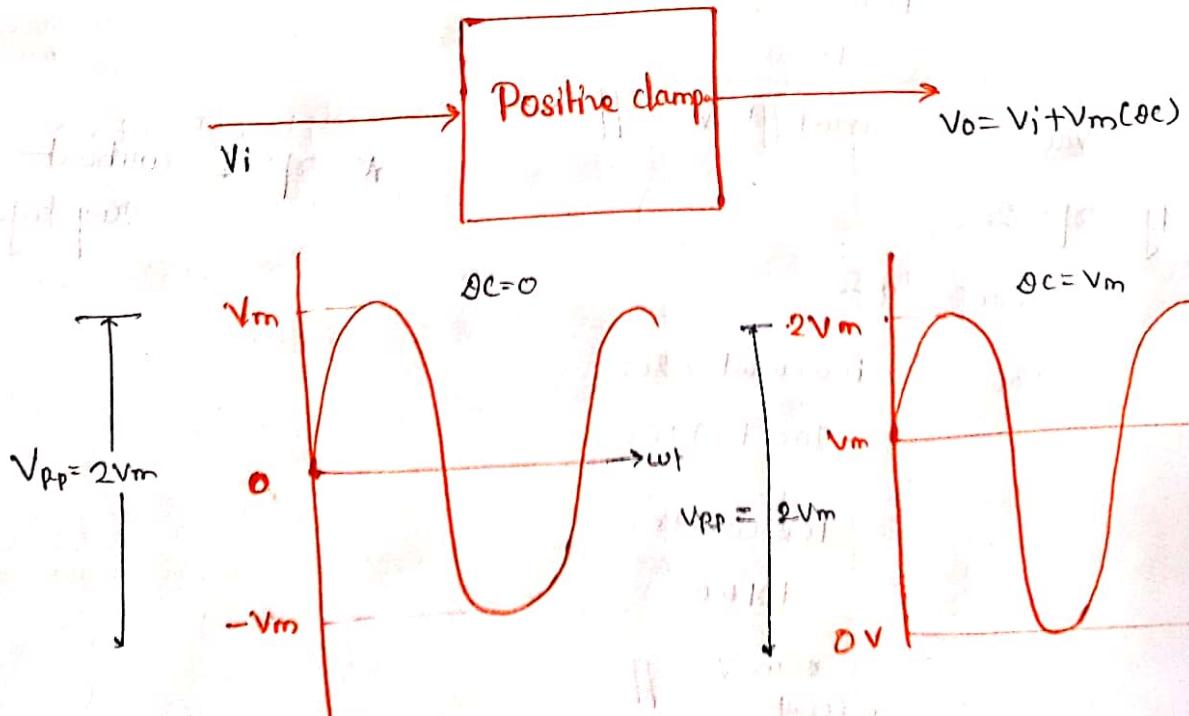1. The circuit which is used to add a DC level as per the requirement to ac output signal is called clamper circuit.
2. Clamper circuit is also called as DC restorer or DC inserter or DC xlator.
3. Clamper circuit is used for clamping the complete waveform above or below zero reference level.
4. If a waveform is clamped above zero reference level then it is called positive clamper and below zero reference level is called negative clamper.
5. In positive clamper circuit we add positive DC level.



- Peak-to-Peak Value remain Same.

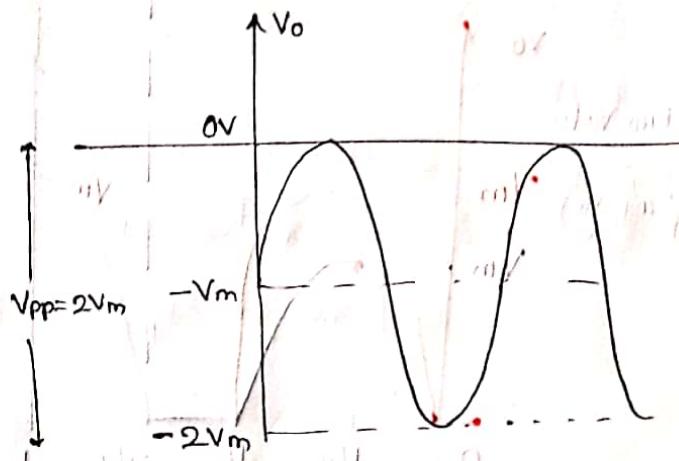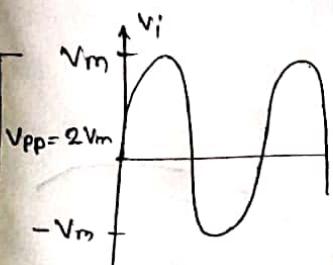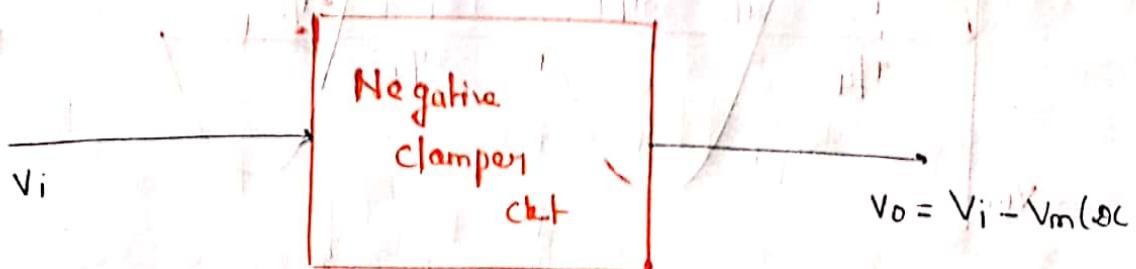- In negative clapper ckt we add Negative DC Level






- The Main ckt element of clapper ckt is Capacitor.

- Working of clapper ckt is based on Ideal charging

- and discharging of Capacitor:

1. Positive Clapper ckt :-

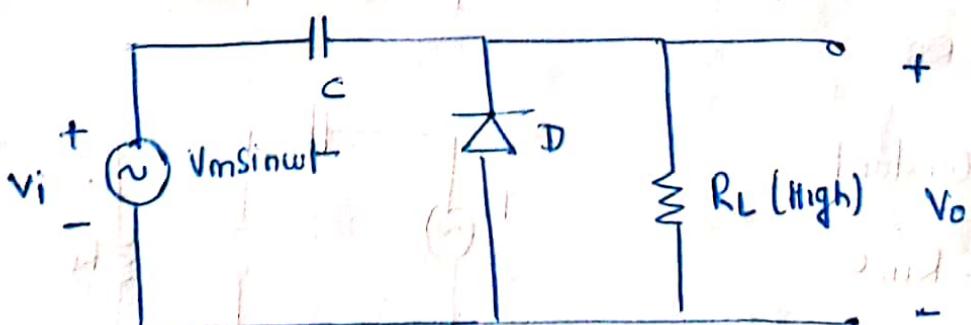

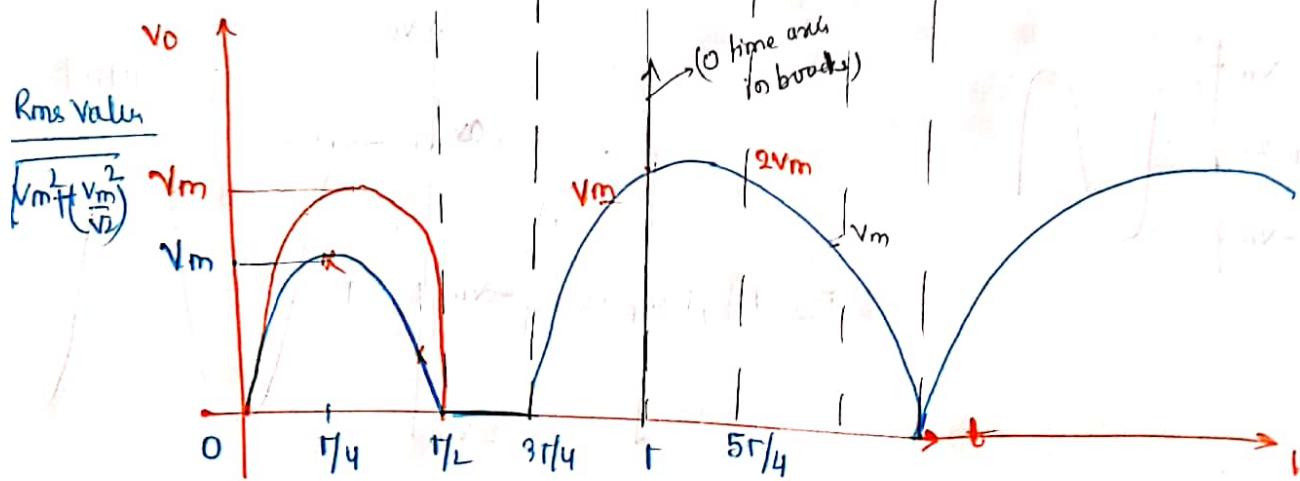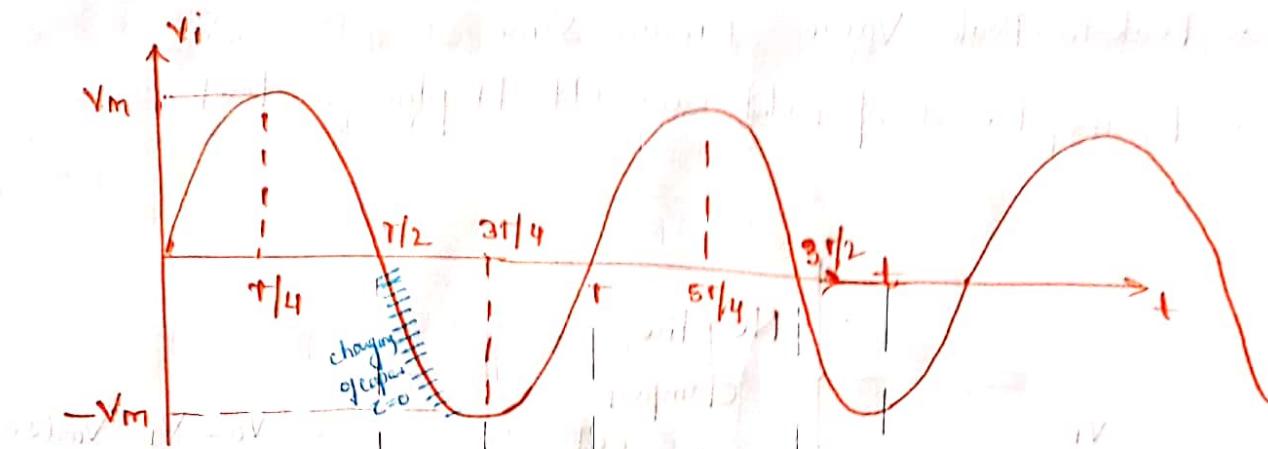

Working

$$1) \quad 0 < t < T/4 \text{ (PHC)}$$

$$0 < V_i < V_m$$



$$\text{Assume, } V_c(0) = 0 \text{ V}$$

C = uncharged Capacitor



$$D = R_B$$

Charging time constant

$$\tau_C = R_B C$$

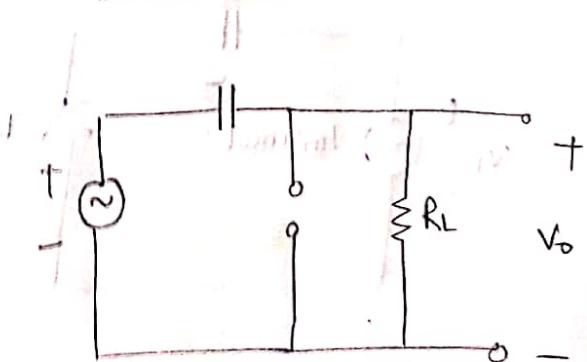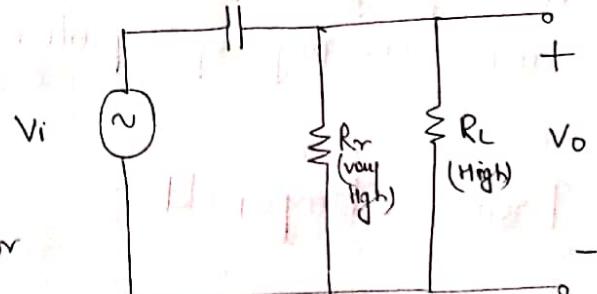
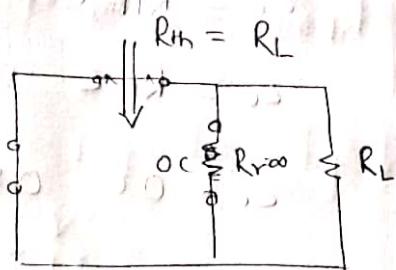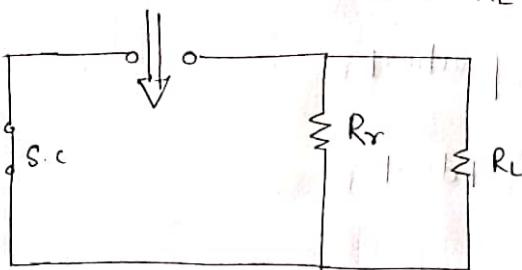
$$R_{th} = R_s \parallel R_L \approx R_L$$



key point: for proper operation of clamping circuit the value of R_{LC} should be higher than time period of input sig

$$R_L C \gg T$$

$$\therefore Z_C = R_L C$$

$$f = 50 \text{ Hz}$$

$$T = \frac{1}{f} \text{ sec} = 20 \text{ ms}$$

$$R_L C = 200 \text{ ms}$$

Capacitor will not charge



$$V_C(t/4) = 0V$$

$$T/4 < t < T(\text{sec})$$

$$V_C(T) = 0V$$

$$\text{II) } T/2 < t < 3T/4 \text{ (NHC)}$$

$$\omega = f B$$

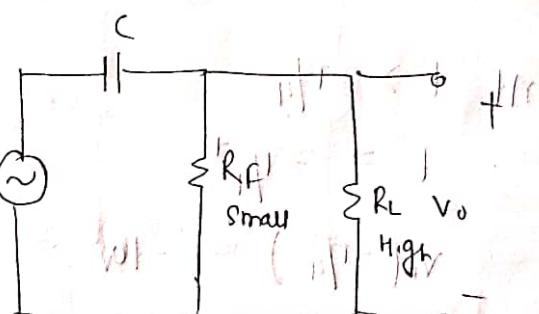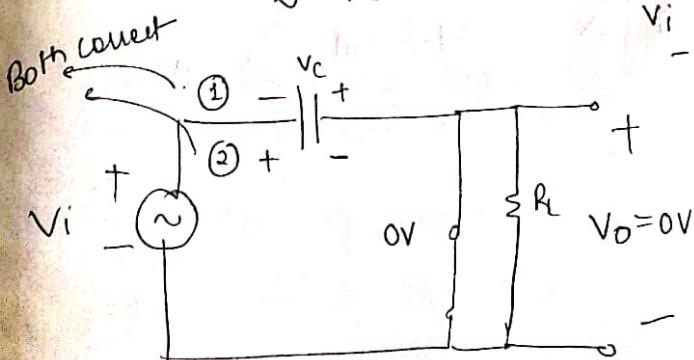

$$Z_c = R_{th} C$$

$$Z_c = R_f C \text{ see } \{ \text{practical} \}$$

$$Z_c = 0 \text{ see } \{ \text{ideal} \}$$

$$R_{th} = R_f \text{ } \{ \text{practical} \}$$

$$R_{th} = 0 \text{ } \{ \text{ideal} \}$$

kvl(1) :-

$$-V_i - V_c + 0 = 0$$

$$V_c = -V_i$$

$$V_c(t=3\pi/4) = -V_i(t=\frac{3\pi}{4})$$

$$= -[-V_m]_{\text{max}}$$

$$V_c(t=3\pi/4) = V_m$$

kvl(2) :- $-V_i + V_c + 0 = 0$

$$V_c = V_i$$

$$V_c(3\pi/4) = V_i(3\pi/4) = V_m$$

Both case same (capacitor polarity can be either way)

At $t > 3\pi/4$

$$t = 3\pi/4 +$$


$$V_i(3\pi/4) = -10$$

$$V_c(3\pi/4) = +10$$

$$V_i \left(\frac{3T}{4}\right)^+ = -g \cdot g V$$

$$V_c \left(\frac{3T}{4}\right)^+ = V_c \left(\frac{3T}{4}\right)$$

$$= 10V$$

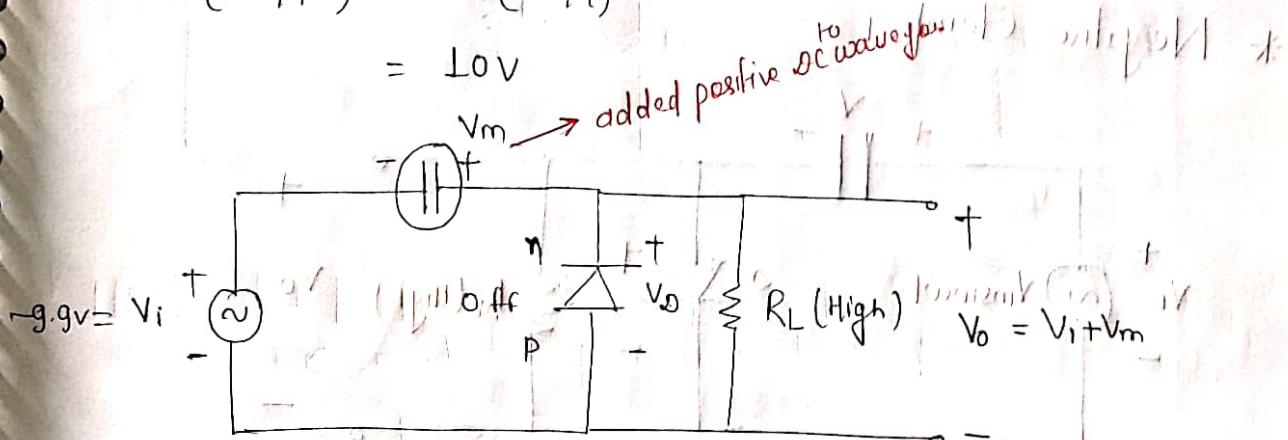

$$kvi: -V_i - 10 + V_o = 0$$

$$V_o = V_i + 10$$

$$V_o = -g \cdot g + 10 = 0.1V$$

$\theta = \text{off}$

Case for $\theta = \text{ON}$

$\theta = \text{ON}$

$$V_o < 0V$$

$$-V_i - V_m + V_o = 0$$

$$V_i + V_m < 0V$$

$$V_i < -V_m \quad (\text{Not possible})$$

& Hence $\theta = \text{off}$ always

$$V_o = V_o = V_i + V_m$$

fig. $t > 3T/4$ [Steady state]

(all off) $V_o = 0$

$V_o = 0V$


t	V_i	$V_o = V_i + V_m$
T	0	V_m
$\frac{5T}{4}$	V_m	$2V_m$
$\frac{3T}{2}$	0	V_m

Avg. Value of Input = 0

Avg. Value of o/p = V_m

$$R_{L\min} = \sqrt{R_f \times R_s}$$


* Negative Clamper

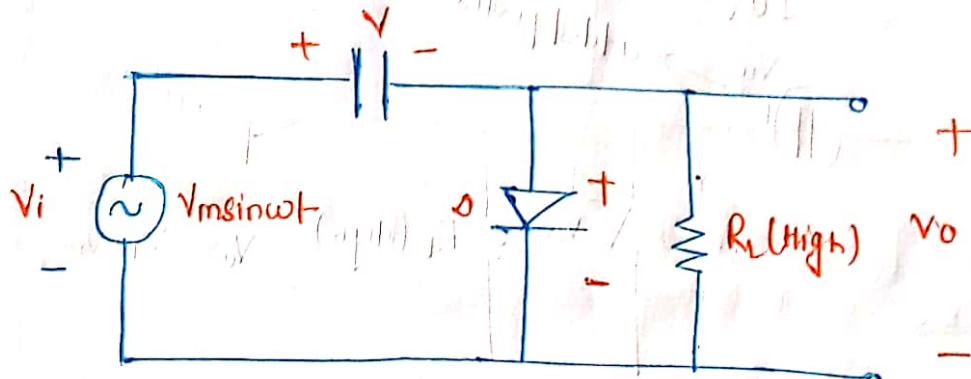


i) $0 < t < T/4$ (PHC)

$$\theta = \text{ON} / f_B$$

$$V_C = 0V$$

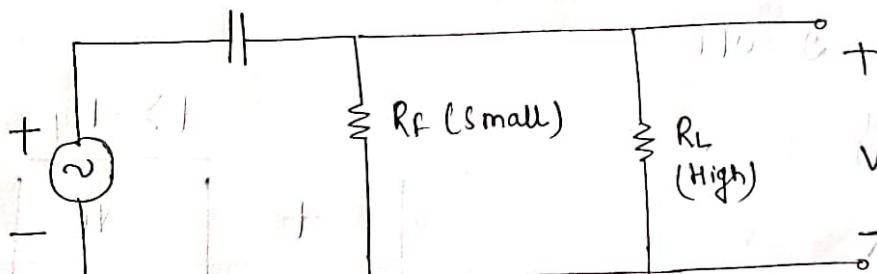

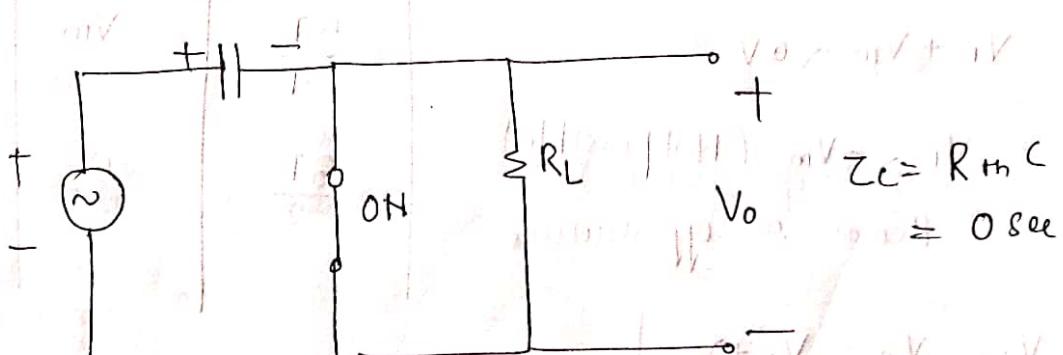
$$\frac{1}{Z_C} = R_{th} C = R_f C \text{ (small)}$$



$$\text{kVi: } -Vi + V_C = 0$$

$$V_C = Vi$$

$t > T/4$

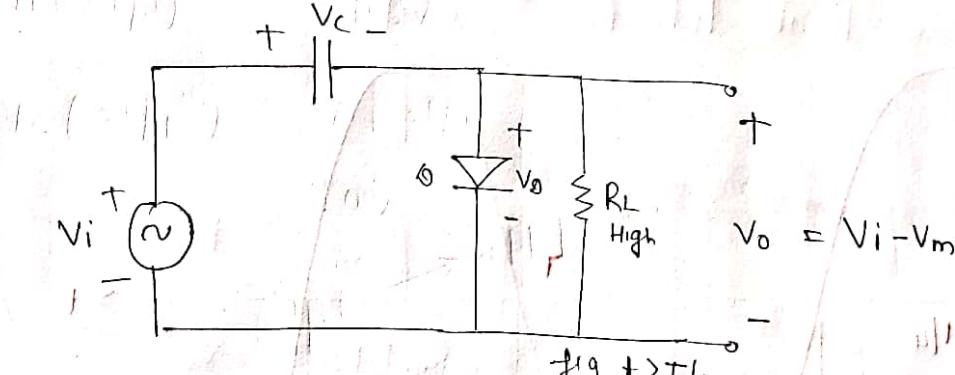

$$-V_i + V_c + V_d = 0$$

$$V_d = V_i - V_c$$

$$V_d = V_i - V_m$$

fig $t > T/4$

$$\{ V_c = V_m \}$$

for $\theta = 0^\circ$


$$V_d > 0$$




$$V_i - V_c > 0$$

$V_i > V_m$, Not possible

diode remain off

t	V_i	$V_o = V_i - V_m$
$T/2$	0	$-V_m$
$3T/4$	$-V_m$	$-2V_m$
T	0	$-V_m$
$5T/4$	V_m	0

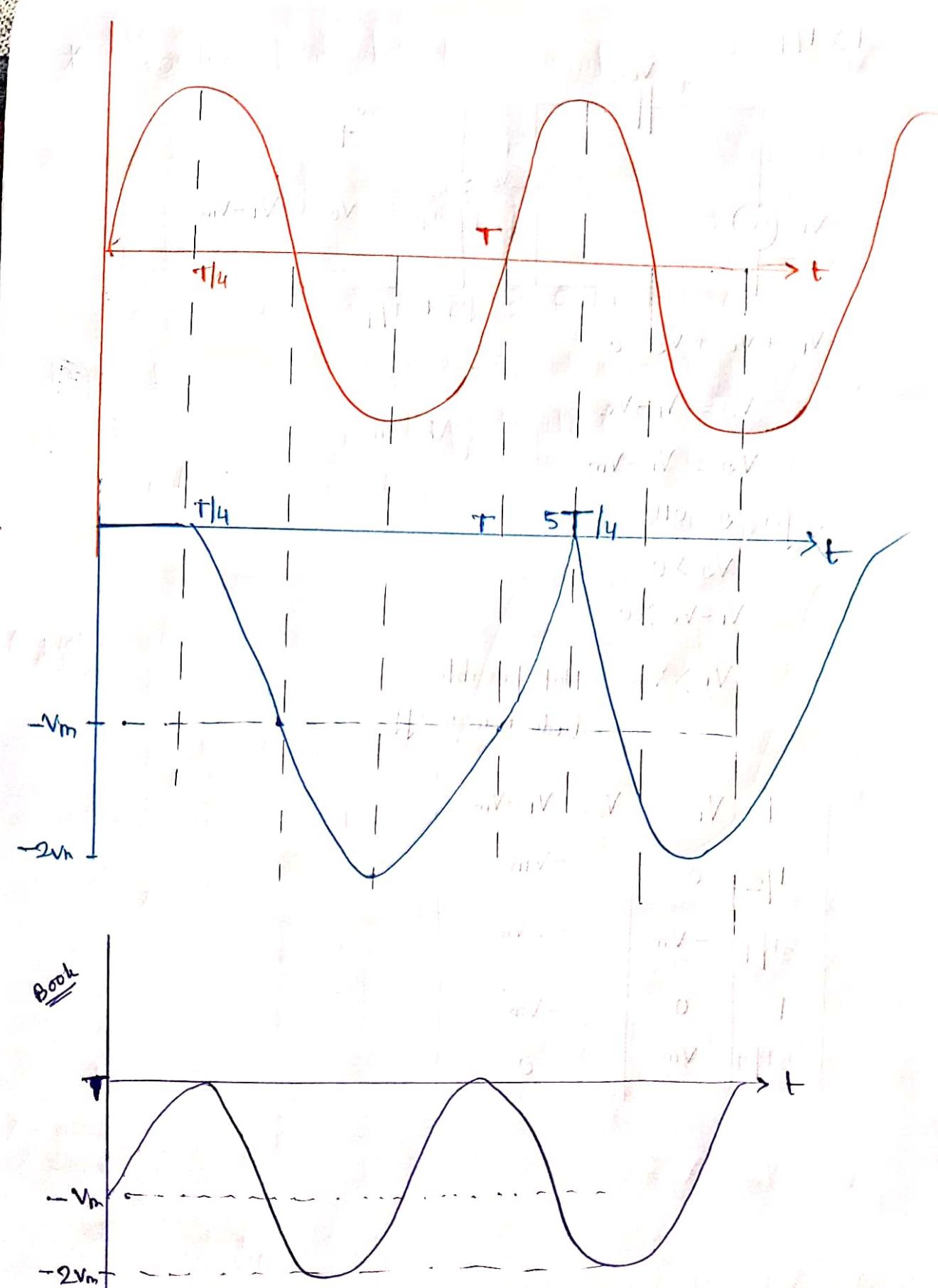

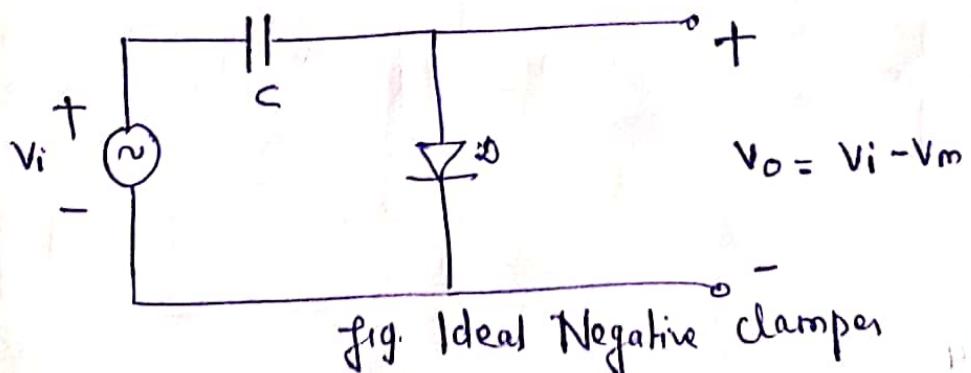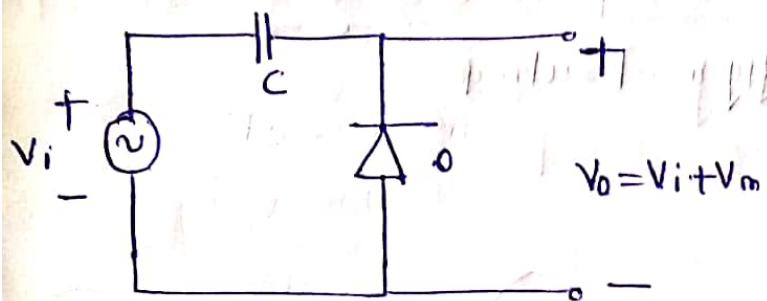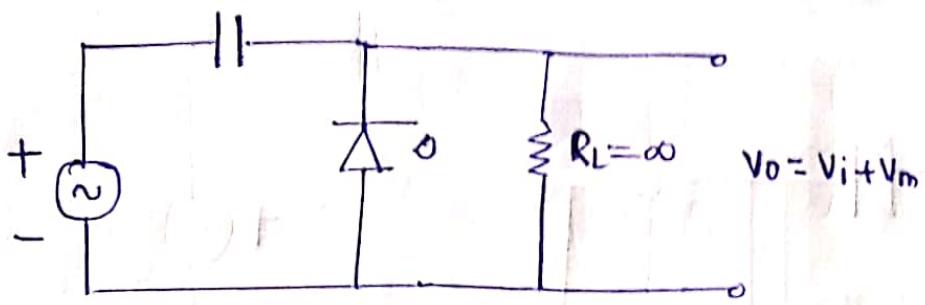

* Positive Peak detector Circuit



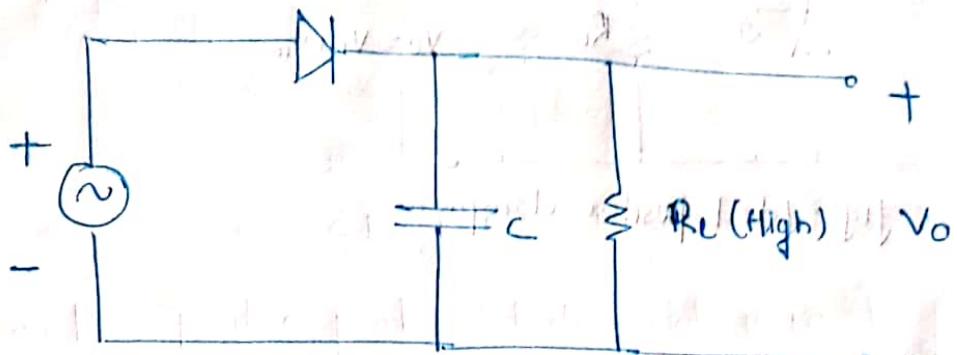


fig 9 Practical

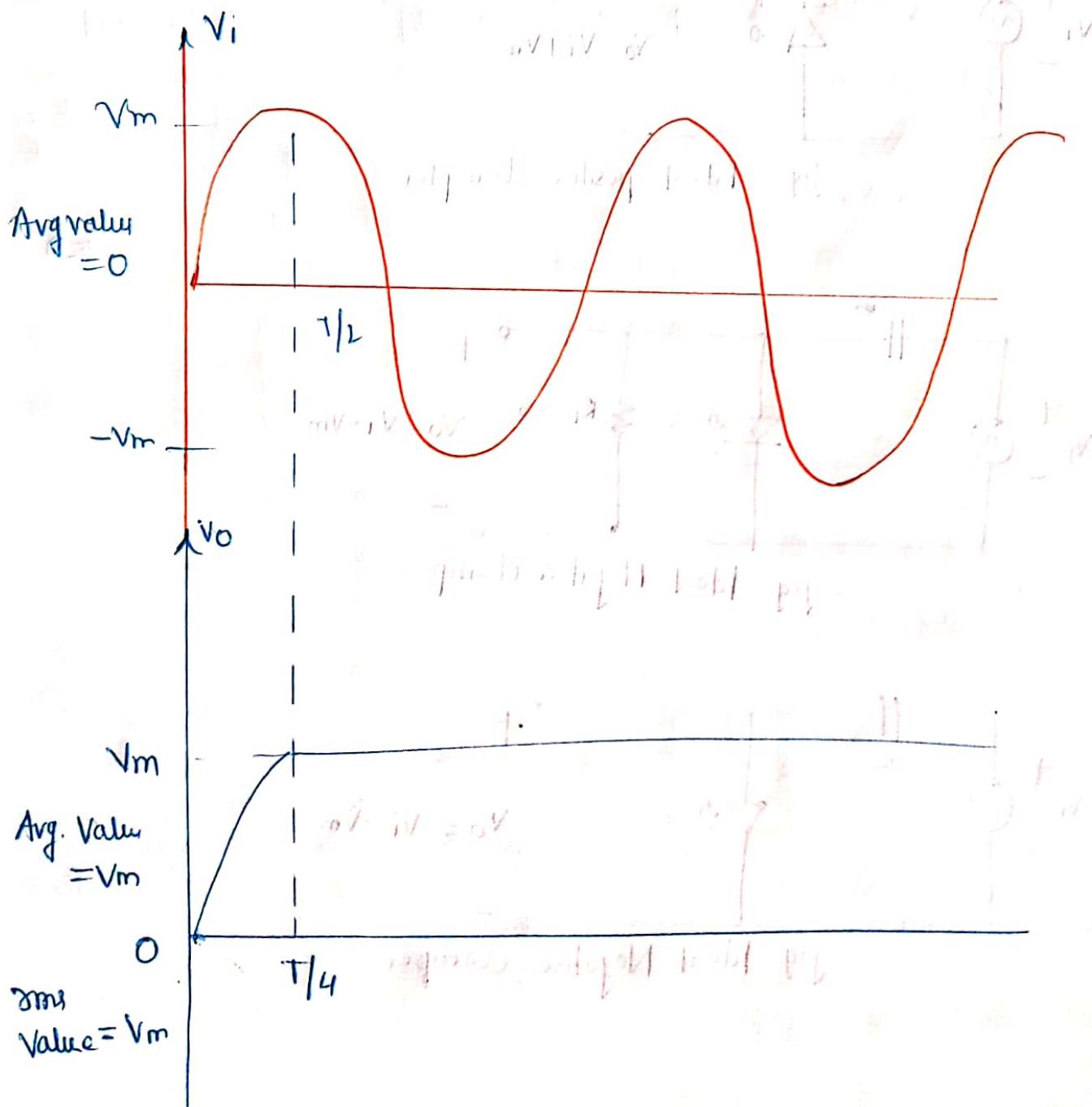


i) $0 < t < T/4$ (PHC)

$$V_C(0) = 0V$$

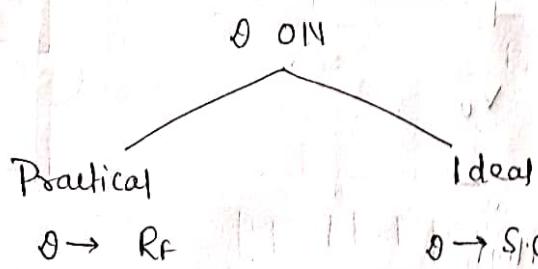

capacitor = charging


$$V_C = V_i = V_o \quad [V_o = 0V]$$

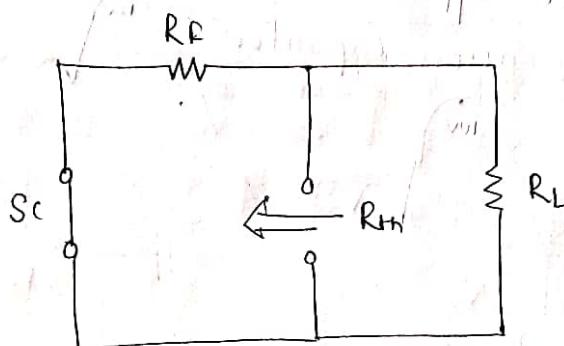

$$R_{th} = R_F || R_L \approx R_F$$

$$Z = R_{th} C$$


$$Z = R_F C \text{ (small)}$$

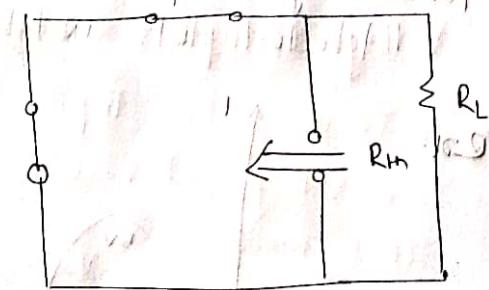

$$R_{th} = 0 \Omega$$


$$Z = 0S_{LC}$$

ii) $t > T/4$

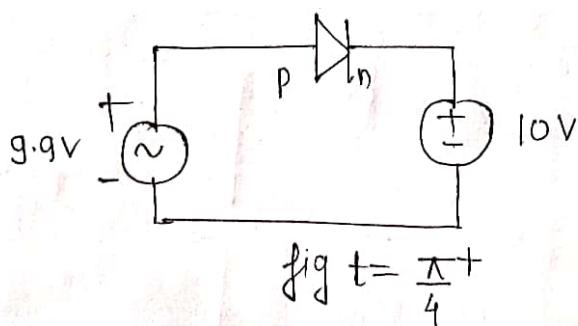

$$\text{fig } t = \frac{\pi}{4} +$$


Now Diode is off $V_o = V_D = 6.0V$

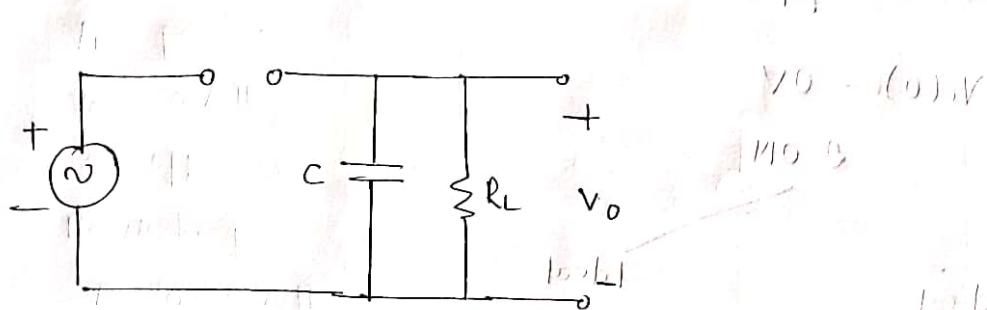

$$Z_d = R_L C = \text{High}$$

key point: Positive peak detector clt is used for recovery of message signal from SSB-SC. This clt is also referred as envelope detector.

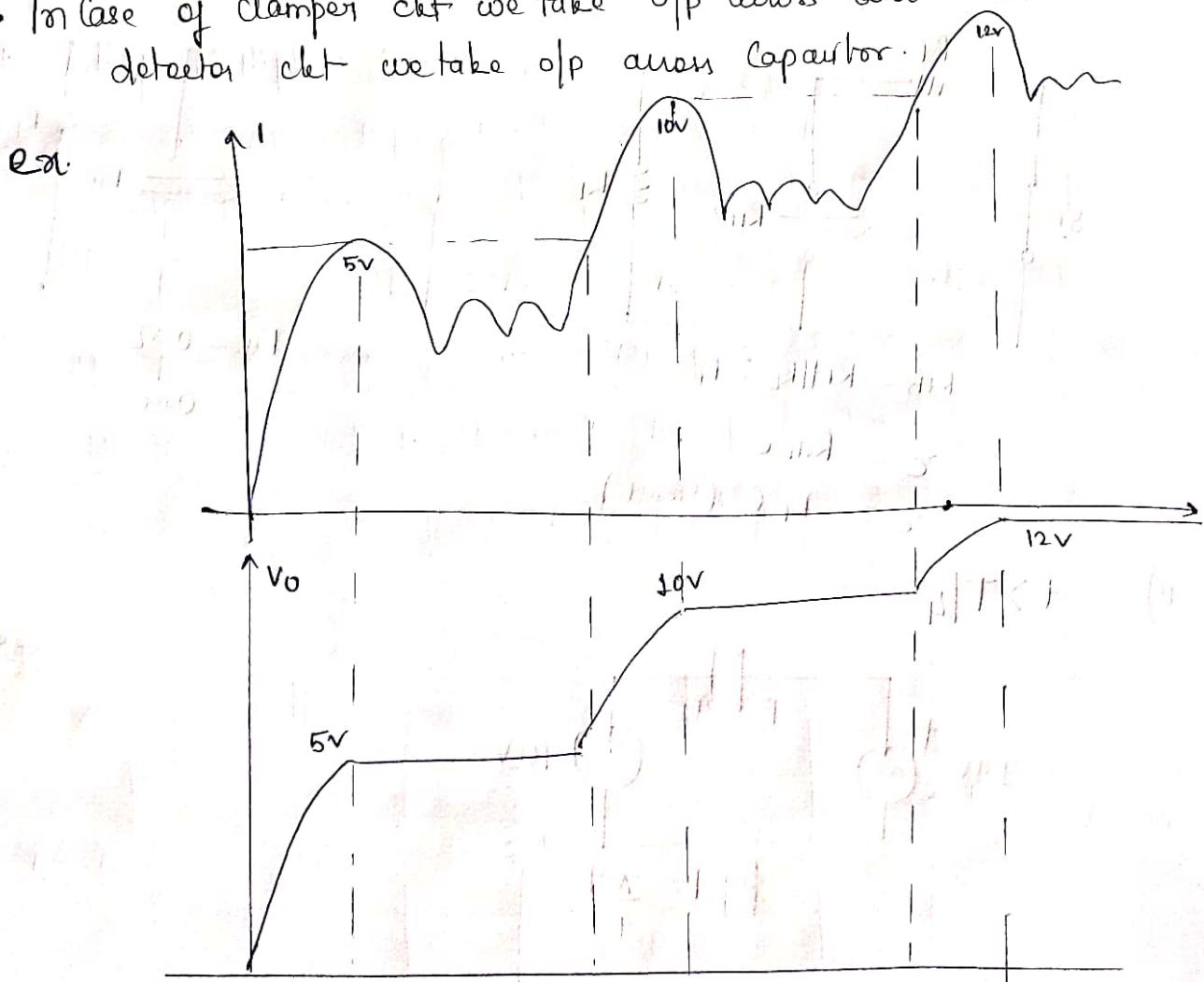- In case of clumper clt we take o/p across diode and in detector clt we take o/p across capacitor.



* Negative peak detector (Absilute)

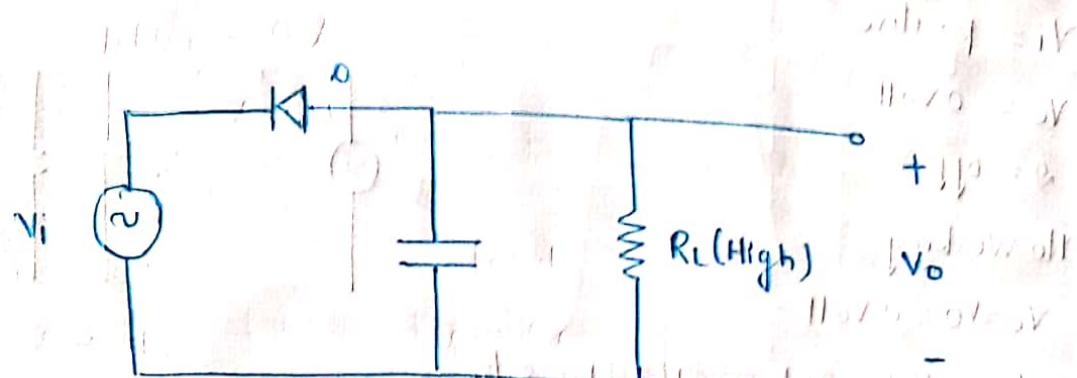


fig. $R_L C \gg \text{High}$ { greater than time period of $1/p$ }


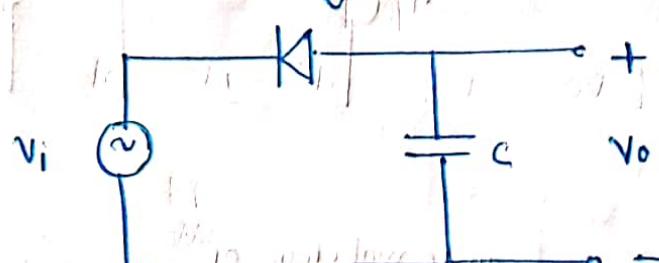


fig. Ideal neg. peak detector

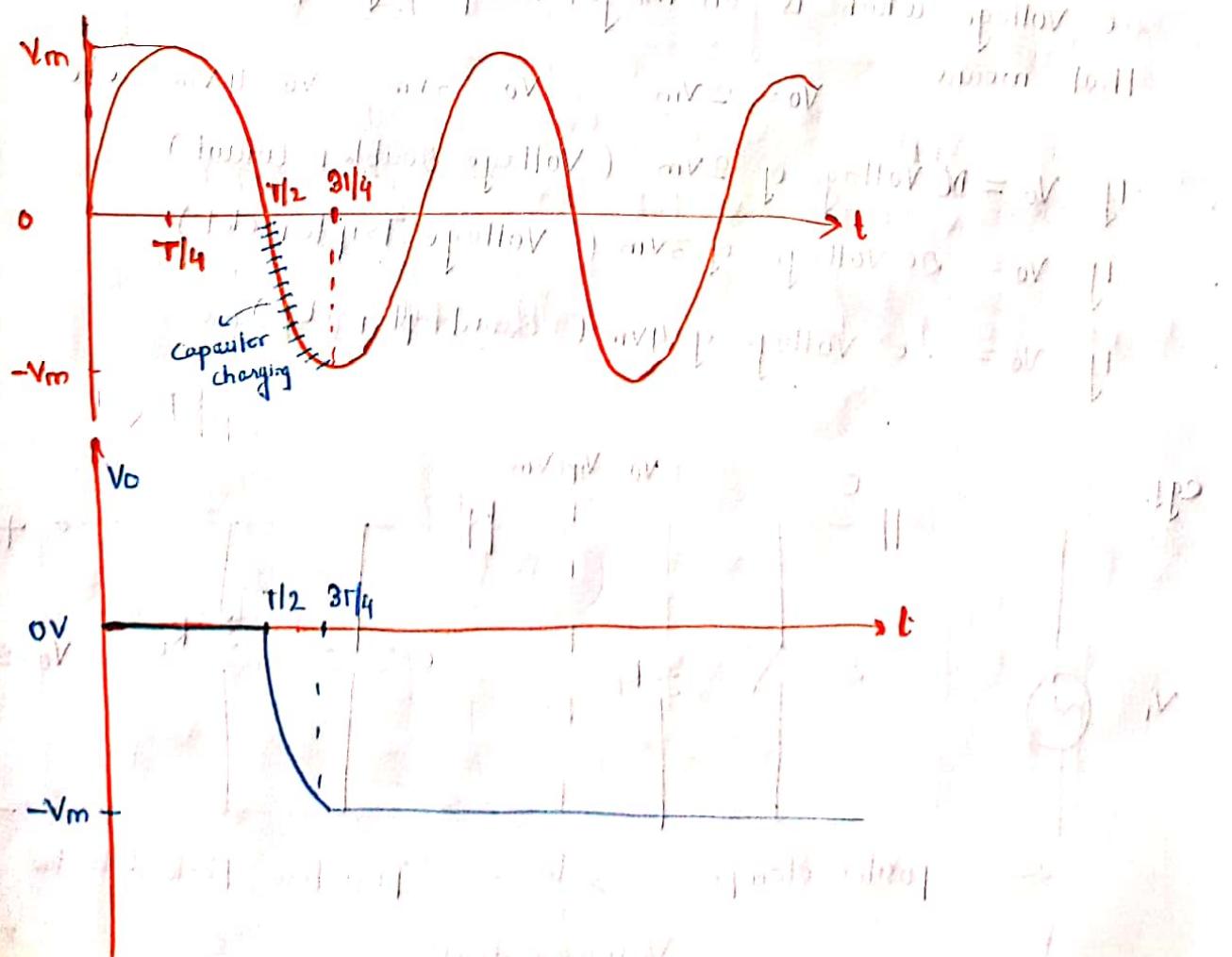

During positive Half Cycle ($0 < t < T/2$) *(Half Wave Diode Clamper)*


V_i = positive

$V_c = 0 \text{ Volt}$

D = off

No Working

$V_c = V_o = 0 \text{ Volt}$

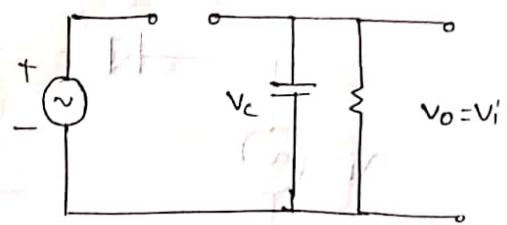


During Negative Half Cycle ($T/2 < t < 3T/4$)

Diode ON

$V_c = V_i$


$V_o = V_c = V_i$

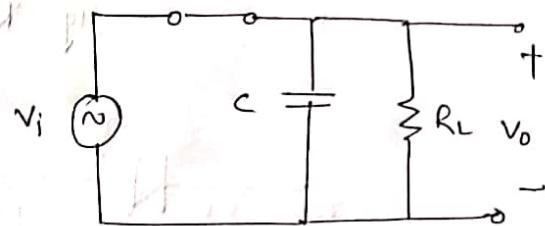


* Voltage Multiplier Circuit

- A circuit whose input waveform is peak value v_m and op is DC voltage which is an integer multiple of peak AC input
- That means, $V_o = 2v_m$, $V_o = 3v_m$, $V_o = 4v_m$ etc.
- If $V_o = \text{DC Voltage of } 2v_m$ (Voltage Doubler Circuit)
- If $V_o = \text{DC Voltage of } 3v_m$ (Voltage Tripler Circuit)
- If $V_o = \text{DC Voltage of } 4v_m$ (Quadrupler Circuit)


e.g.

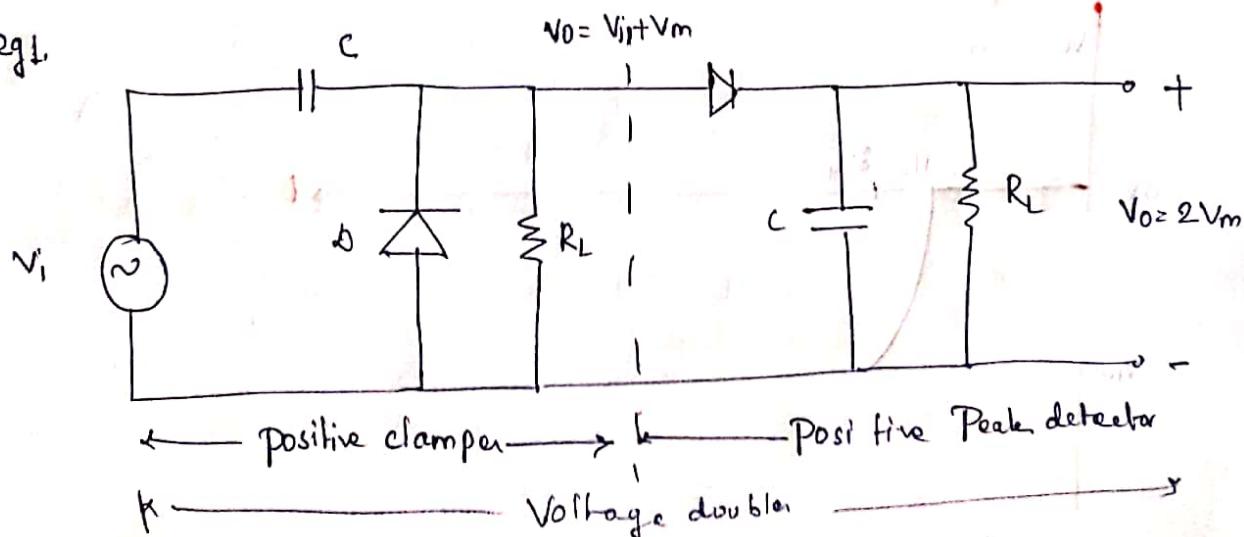


(2)

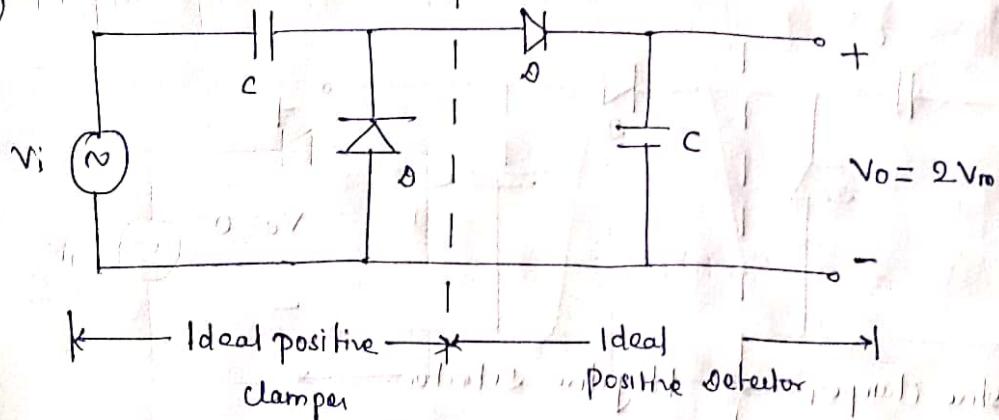


(3)

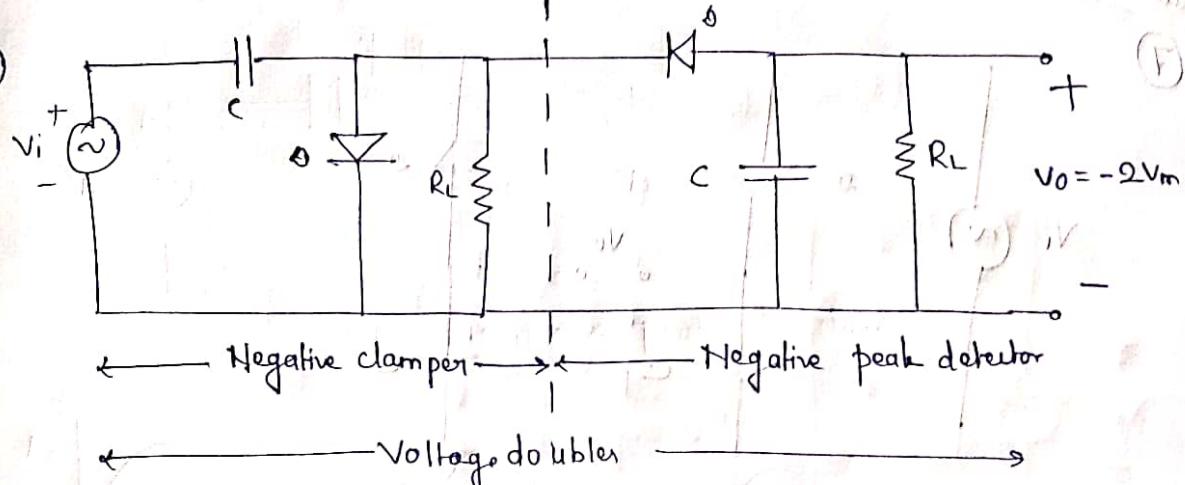


(4)

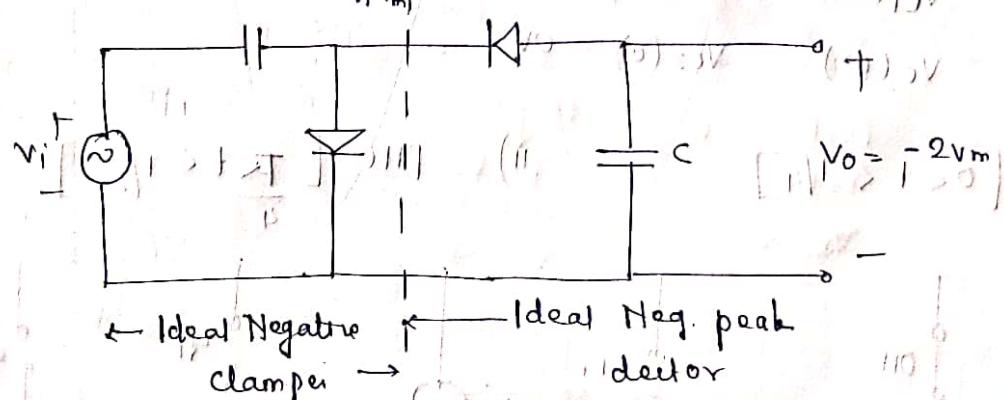

(5)

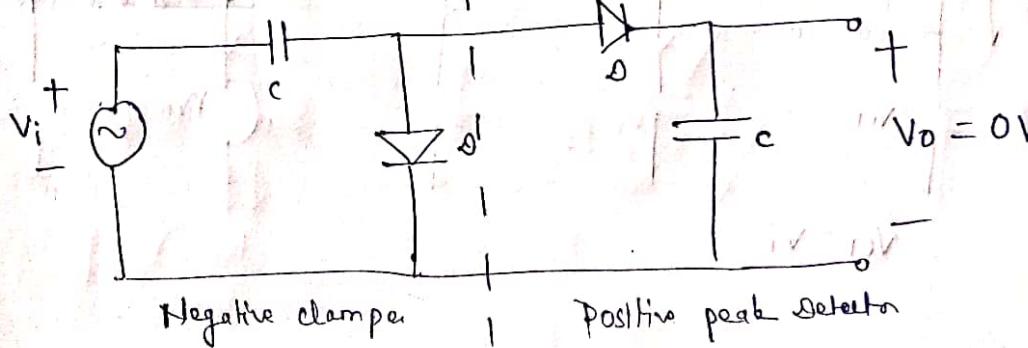


(6)

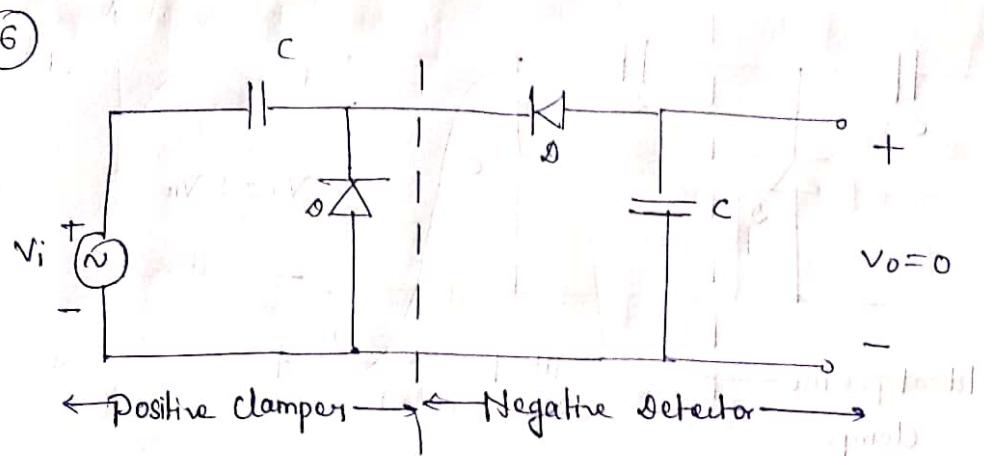


Gate 2004

(7)

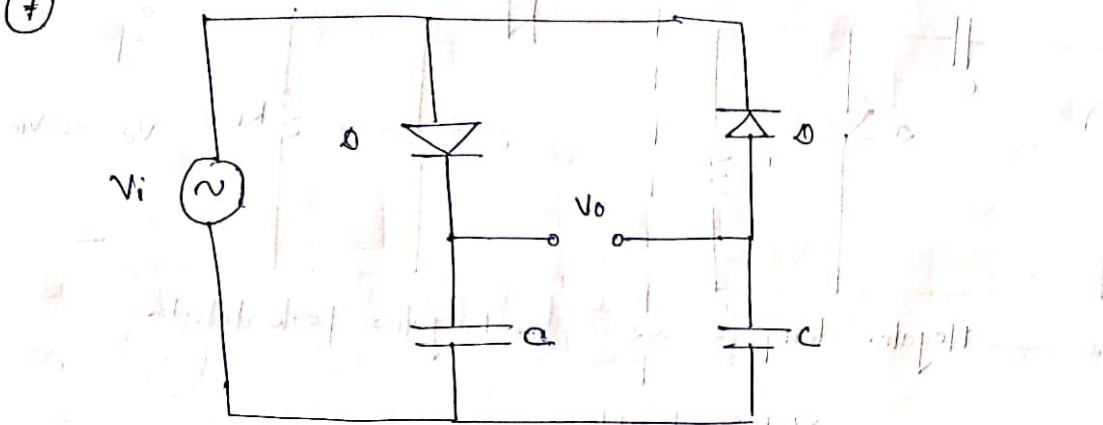
Sol

$$v_{c_1}(0^-) = v_{c_1}(0^+) = 0V$$

$$v_{c_2}(0^-) = v_{c_2}(0^+) = 0V$$

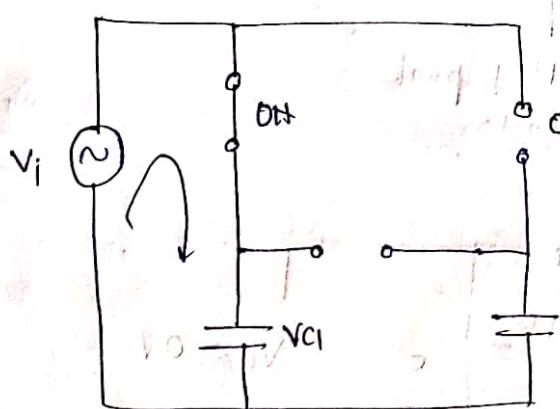i) PHC $[0 < t < T/4]$ ii) PHC $\left[\frac{T}{4} < t < \frac{T}{2}\right]$ 


$$v_{c_1} = v_i$$

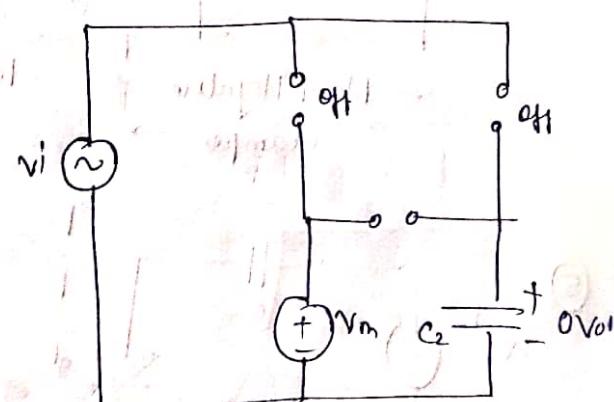

$$v_o = v_m$$

D_1 can never ON because Capacitor is charged to Max^m of V_i

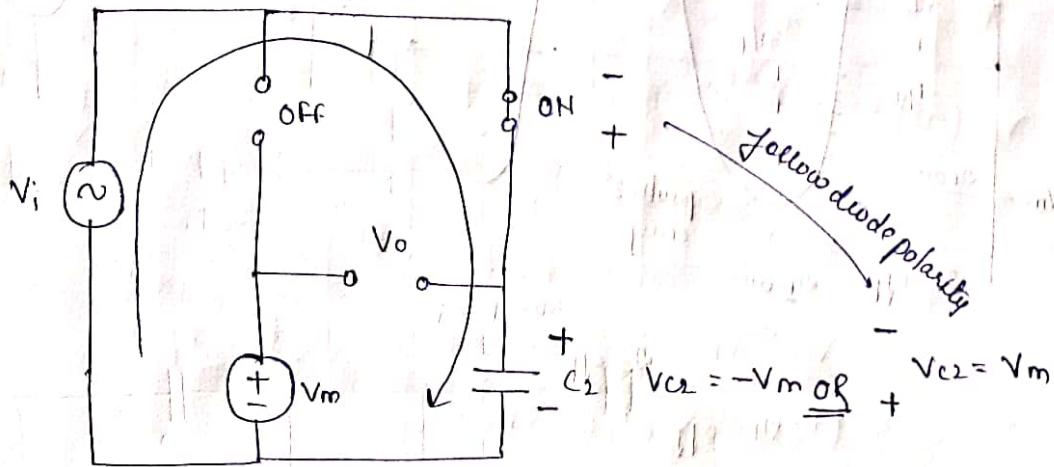During Negative Half Cycle $\frac{T}{2} < t < \frac{3T}{4}$




$$-V_i + 0 + V_{C2} = 0$$

$$V_{C2} = V_i$$

$$V_{C2}(\frac{3T}{4}) = -V_m$$

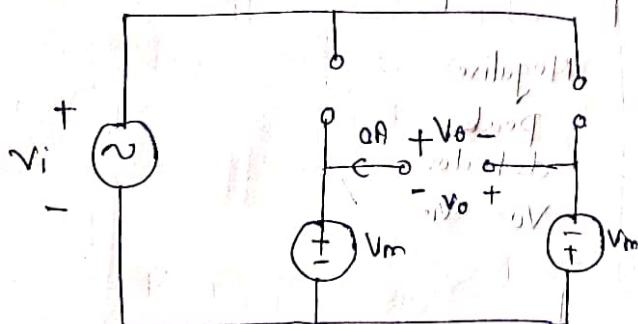After $t = \frac{3T}{4}$ V_{C2} always $-V_m$






Although applying fig $t > \frac{3T}{4}$ steady state figure

$$-V_m + V_o - V_m = 0$$



$$V_o = 2V_m$$

This circuit is a Voltage Doubler

With full wave
clamping polarized

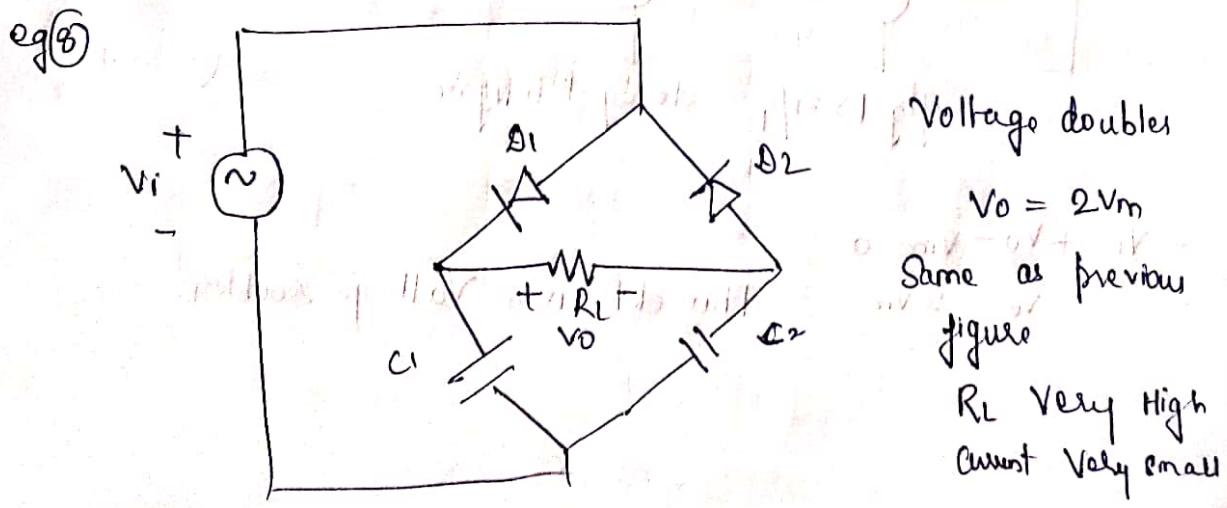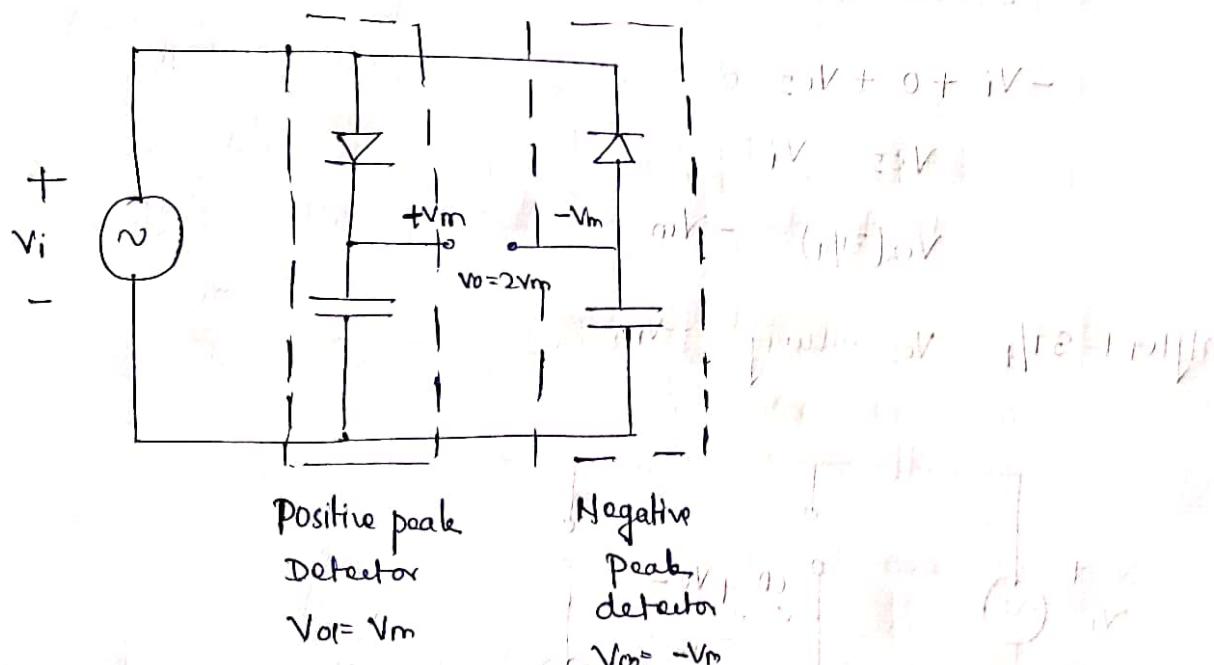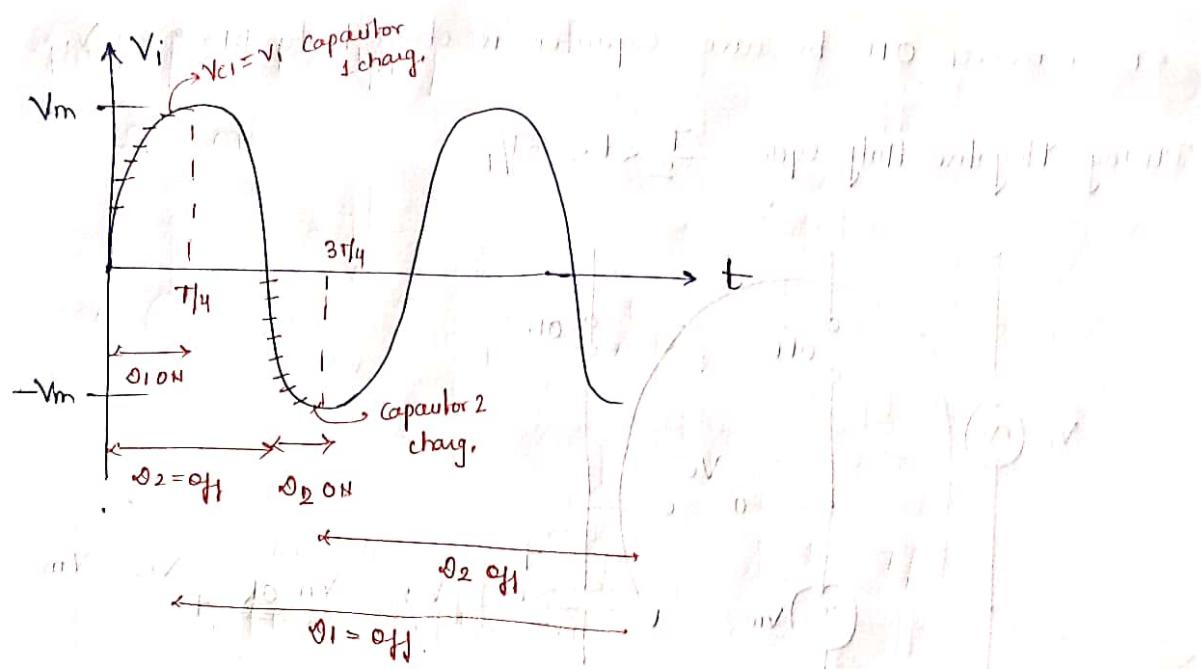


eg 9

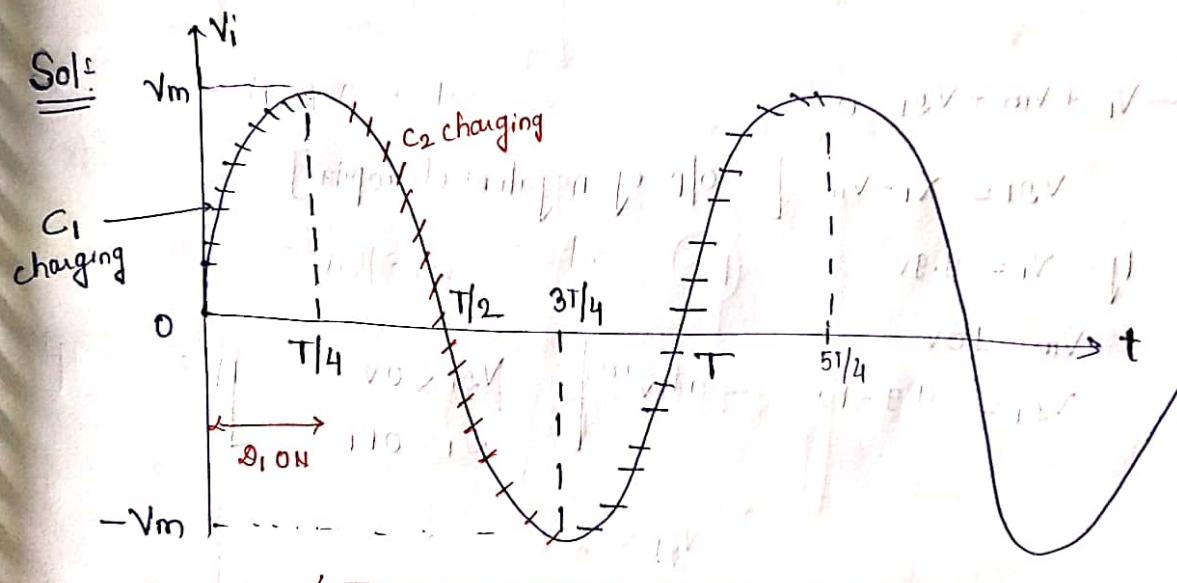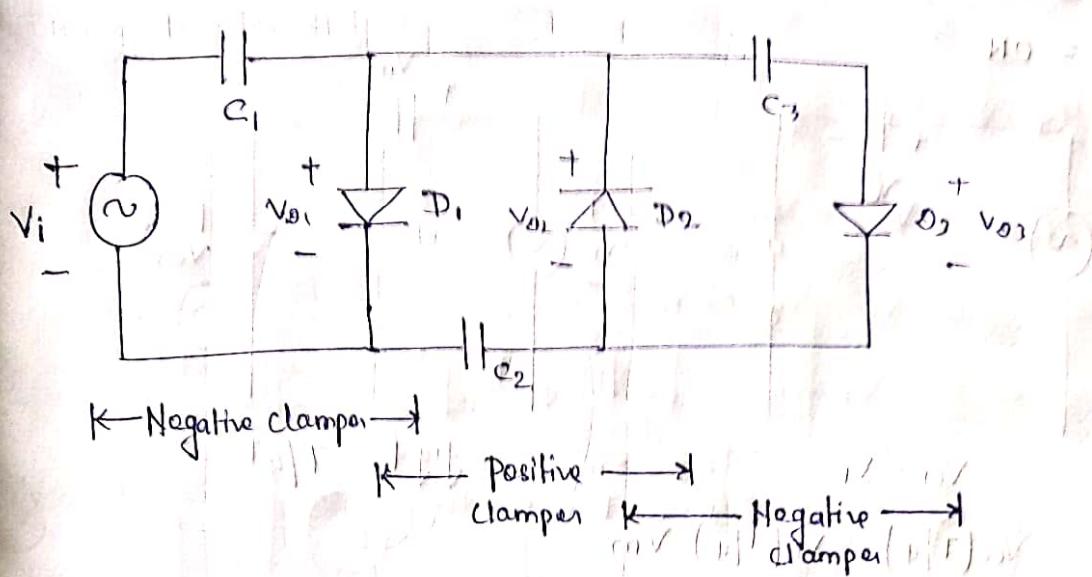


PHC $[0 < t < T/4]$

$D_1 = \text{ON}$

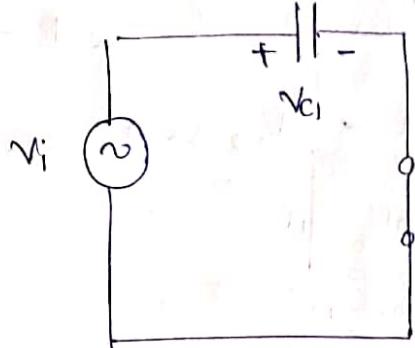

$$V_{C1} = V_i$$

$$V_{C1}(T/4) = V_i(T/4) = V_m$$

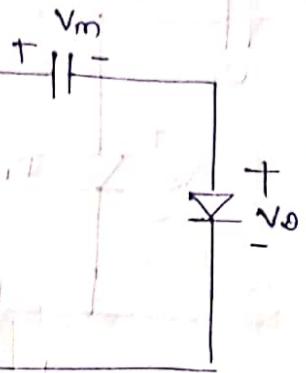

$$\text{fig } t = T/4$$

$$-V_i + V_m + V_{D1} = 0$$

$$V_{D1} = V_i - V_m \quad [\text{Op of negative clapper}]$$


$$\text{If } V_i = 9.9V$$

$$V_m = 10V$$

$$V_{D1} = 9.9 - 10 = -0.1V$$

$$V_{D1} < 0V$$

$D_1 = \text{OFF}$

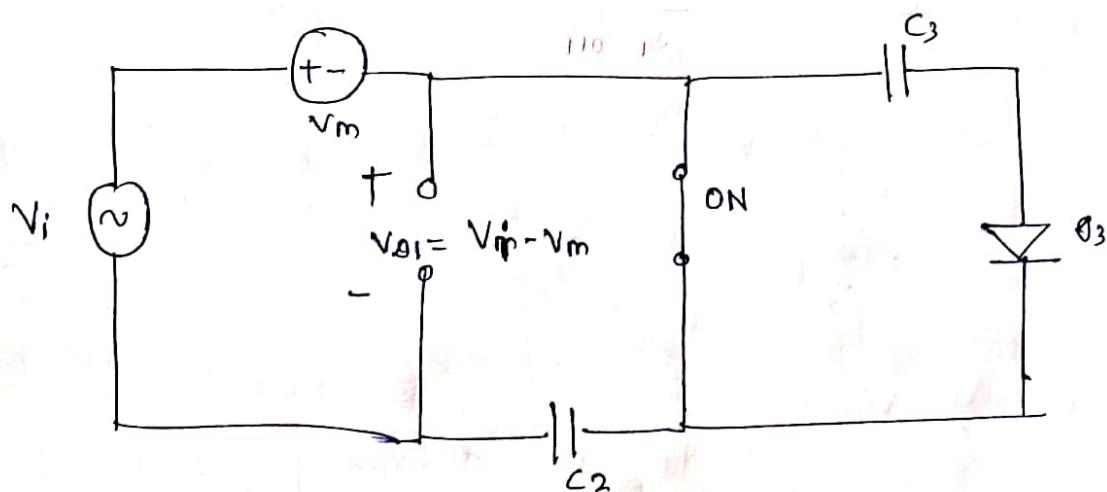

$$\text{fig } t > T/4$$

$$\frac{T}{4} < t < \frac{3T}{4}$$

$$-V_{D1} + 0 - V_{C2} = 0$$

$$V_{C2} = -V_{D1}$$

$$\Rightarrow V_{C2} = V_m - V_i$$

$$V_{C2}(T/4) = V_m - V_i(T/4)$$

$$= V_m - V_m$$

$$= 0V$$

$$V_{C2}(3T/4) = V_m - V_i(3T/4)$$

$$= V_m - (-V_m)$$

$$= 2V_m$$

At $t = 3T/4 +$

$$-V_{D1} + V_{D2} - V_{C2} = 0$$

$$V_{D2} = V_{D1} + V_{C2}$$

$$= V_i + V_m + 2V_m$$

$$V_{D2} = V_i + V_m$$

At $t > 3T/4$

$$V_{D3} = V_{D2}$$

$$D_3 = ON, D_2 = OFF$$


C_3 charging

$$-(V_i + V_m) + V_{C3} + V_{D3} = 0$$

$$V_{C3} = V_i + V_m$$

$$V_{C3}(5T/4) = V_m + V_m$$

$$= 2V_m$$

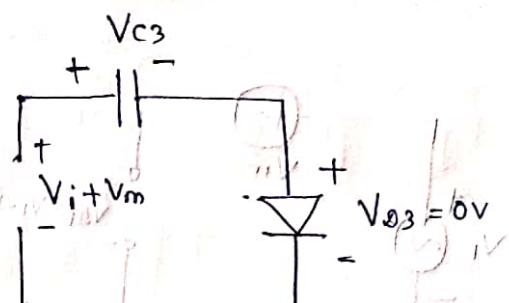



$$\text{At } t = \frac{5T}{4} +$$

$$-V_{02} + V_{C3} + V_{03} = 0$$

$$V_{03} = V_{02} - V_{C3}$$

$$V_{03} = V_i + V_m - 2V_m$$

$$V_{03} = V_i - V_m \quad [\text{O/p of Negative clamped clt}]$$

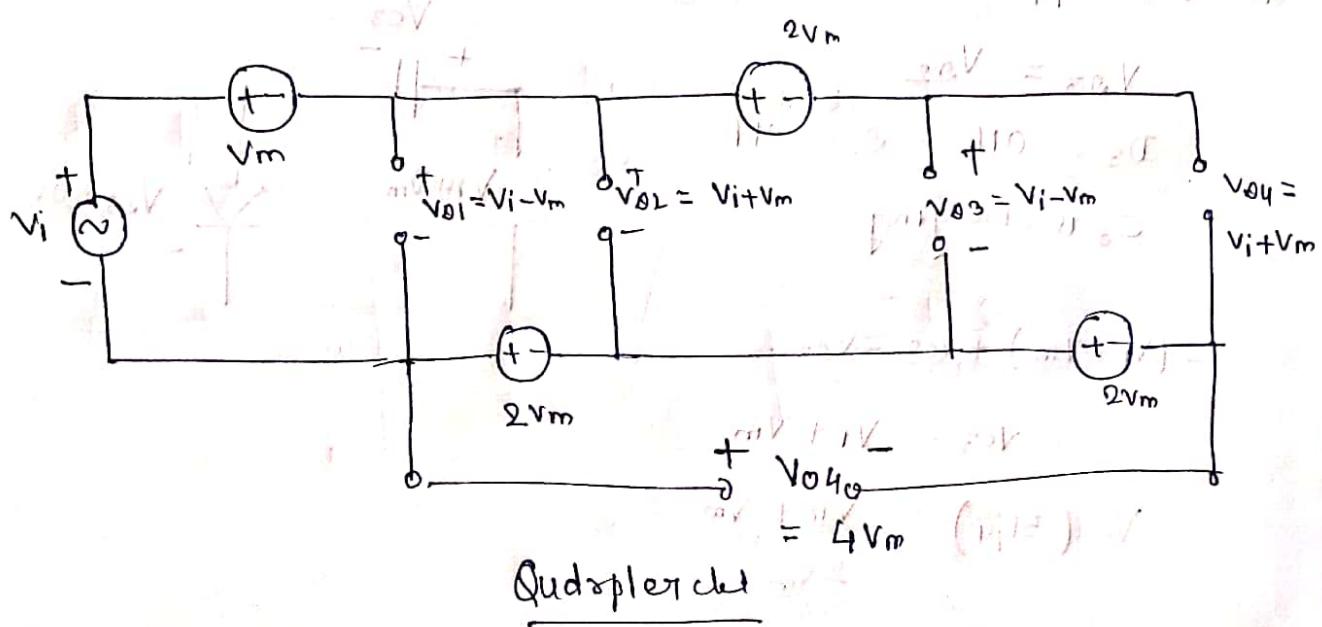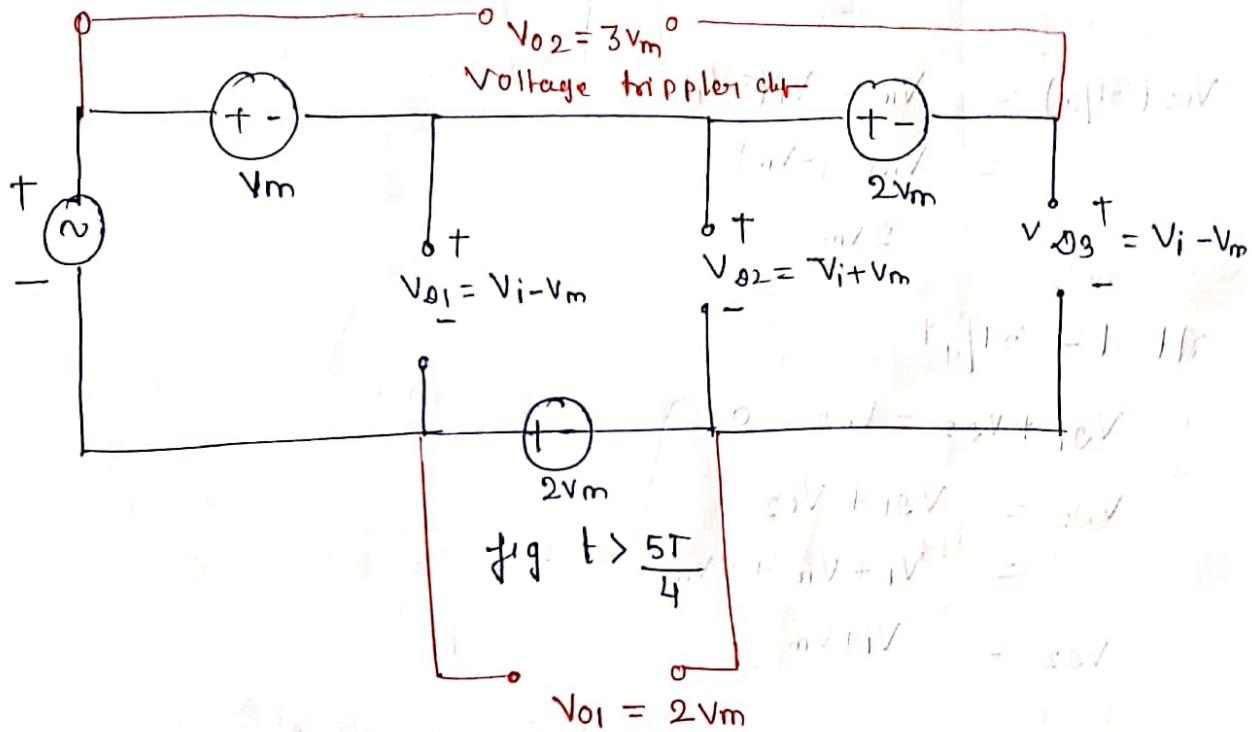

Page 3.7


Q7.

Sol $RC \gg T$

Q6.

Sol The diode and Capacitors in the circuit shown are ideal.

The Voltage $v(t)$ across θ_1 is

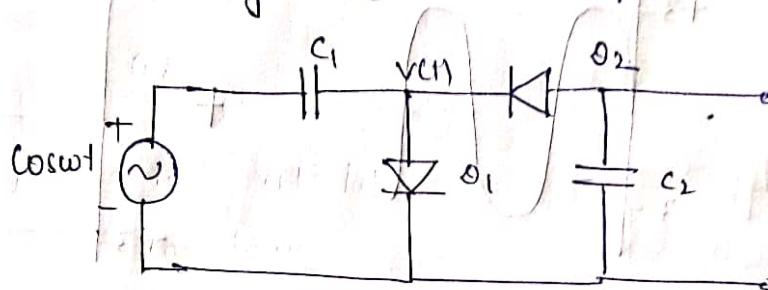


Negative clamp Negative peak detector

$$v(t) = \cos\omega t - 1 \quad \{ v_i - v_m \}$$

Q8.

Sol

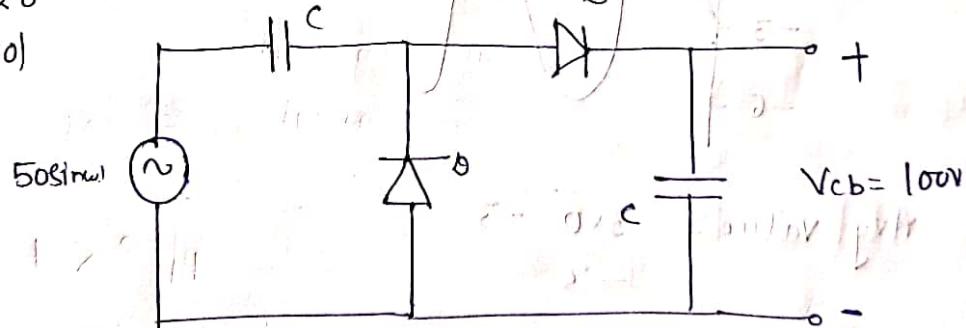

positive clamp

Positive peak detector

$$v_o = 50\sin\omega t + 50$$

Q2.

Sol

$$v_i = 4 + \sqrt{3}\sin\omega t$$

v_i



v_o

By Concept 1) + Capacitor blocks 4v dc
 $V_i = 4 + 3 \sin \omega t$

The clt is negative clamp

$$V_o = V_i - V_m$$


$$V_o = 3 \sin \omega t - 3$$

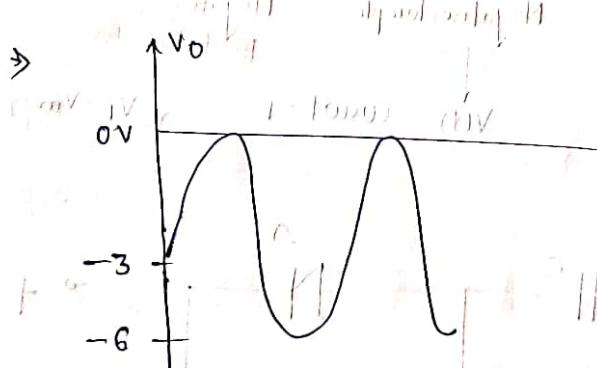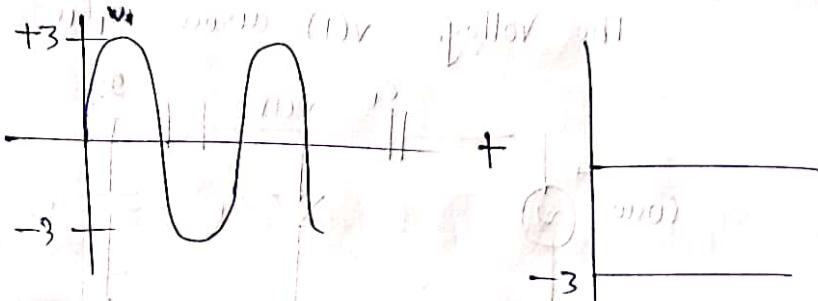

$$\text{Avg value} = 3 \times 0 - 3 = -3$$

By Concept 2) without blocking 4v dc

$$V_i = 4 + 3 \sin \omega t$$

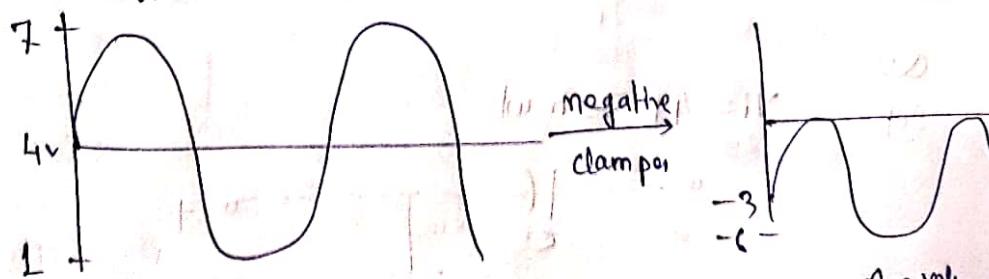


$$V_o = V_i - V_m \Rightarrow V_i - 7$$

$$\text{Avg val} = -3$$

Q4

230V

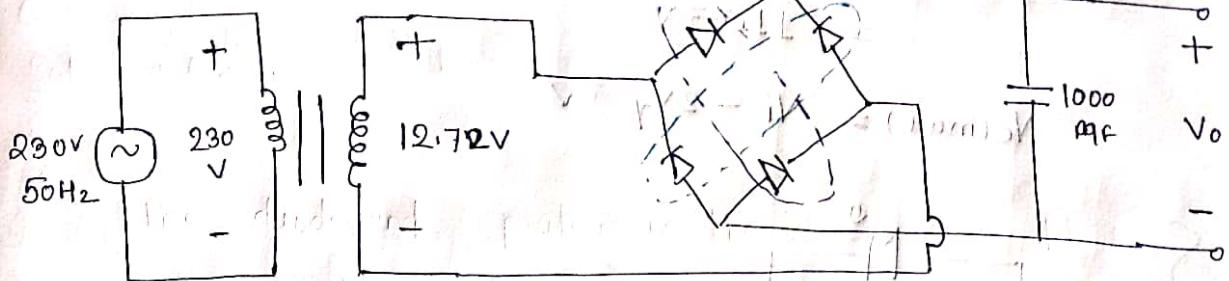

$$V_p(\text{rms}) = 230\text{V}$$

$$\frac{V_p(\text{rms})}{V_s(\text{rms})} = \frac{230}{9}$$


$$\frac{230}{V_s(\text{rms})} = \frac{230}{9}$$

$$V_s(\text{rms}) = 9$$

$$V_s(\text{peak}) = 9\sqrt{2} = 12.72\text{V}$$

Given :- Diode Cut-in Voltage 0.7V

i) During PHC

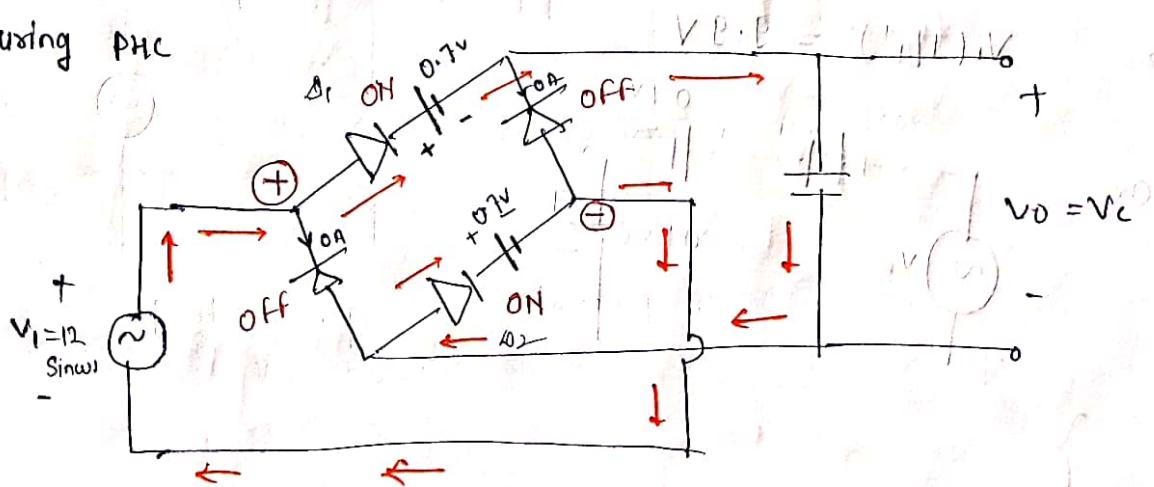



$$-Vi + 0.7 + Vc + 0.7 = 0$$

$$Vi = Vc + 1.4$$

$$Vc = Vi - 2V_d$$

$$V_c(\max) = 12.72 - 2 \times 0.7 \\ = 11.33 \text{ V}$$

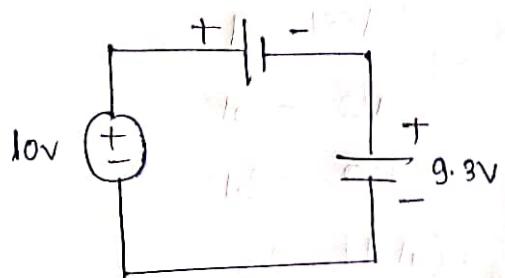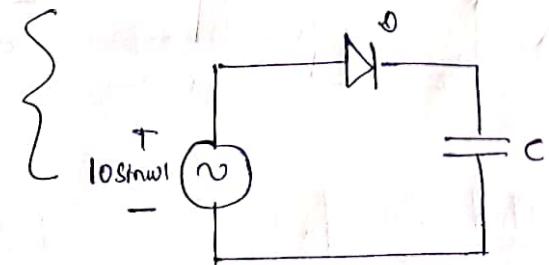
$$V_c(\max) = V_i - 2V_y \quad \checkmark$$



$$V_c(T/4) = 9.3 \text{ V}$$

$$V_c(T/4)^+ = 9.3 \text{ V}$$
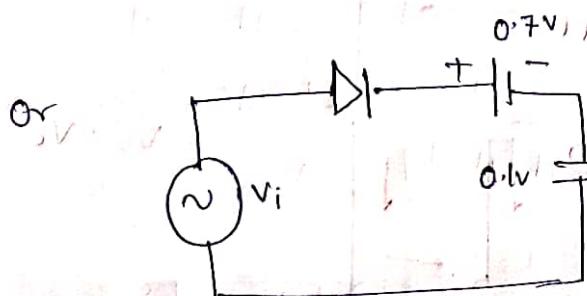
$$\Rightarrow V_i(T/4)^+ = 9.9 \text{ V}$$



}

$$t = \frac{T}{4}^+$$

$$V_c(T/4) = 11.33 \text{ V}$$


$$V_i(T/4^+) = 12.0V$$

$$V_i(T/4^+) > V_c(T/4)$$

$D_1 = ON X$

$D_2 = ON X$

During Negative Half Cycle

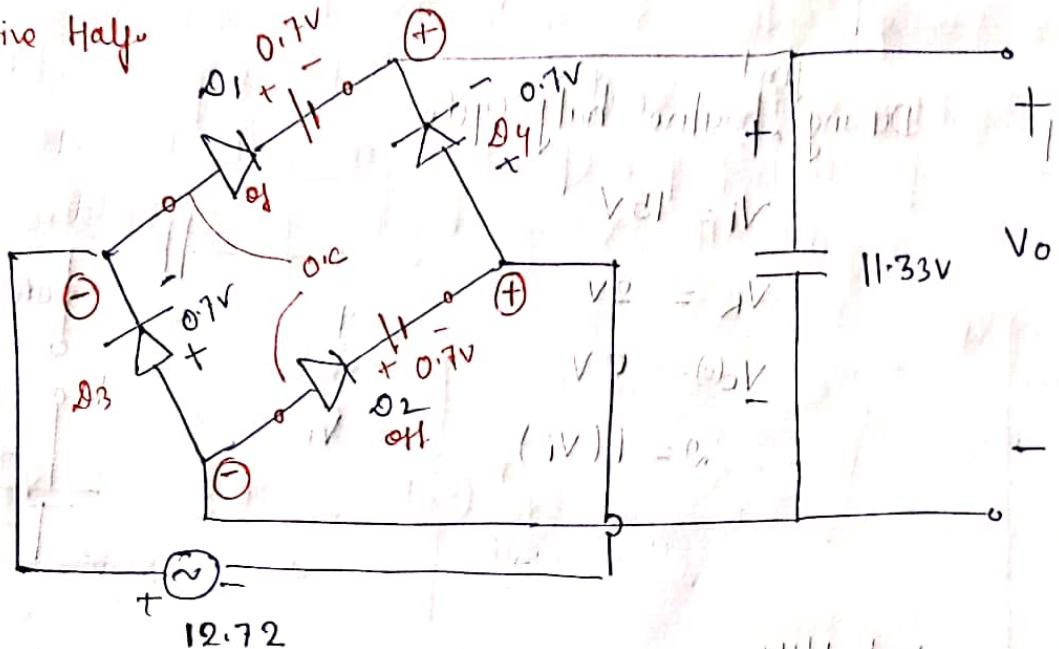


D_1 - Capacitor - D_2 are in Series


$$0.7 + 11.33 + 0.7 = 12.72$$

Diode D_3 & D_4 will not conduct

$$V_0 = 11.33 V$$

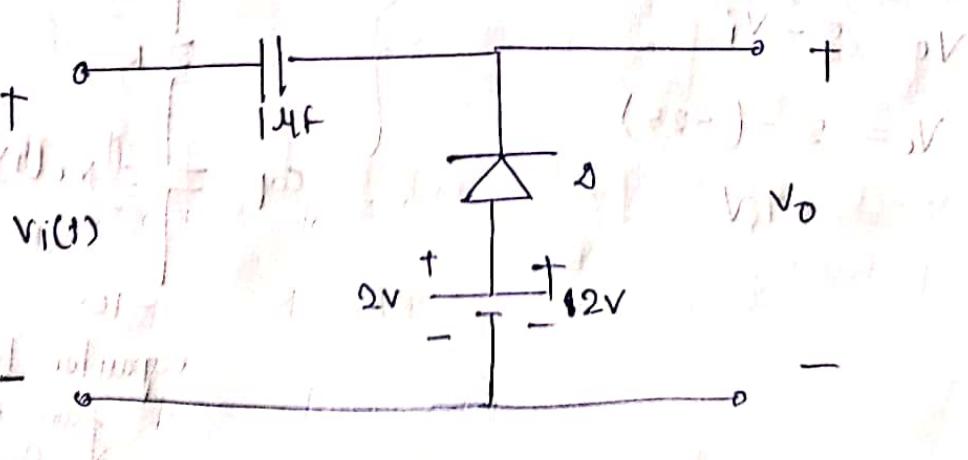Ques. Draw O/P wave for the given below figure.



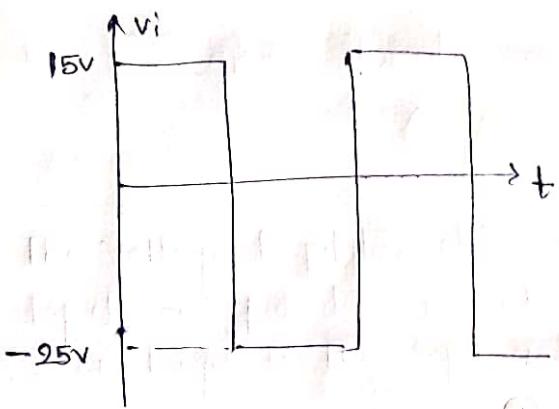


Sol: During first positive half cycle

$$Vi = 15V$$

$$VR = 2V$$

$$Vc(0) = 0V$$

$$\theta = f(Vi)$$

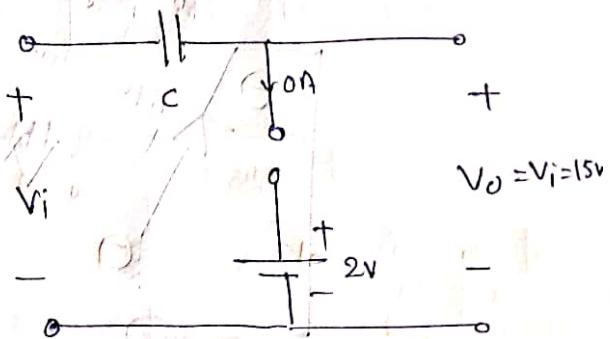


During first NHC

$$Vi = -25V$$

$$VR = 2V$$

$$Vc(+1/2) = 20V$$

$$\theta = f(Vi/VR)$$

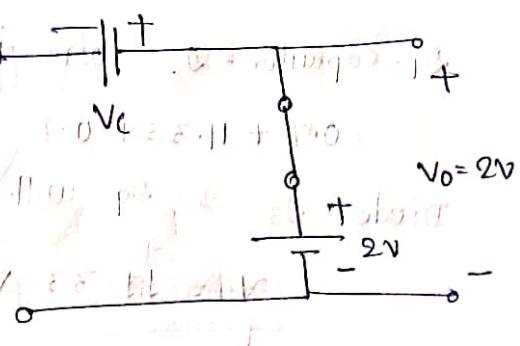


$$-Vi - Vc + 2$$

$$Ve = 2 - Vi$$


$$Vc = 2 - (-25)$$

$$= 27V$$

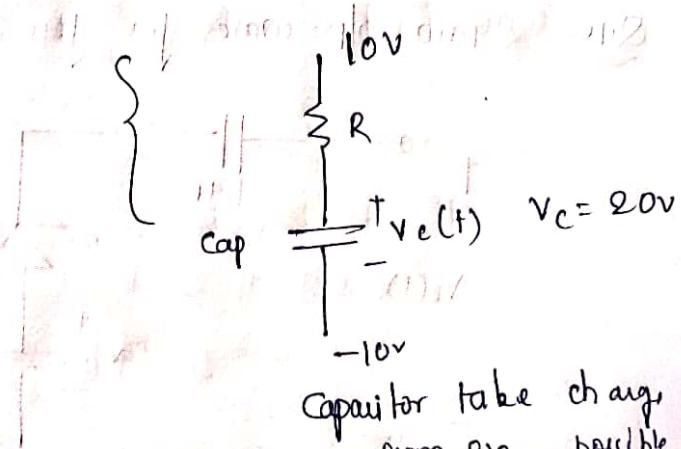

capacitor take charge
from every possible
source



During Second Positive Half Cycle

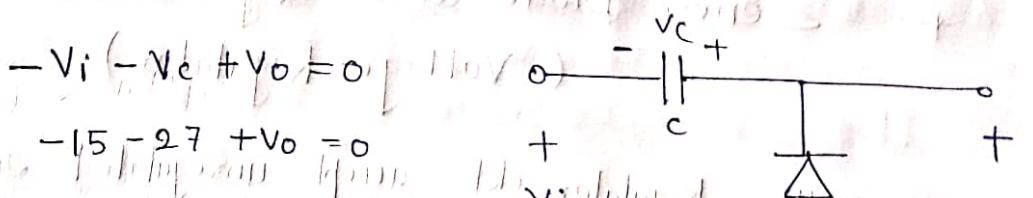

After $V_o = 42$



$\omega = \text{off}$

Second Negative Half Cycle

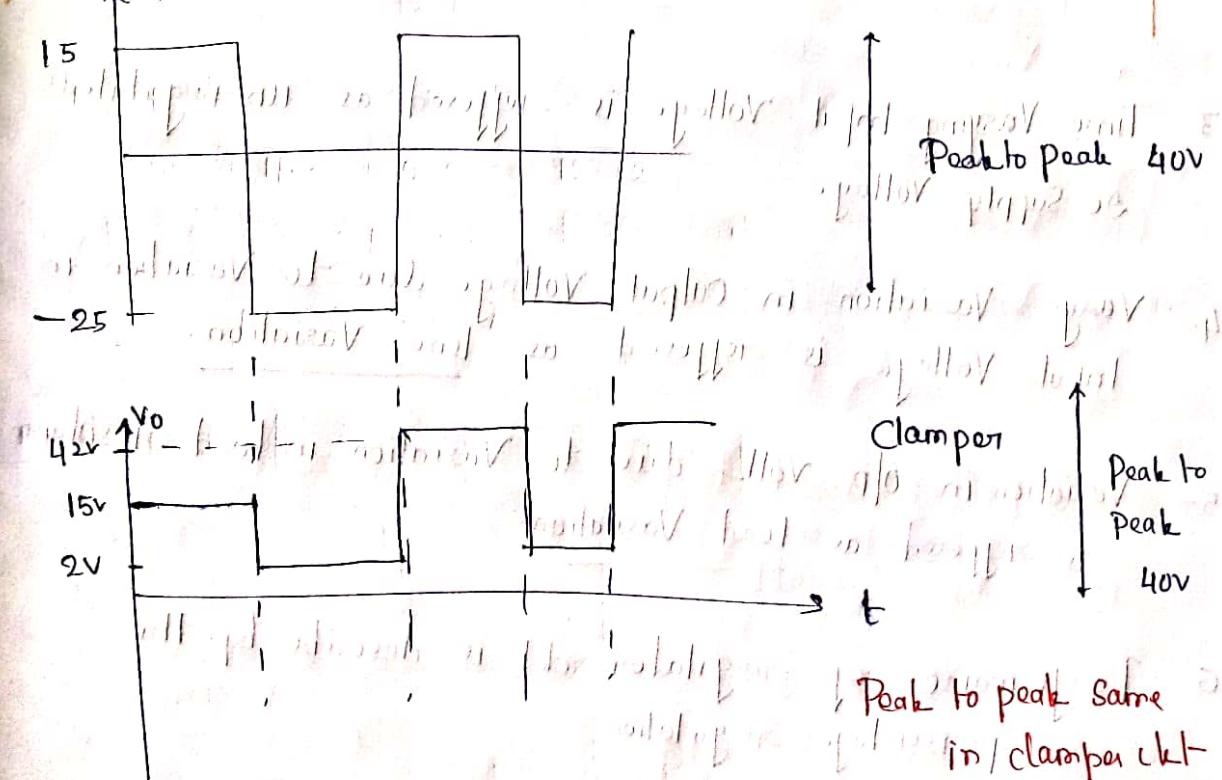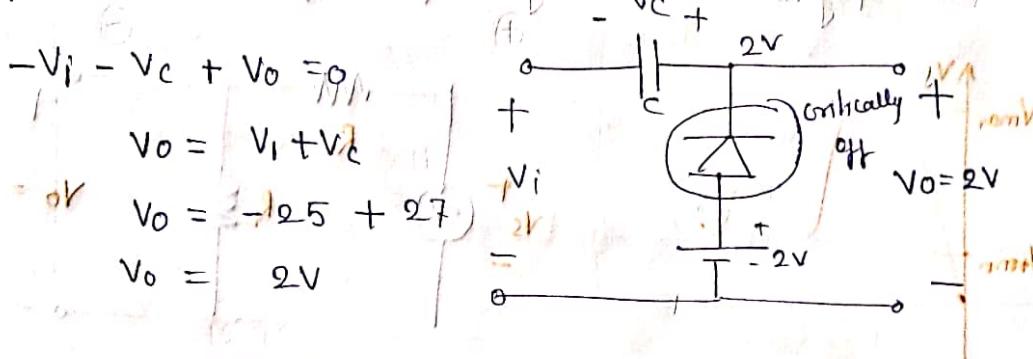

* Zener Diode as a Regulator Circuit (Voltage Regulator)

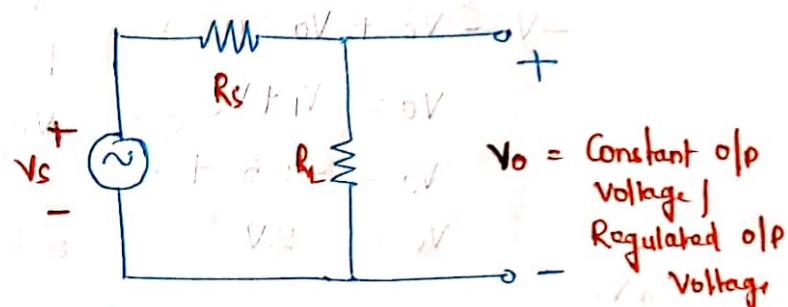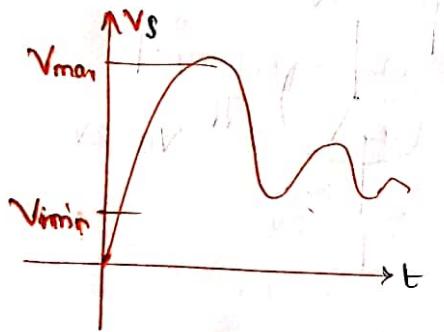1. The Voltage Regulator, ckt accept unregulated DC as an Input and provide Constant DC Output Voltage irrespective of changes in the Input Voltage and Load Current.
2. Most of the electronic Circuit require stable DC voltage for their proper operation. Hence it is necessary to regulate the Voltage before giving it to the electronic ckt.



3. Time Varying Input Voltage is referred as Unregulated DC Supply Voltage.
4. Any Variation in Output Voltage due to Variation in Input Voltage is referred as Line Variation.
5. Variation in o/p volt due to Variation in load resistance is referred as Load Variation.
6. Performance of regulator ckt is describe by the Percentage regulation.

7. Percentage Regulation is defined by -

$$\% R = \frac{V_o[NL] - V_o[FL]}{V_o[FL]} \times 100$$

$V_o[NL]$:-

$$R_L = \infty$$


$$I_L = 0A$$

$V_o[FL]$:-


$$R_{L\min}$$

$$I_L = \max$$


eg

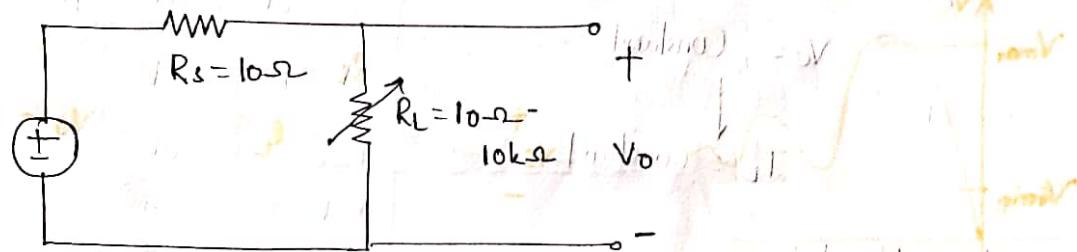

$V_o[NL]$:-

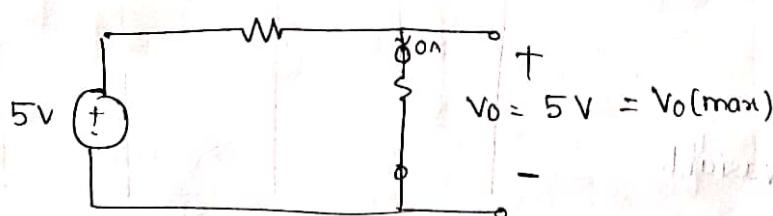

$V_o[FL]$:-

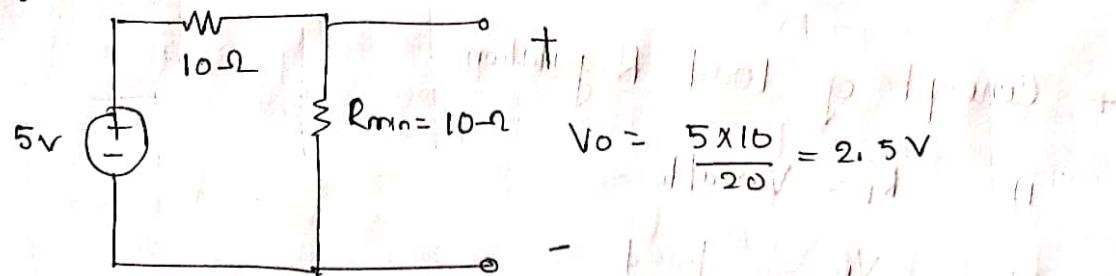

$$\% R = \frac{V_o(NL) - V_o(FL)}{V_o(FL)} \times 100$$

$$\frac{5 - 2.5}{2.5} \times 100 = 100\%$$

8. For better performance of a Regulator $\% R$ should be as low as possible.

Ideally $V_o[fL] = V_o[NL]$

$$\therefore R = 0 \Omega$$

* Concept of Line Regulation:

i) $R_L = \text{fixed}$

ii) $V_{in} = \text{Variable}$

iii) $V_o = I_L R_L$

$V_o = \text{Constant}$

\downarrow
 $I_L = \text{Constant}$

Line Regulation

i) $V_{in} = \text{Variable}$

ii) $V_o = \text{Constant}$

Line Variation

i) $V_{in} = \text{Variable}$

ii) $V_o = \text{Variable}$

* Concept of Load Regulation:

i) $R_L = \text{Variable}$


ii) $V_{in} = \text{fixed}$

iii) $V_o = I_L R_L$


$V_o = \text{Const}$



Types of Voltage Regulator

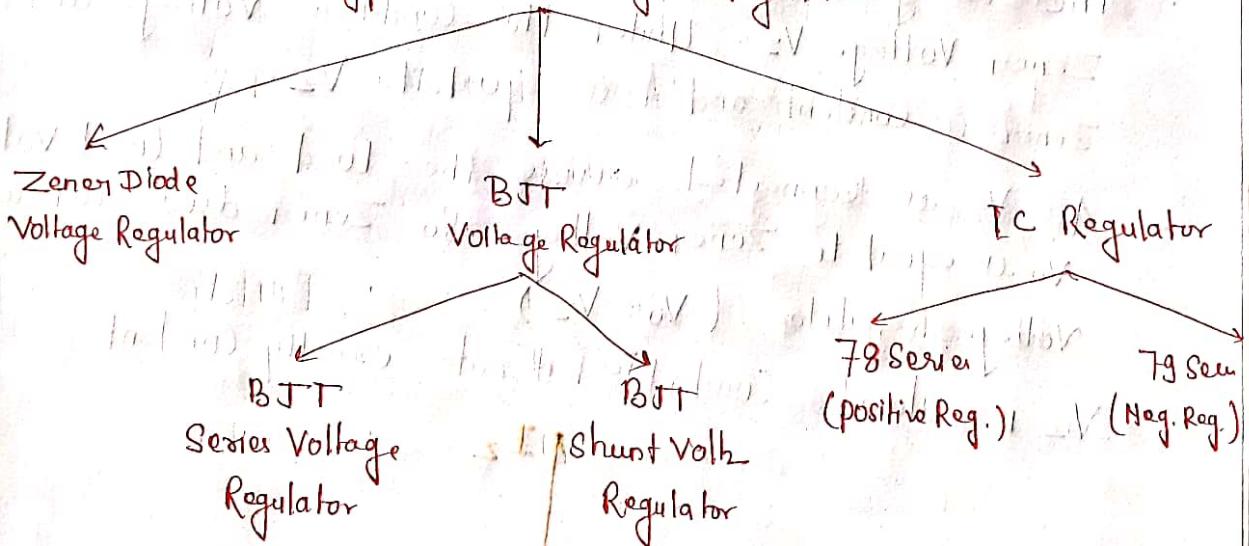

* Zener Diode Voltage Regulator Circuit

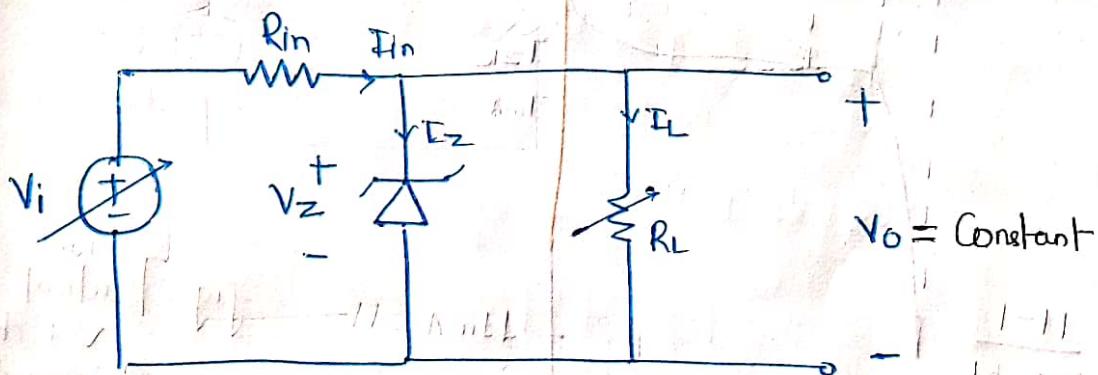

- Zener diode is called Voltage Regulator diode if it maintains Constant Voltage across load.
- Zener diode is used in reverse bias region under this condition, the current through Zener diode is very small when sufficient voltage is applied the Zener breakdown occurs. (Zener diode Conducts) and the large current flow through the Zener diode.
- Zener knee Current I_{ZK} represent Minimum Zener Current which is required to breakdown the Zener diode.

- The Voltage at which Zener diode conducts is called Zener Voltage V_z . Under this condition voltage across Zener is constant and it is equal to V_z .

As V_z is connected across the load and load voltage V_o is equal to Zener voltage. So Zener diode acts as a Voltage Regulator ($V_o = V_z$)

- V_z is almost constant but not exactly constant.


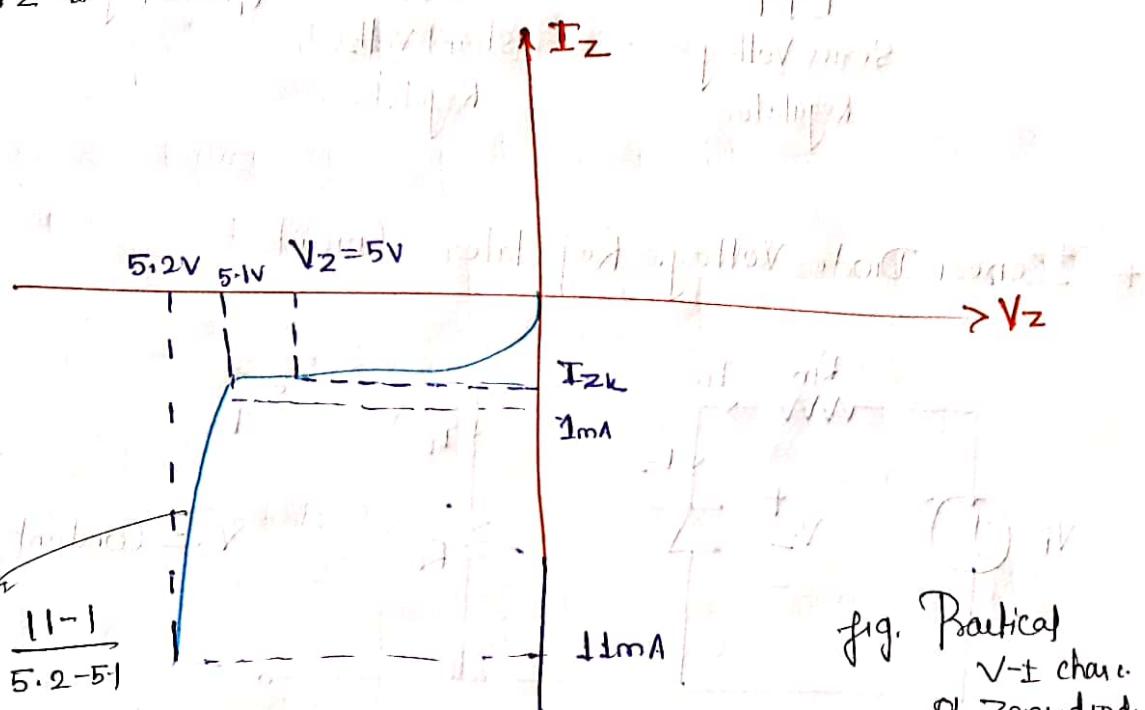
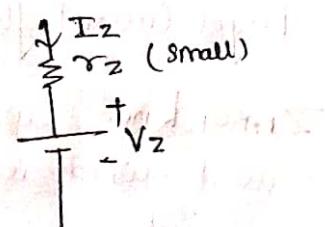


fig. Practical
V-I char.
of Zener diode


r_Z = Zener Resistance in BO region

$$r_Z = \frac{1}{\text{slope}} = \frac{1}{100} = \frac{1000}{100} = 10\Omega \text{ (small)}$$

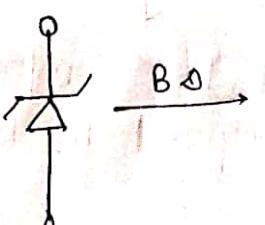- Practical equivalent circuit of Zener diode in breakdown region is given by -



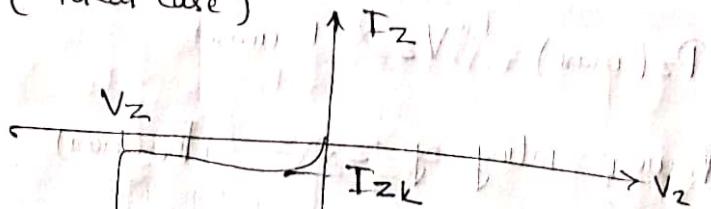
- If Zener Resistance R_Z is not given then assume
 $R_Z = 0 \Omega$ (Ideal Case)



$\frac{1}{R_Z} = \infty$

fig. Ideal VI characteristic of Breakdown Zener diode

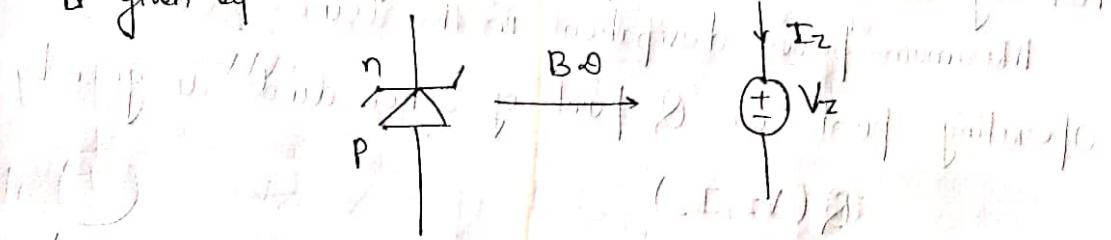- Ideal equivalent circuit of Zener diode in breakdown Region is given by



Range of parameters

$$I_{L\min} < I_L < I_{L\max}$$

$$I_{Z\min} < I_Z < I_{Z\max}$$

$$R_{L\min} < R_L < R_{L\max}$$

$$V_{in\min} < V_{in} < V_{in\max}$$

* If $I_{Z\min}$ is not given then we can assume $I_{Z\min} = I_{ZK} = 0A$

* If $I_{L\min}$ is not given then we can assume $I_{L\min} = 0$ (conditional)

- Power dissipation across Zener diode is given by

$$P_Z = V_Z I_Z \text{ W}$$

$$P_z(\text{min}) = V_z \times I_z(\text{min})$$

$$P_z(\text{max}) = V_z \times I_z(\text{max})$$

Power rating of $Z_D = P_z(\text{max})$

or

Minimum power rating of $Z_D = P_z(\text{min})$

- $I_z \text{ max}$ (Maximum Current across Zener diode) depends on its power rating.
- The power Rating of any device is Maximum allowed Power dissipation.
- for any device minimum power rating should be equal to Maximum power dissipation in the device.
- Operating point or Q point of Zener diode is given by $Q(V_z, I_z)$

• Zener diode is a special purpose diode having greater power handling capability.


• Heavily doped Zener diode have low breakdown voltage and breakdown occur with Zener process.

• Lightly doped Zener diode have high breakdown voltage & breakdown occur with Avalanche process.

• Since Zener diode and load resistance is connected in shunt so circuit is known as shunt Regulator.

• In Zener diode shunt Regulator circuit R_{in} represent current limiting resistance which prevent flow of heavy current through Zener diode

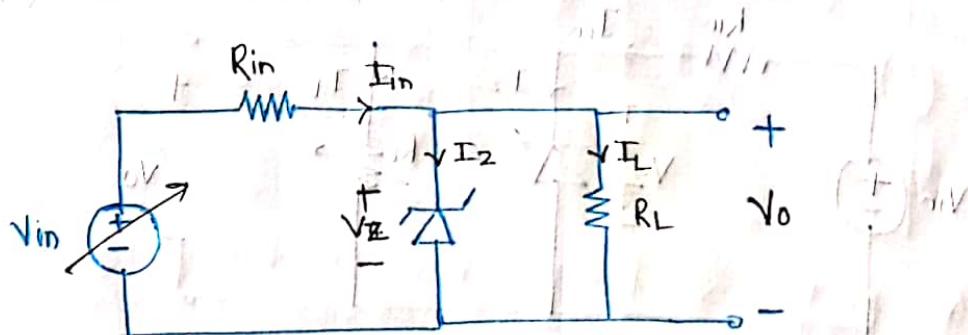Case I - Line Regulation ($V_{in} = \text{Varying}$, $R_L = \text{fixed}$)



$$I_{in} = \frac{V_{in} - V_z}{R_{in}} \quad \text{--- (1)}$$

$$I_{in} = I_L + I_z \quad \text{--- (2)}$$

$$\frac{V_{in} - V_z}{R_{in}} = I_z + I_L \quad (\text{fixed}) \quad \text{--- (3)}$$


$$\frac{V_{in(\min)} - V_z}{R_{in}} = I_{in(\min)} = I_{z(\min)} + I_{L(\min)} \quad \text{--- (4)}$$

$$\frac{V_{in(\max)} - V_z}{R_{in}} = I_{in(\max)} = I_{z(\max)} + I_{L(\max)} \quad \text{--- (5)}$$

points :- 1) It is a process of Maintaining DC output Voltage Constant irrespective of Variation in Line Voltage.

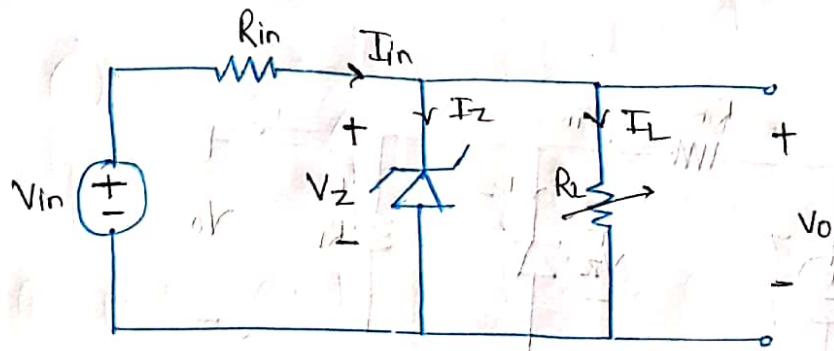- i) In Line Regulation Load Current is assumed to be constant.
- ii) Minimum Input Voltage provide Minimum Input Current and Minimum Input Current provide Minimum Zener Current.
- iii) Max. Input Voltage provide Max. Input Current & Max Input Current provide Max. Zener Current.
- iv) In Case $I_{z(\min)}$ is not given Then assume $I_{z\min} = 0$

Case II Load Regulation ($M_{in} = \text{fixed}$, $R_L = \text{Variable}$)



$$I_{in} = \frac{V_{in} - V_z}{R_{in}} \quad (1)$$

$$I_{in} = I_z + I_{L(\text{var})} \quad (2)$$

$$\frac{V_{in} - V_z}{R_{in}} = I_z + I_{L(\text{var})} \quad (3)$$

$$\frac{V_{in(\text{fix})} - V_z}{R_{in}} = I_{in(\text{fix})} = I_{z(\text{max})} + I_{L(\text{min})} \quad (4)$$

$$\frac{V_{in(\text{fix})} - V_z}{R_{in}} = I_{in(\text{fix})} = I_{z(\text{min})} + I_{L(\text{max})} \quad (5)$$

Keypoint: i) It is the process of maintaining DC o/p Voltage constant irrespective of variation in load current.

ii) In Load Regulation Line Voltage or O/P Voltage is assumed to be constant.

$$V_o = I_L R_L = \text{constant}$$

$$I_L = \frac{V_o}{R_L}$$

$$I_{L\text{min}} = \frac{V_o}{R_{L\text{max}}} \quad I_{L\text{max}} = \frac{V_o}{R_{L\text{min}}}$$

In Case of no Load Condition $R_L = \infty$ that means
 $I_{L\min} = 0$

* Concept of Breakdown :-
Initially $Z = \text{Reverse bias } [0.0]$

$$V_o = V_{in} \frac{R_L}{R_{in} + R_L}$$

when $V_o > V_Z$ \Rightarrow $V_o = V_Z$
 $Z = B \cdot 0$

$$V_{in} \frac{R_L}{R_{in} + R_L} > V_Z$$

$$\Rightarrow V_{in} > V_Z \left[\frac{R_{in} + R_L}{R_L} \right]$$


at designing

$$\textcircled{1} \quad R_L \gg R_{in} \Rightarrow V_{in} > V_Z$$

$$\textcircled{2} \quad R_L = \infty \Rightarrow V_{in} > V_Z$$

GrEC 92

Ques.

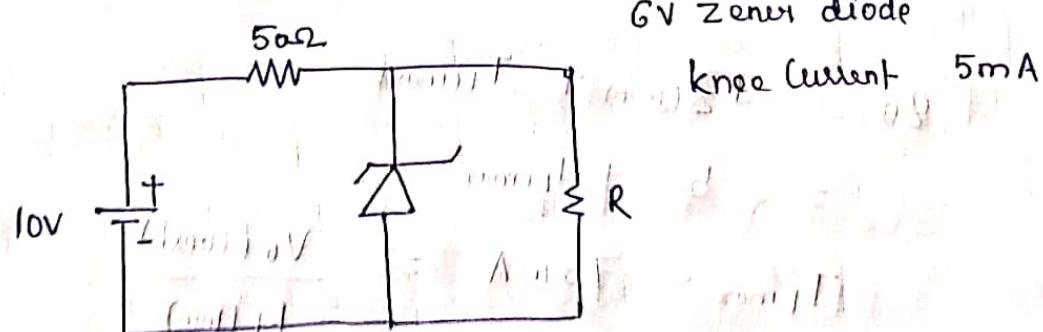


Sol Given, $V_{Zr} = 0$

Zener knee Current = Min knee Current = 5mA

$$V_Z = 6V$$

Min. Value of R for
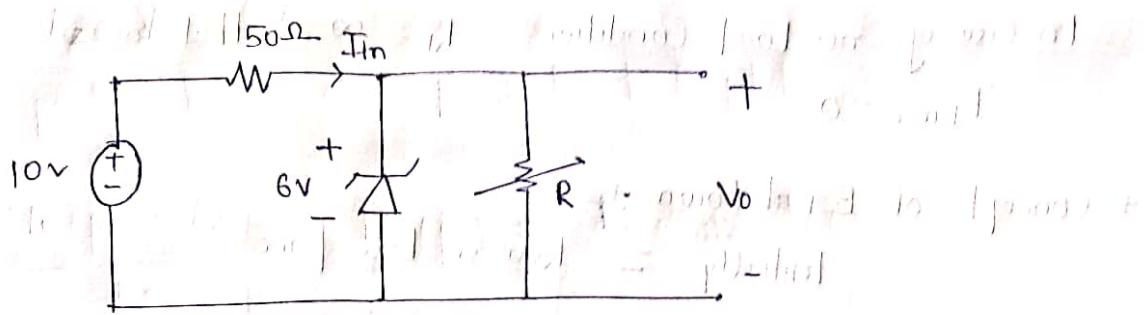
$$\text{output } V_{OL} = B_V \text{ (constant)}$$



This Concept is Question is based on Concept of Load Regulation.

$$\frac{V_{in(yia)} - V_Z}{R_{in}} = I_{in(yia)} = I_{Z(\max)} + I_{L(\min)}$$

$$\frac{V_{in(yia)} - V_Z}{R_{in}} = I_{in(yia)} \leq I_{Z(\min)} + I_{L(\max)}$$

$$I_{in(yia)} = \frac{V_{in(yia)} - V_Z}{R_{in}}$$

$$= \frac{10 - 6}{50} = \frac{4}{50} = 0.08 \text{ A}$$

$$I_{in(yia)} = 80 \text{ mA}$$

$$80 = I_{Z(\min)} + I_{L(\max)}$$

$$= 5 + I_{L(\max)}$$

$$I_{L(\max)} = 75 \text{ mA} = \frac{V_o (\text{const})}{R_{L(\min)}}$$

$$R_{L(\min)} = \frac{V_o (\text{const})}{75 \text{ mA}}$$

$$= \frac{6}{75 \text{ mA}} = \frac{6000}{75}$$

$$(Ans) R_{L(\min)} = 80 \Omega //$$

Concept:

$$V_{in} > V_Z \left[\frac{R_L + R_{in}}{R_L} \right]$$

$$V_{in} > V_Z \left[\frac{80 + 50}{80} \right] = 1.75 V$$


$$V_{in} > 9.75$$

R_L Cannot be less than 60Ω for Zener diode to work as a Regulator.

$$\text{If } R_L = 50\Omega$$

$V_o = 15\Omega$ ($Z = R_B$) That means no Regulation

Q.2

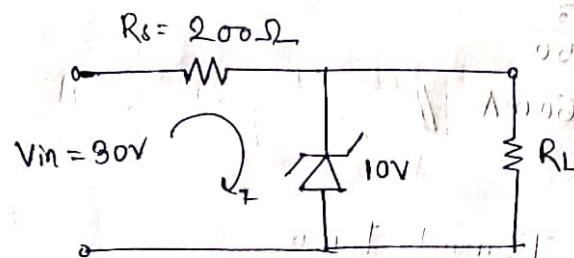


Sol

No information of R_L . Assume $R_L = \infty$ $Z = B.D$

$$I = \frac{30 - 10}{200} = 0.01 \text{ A}$$

$$P = I^2 R = 0.01 \times 200 = 2 \text{ W}$$

Q.3.

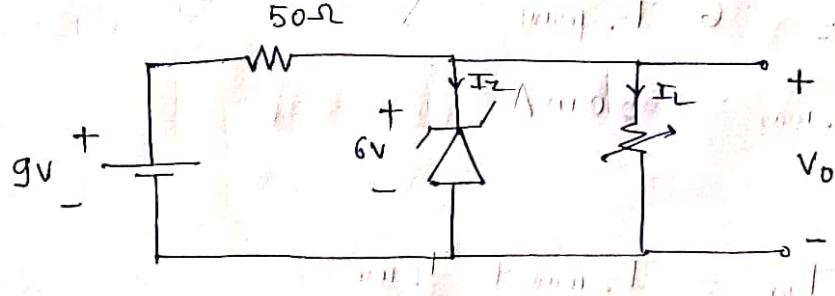

$$I_z \text{ min} = 5 \text{ mA}$$

Max allowed power dissipation of Zener diode = 300mW

$$P_z(\text{max}) = 300 \text{ mW}$$

$$V_Z = V_0 = 6V$$

This question based on Concept of Load Regulation

$$\frac{V_{in(yix)} - V_Z}{R_{in}} = I_{in(yix)} = I_{Z(\max)} + I_{L(\min)}$$

$$\frac{V_{in(yix)} - V_Z}{R_{in}} = I_{in(yix)} = I_{Z(\min)} + I_{L(\max)}$$

$$I_{in(yix)} = \frac{9 - 6}{50}$$

$$= \frac{3}{50}$$

$$= 60 \text{ mA}$$

from ① eqn

$$60 \text{ mA} = I_{Z\min} + I_{L\max}$$

$$60 = 5 + I_{L\max}$$

$$I_{L\max} = 55 \text{ mA}$$

$$P_{Z(\max)} = V_Z I_{Z(\max)}$$

$$300 = 6 I_{Z\max}$$

$$I_{Z\max} = 50 \text{ mA}$$

from ①


$$I_{in} = I_{Z\max} + I_{L\min}$$

$$60 - 50 = I_{L\min}$$

$$I_{L\min} = 10 \text{ mA}$$

Concept: If P_z was not given
 Then consider no load i.e. $R_L = \infty$
 i.e. $I_L(\text{min}) = 0 \text{ mA}$
 Hence in this case, I_L vary 0mA to 50mA

Que 6

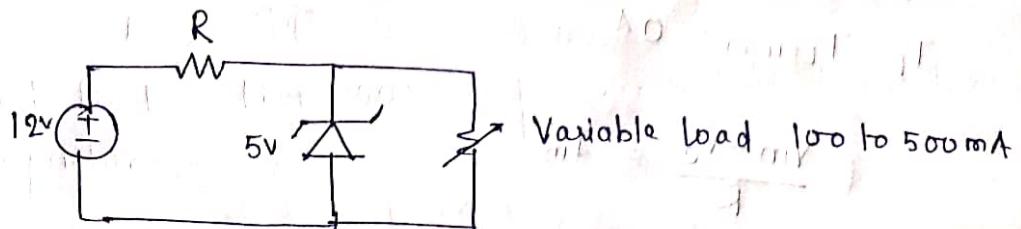

Sol

$$I_{L\text{min}} = 100 \text{ mA} \quad I_{L\text{max}} = 500 \text{ mA} \quad \text{Load Regulation}$$

$$\sigma_z = 0 \quad I_z = \text{negligible}$$


$$R = ?$$

$$I_{L(\text{avg})} = \frac{I_{L\text{min}} + I_{L\text{max}}}{2} = \frac{100 + 500}{2} = 300 \text{ mA}$$

$$\frac{12 - 5}{R} = 0 + 300 \Rightarrow R = \frac{7}{300} = 23.33 \Omega$$

$$R = \frac{12 - 5}{500 \text{ mA}} = \frac{7}{500} = 14 \Omega$$

Que 8

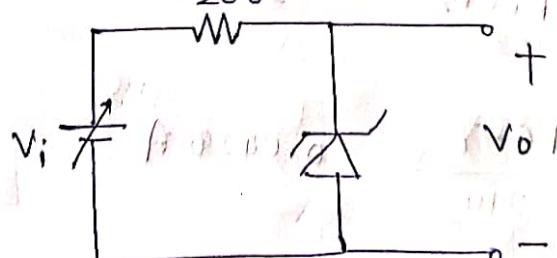

$$\text{Given } V_i = 10 \text{ to } 16 \text{ V}$$

$$R = 200 \Omega$$

$$Z = \sqrt{V_i} \text{ V (B.s)}$$

Question is based on line Regulation becaz Var 1/p Volt

$$V_Z = 7V \quad I_{Z(\min)} = 0$$

$$\tau_Z = 10\Omega \quad \text{from fig.}$$

from fig., $R_L = \infty$ (No load condition)

$$R_{L(\max)} = \infty$$

$$I_L = I_{L(\min)} = 0A$$

Now, also, $\frac{V_{in} - V_0}{R} = I_{in}$

$$V_{in(\text{var})} - V_0 = I_{in(\text{var})} R$$

$$I_{in(\text{var})} = I_{Z(\text{var})} + I_{L(\text{var})}$$

$$I_{in(\min)} = I_{Z(\min)} + 0$$

$$I_{in(\max)} = I_{Z(\max)} + 0$$

$$I_{in(\min)} = \frac{V_{in(\min)} - V_0}{R_{in}}$$

$$I_{in(\min)} = \frac{V_{in} - V_Z}{R_{in} + \tau_Z} = \frac{10 - 7}{200 + 10} = \frac{3}{210} = 0.014A$$

$$\text{also } I_{in(\max)} = \frac{16 - 7}{210} = 0.0428A$$

$$V_0 = I_Z \tau_Z + V_Z$$


$$V_{0(\min)} = 0.014 \times 10 + 7 = 7.14V$$

$$V_{0(\max)} = 0.042 \times 10 + 7 = 11.28V$$

Variation
due to τ_Z

B

Q.10.

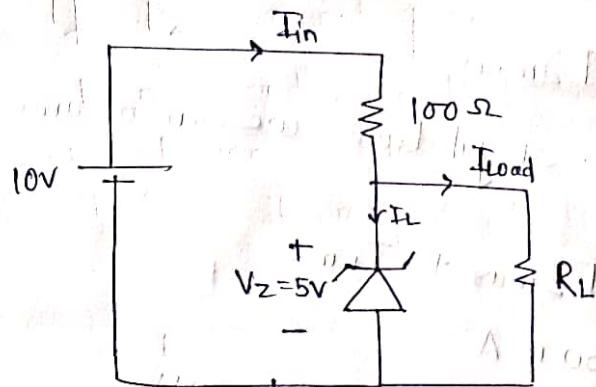

$$I_{z\min} = 10 \text{ mA}$$

$$V_o = 5V$$

$R_L \text{ min} = ?$ Power Rating of zener diode
in mW

So Given $V_z = 5V$

Load Regulation

$$I_{in} = \frac{10 - 5}{100} = 0.05 \text{ A}$$

$$I_{in(\text{min})} = 0.05 \text{ A}$$

$$V_{in(\text{min})} =$$

$$I_{in\min} = I_{L\max} + I_{z\min}$$

$$0.05 = I_L + 0.010$$

$$I_{in\max} = I_z + I_{L\max}$$

$$I_{L\max} = 0.05 + 0.010 = 40 \text{ mA}$$

$$V_o = 5V$$

$$I_L = \frac{V}{R}$$

$$R_{\min} = \frac{5}{I_{L\max}} = \frac{5 \times 10^{-3}}{40} = 125 \Omega$$

ii) $P_{z\min} = V_z I_{z\min}$

$$P_{z\max} = V_z I_{z\max}$$

$$P_{Z\max} = V_Z I_{Z(\max)}$$

In Case of Load regulation we can assume $I_{L\min} = 0$

$$I_{in} = I_{Z\max} + I_{L\min}$$

$$I_{Z\max} = 50 \text{ mA}$$

$$P_{Z\max} = 5 \times 50$$


minimum output power = 250 mW

concept

$$\left. \begin{array}{l} \text{min power of Zener diode} = P_{Z\min} = I_{Z\min} V_Z \\ \text{min power rating of Zener diode} = P_{Z\max} = I_{Z\max} V_Z \end{array} \right\}$$

$$\left. \begin{array}{l} \text{min power of Zener diode} = P_{Z\min} = I_{Z\min} V_Z \\ \text{min power rating of Zener diode} = P_{Z\max} = I_{Z\max} V_Z \end{array} \right\}$$

Ques.

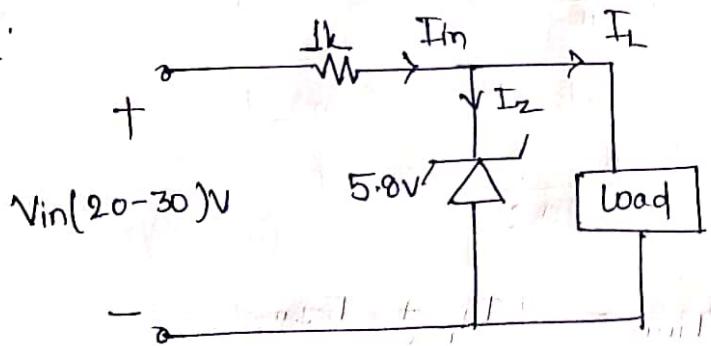

Sol

$$V_Z = 5.8 \text{ V}$$

$$I_{Z\min} = 0.5 \text{ mA}$$

$$V_{in} = 20 \text{ to } 30 \text{ V} \quad I_{L\max} = ?$$

Line Regulation

$$\frac{V_{in(\text{var})} - 5.8}{1k} = I_{in}$$

$$\frac{V_{in(\min)} - 5.8}{1k} = I_{in\min} = \frac{20 - 5.8}{1k} = 14.2 \text{ mA}$$


$$\frac{V_{in(max)} - 5.8}{1k} = I_{in(max)} = 24.2 \text{ mA}$$

$$I_{in(min)} = I_{zmin} + I_{fix} \Rightarrow I_{fix} = 14.2 - 0.5 = 13.7 \text{ mA}$$

$$I_{in(max)} = I_{zmax} + I_{fix}$$

There is no I_{zmax} . Hence it can only ask for simply load current because load current is fix.

Q11.

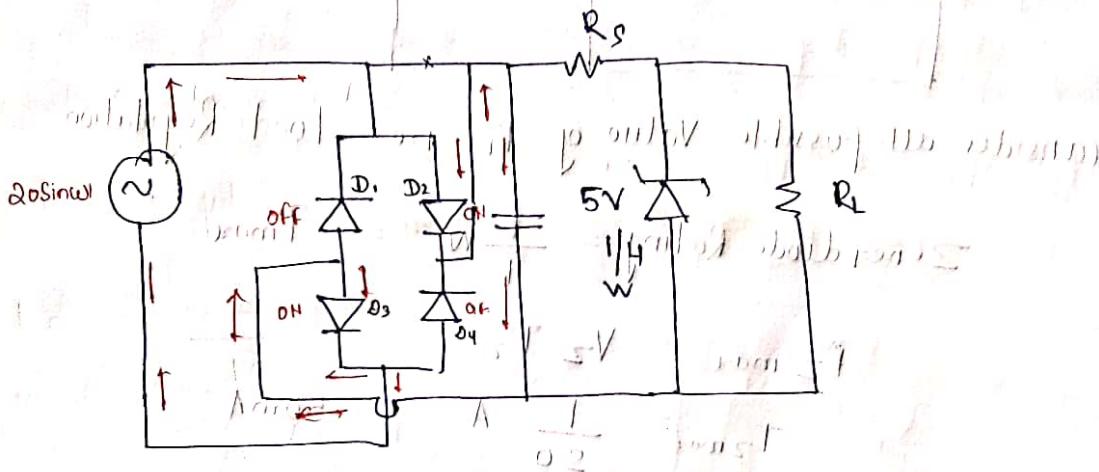

At $T^+ \frac{T}{4}$

$$V_C(T/4)^+ = V_C(T/4) = 20V$$

$$V_{in}(T/4) > V_{in}(T/4)$$

$$V_{in}(T/4) < 20V$$

D_2 off due to V_C

D_3 off due to V_C

At $T > T/4$ all diodes are off.

$D_1 = \text{off}$



$D_2 = \text{off}$

$D_3 = \text{off}$

$D_4 = \text{off}$

$$V_C(\infty) = 20V$$

Positive peak detection

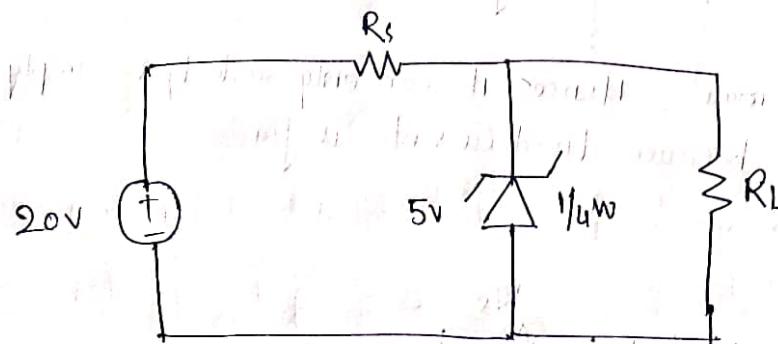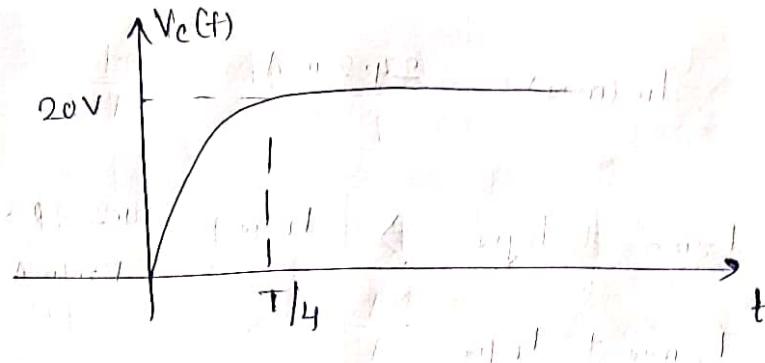

Consider all possible Value of R_L i.e Load Regulation

$$\text{Zener diode Rating} = \frac{1}{4} \text{W} = P_{\max}$$

$$P_{z\max} = V_z I_z$$

$$I_{z\max} = \frac{1}{20} \text{A} = 50 \text{mA}$$

$$I_{in(\text{fix})} = I_{z\min} + I_{L\max}$$

$$I_{in(\text{fix})} = \frac{V_{BE}}{T_{z(\max)} + T_{L(\min)}} = \frac{V_{BE}}{(T_{z(\max)})} \approx 0$$

$$I_L \rightarrow 0 \text{ to } \infty \rightarrow (I_{L\min}) \approx 0 \quad \text{and} \quad (I_{L\max})$$

$$I_{in(\text{fix})} = I_{z\max} + I_{L\min} = 50 \text{mA}$$

$$= 50 \text{mA} \quad \text{at } 0$$

$$I_{in(\text{fix})} = 50 \text{ mA}$$

$$\frac{N_{in(\text{fix})} - V_{z\max}}{R_s} = 50 \text{ mA} \Rightarrow R_s = \frac{20 - 5}{50} = 300 \Omega$$

$$R_s = 300 \Omega$$