

Number System

* Binary

Radix = 2

Unique digit =
0 ↓

Sequence: 0

1
10
11
1100
101
110
111
1000

Octal

Radix = 8

Unique digit =
0, 1, 2, 3, 4, 5, 6, 7

Sequence:

0 10 ... 70 100
1 11 ... 71 101
2 12 ... 72 102
3 13 ... 73 103
4 14 ... 74 104
5 15 ... 75 105
6 16 ... 76 106
7 17 ... 77 107

Decimal

Radix = 10

Unique digit =
0, 1, 2, 3, 4, 5, 6, 7, 8, 9

Sequence:

0 10 ... 90 100
1 11 ... 91 101
2 12 ...
3 13 ...
4 14 ...
5 15 ...
6 16 ...
7 17 ...
8 18 ...
9 19 ...
A 1A ...
B 1B ...
C 1C ...
D 1D ...
E 1E ...
F 1F ...
G 1G ...
H 1H ...
I 1I ...
J 1J ...
K 1K ...
L 1L ...
M 1M ...
N 1N ...
O 1O ...
P 1P ...
Q 1Q ...
R 1R ...
S 1S ...
T 1T ...
U 1U ...
V 1V ...
W 1W ...
X 1X ...
Y 1Y ...
Z 1Z ...

Hexadecimal

Radix = 16

Unique digit =
0, 1, 2, 3, 4, 5, 6, 7

B, 9, A, B, C, D,
E, F

Sequence

0 10 ... 90 100 ... F0
1 11 ... 91 101 ... F1
2 12 ...
3 13 ...
4 14 ...
5 15 ...
6 16 ...
7 17 ...
8 18 ...
9 19 ...
A 1A ...
B 1B ...
C 1C ...
D 1D ...
E 1E ...
F 1F ...
G 1G ...
H 1H ...
I 1I ...
J 1J ...
K 1K ...
L 1L ...
M 1M ...
N 1N ...
O 1O ...
P 1P ...
Q 1Q ...
R 1R ...
S 1S ...
T 1T ...
U 1U ...
V 1V ...
W 1W ...
X 1X ...
Y 1Y ...
Z 1Z ...

* Any Number System to Decimal Number System

Conversion

$$1. \quad (10101.1101)_2$$

$$\begin{array}{r} \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \\ 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^{-4} \end{array}$$

$$\text{Sol} \quad \Rightarrow 2^4 + \frac{1}{2^4} = (21.8101)_10$$

$$2. \quad (714.35)_8 = 7 \times 8^2 + 1 \times 8^1 + 4 \times 8^0 + 3 \times 8^{-1} + 5 \times 8^{-2}$$

$$= (460.45)_10$$

$$3. \quad (A2.C37)_{16} = A \times 16^3 + 2 \times 16^2 + 12 \times 16^{-1} + 3 \times 16^{-2} + 7 \times 16^{-3}$$

$$= 160 + 2 + \frac{12}{16} + \frac{3}{256} + \frac{7}{4096}$$

$$= (162.763)_{16}$$

$$4. \quad (45.12)_6 = 4 \times 6^1 + 5 + \frac{1}{6} + \frac{2}{36}$$

$$= 29 + \frac{1}{6} = (29.22)_6$$

$$5) (25.31)_9$$

$$\text{Sol} \quad 2 \times 9 + 5 + \frac{3}{9} + \frac{1}{81}$$

$$\Rightarrow 23 + \frac{27+1}{81}$$

$$\Rightarrow 23 + \frac{28}{81} = (23.34)_{10}$$

* Decimal number system to any number system-

$$1) (29.20)_{10} \longrightarrow (\quad)_2$$

$$\begin{array}{r} 2 | 29 \\ 2 | 14 . \quad 1 \\ 2 | 7 \quad 0 \\ 2 | 3 \quad 1 \\ 2 | 1 \quad 1 \\ 0 \quad 1 \end{array} \quad (29)_{10} = (11101)_2$$

$$0.20 \times 2$$

$$= 0.40 \times 2$$

$$= 0.80 \times 2$$

$$= 1.60$$

$$= 0.60 \times 2$$

$$= 1.20$$

$$\begin{array}{r} 0 \\ 0 \\ 1 \\ 1 \\ 1 \end{array}$$

$$(0.20)_2 = (0.011)_2$$

$$(29.20)_{10} \longrightarrow (11101.00110)_2$$

$$\begin{array}{l} 0.20 \times 2 = 0.40 \\ 0.40 \times 2 = 0.80 \\ 0.80 \times 2 = 1.60 \\ 0.60 \times 2 = 1.20 \\ 0.20 \times 2 = 0.40 \end{array}$$

$$\textcircled{2} \quad (321, 35)_{10} \longrightarrow (\quad)_8$$

Sol

	321
8	40
8	5
8	0

↓ ↓ ↑
 1 0 5

$$\begin{array}{l}
 0.35 \times 8 = 2.80 \\
 0.80 \times 8 = 6.40 \\
 0.40 \times 8 = 3.20 \\
 0.20 \times 8 = 1.60 \\
 0.60 \times 8 = 4.80 \\
 0.80 \times 8 = 6.40
 \end{array}$$

$$(0.35)_{10} = 263146$$

$$(321, 35)_{10} \longleftrightarrow (501, 263146)_8$$

$$\textcircled{3} \quad (1250, 25)_{10} \longleftrightarrow (\quad)_{16}$$

Sol

	1250
16	78
16	4
16	0

↓ ↓ |
 2 14 |

$$\begin{array}{l}
 0.25 \times 16 = 4.00 \\
 0.00 \times 16 = 0.00
 \end{array}
 \quad (2E2)_{16}$$

$$(1250, 25)_{10} \longleftrightarrow (2E2, 40)_{11}$$

Ques. $(523, 4)_6 \longleftrightarrow (\quad)_9$

$\longleftrightarrow (\quad)_{10}$

$$\underline{\text{Sol}} \quad (523.4)_6$$

$$\begin{array}{r} 523 \\ \downarrow \\ 5 \times 6^2 + 2 \times 6^1 + 3 \times 6^0 + \frac{4}{6} \end{array} \rightarrow (195.66)_{10}$$

$$\begin{array}{r} 9 | 195 \\ 9 | 21 \rightarrow 6 \\ 9 | 2 \rightarrow 3 \\ 0 \rightarrow 2 \end{array}$$

$$0.66 \times 9 = 5.94$$

$$0.94 \times 9 = 8.46$$

$$0.46 \times 9 = 4.14$$

$$0.14 \times 9 = 1.26$$

$$0.26 \times 9 = 2.34$$

$$(523.4)_6 \longrightarrow (236.584)_9$$

Que. The decimal equivalent of Binary number (10110.11)

Ans —

$$\underline{\text{S9}} \quad 22 + \frac{2+1}{4} = (22.75)_{10}$$

$$\underline{\text{Q4e}} \quad \sqrt{(224)_2} = (13)_8 \quad \gamma = ?$$

$$\Rightarrow \sqrt{2 \times \gamma^2 + 2 \times \gamma^1 + 4 \times \gamma^0} = 1 \times \gamma + 3$$

$$2\gamma^2 + 2\gamma + 4 = \gamma^2 + 6\gamma + 9$$

$$\gamma^2 - 4\gamma - 5 = 0$$

$$\therefore \frac{4 \pm \sqrt{16 + 20}}{2} \Rightarrow \frac{4 \pm 6}{2} = 5 \checkmark \quad \text{h} - 1$$

(γ cannot be negative)

Ques. The number of ones present in binary Representn of $15 \times 256 + 5 \times 16 + 3$ are 8.

Sol $15 \times 16^2 + 5 \times 16^1 + 3 \times 16^0$

$$(F\ 5\ 3)_{16} \longrightarrow 1111\ 101\ 011$$

* Hexadecimal & Octal to Binary:

i) $(641.23)_8 \longrightarrow (\quad)_2$

$$\begin{array}{ccccc} 6 & 4 & + & 2 & 3 \\ | & | & | & | & | \\ 1 & 10 & 100 & 001 & 010 \\ | & | & | & | & | \\ 1 & 10 & 100 & 001 & 011 \end{array}$$

$$\Rightarrow (110100001.010011)_2$$

ii) $((59.4)_{16} \longrightarrow (\quad)_2)$

$$\begin{array}{c} | \\ 1100\ 0101\ 1001.0100 \end{array}$$

$$\Rightarrow (110001011001.0100)_2$$

Ques.

* Binary to octal & Hexadecimal:

i) $(1101.10101)_2 \longrightarrow (\quad)_8$

Sol $\underbrace{001}_{\leftarrow}\underbrace{101}_{\rightarrow}.\underbrace{10101}_{\rightarrow} \rightarrow (15.52)_8$

$$\underbrace{1101}_{\leftarrow}.\underbrace{10101000}_{\rightarrow} \rightarrow (D.A8)_{16}$$

* Octal addition

$$\begin{array}{r}
 742 \cdot 53 \\
 + 543 \cdot 27 \\
 \hline
 (150602)_8
 \end{array}
 \quad \text{OR} \quad 10 - 8 = 2$$

$$\begin{array}{r}
 8 | 10 \\
 8 | 1 \rightarrow 2 \\
 \hline
 1
 \end{array}$$

Base 6 addition:

$$\begin{array}{r}
 343 \cdot 25 \\
 + 532 \cdot 34 \\
 \hline
 (1320.03)_6
 \end{array}$$

$$\begin{array}{r}
 6 | 9 \\
 6 | 1 \rightarrow 3 \\
 \hline
 1
 \end{array}$$

Subtract by radix.

$$\text{Que. } (135)_x + (144)_x = (323)_x$$

Sol

$$\begin{array}{r}
 135 \\
 + 144 \\
 \hline
 \cancel{9} = 4
 \end{array}$$

note

$$9 - x = 3$$

$$x = 6 //.$$

$$\text{Que. } 24 + 14 = 21$$

$$8 - x = 1$$

$$x = 7 //$$

$$\text{Que. } (2.3)_4 + (1.2)_4 = (12)_4$$

Sol

$$\begin{array}{r}
 3 \\
 2 \\
 \hline
 6 \leftarrow 4 = -2
 \end{array}$$

$$\begin{array}{r}
 2.3 \\
 1.2 \\
 \hline
 10.01
 \end{array}$$

$$(10.1)_4 //$$

Que $(235)_{R_1} = (565)_{R_0} = (865)_{R_2}$

Sol $2 \times R_1^2 + 3 \times R_1 + 5 = 565$

$$2R_1^2 + 3R_1 + 5 = 565$$

$$\rightarrow 2R_1^2 + 3R_1 - 560 = 0$$

$$\rightarrow 2R_1^2 + 3R_1 - 560 = 0$$

$$\rightarrow R_1 = \frac{-3 \pm \sqrt{9 + 560 \times 4 \times 2}}{4}$$

$$R_1 = 16$$

Que. $(43)_n = (83)_8$ no. of possible solⁿ u

Sol $4x+3 = 8y+3$

$$4x = 8y$$

$$\frac{x}{y} = 2$$

$$x = 2y$$

$$y = \underline{\underline{1, 2, 3}}$$

$$x = \underline{\underline{2, 4, 6, 8}}$$

	x	y
1	2	1
2	4	2

6	3
8	4
10	5
12	6
14	7
16	8

5 solⁿ

Ques. $(123)_5 = (xy)_7$

Sol] $25 + 10 + 3 = xy + 8$

$$xy = 30$$

$$y = \frac{30}{x}$$

y	30	1
15		2
10		3
7		4
		5

∴

3 possible soln

- ① $(x < y)$
- ② $y_{\min} = 9$

5	6
6	5
1	30
2	15
3	10

* Representation of Signed binary Number


Sign Magnitude form

Complement form

1's Complement

2's Complement

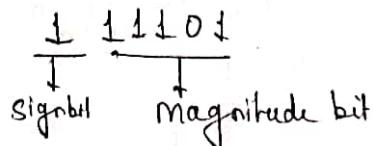
i) $-29 \rightarrow$ Signbit Magnitude (29)



This is Sign Magnitude form.

ii) -29 in 1's Complement \Rightarrow $\underbrace{1, 00010}_{\text{Signbit} \quad \text{1's comp of } 29}$

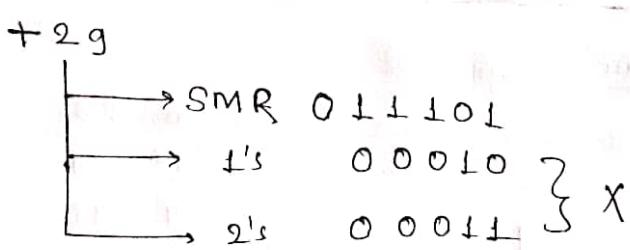iii) -29 in 2's Complement \Rightarrow $\begin{array}{r} 100010 \\ +1 \\ \hline 100011 \end{array} = 100011$



Ques. positive number Sign Mag. = 1's Comp = 2's Comp

$$+29 = \begin{array}{l} \text{SMR } 0\underset{\text{Signbit}}{1}1101 \\ \text{1's } 0.\underset{\text{Signbit}}{1}1101 \\ \text{2's } 011101 \end{array}$$

short cut of
2's complement
 $\begin{array}{r} 1011011 \\ \underline{-110} \\ 100010 \end{array}$
4 bits to first 1
as 1111

Que. find 2's Complement of $\underline{1}00011$

$$\begin{array}{r} \text{Sol} \quad \text{1's Comp. } 0111100 \\ \text{2's Comp. } 0111100 \\ \qquad \qquad \qquad + 1 \\ \hline 0111101 = -29 // \end{array}$$

Note 2's Comp
-ve no.
 $\underline{1}00011$
+ 1
arbitrary
2's C. of
only this

Note: 2's Comp. of 2's Comp. of a number is number itself
1's Comp. of 1's Comp. of a no. is no. itself.

Que. 2's Comp. of some numbers are given. Find out the original

no.

i) 11010

Sol) 101010 $\Rightarrow -6 //$

- ii)
- a) 000 \rightarrow 111 { X numbers are positive
 - b) 001 \rightarrow 111
 - c) 010 \rightarrow 110
 - d) 011 \rightarrow 101
 - e) 100 \rightarrow 011 $\rightarrow -3$ Special Case
 - f) 101 \rightarrow 011 $\rightarrow -3$
 - g) 110 \rightarrow 010 $\rightarrow -2$
 - h) 111 \rightarrow 001 $\rightarrow -1$

000	+0
001	+1
010	+2
011	+3

Special Case of 2's Complement

1 0 0
1 0 0 0 0
1 0 0 0 0 0

No. of zeros
2

4
5

Original no
 $-2^2 = -4$
 $-2^4 = -16$
 $-2^5 = -32$

⇒ Special Case in 1's complement form:

- * The Range of decimal number that can be represented using n bit 2's Complement Representation is

$$-(2^{n-1}) \text{ to } (2^{n-1}-1)$$

Ques. 1's Complement representation of some no are given
find out the original number.

Sol

a) 0 0 0	$\xrightarrow{+1}$	0 0 0	+ 0
b) 0 0 1		0 0 1	+ 1
c) 0 1 0		0 1 0	+ 2
d) 0 1 1		0 1 1	+ 3
e) 1 0 0		1 1 1	- 3
f) 1 0 1		1 1 0	- 2
g) 1 1 0		1 0 1	- 1
h) 1 1 1		1 0 0	- 0

Note:- In 1's Complement Representation we have

two separate representation for +0 & -0

Where as in 2's Complement we have single representation for zero.

The Range of decimal numbers that can be Represented using n bit 1's Comp. form is $-(2^{n-1}-1)$ to $(2^{n-1}-1)$

Que. 11001, 1001 & 111001 correspond to 2's Comp Representation of which of the following set of no.

- a) 25, 9, 57 b) -6, -6 & -6 c) -7 7 87
d) -25, -9, -57


Sol:

$$\begin{aligned}11001 &\rightarrow 10110 = -7 \\1001 &\rightarrow 1111 \rightarrow -7 \\111001 &\rightarrow 100111 \rightarrow -7\end{aligned}$$

Que. +6 → 5 bit 2's Comp

00110 //

eg. +6 in 8 bit 2's Comp

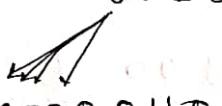min = 0110


in 7 bit 2's Comp 00000110

eg. -7 in 8 bit 2's

min. 0111
-7 
in 8 bit 11111001

Que. A no. in 4-bit 2's Complement form is $x_3 x_2 x_1 x_0$. This no. when stored using 8-bit will be

(Note)

Sol $x_3 x_2 x_1 x_0 x_3 x_2 x_1 x_0$

Que. Let $A = 11111010$
 $B = 00001010$ be two 8-bit 2's Comp.
 represent. Their product in 2's Comp. is

Sol $11111010 \rightarrow 10000110 = -6$

$$00001010 \rightarrow 1010 = 10$$

Note
 There is no need of finding 2's c of the number $\rightarrow 100111100$

$$\begin{array}{r} 32 \\ 16 \\ 48 \\ 8 \\ 56 \\ 4 \end{array}$$

$$11000100 //.$$

Que. Assuming all no. in 2's complement which of the following no. is divisible by 11111011

Sol $11111011 \xrightarrow{2^8} 10000110 = (-5)$
~~64 + 32 + 16 + 8 + 2 + 1~~
 $\Rightarrow +25$

A) $11100111 \xrightarrow{2^8} -25$

B) 11100100

C) 1011101

D) 1111011

* Complements Arithmetic

†) 1's Complement

e.g. $-26 + 9$

let $-26 + 9 = x$

$$(1's \text{ comp. of } -26) + (1's \text{ comp. of } 9) = 1's \text{ comp. of } x$$

$$\begin{array}{r} -26 \\ \xrightarrow{\text{1's}} \\ 111010 \\ 100101 \end{array}$$

$$\begin{array}{r} 9 \\ \xrightarrow{\text{1's}} \\ 01001 \\ 00110 \end{array}$$

Note
Answer is in 1's Comp.
form so to get original
no. 1's Comp. the answer
↓

$$\begin{array}{r} \text{now } 100101 \\ 001100 \\ \hline 101101 \end{array} = 101101$$

$$\begin{array}{r} 1's \text{ comp. of } 101101 \\ \longrightarrow 101101 \\ -17 // \end{array}$$

e.g. $+26 - 9$

Sol $26 \rightarrow 011010$

$-9 \rightarrow 110110$

zero is used for +ve

$$\begin{array}{r} 011010 \\ 110110 \\ \hline 010000 \end{array}$$

note
To adjust equal bits in both numbers for -ve numbers 1 is used

note
Positive no. $\neq 0$ need to complement

Difference b/w 1's & 2's comp arithmetic

- In 1's Complement arithmetic we add the carry (If generated) to the result whereas in 2's Complement arithmetic we ignore the carry (If generated)

Q1.

Concept of Overflow

Q. Using Q's Comp. arithmetic, Solve

$$\textcircled{1} -2+3 \quad \textcircled{2} -3+2 \quad \textcircled{3} 3+2 \quad \textcircled{4} -3-2$$

Sol: $-2 \xrightarrow{2^3} 110$
 $3 \xrightarrow{} 011$
 $+ \xrightarrow{} 1001$
 Carry ignore = $001 \xrightarrow{2^3} 001$ (+ve no)

Let,
 $-2+3 = x$

$$2^1c(-2) + 2^1c(3) = 2^1c(x)$$

$$\begin{array}{r} -3 \xrightarrow{2^3} 101 \\ 2 \xrightarrow{2} 010 \end{array}$$

$$\textcircled{1} -3+2 = \begin{array}{r} 101 \\ 010 \\ \hline 111 \end{array} \xrightarrow{2^3} 101 = -1$$

$$\textcircled{2} 3+2 = \begin{cases} +ve & 011 \\ +ve & 010 \\ \text{not possible} & -ve \end{cases} \xrightarrow{2^3} 111 = -3 \quad X$$

$$\textcircled{3} -3-2 \begin{cases} -ve & 101 \\ -ve & 110 \\ NP & \end{cases} \xrightarrow{2^3} 011 + 3 \quad X$$

Note:

- 1) Overflow can never occur on addition of two numbers with opposite sign. Overflow may occur on addition of two numbers with same sign.
- 2) Addition of two positive numbers should never give a negative. If such condition occurs it indicates Overflow
- 3) In MSB If $C_{in} \oplus C_{out} = 1$ indicates overflow

$$\begin{array}{r}
 C_{in} \ 0 \\
 + \ 1 \ 0 \ 1 \\
 0 \ 1 \ 0 \\
 \hline
 C_{out} \ 0 \ 1 \ 1
 \end{array}
 \quad C_{in} \oplus C_{out} = 0 \text{ no overflow}$$

$$\begin{array}{r}
 C_{in} \ 0 \\
 + \ 1 \ 0 \ 1 \\
 1 \ 1 \ 0 \\
 \hline
 C_{out} \ 1 \ 0 \ 1
 \end{array}
 \quad C_{in} \oplus C_{out} = 1 \text{ overflow}$$

Que. (1) $\begin{array}{r}
 1 \ 1 \ 0 \ 0 \\
 + \ 1 \ 0 \ 1 \ 1 \\
 \hline
 1 \ 0 \ 1 \ 1 \ 1
 \end{array}$

$$0 \oplus 1 = 1 \text{ ov}$$

(ii) $\begin{array}{r}
 1 \ 0 \ 0 \ 1 \\
 + \ 1 \ 1 \ 1 \ 0 \\
 \hline
 1 \ 0 \ 1 \ 1 \ 1
 \end{array}$

$$1 \oplus 0 = 1 \text{ ov}$$

(iii) $\begin{array}{r}
 0 \ 1 \ 1 \ 0 \\
 + \ 1 \ 0 \ 1 \ 0 \\
 \hline
 1 \ 0 \ 0 \ 0 \ 0
 \end{array}$

$$C_{in} \oplus C_{out} = 0 \text{ nof}$$

(iv) $\begin{array}{r}
 1 \ 1 \ 1 \ 1 \\
 + \ 0 \ 1 \ 1 \ 0 \\
 \hline
 1 \ 0 \ 0 \ 1
 \end{array}$

$$1 \oplus 0 = 0 \text{ v}$$

Ques. Two 2's Complement no. having Sign bit, x and y are added and the sign bit of the Result is z which Boolean function indicates the occurrence of overflow.

$x = -$ for overflow

$$\begin{array}{r} y \\ + z \\ \hline \end{array}$$

~~out~~

x	y	z	Overflow 'f'
0	0	0	0
0	0	1	negab
0	1	0	1
0	1	1	0
opposite sign	0	0	0
	1	0	0
1	0	1	0
1	0	0	1
1	1	1	0

overflow occur.

no overflow

x	y	z
0	1	0
0	0	1

$$f = \bar{x}\bar{y}z + x\bar{y}z$$

$$= 0011$$

Sol

x	$y+z$	$y+\bar{z}$	$\bar{y}+z$	$\bar{y}+\bar{z}$
0	0	1	0	0
0	0	0	0	1

$$(y+z) * (\bar{x}+\bar{z}) * (x+\bar{y})$$

$$(y+z)(\bar{x}+\bar{z})(x+\bar{y})$$

Code Converter


1. Binary to Gray (4bit)

	Input				Output			
	b_3	b_2	b_1	b_0	g_3	g_2	g_1	g_0
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	0	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	1
8	1	0	0	0	0	1	0	0
9	1	0	0	1	1	1	0	0
10	1	0	0	1	1	1	0	1
11	1	0	1	0	1	1	1	1
12	1	0	1	1	1	1	1	1
13	1	1	0	0	1	0	1	0
14	1	1	0	1	1	0	1	0
15	1	1	1	0	1	0	1	1
16	1	1	1	1	1	0	0	1
17	1	0	0	0	1	0	0	0

note

Gray Code

0	1	1	0
1	0	1	1
2	1	0	1
3	0	0	1
4	1	1	1
5	0	1	0
6	1	0	0
7	0	0	0
8	1	1	0
9	0	1	1
10	1	0	1
11	0	0	1
12	1	1	1
13	0	1	0
14	1	0	0
15	0	0	0

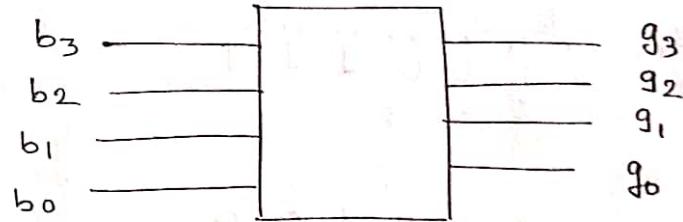

$b_3 b_2$	$b_1 b_0$	$\bar{b}_1 \bar{b}_0$	$b_1 \bar{b}_0$	$\bar{b}_1 b_0$
0	1	1	0	0
1	0	0	1	1
2	1	1	1	0
3	0	0	0	1
4	1	1	0	1
5	0	1	1	0
6	1	0	0	1
7	0	0	1	0
8	1	1	1	1
9	0	1	0	0
10	1	0	1	1
11	0	0	0	0
12	1	1	0	1
13	0	1	1	0
14	1	0	0	1
15	0	0	1	0

$$g_3(b_3, b_2, b_1, b_0) = b_3$$

\bar{b}_3	b_2	\bar{b}_1	b_0
0	1	1	1
1	0	1	0
2	1	0	1
3	0	0	0
4	1	1	1
5	0	0	1
6	1	1	0
7	0	0	0
8	1	1	1
9	0	1	0
10	1	0	1
11	0	0	0
12	1	1	1
13	0	1	0
14	1	0	1
15	0	0	0

$$g_2(\bar{b}_3, b_2, \bar{b}_1, b_0) = \bar{b}_3 b_2 + b_3 \bar{b}_2$$


$$= b_2 \oplus b_3$$

\bar{b}_3	b_2	\bar{b}_1	b_0
0	1	1	1
1	0	1	0
2	1	0	1
3	0	0	0
4	1	1	1
5	0	0	1
6	1	1	0
7	0	0	0
8	1	1	1
9	0	1	0
10	1	0	1
11	0	0	0
12	1	1	1
13	0	1	0
14	1	0	1
15	0	0	0

$$g_1(b_2, \bar{b}_1, b_0) = b_2 \oplus \bar{b}_1$$

\bar{b}_3	b_2	\bar{b}_1	b_0
0	1	1	1
1	0	1	0
2	1	0	1
3	0	0	0
4	1	1	1
5	0	0	1
6	1	1	0
7	0	0	0
8	1	1	1
9	0	1	0
10	1	0	1
11	0	0	0
12	1	1	1
13	0	1	0
14	1	0	1
15	0	0	0
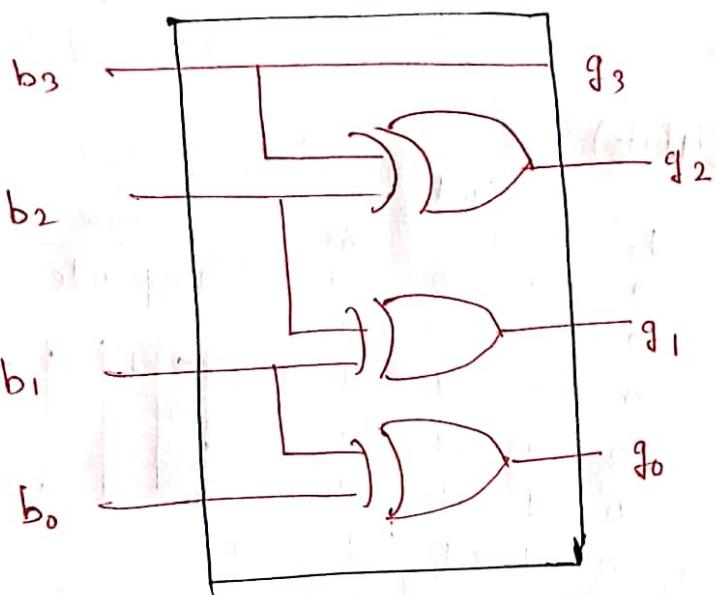
$$g_0(b_1, \bar{b}_0) = b_1 \oplus \bar{b}_0$$



ckt. Binary to Gray Converter

eg. $(0110)_{b_3 b_2 b_1 b_0} \rightarrow q_3 = 0 \quad (0101)$

$$q_2 = 1$$

$$q_1 = 0$$

$$q_0 = 1$$

eg.

$0 \quad \perp \quad \perp \quad 0$	$(0 \quad 1 \quad 1 \quad 0)_2$
\downarrow	\downarrow
$0 \quad + \quad + \quad 0$	$(0 \quad \perp \quad 0 \quad 1)_\text{gray}$

eg.

$0 \quad 1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 0 \quad 1 \quad 0 \quad 1 \quad 1$
\downarrow
$0 \quad 1 \quad 0 \quad 1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 0$

* Gray to binary (4bit) Converter

g_3	g_2	g_1	g_0	
0	0	0	0	0
1	0	0	0	1
3	0	0	1	1
2	0	0	1	0
6	0	1	1	0
7	0	1	1	1
5	0	1	0	1
4	0	1	0	0
12	1	1	0	0
13	1	1	0	1
15	1	1	1	1
14	1	1	1	0
10	1	0	1	0
11	1	0	0	1
9	1	0	0	1
8	1	0	0	0

b_3	b_2	b_1	b_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

			b_2
1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

		b_2	
0	0	1	0
1	0	1	0
1	1	1	0
1	1	1	0

		b_2	
1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

		b_2	
1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

		b_2	
1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$b_3 = g_3$$

$$b_2 = g_3 \oplus g_2 = b_3 \oplus g_2$$

$$b_1 = g_3 \oplus g_2 \oplus g_1 = b_2 \oplus g_1$$

$$b_0 = \overline{g_3} \overline{g_2} (g_1 \oplus g_0) + \overline{g_3} g_2 (\overline{g_1} \oplus g_0)$$

$$+ g_3 \overline{g_2} (\overline{g_1} \oplus g_0) + g_3 \overline{g_2} (\overline{g_1} \oplus \overline{g_0})$$

$$b_0 = (g_1 \oplus g_0) (\overline{g_3} \oplus \overline{g_2}) + (\overline{g_1} \oplus \overline{g_0}) (g_3 \oplus g_2)$$

$$b_0 = g_0 \oplus g_1 \oplus g_2 \oplus g_3 = b_1 \oplus g_0$$


Standard result

ab	cd	1	1
1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$\rightarrow a \oplus b \oplus c \oplus d$$

ab	cd	1	1
1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1
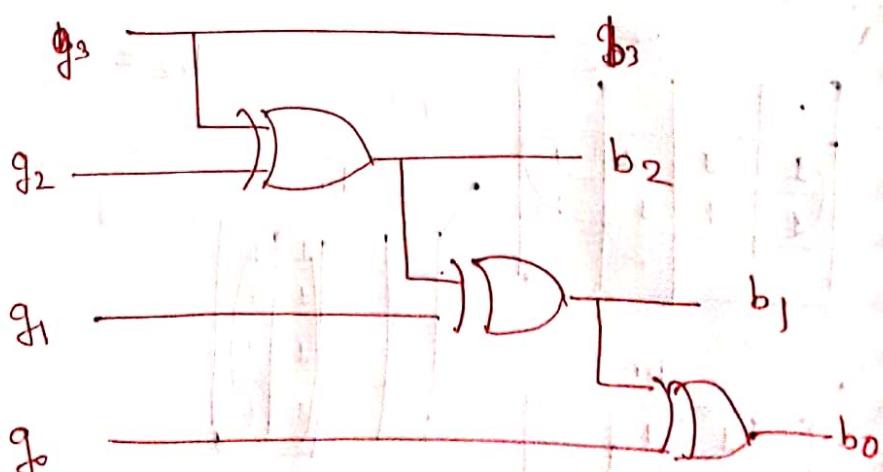
$$\rightarrow a \oplus b \oplus c \oplus d$$



* delay of G to B conv. is $>$ delay of B to G conv.

$$n \Delta t$$

$$\Delta t_{soc}$$

eg. $\begin{array}{cccc} 1 & 1 & 0 & 0 \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 1 & 0 & 0 & 0 \end{array}$ $\begin{array}{cccc} 1 & 0 & 0 & 1 \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 1 & 1 & 1 & 0 \end{array}$

eg. $\begin{array}{cccccc} 1 & 0 & 1 & 1 & 0 & 0 & 1 \\ \downarrow & & & & & & \\ 1 & 1 & 0 & 1 & 1 & 0 & 0 \end{array}$

Ques. $(24)_8 \rightarrow \text{gray}$

$010100 \rightarrow 011110$

* Xs-3 Code to BCD Code

$a_3 \ a_2 \ a_1 \ a_0$	$b_3 \ b_2 \ b_1 \ b_0$
0 0 1 1	0 0 0 0
0 0 1 0	0 0 0 1
0 1 0 1	0 0 1 0
0 1 1 0	0 0 1 1
0 1 1 1	0 1 0 0
1 0 0 0	0 1 0 1
1 0 0 1	0 1 1 1
1 0 1 0	1 0 0 0
1 0 1 1	1 0 0 1
1 1 0 0	1 1 1 1

eg. $\begin{array}{cccc} \top & \top & 0 & 0 \\ \downarrow 0 & \downarrow 0 / \downarrow 0 & & \\ 1 & 0 & 0 & 0 \end{array}$

$\begin{array}{cccc} 1 & 0 & 0 & 1 \\ \downarrow & & & \\ 1 & 1 & 1 & 0 \end{array}$

eg. $\begin{array}{cccccc} \top & 0 & 1 & 1 & 0 & 0 & 1 \\ \downarrow & & & & & & \\ 1 & 1 & 0 & 1 & 1 & 0 & 0 \end{array}$

Ques. $(24)_8 \rightarrow \text{gray}$

$010100 \rightarrow 011110$

* Xs-3 Code to BCD Code

$a_3 \ a_2 \ a_1 \ a_0$	$b_3 \ b_2 \ b_1 \ b_0$
0 0 1 1	0 0 0 0
0 1 0 0	0 0 0 1
0 1 0 1	0 0 1 0
0 1 1 0	0 0 1 1
0 1 1 1	0 1 0 0
1 0 0 0	0 1 0 1
1 0 0 1	0 1 1 0
1 0 1 0	1 0 0 0
1 0 1 1	1 0 0 1
1 1 0 0	1 0 1 0

\bar{x}_3x_2	$\bar{x}_3\bar{x}_2$	x_3x_2	$x_3\bar{x}_2$	$\bar{x}_3\bar{x}_2$
x_3x_2	X	X	X	
$\bar{x}_3\bar{x}_2$	1		1	1
$x_3\bar{x}_2$	1	X	X	X
$\bar{x}_3\bar{x}_2$	1		1	

$$B_0 = \cancel{x_3x_2} + \cancel{\bar{x}_3\bar{x}_2} + \cancel{x_1x_2}$$

$$B_0 = \bar{x}_1\bar{x}_2 + x_1\bar{x}_2$$

\bar{x}_3x_2	$\bar{x}_3\bar{x}_2$	x_3x_2	$x_3\bar{x}_2$	$\bar{x}_3\bar{x}_2$
x_3x_2	X	X	X	
$\bar{x}_3\bar{x}_2$	1		1	
$x_3\bar{x}_2$	X	X	X	
$\bar{x}_3\bar{x}_2$	1		1	

$$B_1 = \bar{x}_1x_2 + x_1\bar{x}_2$$

$$= x_0 \oplus x_4$$


x_3x_2	$\bar{x}_3\bar{x}_2$	$x_3\bar{x}_2$	\bar{x}_3x_2	$\bar{x}_3\bar{x}_2$
$\bar{x}_3\bar{x}_2$	X	X	X	
$x_3\bar{x}_2$	1		1	
\bar{x}_3x_2	X	X	X	
$x_3\bar{x}_2$	1	1	1	

$$B_2 = \bar{x}_2\bar{x}_1 + \bar{x}_0\bar{x}_2 + x_2x_1x_0$$



1		

$$B_3 = \bar{x}_1x_0x_3$$

Electronics System & Circuits

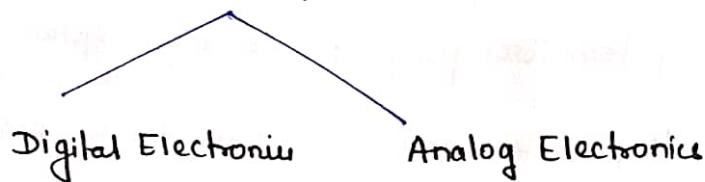

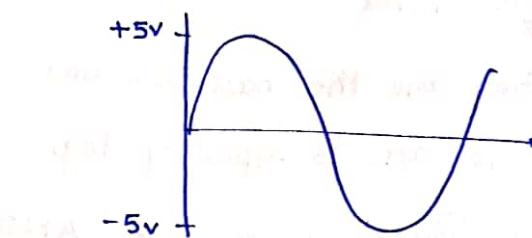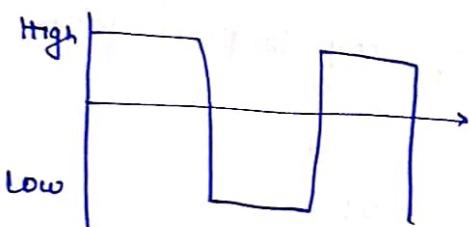- In Analog Electronics, Voltage may take any of the infinite possible values whereas in Digital Electronics we consider only two levels - logic high and logic low.



- Both Analog and Digital Electronics use same components.
- Digital circuit is also called logic circuit or switching ckt.
- Transition time of digital system is assumed to be zero.

Advantages of Digital Electronics

- Designing of Digital ckt is easy.
- Information storage is easy.
- Effect of Noise is less.
- Digital Circuits are more Versatile (Reusable)

Application of DE :-

- It is preferred in field of measurement, control system, comm, and data processing over Analog Electronics.

Disadvantages of Digital Electronics :-

- Real World is analog. Hence required A/D, D/A in the system.

* Designing of Digital System

Step 1:- System Designing : Complete System divided into various block and their interconnection

Step 2:- logic Designing : Each block design using logic gate

Step 3:- Circuit Designing : Technology used to design gates

* Logic Gates

→ They are the basic building block of any Digital System

There are 3 types of logic Gates

i) Basic Gates → AND OR NOT

ii) Universal Gates → NAND NOR

iii) Special purpose Gates → Ex-OR Ex-NOR

I. Basic Gates

i) AND Gate

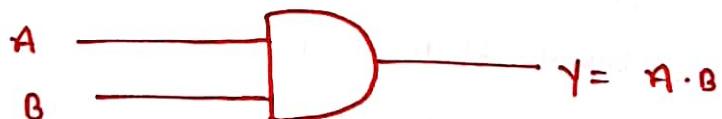


fig. Logic Symbol of 2^{1/p}
AND gate

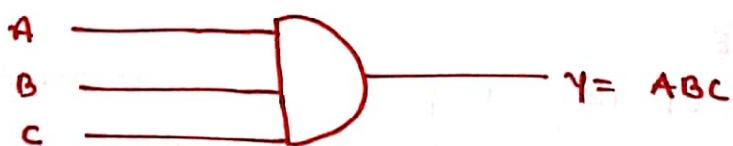


fig. Logic Symbol of 3^{1/p}
AND gate

AND gate is a logic gate whose o/p is high only when all the input are high

OR AND gate is a logic gate whose o/p is logic low if atleast one of the input is at logic low

Truth table :-

A	B	C	$y = A \cdot B \cdot C$
L	L	L	L
L	L	H	L
L	H	L	L
L	H	H	L
H	L	L	L
H	L	H	L
H	H	L	L
H	H	H	H

Note:- Truth table is a table which consist of all the possible combination of 1/p along with their corresponding o/p.

ii) OR Gate

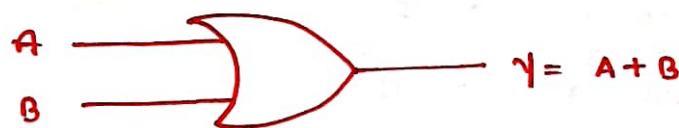


fig: Logic Symbol of
2 /p OR gate

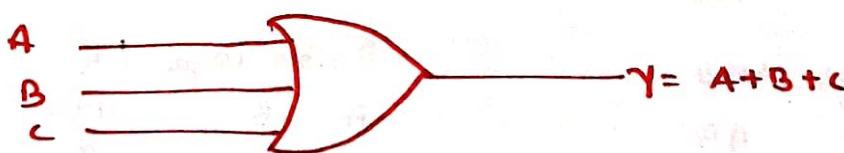


fig. 3 /p OR gate

OR gate is a logic gate whose o/p is logic High when any one input is logic High.

OR gate is a logic gate whose o/p is logic low only when all inputs are logic low.

Truth Table :-

A	B	C	$\gamma = A + B + C$
L	L	L	L
L	L	H	H
L	H	L	H
L	H	H	H
H	L	L	H
H	L	H	H
H	H	L	H
H	H	H	H

Note:- Positive Logic Digital System

$$\text{High} \longleftrightarrow '1'$$

$$\text{Low} \longleftrightarrow '0'$$

Negative Logic Digital System

$$\text{High} \longleftrightarrow '0'$$

$$\text{Low} \longleftrightarrow '1'$$

Positive Logic AND

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

Positive Logic OR

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

Negative Logic AND

A	B	AB
1	1	1
1	0	1
0	1	1
0	0	0

Negative Logic OR

A	B	$A+B$
1	1	1
1	0	0
0	1	0
0	0	0

Key point :- Positive logic AND \equiv Negative logic OR
Negative logic AND \equiv Positive logic OR

III) NOT gate



Fig. logic symbol of
NOT gate


NOT gate has only one input

Truth Table

A	$y = \bar{A}$
0	1
1	0


NOT gate is a logic gate whose output is complement of its input.

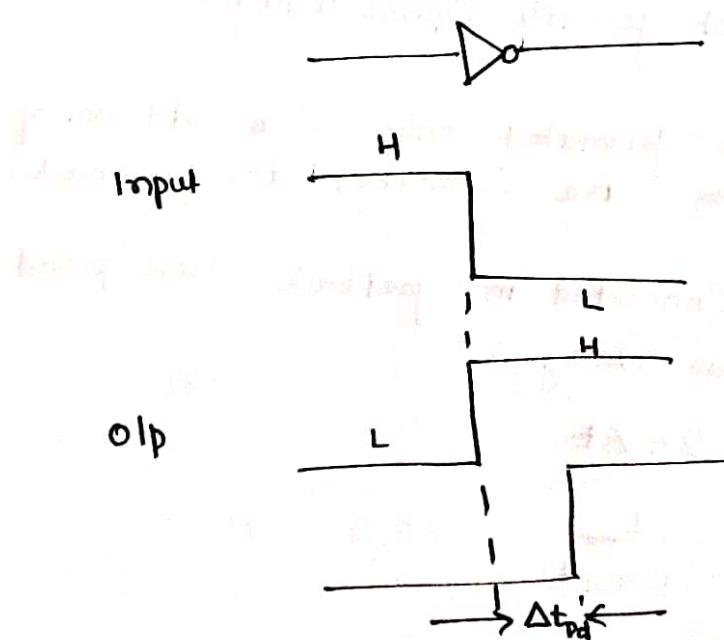Propagation Delay :- Time taken by the gate to reflect the change in Input to the output




where, Δt_{pd} is delay time.

ex. Consider a Circuit

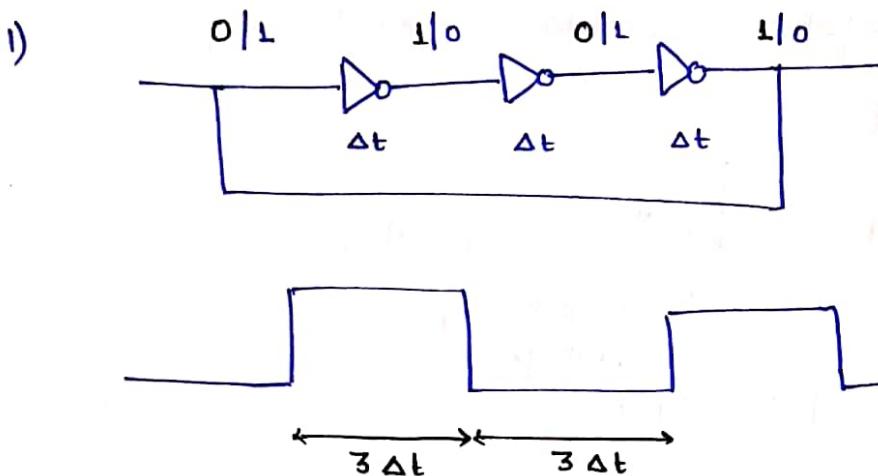

$$T = 6 \Delta t$$

$$f = \frac{1}{6 \Delta t}$$

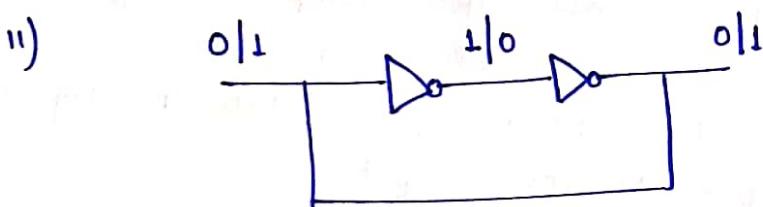

It will not generate Square waveform


note:- Square Wave is generated only when odd no. of Cascaded Inverters are Connected in feed back.

For 'n' Inverters Connected in feed back time period of generated Square Wave form

$$T = 2n \Delta t$$

$$f = \frac{1}{2n \Delta t}$$

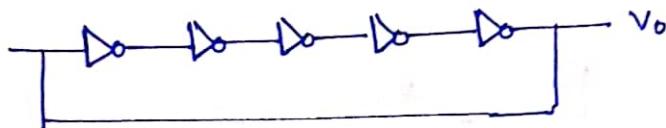
Que. For the Ring Oscillator shown in fig. The propagation delay of each inverter is 2ns. What is fundamental frequency of the oscillator?



Sol. $n = 5$

$$f = \frac{1}{2 \times 5 \times 100} = 1 \text{ GHz}$$

Que.

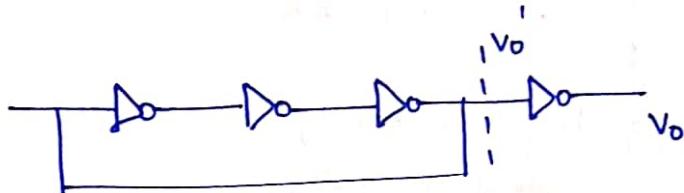

Propagation delay of each not gate is 2ns. The Time period of generated square wave is

Sol.

$$T = 6 \Delta t + \Delta t$$


Wrong

$$= 12 \text{ ns} + 2 \text{ ns}$$


$$= 14 \text{ ns}$$

Shifting does not affect time period

If $V_o' =$

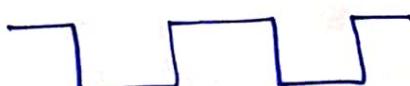

$V_o =$

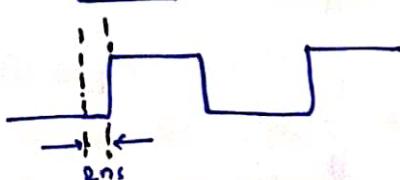


$$T = 6 \Delta t$$

$$= 12 \text{ ns} //$$

Universal Gate:

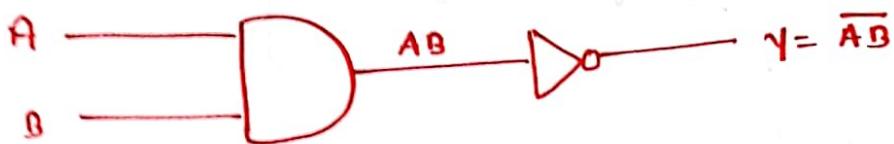1) NAND gate:- It is an AND gate followed by a NOR gate



OR

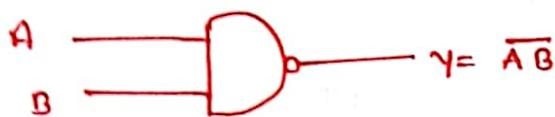


fig. Logic Symbol of
2p NAND gate

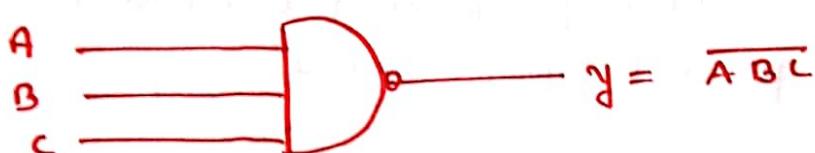


fig. Logic Symbol of
3p NAND gate

Truth Table:

A	B	C	A-B-C	$y = \overline{ABC}$
L	L	L	L	H
L	L	H	L	H
L	H	L	L	H
L	H	H	L	H
H	L	L	L	H
H	L	H	L	H
H	H	L	L	H
H	H	H	H	L

NAND gate is a logic gate whose output is logic low only when all the inputs are at logic high.


OR

NAND gate is a logic gate whose op is logic high when any of the inputs is at logic low.

ex.

A	B	\overline{AB}	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0
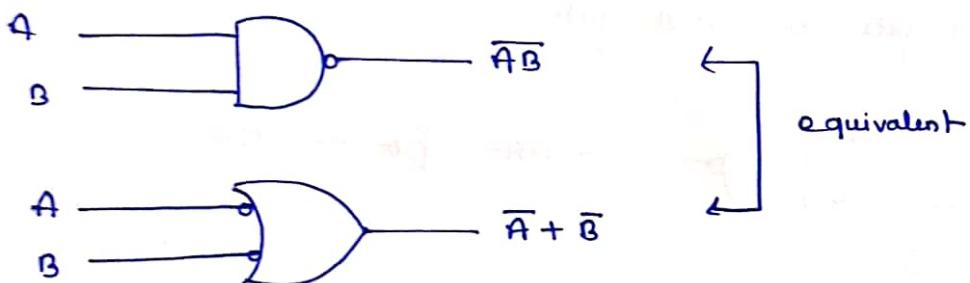
$$\overline{AB} = \overline{A} + \overline{B}$$




Keypoint: NAND gate is bubbled OR gate.

bubbled OR gate is active low OR gate or negative OR gate
Normal OR gate is active High OR gate or

Basic Gates :- AND, OR, NOT are called as basic gates as we can implement a digital circuit of any complexity using combination of these basic gates.

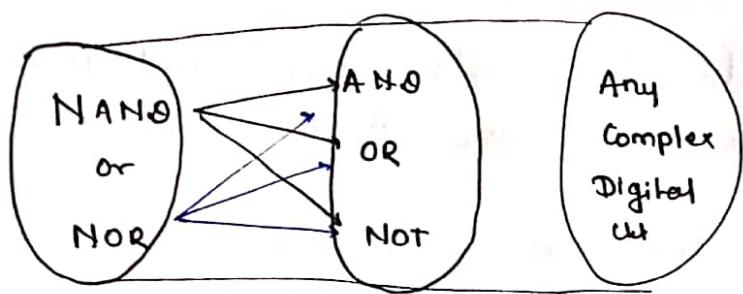Universal Gate :- NAND & NOR Gates are called as Universal gate as these gates (either NAND or NOR gate) are single handedly capable of designing a digital circuit of any complexity.



Ques. Justify NAND gate as NOT gate

Sol

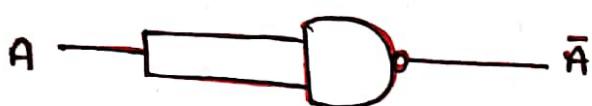


fig. NAND gate as NOT gate

NAND gate as AND gate

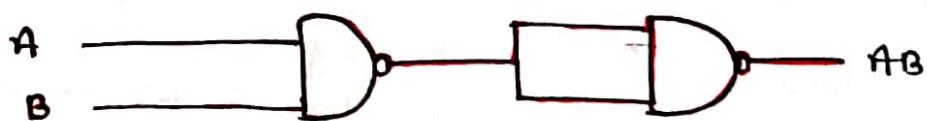


fig. NAND gate as AND gate

NAND gate as OR gate

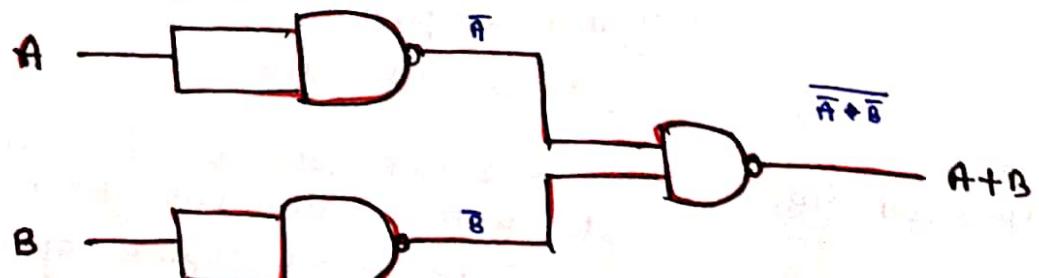


fig. NAND gate as OR gate

$$\text{Required function} = A + B = \overline{\overline{A+B}} \\ = \overline{\overline{A} \cdot \overline{B}}$$


Que. find the Min. no. of two input NAND gate required to design the following functions

- ① $f_1 = A + B$
- ② $f_2 = AB + CD$
- ③ $f_3 = A + BC$

Sol 1 :- Step 1: $A + B = \overline{\overline{A+B}}$


Step 2: Demorgan Law $\overline{\overline{A+B}} = \overline{\overline{A} \cdot \overline{B}}$
 $= A + B$

Sol 2: $AB + CD = \overline{\overline{AB+CD}}$
 $= \overline{\overline{AB} \cdot \overline{CD}}$

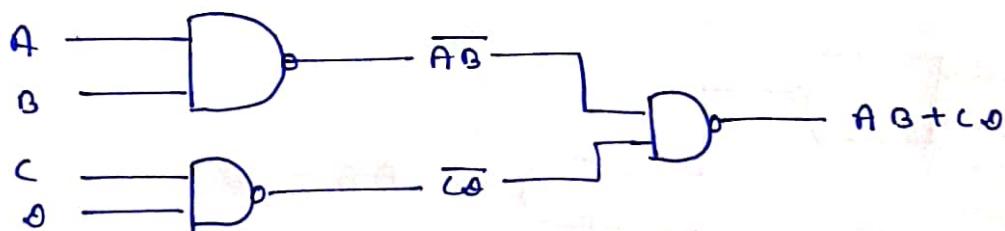


Sol 3: $f_3 = A + BC$
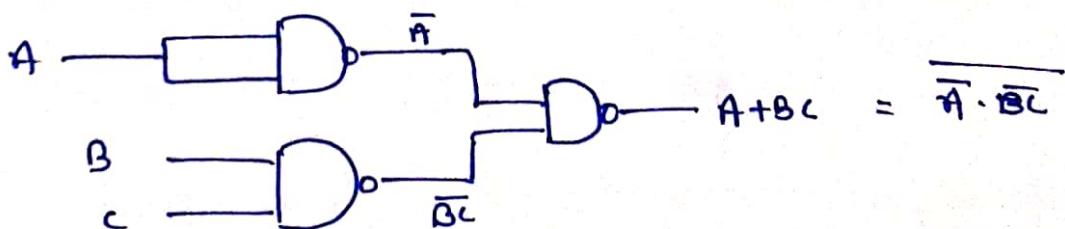
$$= \overline{\overline{A+BC}} \\ = \overline{\overline{A} \cdot \overline{BC}}$$




$$④ F = AB + CD + EF$$

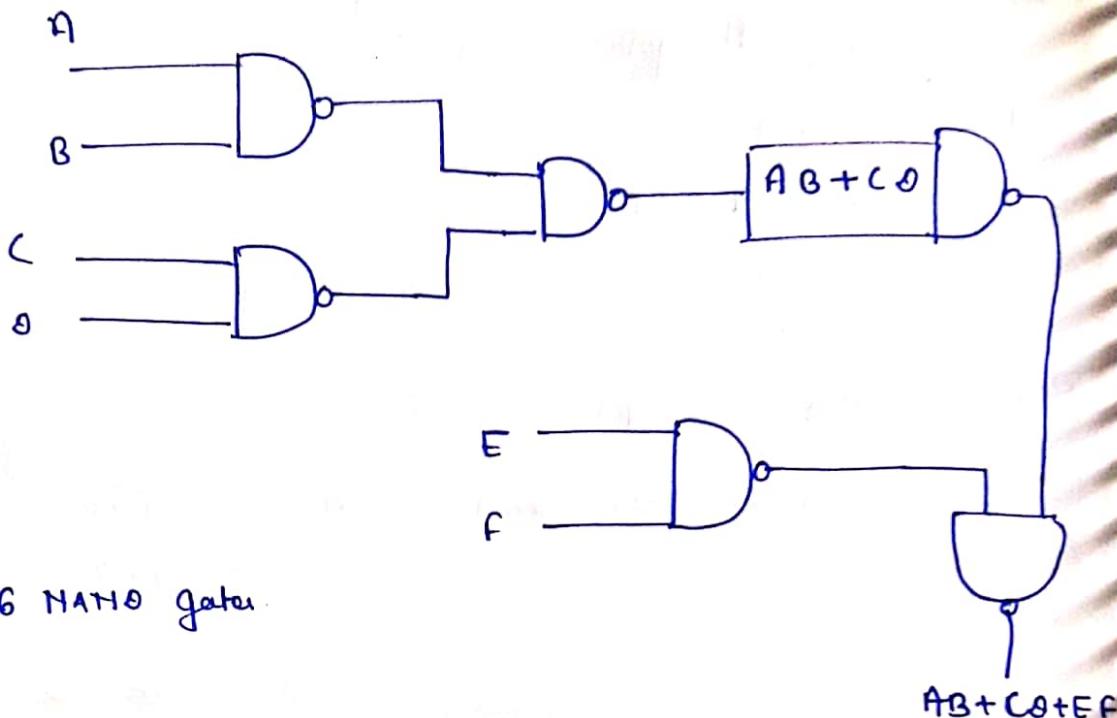

Total 6 NAND gates.


Note:

$$F = AB + CD \text{ form}$$

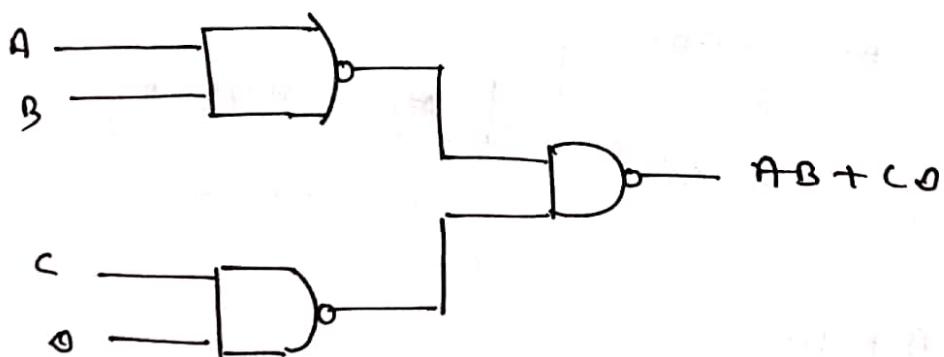

Try to adjust in form of $AB + CD$

Q. $F = AB + BC + CD$

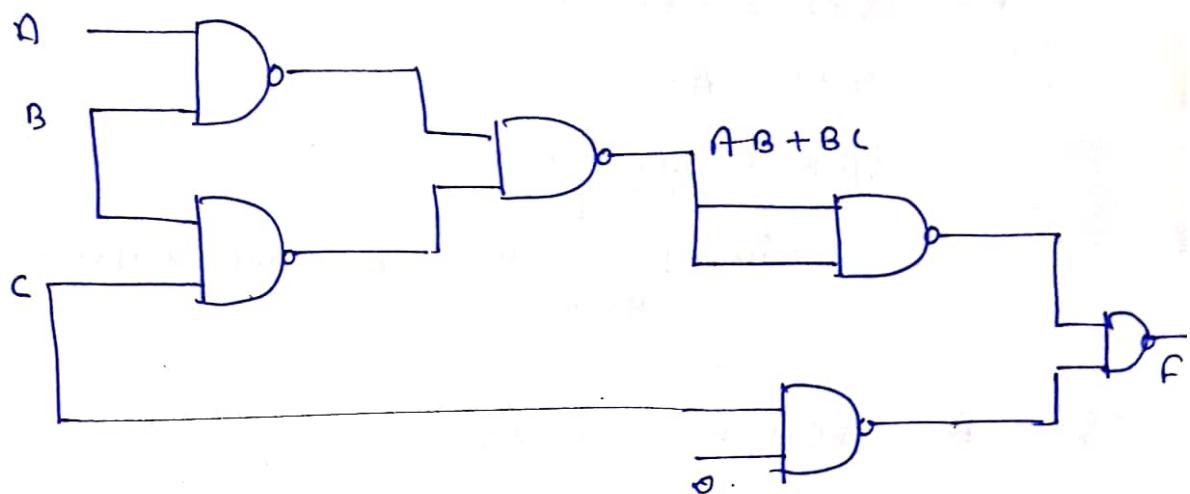


OR

$$F = AB + BC + CD$$

$$= B(A+C) + CD$$

$$= B(AA+CC) + CD$$

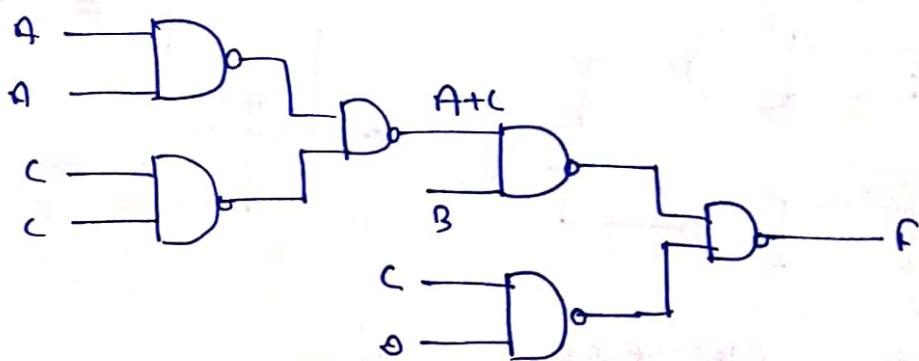

Que. $F = AB + BC + CD + DA$

$$= (A+C)B + D(C+A)$$

$$= \frac{(AA+CC)}{X}B + \frac{D(CC+AA)}{Y}$$

$X = 3$ NAND gate

$Y = 3$ NAND gate

$$\text{now } F = BX + DY$$

$F = 3$ Hard gate So total 9

OR $F = AB + BC + CA + DA$

$$F = B(A+C) + D(A+C)$$

$$= (B+D)(A+C)$$

$$= \underbrace{(B \cdot B + D \cdot D)}_{3 \text{ NAND}} \cdot \underbrace{(A \cdot A + C \cdot C)}_{3 \text{ NAND}} \\ \downarrow \qquad \qquad \qquad \downarrow \\ 2 \text{ NAND}$$

= Total 8 NAND gate


OR $F = AB + BC + CA + DA$

$$= B(A+C) + D(A+C)$$

$$= Bx + Dx \\ \downarrow \\ 3 \text{ NAND}$$

$$\text{and } A+C = AA+CC = 3 \text{ NAND}$$

So total 6 NAND gate 11.

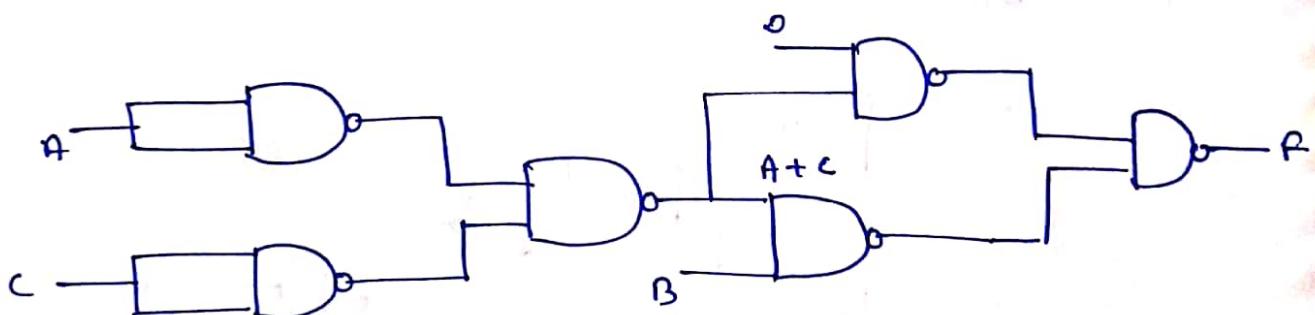

7. $F = ABC + DE$

$$= \overline{\overline{ABC} + \overline{DE}} = \overline{\overline{ABC} \cdot \overline{DE}}$$

$$= \overline{ABC} + \overline{DE}$$

$$= Ax + Dx \\ \downarrow \\ 3 \text{ gate} + 2 \text{ gate (x)}$$

$$= 5 \text{ gate}$$


$$8. \quad \overline{A} + \overline{B} + ABC$$

$$\text{So} \quad \overline{A} \cdot \overline{A} + \overline{B} \cdot \overline{B} + AX$$

$$F = \overline{A} + \overline{B} + ABC$$

$$= \underline{\overline{AB}} + \underline{ABC}$$

1 gab

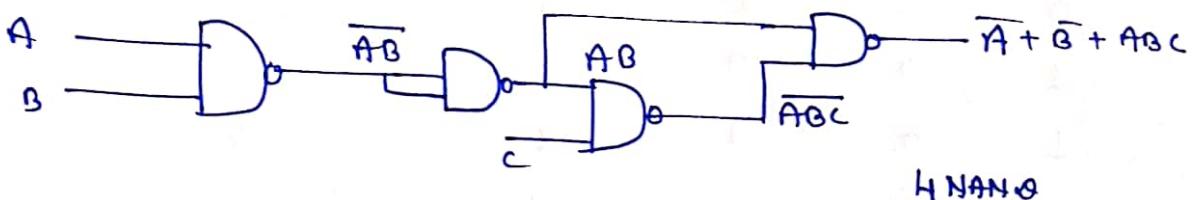

ANSWER

$$f = \overline{A} + \overline{B} + ABC$$

$$= \underline{\overline{AB}} + \underline{ABC}$$

$$= \underline{\overline{AB}} + \underline{\overline{ABC}}$$

$$= \underline{\overline{AB}} \cdot \underline{\overline{ABC}}$$

II. NOR gate:- NOR gate is an OR gate followed by a NOT gate

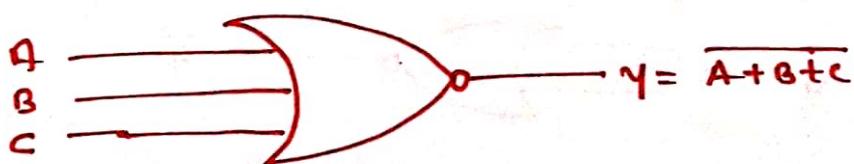
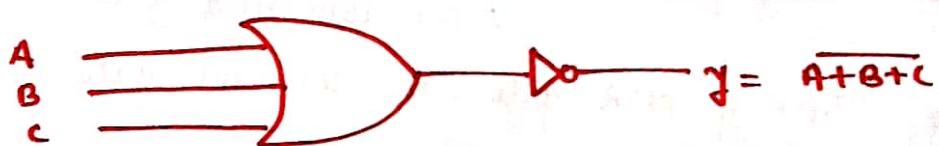


fig. Logic diag. of 3 \rightarrow 1
NOR gate

Truth table:

A	B	C	$A+B+C$	$\overline{A+B+C}$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

NOR gate is a logic gate whose o/p is logic high only when all the i/p are logic low

OR

NOR gate is a logic gate whose o/p is logic low if any of its input is logic high.

Note: NOR gate \equiv Bubbled AND gate / Negative AND Gate / Active low AND gate


Ques. Justify NOR gate as universal gate

i) NOT gate



$$\left. \begin{array}{l} \overline{A+A} = \bar{A} \\ A+\bar{A} = A \end{array} \right\}$$

ii) OR gate

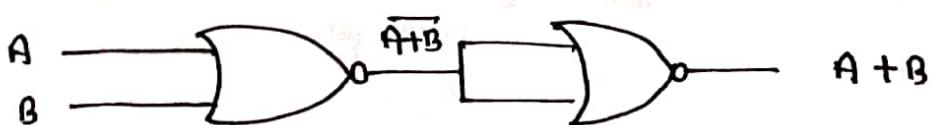

$$A+B$$

III) AND gate

$$\begin{aligned}Y &= A \cdot B \\&= \overline{\overline{A} \cdot \overline{B}} \\&= \overline{\overline{A} + \overline{B}}\end{aligned}$$


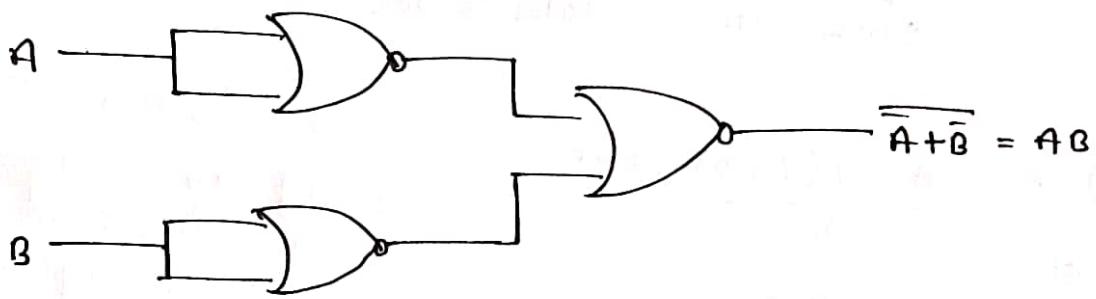
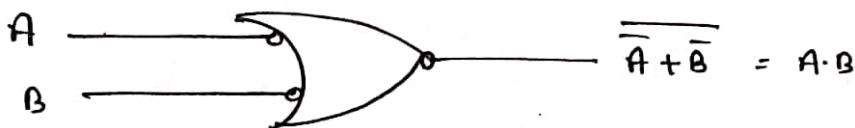


fig. AND gate using NOR


Note :

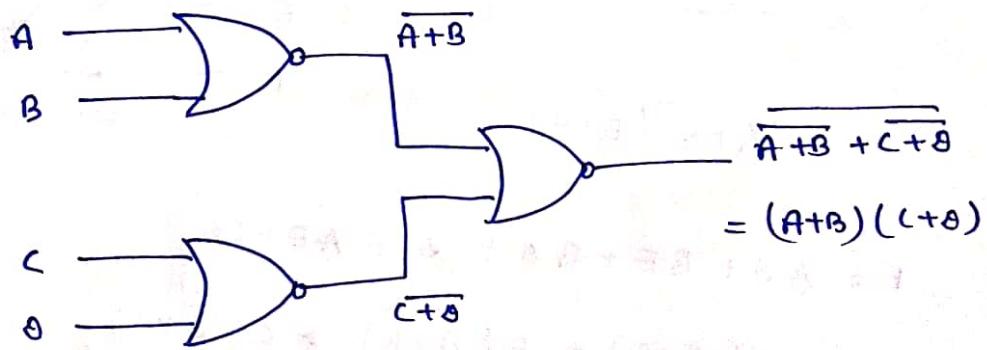

Ques. Design following function using Min. no. of 2/p NOR gates.

i) $F = A \cdot B$

Sol $F = A \cdot B = (A+A) \cdot (B+B)$

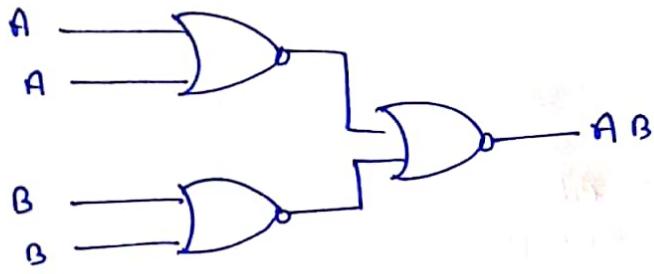


$$\text{II) } F = A(B + C)$$

$$= (A+A) \cdot (B+C)$$

\downarrow \downarrow
2 NOR 1 NOR Total 3 NOR

$$\text{III) } F = \frac{(A+B)(C+\theta)(E+F)}{X}$$

Sol

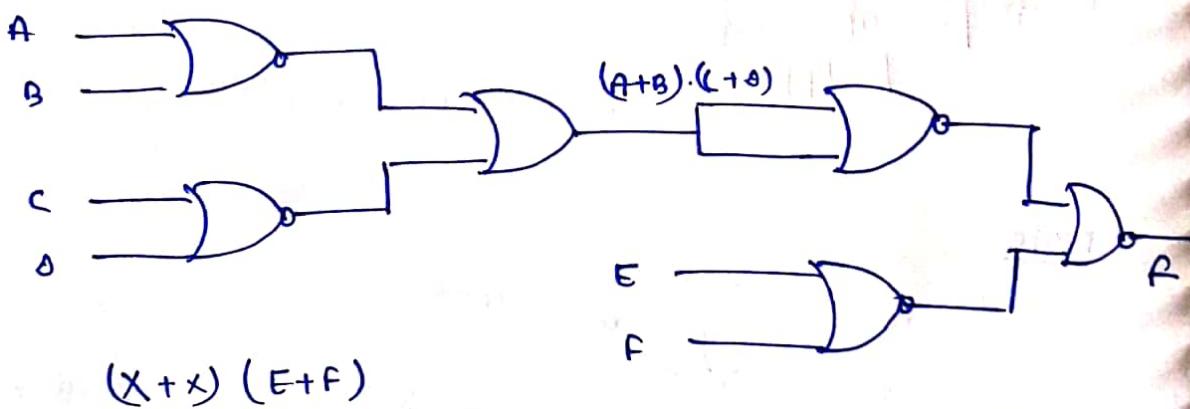

$$\text{IV) } F = AD + BE + BD + CD + AE + CE$$

$$= A(A+B) + E(A+B) + C(\theta+E)$$

$$= (A+B)(\theta+E) + C(\theta+E)$$

$$= (\theta+E)(A+B) + (C+C)(\theta+E)$$


$$= (A+B)X + X(C+C)$$

$$= (A+B)(X+X) + (X+X)(C+C)$$

$$\begin{aligned}
 F &= (A+B+C)(D+E) \\
 &= \underbrace{(X+C)}_{2 \text{ gate}} \underbrace{(D+E)}_{3 \text{ gate}} = 5 \text{ gate}
 \end{aligned}$$

* Switching Circuit representation of logic gates :-

i)

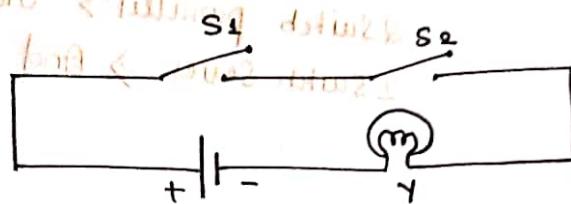

Switch ON \Rightarrow short circuited i.e. high

Switch OFF \Rightarrow open circuited i.e. low


Bulb glowing \Rightarrow High

Bulb not glowing \Rightarrow Low

S_1	S_2	Y
OFF 0	OFF 0	not glow 0
OFF 0	ON 1	not glow 0
ON 1	OFF 0	not glow 0
ON 1	ON 1	glow 1

Hence this switching ckt represents ANo gate.


ii)

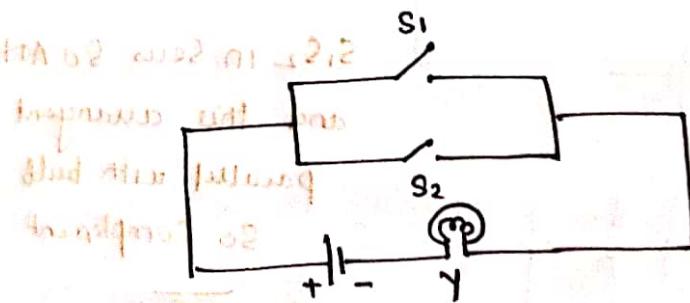

S_1	S_2	Y
0	0	0
0	1	1
1	0	1
1	1	1

It Represent OR gate

III)

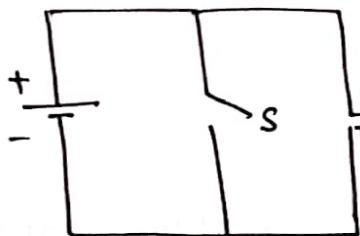


~~A AND~~ → Series with bulb
~~A NOR~~ → parallel with bulb

2 switch parallel \Rightarrow OR
 2 switch series \Rightarrow And


S	Y
0	1
1	0

This is NOT gate

IV)

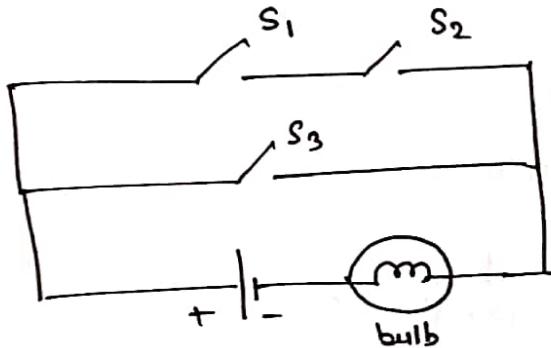

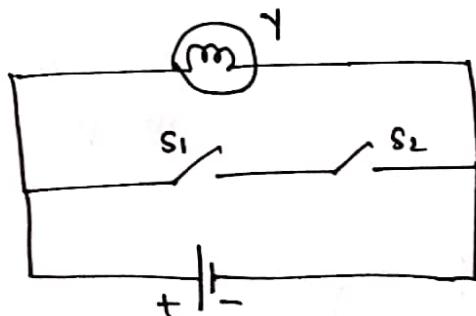$S_3 + S_1 S_2$
 and this arrangement
 Series with bulb
 Hence no complement
 applied




This is NOR gate

$S_1 S_2$ in Series So AND
 and this arrangement
 parallel with bulb
 So Complement

S_1	S_2	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{S_1 S_2}$$

v)

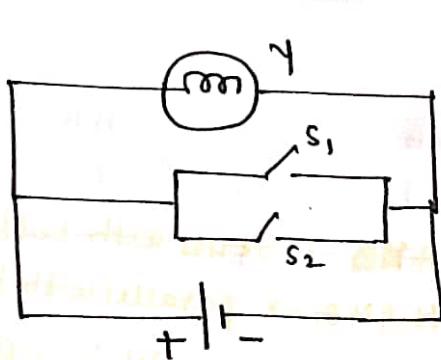


S_1	S_2	Y
0	0	1
0	1	0
1	0	0
1	1	0

This arrangement is NOR gate

Que. Derive the Truth table & Switching Circuit.

$$F = \overline{AB + CDE}$$

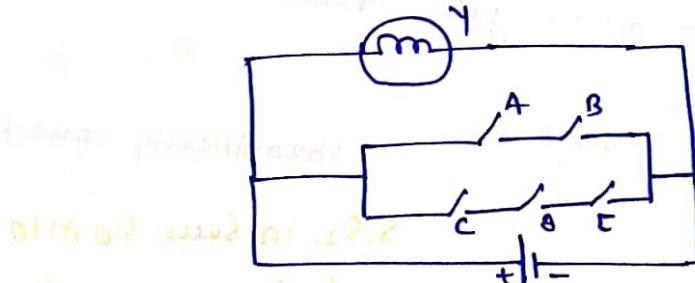

Parallel with bulb
ie Complement
applied.

* Special Purpose gates :-

1) Exclusive OR gate (Ex-OR) :-

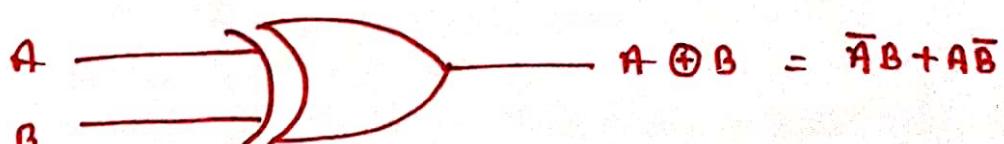


fig. logic Symbol of
2 ip ex-OR gate

Truth Table

A	B	\bar{A}	\bar{B}	$\bar{A} \oplus B$	$A \oplus \bar{B}$	$\bar{A} \oplus \bar{B}$
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

both I/p different



Dg.: - Ex-OR gate is a logic gate whose o/p is logic high when both the input are unequal or different

OR

Ex-OR gate is a logic gate whose o/p is logic low when both the input are similar or equal.

- Ex-OR gate detects unequal inputs by producing logic high at the output so it is also called inequality detector.

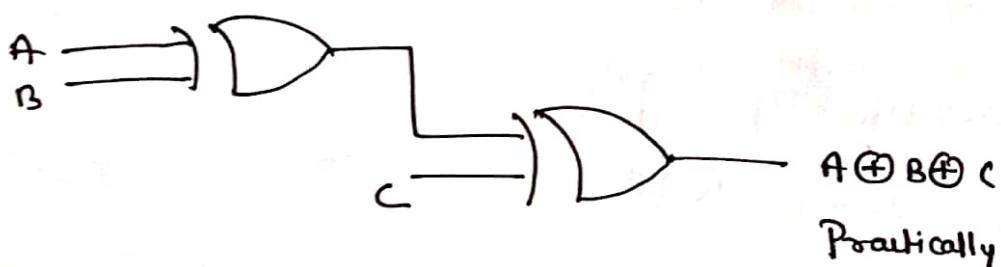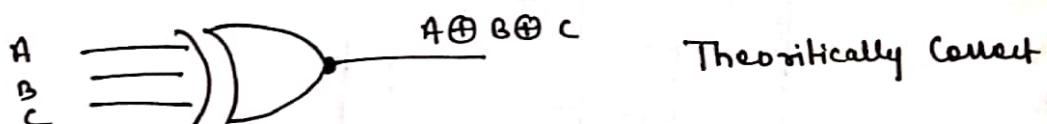Note:- 3 or more Input ex-or gate does not exist.



Ex.

A	B	C	$A \oplus B$	$(A \oplus B) \oplus C$	No. of 1's in A, B & C
0	0	0	0	0	even
0	0	1	0	1	→ odd
0	1	0	1	1	→ odd
0	1	1	1	0	even
1	0	0	1	1	→ odd
1	0	1	1	0	even
1	1	0	0	0	even
1	1	1	0	1	→ odd

Ex-OR gate is an
odd number of 1's detector

Ex. $1 \oplus 0 \oplus 1 \oplus 0 \oplus 0 \oplus 1 = 1$

Que. find

1) $A \oplus 0 = A$

2) $A \oplus 1 = \bar{A}$

3) $A \oplus A = 0$

4) $A \oplus \bar{A} = 1$

Que. If $A \oplus B = C$

$A \oplus C = ?$

Sol $\bar{A}B + A\bar{B} = C$

$A \oplus C$

$\Rightarrow A \oplus A \oplus B$

$\Rightarrow 0 \oplus B$

$= B$

$$5) A \oplus B = C$$

Note

$$A \oplus C = B$$

$$6) \text{ If } A \oplus B = C$$


then $A \oplus B \oplus C =$

Sol

$$C \oplus C = 0$$

$$A \oplus B \oplus C = 0$$

ii) Ex-NOR gate :-

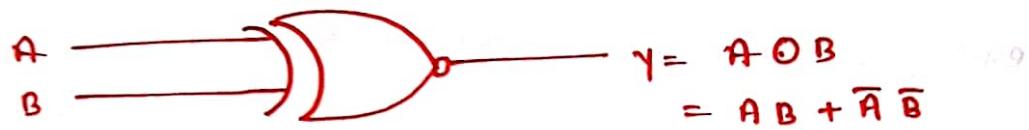

Ex-nor gate is an ex-or gate followed by an inverter.

	A	B	\bar{A}	\bar{B}	$A \oplus B$	$\bar{A} \bar{B}$	$A B + \bar{A} \bar{B}$
both I/p equal	0	0	1	1	0	1	1
	0	1	1	0	0	0	0
	1	0	0	1	0	0	0
both I/p equal	1	1	0	0	1	0	1

dy. Output is logic high when both input are similar
in case of ex-nor gate.

O/p is logic low when both I/p are different
in case of ex-nor gate.

Ex-nor gate is also called equality detector
because it give o/p logic high when both inputs
are equal.

$$\begin{aligned}
 A \oplus B \oplus C &= A \oplus B \cdot \bar{C} + C \cdot \bar{A \oplus B} \\
 &= \bar{A \oplus B} \cdot \bar{C} + C \cdot \bar{A \oplus B} \\
 &= \bar{A \oplus B} \cdot \bar{C} + C \cdot A \oplus B \\
 &= \bar{x} \bar{y} + xy \\
 &= x \oplus y \\
 \Rightarrow A \oplus B \oplus C &
 \end{aligned}$$

Hence

$$\boxed{A \oplus B \oplus C = A \oplus B \oplus C}$$

Concept:-

$$\overline{A \oplus B} = A \oplus B$$

$$A \oplus B \oplus C = A \oplus B \oplus C$$

$$\overline{A \oplus B \oplus C \oplus D} = A \oplus B \oplus C$$

$XOR = \overline{XNOR}$; for even no. of Input

$XOR = XNOR$; for odd no. of I/p

for odd no. of Input

$XOR = XNOR$ i.e. ~~XNOR is odd no. of I/p's detector if I/p are odd~~

for even no. of Input

$\overline{XOR} = XNOR$ i.e. ~~XNOR is even detector if I/p are even~~

$$\text{eg. } 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 1 = \text{even 1's} \quad \text{o/p} = 0$$

$$\text{ii) } 1 \oplus 1 \oplus 0 \oplus 1 \oplus 1 \oplus 1 \oplus 0 = \text{odd 1's} \quad \text{o/p} = 1$$


$$\text{iii) } 1 0 0 0 0 0 0 1 0 1 0 1 = \text{even 1's and even 1/p}_c \\ \text{o/p} = '1'$$

$$\text{iv) } 1 0 0 0 1 0 0 0 1 = \text{odd 1's and odd 1/p} \\ \text{o/p} = '1'$$



Que. find Min. two 1/p NAND gate to design an XOR fun.

Sol $A \oplus B$
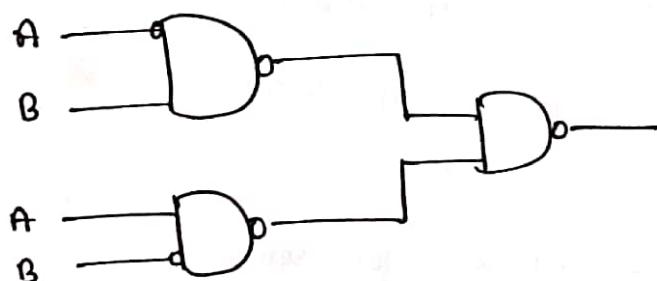
$$= \overline{\overline{A}B + A\overline{B}}$$




Hence total 5 NAND gate

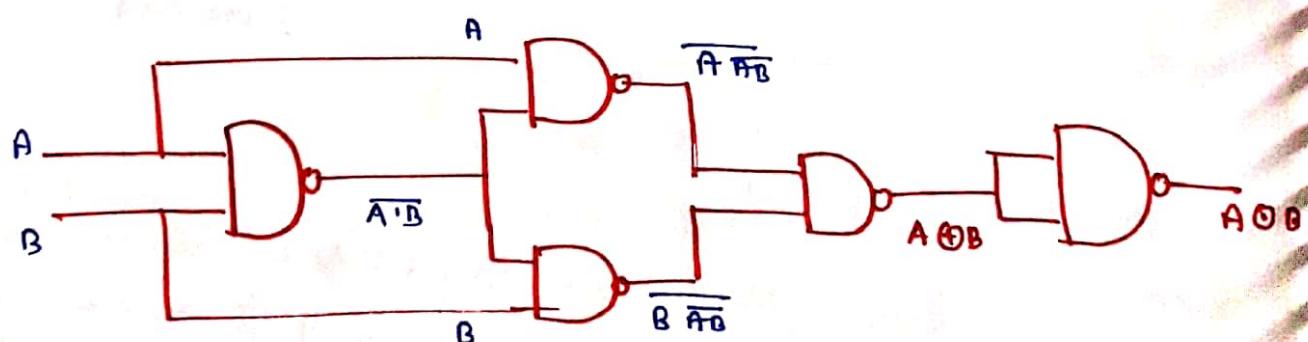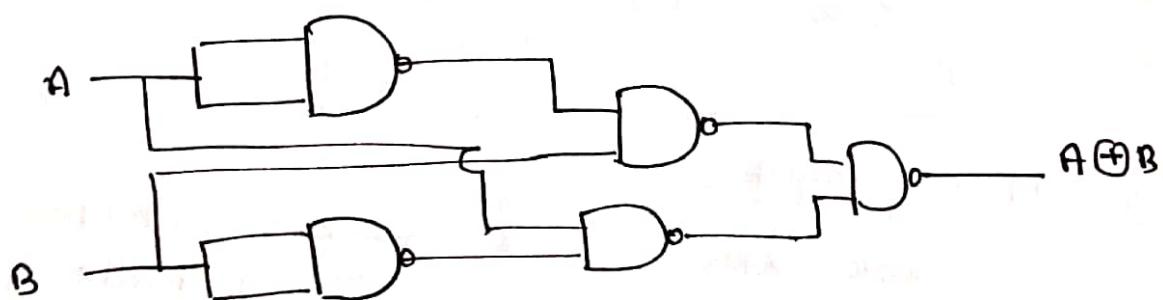


- 4 NAND gate required to design XOR function
- 5 NAND gate required to design XNOR function

Q40. Design XOR gate using NOR gate

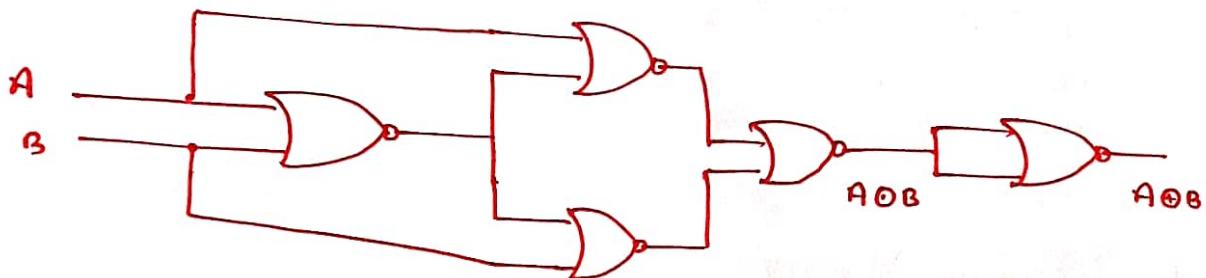

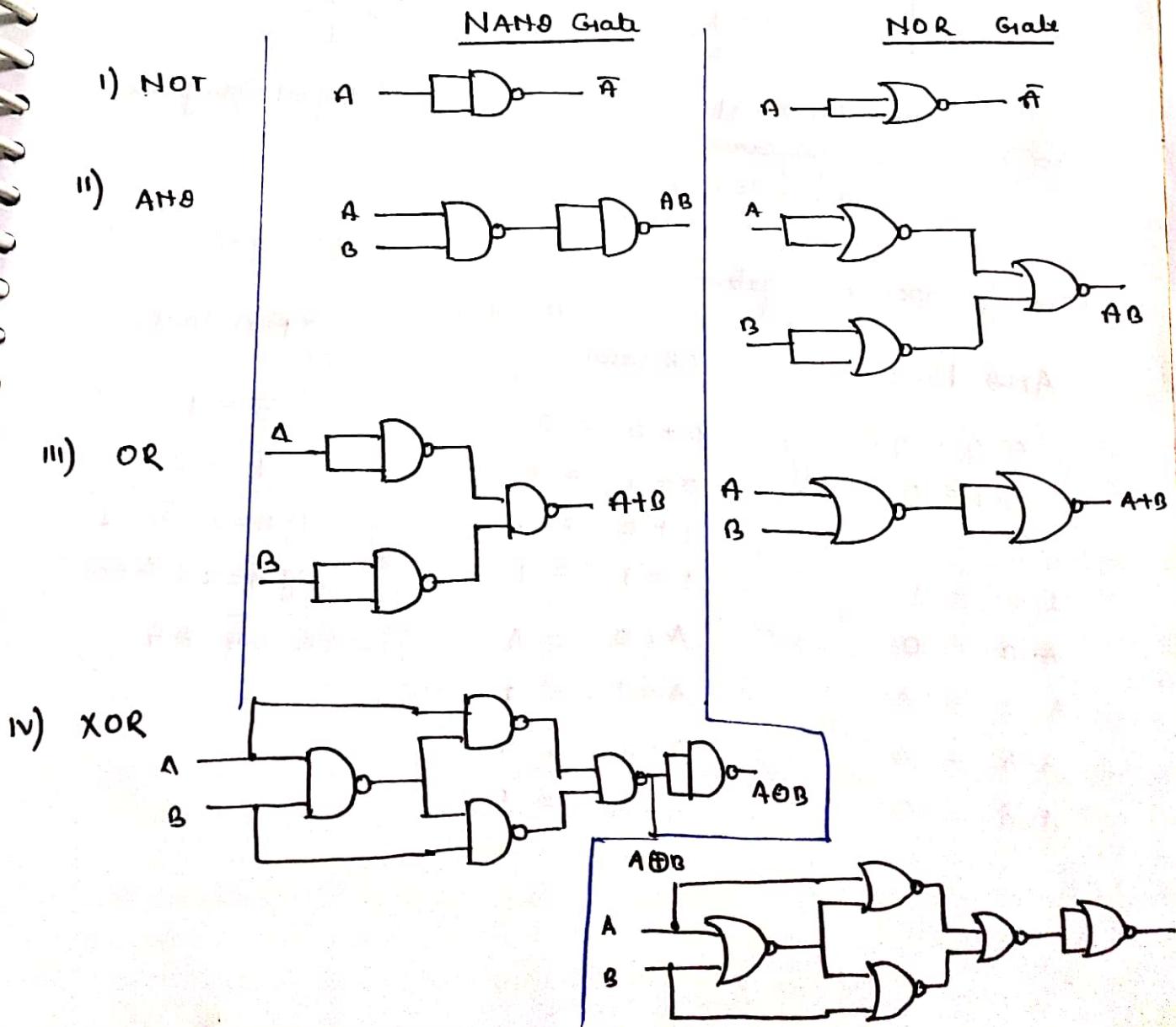- 4 NOR gate Required to design XNOR function
- 5 NAND gate required to design XOR function



No. of Gates

	NA AND	NOR
NOT	1	1
AND	2	3
OR	3	2
XOR	4	5
XNOR	5	4

* Boolean Algebra

Binary	Decimal
$\begin{array}{r} 1 \\ + 1 \\ \hline 0 \end{array}$	$\begin{array}{r} 1 \\ + 1 \\ \hline \frac{1}{2} \end{math}$

Both Numerical
Significance
but not logical

Boolean

$$\begin{array}{r} 1 \\ + 1 \\ \hline 1 \end{array}$$

Logical Significance

Laws of Boolean Algebra

AND Laws

$$\begin{aligned} 0 \cdot 0 &= 0 \\ 0 \cdot 1 &= 0 \\ 1 \cdot 0 &= 0 \\ 1 \cdot 1 &= 1 \\ A \cdot 0 &= 0 \\ A \cdot 1 &= A \\ A \cdot A &= A \\ A \cdot \bar{A} &= 0 \end{aligned}$$

OR Laws

$$\begin{aligned} 0 + 0 &= 0 \\ 0 + 1 &= 1 \\ 1 + 0 &= 1 \\ 1 + 1 &= 1 \\ A + 0 &= A \\ A + 1 &= 1 \\ A + A &= A \\ A + \bar{A} &= 1 \end{aligned}$$


NOT Laws


$$\begin{aligned} \bar{0} &= 1 \\ \bar{1} &= 0 \\ \text{If } A = 0 \quad \bar{A} &= 1 \\ \text{If } A = 1 \quad \bar{A} &= 0 \\ \bar{\bar{A}} &= A \end{aligned}$$

Commutative Law

- i) $A \cdot B = B \cdot A$
- ii) $A + B = B + A$
- iii) $\overline{A \cdot B} = \overline{B \cdot A}$
- iv) $\overline{A + B} = \overline{B + A}$
- v) $A \oplus B = B \oplus A$
- vi) $A \ominus B = B \ominus A$

Associative Law

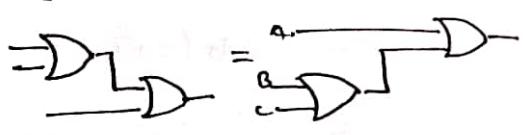- i) $(A + B) + C = A + (B + C)$ OR

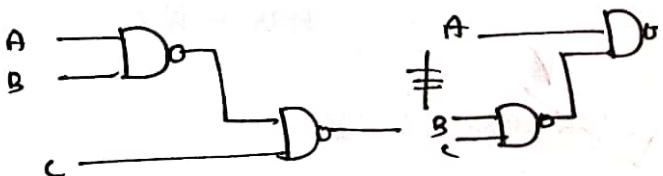- ii) $(A \cdot B) \cdot C = A \cdot (B \cdot C)$ AND
- iii) $(A \oplus B) \oplus C = A \oplus (B \oplus C)$ XOR
- iv) $(A \ominus B) \ominus C = A \ominus (B \ominus C)$ XNOR
- v) $\overline{(A \cdot B) \cdot C} \neq \overline{A \cdot (B \cdot C)}$ NAND and NOR do not follow associative law.



Distributive Law

- 1) $A(B + C) = AB + AC$
- 2) ~~$A + BC = (A+B)(A+C)$~~

Absorption Law

- 1) $A + AB = A$
- 2) $A(A+B) = A$

Que. Simplify

$$\begin{aligned} F &= AB + \overline{B}C + AC \\ &= A\cancel{B}(C+\overline{C}) + \overline{B}C(A+\overline{A}) + AC(B+\overline{B}) \quad \text{wrong} \\ &\Rightarrow \overline{AB} + \overline{B}C + AC \\ &\Rightarrow \overline{AB} \end{aligned}$$

Sol :- $AB + \overline{B}C + AC$

$$\begin{aligned} &AB + \overline{B}C + AC(B+\overline{B}) \\ &\Rightarrow AB + \overline{B}C + ACB + AC\overline{B} \\ &\Rightarrow AB(1+C) + \overline{B}C(1+A) \\ &\Rightarrow AB + \overline{B}C \end{aligned}$$

* Complement Law

i) $AB + BC + AC = BC + A\bar{C}$

Hence only one variable C present in two variable in both normal and complemented form. Thus in output we get only those two terms having C and to get op $AB(C+\bar{C})$ is applied

ii) $\overline{AB} + BC + AC = \overline{AB} + AC$

iii) $\overline{AB} + \overline{BC} + \overline{AC} = \overline{AB} + \overline{BC}$

* iv) $(A+B)(B+C)(\overline{A}+C) = (A+B)(\overline{A}+C)$

v) $(A+\overline{B})(B+C)(A+C) = (A+\overline{B})(B+C)$

$$\text{Proof: } (A+B)(B+C)(\bar{A}+C) = (A+B)(\bar{A}+C)$$

Sol LHS

$$\begin{aligned}
 & (A+B)(B+C+0)(\bar{A}+C) \\
 \Rightarrow & (A+B)\left(\underbrace{B+C}_{x} + \underbrace{A\bar{A}}_{yz}\right)(\bar{A}+C) \\
 \Rightarrow & (A+B)(A+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+C) \\
 \Rightarrow & (\underbrace{A+B+0}_{x+y})(\underbrace{A+B+C}_{x+z})(\bar{A}+\bar{B}+C)(\bar{A}+C+0) \\
 \Rightarrow & (A+B+0 \cdot C)(\bar{A}+C+0 \cdot B) \\
 = & (A+B)(\bar{A}+C) \quad //.
 \end{aligned}$$

* DeMorgan Theorem

$$i) \overline{A+B} = \bar{A} \cdot \bar{B}$$

$$ii) \overline{A \cdot B} = \bar{A} + \bar{B}$$

$$iii) \overline{A+B+C+\dots} = \bar{A} \cdot \bar{B} + \bar{C} \cdot \bar{D} + \dots$$

$$iv) \overline{A \cdot B \cdot C \cdot D \cdot E} = \bar{A} + \bar{B} + \bar{C} + \dots$$

* Principle of Duality

$$i) '0' \longleftrightarrow '1'$$

$$ii) '0' \longleftrightarrow '1'$$

iii) Don't Complement Variable

$$\text{eg. i) } f = AB + CD$$

$$f = A \cdot B + C \cdot D$$

$$f^D = (A + B) \cdot (C + D)$$

$$\text{ii) } f_2 = A \cdot 1$$

$$f_2^D = A + 0$$

Principle:- It states that " If we have a valid boolean eq"
Then its dual eq is also valid"

$$\text{eg. } A + BC = (A+B)(A+C)$$

Apply dual

$$A \cdot (B+C) = A \cdot B + A \cdot C$$

$$\text{eg. } A \cdot \bar{A} = 0$$

$$\xrightarrow{\text{dual}} A + \bar{A} = 1$$

$$\text{eg. } A + AB = A$$

$$\text{dual } A \cdot (A+B) = A$$

Que. $f = AB + BC + AC$ find dual

$$f^D = (A+B)(B+C)(A+C)$$

$$= (AB + AC + B + BC)(A+C)$$

$$= AAB + AAC + AC + AB + BAC + ACC + BC + BCC$$

$$= AB + AC + AC + AB + ACC + BC + B + ABC$$

$$= AB + AC + BC + ABC$$

$$= AB + BC + AC$$

$f = f^D \Rightarrow$ This type of function are called
Self dual function

Ques. How many unique functions are possible using only two variables?

Sol	A	\overline{AB}	$A + \overline{B}$
	B	AB	\overline{A}
	$\overline{A} B$	$A + \overline{B}$	\overline{B}
	$A \overline{B}$	$\overline{A + B}$	$\overline{AB} + A\overline{B}$
	0	$\overline{A} \overline{B}$	$\overline{AB} + AB$
	1	$\overline{A} + B$	$A + \overline{AB}$

By 0lp Combinations

A		B		Y = f(A, B)															
0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1	

2^{2^n} unique functions can be formed by using n input.

Total no. of Self dual function $2^{2^{n-1}}$

Ques. $f = A \oplus B$ find Complement & dual

$$\overline{f} = \overline{A \oplus B}$$

$$\overline{f} = \overline{AB} + AB$$

$$f^D = \overline{AB} + A\overline{B}$$

$$= (\overline{A} + B)(A + \overline{B})$$

$$= \overline{A}A + \overline{A}\overline{B} + AB + B\overline{B}$$

$$= \overline{A}\overline{B} + AB$$

Note:- XOR is such function $f^D = \overline{f}$

Que. $x = \{ (a+b\bar{c})d + e \} \bar{f} + g$

find \bar{x}

Sol $\{ (a+b\bar{c})d + e \} \bar{f} + g$

$$\Rightarrow \{ (a+b\bar{c})d + e \} \bar{f} * \bar{g}$$

$$\Rightarrow (\overline{(a+b\bar{c})d} + \bar{e}) + f * \bar{g}$$

$$\Rightarrow (\overline{(a+b\bar{c})} \cdot \bar{d}) + \bar{e} + f * \bar{g}$$

$$\Rightarrow \{ (\overline{a+b\bar{c}}) + \bar{d} \} \bar{e} + f * \bar{g}$$

$$\Rightarrow \{ \bar{a} * \bar{b}\bar{c} + \bar{d} \} \bar{e} + f * \bar{g}$$

$$\Rightarrow [\bar{a} \bar{e} \cdot \bar{e} (\bar{b} + c) + \bar{e} \bar{d} + f * \bar{g}] \bar{g} //.$$

$$\Rightarrow (\bar{a} \bar{b} \bar{e} + \bar{a} \bar{e} c + \bar{e} \bar{d} + f) \bar{g}$$

—①

find x^0

Sol $\{ a \cdot (b+\bar{c}) + d \cdot e \} + \bar{f} \cdot g$

$$= [\{ a \cdot (b+\bar{c}) + d \} e + \bar{f}] g$$

↓ Individual Complement all Variable


$$[\{ \bar{a} \cdot (\bar{b} + c) + \bar{d} \} \bar{e} + f] \bar{g} —②$$

eq ① & ② are same Hence to find Complement

i) find dual

ii) Complement Individual

Que.

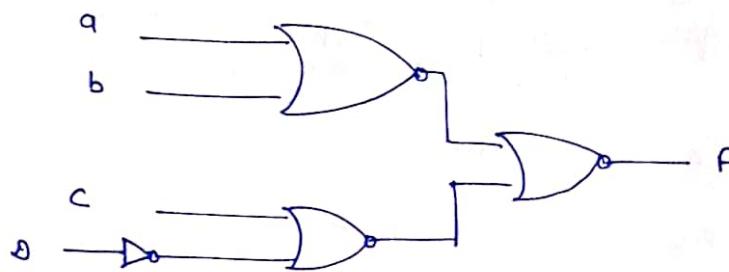

$$F = ?$$

- a) $(a+b)(c+d)$
- b) $(\bar{a}+\bar{b})(c+d)$
- c) $(a+\bar{b})(c+\bar{d})$
- d) $(a+b)(\bar{c}+\bar{d})$

Que. What is the Minimum no. of gate required
to Implement Boolean exp.
 $A \cdot B + C$ if we have to use only two 1/p NOR.

$$\begin{aligned}\text{Sol } F &= A \cdot B + C \\ &= (\bar{A} + \bar{B})(\bar{B} + C) \\ &= \text{3 NOR.}\end{aligned}$$

Ques. The Boolean function $\gamma = A \cdot B + C \cdot D$ is to be implemented using only two 1/p NOR. The Min. no of gate required is 3.

Ques. Assume that only $X \& Y$ logic input are available and their Complement $\bar{X} \& \bar{Y}$ are not available what is Min. no of two 1/p NOR gate req. to implement

$$X \oplus Y$$

$$\text{Sol } 4 \text{ NOR}$$

Q4. The Boolean Exp. $y = A + BC$ is to be realized using two 1/p gates of only one type. What is min. no. of gate required for the implementation?

Sol $y = (A+B)(A+C)$ 3 NOR

OR $y = A \cdot A + BC$ 3 NAND


Q5. Min. no of two 1/p NAND gate required to implement the function

$$Z = A \bar{B} C$$

$$\begin{aligned} &= \overline{\overline{A \bar{B} C}} \\ &= \overline{\overline{A \bar{B}} + \overline{C}} \Rightarrow \overline{\overline{A \bar{B}}} + \overline{\overline{C} \cdot \overline{C}} \\ &= \overline{\overline{A} + B + \overline{C}} \quad \begin{array}{l} X \\ Y \end{array} \rightarrow 3 \text{ NAND} \\ &\quad + \perp \bar{B} \\ &\quad + \perp \bar{A} \bar{B} \\ &\quad + \perp \bar{C} \\ &\quad \hline + \frac{C}{7} \end{aligned}$$

$$Z = A \bar{B} C$$
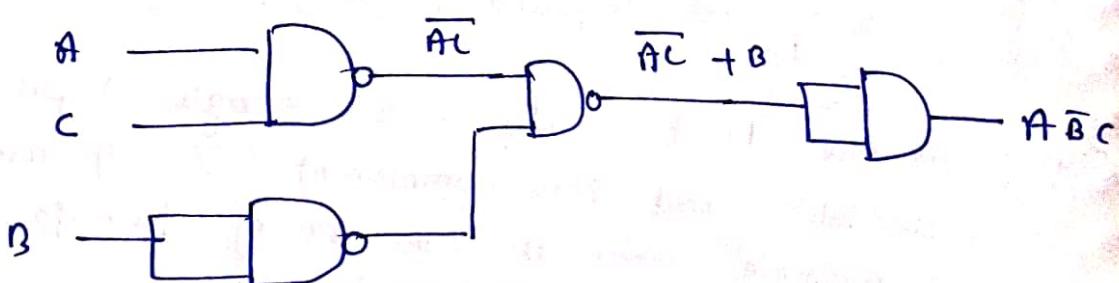
$$\begin{aligned} &= \overline{\overline{A \bar{B} C}} \Rightarrow \overline{\overline{A} C + \overline{B}} \\ &= \overline{\overline{A \bar{B}} + \overline{C}} \quad \overline{\overline{A} C + B \cdot B} \\ &= \end{aligned}$$



Que. $(x+y)(x+\bar{y}) \neq [(\bar{x}\bar{y}) + \bar{x}]$

Sol

$$\begin{aligned} & x + x\bar{y} + xy + 0 + \bar{x}\bar{y} \cdot x && x + y\bar{y} + (\bar{x} + y)x \\ \Rightarrow & x + xy + 0 + (\bar{x} + y)x && x + xy \\ \Rightarrow & x + 0 + xy && x // \\ = & x(1+y) && \\ = & x // \end{aligned}$$

Que. $F(PQRS) = P\bar{Q} + \bar{P}QR + \bar{P}Q\bar{R}S$

Minimal function F w

Sol

$$\begin{aligned} & P\bar{Q} + \bar{P}QR + \bar{P}Q\bar{R}S \\ \Rightarrow & P\bar{Q} + \bar{P}Q(R + \bar{R}S) \\ \Rightarrow & Q[P + \bar{P}(R + \bar{R}S)] \\ \Rightarrow & Q[P + \bar{P}(R + \bar{R})(R + S)] \\ \Rightarrow & Q[P + \bar{P}(R + S)] \Rightarrow Q\{\bar{P}\} \\ \Rightarrow & QP + Q\bar{P}R + Q\bar{P}S \\ \Rightarrow & \dots \end{aligned}$$

Sol

$$Q[P + \bar{P}(R + \bar{R}S)]$$

$x + \gamma_2$

$$Q[(P + \bar{P})(P + R + \bar{R}S)]$$

$$\Rightarrow Q[P + (R + \bar{R})(R + S)]$$

$$\Rightarrow QP + QR + QS //$$

Que Simplify

$$\underbrace{(P + \bar{Q} + \bar{R})}_A \quad \underbrace{(P + \bar{Q} + R)}_B \quad \underbrace{(P + Q + \bar{R})}_C$$


Sol

$$(P + \bar{Q} + \bar{R}) (P + Q + \bar{R})$$

$\left\{ \begin{array}{l} \text{distributive} \\ \text{law} \end{array} \right.$

$$\begin{aligned}
 & \Rightarrow (P + \bar{Q}) (P + Q + \bar{R}) \\
 & \Rightarrow P + PQ + P\bar{Q} + P\bar{R} + \bar{Q}Q + \bar{Q}\bar{R} \\
 & \Rightarrow P(1 + \bar{R}) + Q(Q + \bar{Q}) + \bar{Q}\bar{R} \\
 & \Rightarrow P + \bar{Q} + \bar{Q}\bar{R} \Rightarrow P + \bar{Q}\bar{R} // \\
 & \cancel{\Rightarrow P + (Q + \bar{Q})(Q + \bar{R})} \\
 & \cancel{\Rightarrow P + Q(Q + \bar{R})} \\
 & \cancel{\Rightarrow P + Q + Q\bar{R} //} \\
 & \Rightarrow P + \bar{Q}
 \end{aligned}$$

Que. $F = ?$

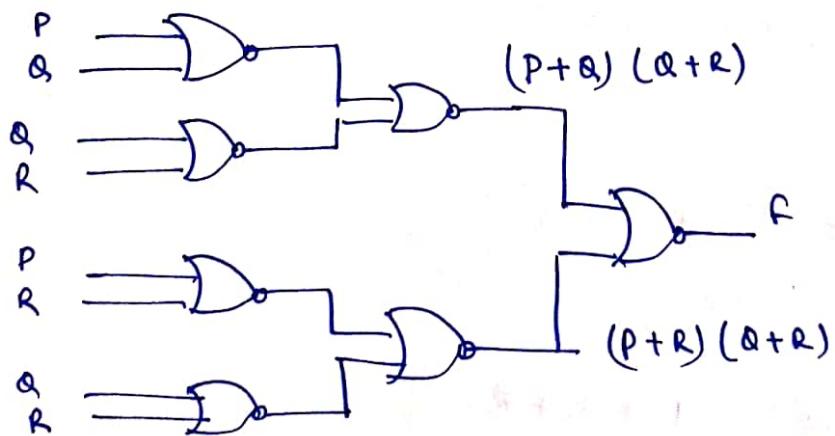

$$F = \overline{(P+Q)(Q+R) + (P+R)(Q+R)}$$

$$= \overline{(Q+R)(P+Q+R)}$$

$$= \overline{Q+R + P \cdot 0} //, = \overline{Q+R} //$$

$\left\{ \begin{array}{l} (Q+R+0)(Q+R+P) \\ Q+R+0 \cdot P \end{array} \right.$

* Representation of Boolean Expressions :-

- i) Sum of product form (SOP)
- ii) Product of sum form (POS)

Product term

$$f = A\bar{B}C$$

$$f = \bar{A}B\bar{C}$$

$$f = AC$$

Sum terms

$$f = \bar{A} + B + C$$

$$f = A + B + \bar{C}$$

$$f = \bar{B} + C$$

Sum of product

$$f = A\bar{B}C + \bar{A}B\bar{C} + AC$$

Bringing

Product of sum term

$$f = (\bar{A} + B + C)(A + B + \bar{C})$$

(B+C)

This is not standard form of POS & SOP

In standard form there is no missing variable in all the terms.

Missing

$$f = A\bar{B}C + \bar{A}B\bar{C} + AC$$

$$= A\bar{B}C + \bar{A}B\bar{C} + AC(B + \bar{B})$$

$$= A\bar{B}C + \bar{A}B\bar{C} + ABC + A\bar{B}C$$

$$\Rightarrow A\bar{B}C + \bar{A}B\bar{C} + ABC$$

now this is in standard
SOP form

$$f = (\bar{A} + B + C)(A + B + \bar{C})(B + C + A \cdot \bar{A})$$

$$= (\bar{A} + B + C)(A + B + \bar{C})(A + B + C)(\bar{A} + B + C)$$

now this is std.
POS

- All the product terms in standard SOP are referred as minterm.
- All the Sum terms in standard POS are referred as Maxterm

			<u>Minterm table</u>	minterms	<u>Dec</u>
A	B	C			
0	0	0	$\bar{A} \bar{B} \bar{C}$	m_0	0
0	0	1	$\bar{A} \bar{B} C$	m_1	1
0	1	0	$\bar{A} B \bar{C}$	m_2	2
0	1	1	$\bar{A} B C$	m_3	3
1	0	0	$A \bar{B} \bar{C}$	m_4	4
1	0	1	$A \bar{B} C$	m_5	5
1	1	0	$A B \bar{C}$	m_6	6
1	1	1	$A B C$	m_7	7

Note: Normal Variable $\longleftrightarrow 1$ Minterm or POS
 Complemented Var. $\longleftrightarrow 0$

			<u>Maxterm table</u>	Maxterm	
A	B	C			
0	0	0	$A + B + C$	M_0	0
0	0	1	$A + B + \bar{C}$	M_1	1
0	1	0	$A + \bar{B} + C$	M_2	2
0	1	1	$A + \bar{B} + \bar{C}$	M_3	3
1	0	0	$\bar{A} + B + C$	M_4	4
1	0	1	$\bar{A} + B + \bar{C}$	M_5	5
1	1	0	$\bar{A} + \bar{B} + C$	M_6	6
1	1	1	$\bar{A} + \bar{B} + \bar{C}$	M_7	7

Note Maxterm or SOP $Y \longleftrightarrow$ Complemented Var.
 $\bar{Y} \longleftrightarrow$ Normal Var.

$$\text{eg. } f = A\bar{B}C + \bar{A}B\bar{C} + ABC$$

$$= \sum m(101 + 010 + 111)$$

$$= \boxed{\sum m(5, 2, 7)} \quad \text{Representation in std. SOP}$$

$$= m_5 + m_2 + m_7$$

$$\text{eg. } f = (\bar{A} + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + \bar{C})$$

$$= \prod (110, 010, 001)$$

$$= \prod (6, 2, 1)$$

$$= M_6 \cdot M_2 \cdot M_1 = \boxed{\prod M(1, 2, 6)}$$

std pos

II.

Ques. $f = A + \bar{B}C$

i) SOP std:

$$A(B + \bar{B})(C + \bar{C}) + \bar{B}C(A + \bar{A})$$

$$\Rightarrow A[B(C + \bar{C}) + \bar{B}(C + \bar{C})] + A\bar{B}C + \bar{A}\bar{B}C$$

$$\Rightarrow ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$= ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$= \sum m(7, 6, 4, 5, 1)$$

ii) POS std:

$$f = A + \bar{B}C$$

$$= A + A\bar{A} + B\bar{B} + \bar{B}C + A\bar{A}$$

$$= (A + B + C)(A + \bar{B} + \bar{C})$$

first change in POS

$$f = (A + C)(A + \bar{B})$$

$$\begin{aligned}
 f &= (A + \bar{B} + C\bar{C})(A + C + B\bar{A}) \\
 &= (A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + \overbrace{C + B})(A + \overbrace{C + \bar{B}}) \\
 &= \prod (010, 011, 000, 010) \\
 &= \prod M(0, 2, 2, 3) \\
 &= M_0 \cdot M_2 \cdot M_2 \cdot M_3 \\
 &= M_0 M_2 M_3 //
 \end{aligned}$$

Note:- There is no need to find both Maxterm & Min term of any function. And only Maxterm or Min and fond missing term to obtain Min or Maxterm
 $\sum m(1, 4, 5, 6, 7)$
 $\prod M(0, 2, 3)$

- SOP & POS are NOT complement of Each other
 SOP and POS are two different ways to represent any boolean function.

Ques. Find Standard SOP form

$$\begin{aligned}
 ① f(A, B, C) &= \overline{A}BC + A\overline{B}\overline{C} \\
 &\stackrel{\text{MSB}}{\uparrow} \stackrel{\text{LSB}}{\uparrow} = \sum m(011, 110) \\
 &= \sum m(3, 6)
 \end{aligned}$$

$$\begin{aligned}
 ② f(B, A, C) &= \overline{A}BC + A\overline{B}\overline{C} \\
 &\stackrel{\text{MSB}}{\uparrow} \stackrel{\text{LSB}}{\uparrow} = \sum m(101, 110) \\
 &= \sum m(5, 6)
 \end{aligned}$$

$$\begin{aligned}
 ③ f(C, A, B) &= \overline{A}BC + A\overline{B}\overline{C} \\
 &\stackrel{\text{MSB}}{\uparrow} \stackrel{\text{LSB}}{\uparrow} = \sum m(101, 011) \\
 &= \sum m(5, 3) = \sum m(3, 5)
 \end{aligned}$$

Que. $f = A + \overline{B}C$

$$\begin{array}{ccc} A & B & C \\ \times & 0 & 1 \\ 0 & 0 & 1 \\ 1 & 0 & 1 \end{array} \rightarrow \begin{array}{c} 1 \\ \perp \\ 5 \end{array}$$

$$\begin{array}{ccc} A & B & C \\ 1 & \times & \times \\ 1 & 0 & 0 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \end{array} \rightarrow \begin{array}{c} 4 \\ 5 \\ 6 \\ 2 \end{array}$$

Hence $\Sigma m(1, 4, 5, 7)$

Que. $f(A, B, C) = \overbrace{\overline{A}B + BC}^1$

$$\begin{array}{ccc} A & B & C \\ \times & 1 & 1 \\ 0 & 1 & 1 \\ 1 & 1 & 1 \end{array} \rightarrow \begin{array}{c} 3 \\ 7 \end{array}$$

$$\begin{array}{ccc} A & B & C \\ 0 & \perp & \times \\ 0 & \perp & 0 \\ 0 & \perp & 1 \end{array} \rightarrow \begin{array}{c} 2 \\ 3 \end{array}$$

$\Sigma m(2, 3, 7) //$

Que $f(A, B, C) = \overline{A} + \overline{B}C$

$$\begin{array}{ccc} A & B & C \\ \times & 0 & 1 \\ 0 & 0 & 1 \\ 1 & 0 & 1 \end{array} \rightarrow \begin{array}{c} 1 \\ 5 \end{array}$$

$$\begin{array}{ccc} A & B & C \\ 0 & \times & \times \\ 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{array} \rightarrow \begin{array}{c} 0 \\ 1 \\ 2 \\ 3 \end{array}$$

$\Sigma m(0, 1, 2, 3, 5) //$

Q4e. $f(C, A, B) = \overbrace{AC}^{\text{F}} + \overbrace{\bar{B}C}^{1}$

$\begin{array}{c cc} F & A & B \\ \hline 1 & \times & \\ 7 & \leftarrow 1 & 1 \\ 6 & \leftarrow 1 & 0 \end{array}$	$\begin{array}{c cc} C & A & B \\ \hline 1 & \times & 0 \\ 1 & 1 & 0 \\ 1 & 0 & 0 \end{array}$	$\xrightarrow{\quad} 6$ $\xrightarrow{\quad} 4$
--	--	--

$$\sum m(4, 6, 7) \quad //$$

Que. Identify whether SOP or POS

- i) $A + B \rightarrow \text{POS}$
- ii) $AB \rightarrow \text{SOP}$ Note
- iii) $A \oplus B \rightarrow \text{Neither SOP nor POS}$
- iv) $A \odot B \rightarrow \text{Neither SOP nor POS}$
- v) $\overline{A+B} \rightarrow \text{Neither SOP nor POS}$
- vi) $\overline{A \cdot B} \rightarrow \text{Neither SOP nor POS}$
- vii) $AB + C \rightarrow \text{SOP}$
- viii) $(A+B)(A+C) \rightarrow \text{POS}$

Que. find SOP POS

A	B		Y
0	0		0
0	1		0
1	0		0
1	1		1

$$\text{SOP} = \overline{A}B$$

$$\text{POS} = \cancel{AB} + \cancel{A\bar{A}} + \cancel{B\bar{B}} + \overline{A}\bar{B}$$

A	B	Y	
0	0	0	
0	1	0	
1	0	0	
1	1	1	

}

$P_{OS} = (A+B)(A+\bar{B})(\bar{A}+B)$

}

$S_{OP} = AB$

$$\begin{aligned}
 Y_{POS} &= (A+B)(A+\bar{B})(\bar{A}+B) \\
 &= (A+B\bar{B})(\bar{A}+B) \\
 &= A\bar{A} + AB \\
 &= AB
 \end{aligned}$$

$$Y_{POS} = S_{OP}$$

Ques. find SOP & POS

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$P_{OP} = (A+\bar{B})(\bar{A}+B)$$

$$P_{OP} = \bar{A}\bar{B} + AB$$


Note:- Reason why '1' considered for SOP & '0' considered for POS in truth table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 S_{OP} &= \cancel{\bar{A}\bar{B} \cdot 0} + \cancel{\bar{A}B \cdot 0} + \cancel{A\bar{B} \cdot 0} \\
 &\quad + AB \cdot 1 \\
 &= AB \quad \text{ie Correspond to 1}
 \end{aligned}$$

$$\begin{aligned}
 P_{OS} &= (A+B+0)(A+\bar{B}+0) \\
 &\quad (\bar{A}+B+0)(\bar{A}+\bar{B}+1)
 \end{aligned}$$


Hence 0 term for POS

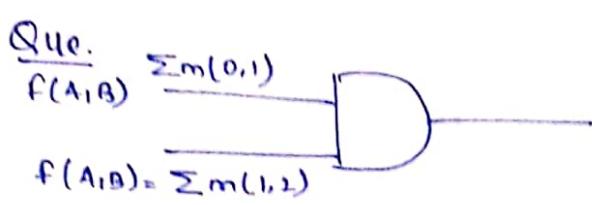

Sol:


$$\begin{aligned} & (\bar{A}\bar{B} + \bar{A}B) (\bar{A}B + A\bar{B}) \\ & \Rightarrow \bar{A}B + \bar{A}\bar{B} A\bar{B} \\ & \quad \bar{A}B \\ & = \sum m(1) \end{aligned}$$

{ Distributive law

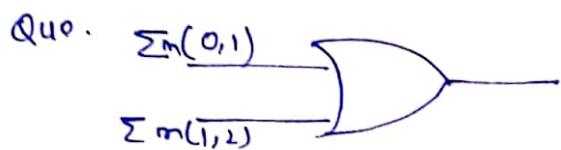

$$\begin{aligned} & (\bar{A}\bar{B} + \bar{A}B) + (\bar{A}B + A\bar{B}) \\ & \Rightarrow \bar{A}\bar{B} + \bar{A}B + \bar{A}\bar{B} \\ & = \sum m(0, 1, 2) \end{aligned}$$

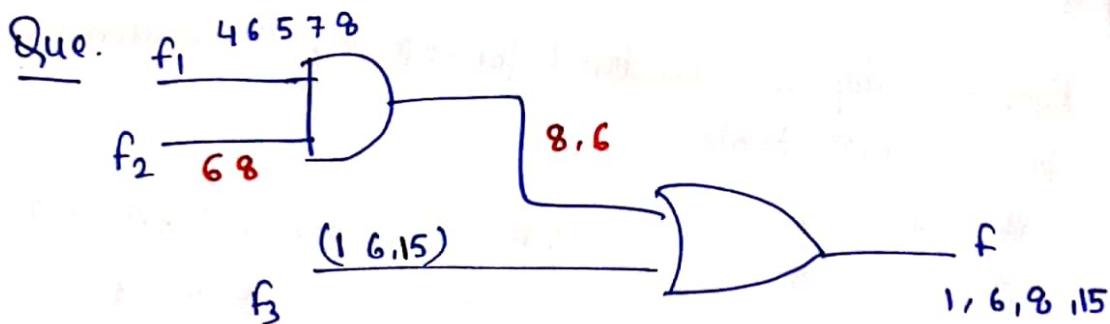Concept:- AND gate pass term which are common in I/P
OR gate pass term which present in all I/P.




$f_2 = ?$

$$1) f_1 = \sum m(8, 9, 10)$$

$$f_2 = \sum m(7, 8, 12, 13, 14, 15)$$

$$f = \sum m(8, 9)$$

$$f_3 = 9$$

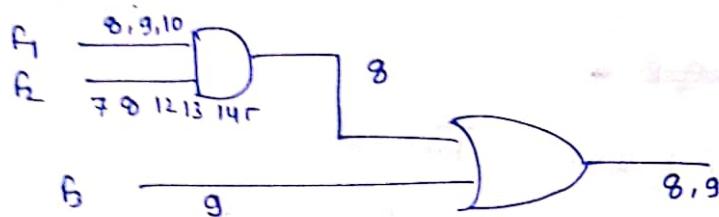

$$f_3 = \sum m(9)$$

$$\text{Que. } f(P, Q, R) = P\bar{Q} + \bar{Q}R + PR$$

$$= PQR + P\bar{Q}\bar{R} + \bar{P}\bar{Q}R + P\bar{Q}R + P\bar{Q}R + P\bar{Q}\bar{R}$$

$$= PQR + P\bar{Q}\bar{R} + \bar{P}\bar{Q}R + P\bar{Q}R$$

$$= \sum m(3, 5, 6, 7)$$

$$\text{Que. } f(P, Q, R) = P\bar{Q} + \bar{Q}\bar{R} + P\bar{R}$$

Sol

P	Q	R	f
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$G, 7, 2, 6, 4, 6$$

$$\Rightarrow \sum m(2, 4, 6, 7)$$

Ques. The boolean expression

$f(P, Q, R) = \pi(0, 5)$ is to be implemented using only 2 input gates which are three gate.

So $\pi(0, 5)$

$\Rightarrow \cancel{PQR} \rightarrow$

$\Rightarrow (P + Q + R)(\bar{P} + Q + \bar{R})$

$\Rightarrow P\bar{P} + Q + (P+R)(\bar{P}+\bar{R})$

$\Rightarrow Q + P\bar{P} + P\bar{R} + R\bar{P} + R\bar{R}$

$\Rightarrow Q + P\bar{R} + R\bar{P}$

$= \text{OR} \& \text{ XOR } //$

{ Distributive Law}

* Karnaugh Map (k-Map)

	a	b	\bar{b}	b
\bar{a}	0	00	1	01
	1	2	3	11
a	1	10		

a	b	y
0	0	
0	1	
1	0	
1	1	

	a	bc	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$b\bar{c}$
\bar{a}	0	0	00	01	11	10
a	1	4	100	101	111	110

a	b	c	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$\bar{a}b$	c	\bar{c}	c
0	0	1	1
000	001		
2	2	3	3
010	011		
6	6	7	7
110	111		
4	4	5	5
100	101		

$\bar{a}b$	cd	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
00	0	1	3	2	2
01	4	5	7	6	6
11	12	13	15	14	14
10	8	9	11	10	10


cd	ab	$\bar{a}b$	$\bar{a}b$	ab	ab
0	0	4	12	8	8
1	1	5	13	9	9
03	03	7	15	11	11
02	02	6	14	10	10

eg.


- Every term is 1 in L-map $0/p = 1$
- Diagonal can't be group together
- group only 2^{n^2} 1's (neighboring 1's)
- common term in a group will be 0/p of that group

Try to make
group with
max^m 1's

eg.

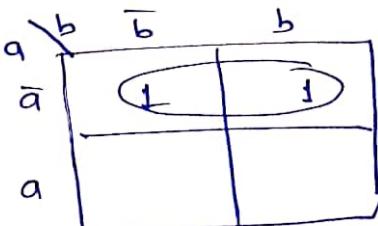


$$Y = \bar{a}$$

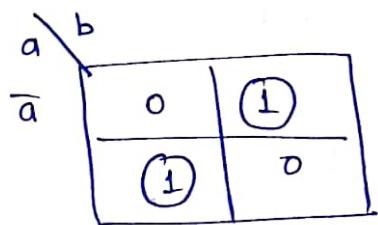

$$Y = \bar{a}b + a\bar{b}$$


eg

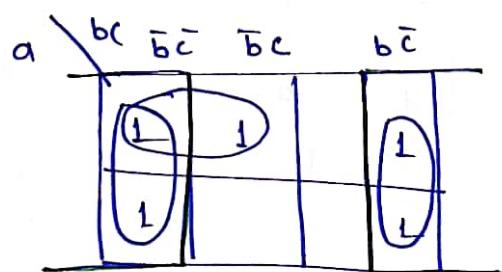

$$Y = \bar{c} + \bar{a}\bar{b}$$

Ques.

Minimize

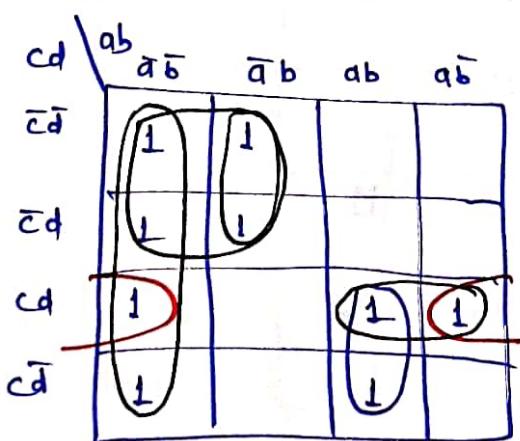


$$Y = \bar{a}\bar{b} + \bar{a}b\bar{c} + cd\bar{a} + \cancel{ab\bar{c}} + abc\cancel{d}$$

$$\text{OR } Y = \bar{a}\bar{b} + \bar{a}\bar{c} + \cancel{a\bar{c}} + \bar{b}cd + abc$$

for above question find Minimal POS form

Sol

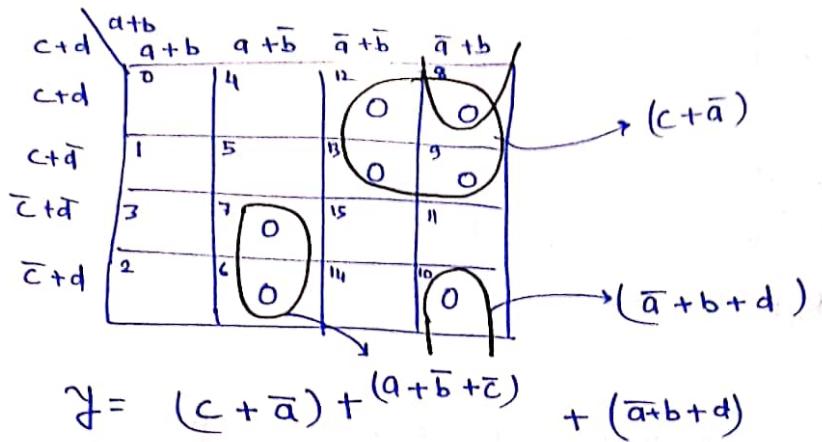

$$Y = (c+a)(a+\bar{b}+\bar{c}) * (\bar{a}+b+d)$$

Note: gray code sequence will be similar

$$Y = \prod M(6, 7, 8, 10, 9, 12, 13)$$

Que. Minimize in POS format

$$f(PQRS) = PR + \bar{P}QS + S$$


$$\sum_m = P R (S+\bar{S})(Q+\bar{Q}) + \bar{P}QS(R+\bar{R})$$

P Q R S	P Q R S	P Q R S
1 0 1 0	0 1 0 1	0 0 0 1
1 0 1 1	0 1 1 0	0 0 1 1
1 1 1 0		0 1 0 1
1 1 1 1		0 1 1 1
		1 0 0 1
		1 0 1 1
		1 1 0 1
		1 1 1 1

$$\sum_m = \{10, 11, 14, 15, 7, 5, 13, 5, 7, 9, 11, 13, 15\}$$

$$\sum_m \{1, 3, 5, 7, 9, 10, 11, 13, 14, 15\}$$

$$\prod M \{02 4 6 8 12\}$$

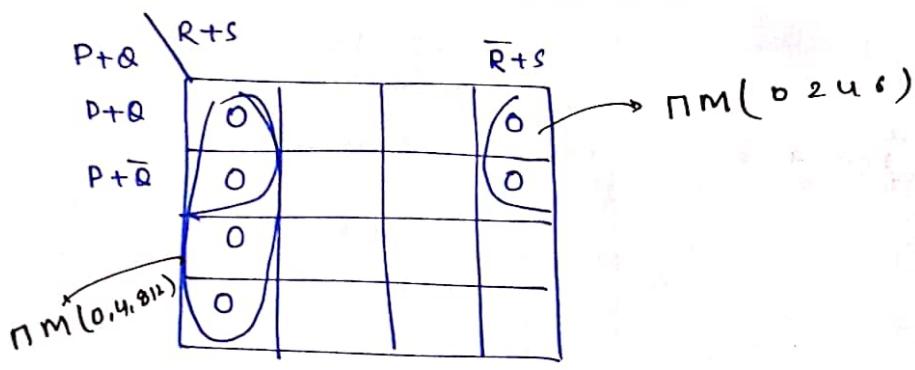


$$Y = (R+S)(P+Q) //$$

Q1. Minimal SOP form of Boolean expression

$$Y = \overline{P} \overline{Q} \overline{R} \overline{S} + P \overline{Q} \overline{R} \overline{S} + P \overline{Q} \overline{R} S + P \overline{Q} R S \\ + P \overline{Q} R \overline{S} + P \overline{Q} R S + \dots$$


Sol)
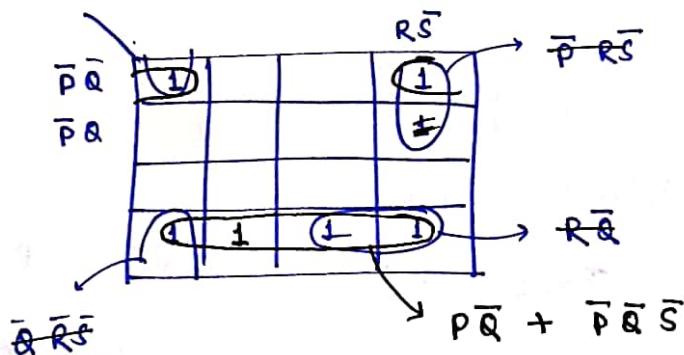
$$\Sigma m \{ 0 \ 2 \ 4 \ 8 \ 10 \ 11 \}$$



$$f = \overline{P} \overline{R} \overline{S}$$
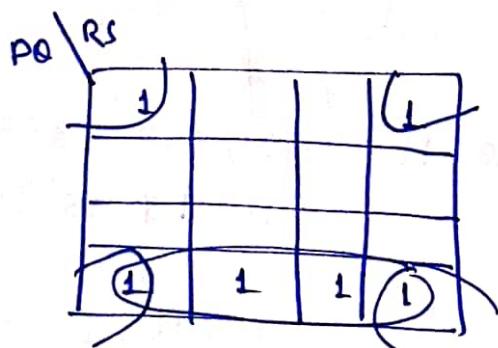
$$Y = P \overline{Q} + \overline{P} \overline{Q} \overline{S} \\ = \overline{Q} + P + \overline{P} \overline{S}$$



$$Y = P \overline{Q} + \overline{Q} \overline{S}$$

Q2.

$cd \swarrow db$

\perp	\perp		\perp
x_1			
x_2			
\perp	\perp		x_1

- find Minimized expression

$$A\bar{L} \quad X_3 = 1 \quad x_1 = x_2 = 0$$

A Karnaugh map for two variables a and b . The columns represent $a = 0$ and $a = 1$, and the rows represent $b = 0$ and $b = 1$. The cells are labeled as follows:


1	1		
0			1
0			
1	1		1

The labels indicate minterms: $\bar{a}\bar{b}$ (top-left), $a\bar{b}$ (top-right), $\bar{a}b$ (middle-right), and ab (bottom-right). The bottom-left cell is labeled (1) , and the bottom-middle cell is also labeled (1) .

$$y = \bar{b}\bar{d} + \bar{a}\bar{d}$$

$$\text{If } x_1 = x_2 = 1 \quad x_3 = 1$$
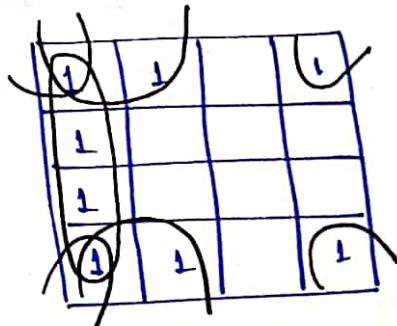
$$j = \overline{b} \overline{d} + \overline{a} \overline{d} + \overline{a} \overline{b}$$



$$Q_3 \quad f(w,x,y,z) = \sum m(0,4,5,7,8,9,13,15)$$

Q3. Which of the following is not equivalent to f

Sol

- A) $\bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}\bar{y} + w\bar{y}z + xz$

B) $\bar{w}\bar{y}\bar{z} + w\bar{z}\bar{y} + xz$

C) $\bar{w}\bar{y}\bar{z} + w\bar{x}\bar{y} + xy\bar{z} + x\bar{y}z$

D) $\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y} + \bar{w}y$

Sol opt A

$$\begin{array}{l} wxyz \\ 1000 \\ 0000 \end{array}$$

$$\begin{array}{l} wxyz \\ 0101 \\ 0100 \end{array}$$

$$\begin{array}{l} wxyz \\ 1001 \\ 1101 \end{array}$$


$$\begin{array}{l} wxyz \\ 0101 \\ 0111 \\ 1101 \\ 1111 \end{array}$$

$$\Sigma m(0, 4, 5, 8, 9, 7, 13, 15)$$

equal to F

opt B, C, D check in similar way

better Method: using K map

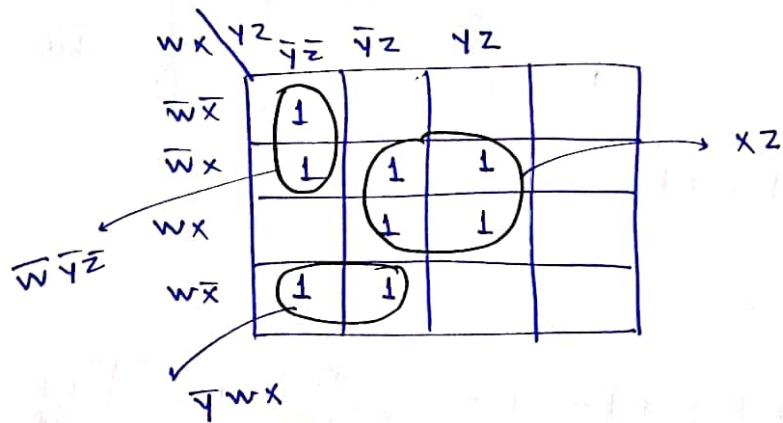

$$f = xz + \bar{w}\bar{y}\bar{z} + \bar{y}wx$$

$$\text{now opt A: } \bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y} + w\bar{y}z + \textcircled{xz}$$

Note
If none of the SOP term present as group in kmap
then that option does not represent given minterms

Ques.

$R\bar{S}$	PQ	$\bar{P}\bar{Q}$	$\bar{P}Q$	$P\bar{Q}$	PP
0	(1)		0	0	
0	(1)		(1)	1	
L			(1)	0	
0	0		1	0	

This Quad will not be grouped

$$\begin{aligned} & \bar{R}\bar{P}Q + \bar{R}SP \\ & + QS + \bar{P}RS \\ & + RPA \end{aligned}$$

Wrong


$R\bar{S}$	PQ	$\bar{P}\bar{Q}$	$\bar{P}Q$	$P\bar{Q}$	PP
0	(1)		0	0	
0	(1)		(1)	1	
L	1	1	L	0	
0	0	L	1	0	

$$\bar{R}\bar{P}Q + \bar{R}SP + \bar{P}RS + RPA$$

Note: Removing .


* Logic Gate Questions





Ques.

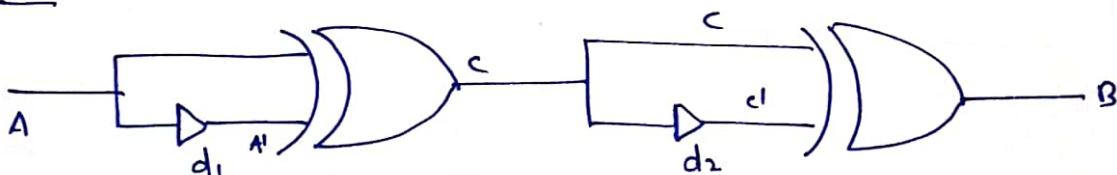

The non Inverting buffer have delays


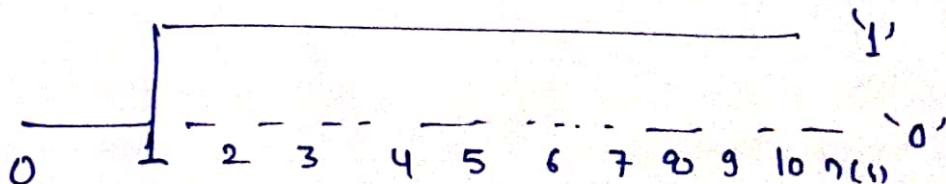
note
if will net invert I/P
 $d_1 = 2\text{ns}$ & $d_2 = 4\text{ns}$ Both XOR gate &
all wire have no delay. Assume all the
gate I/P and O/P are stable at time
Zero. If following wave form is applied at
I/P A. How many Xitions will be there at O/P B?



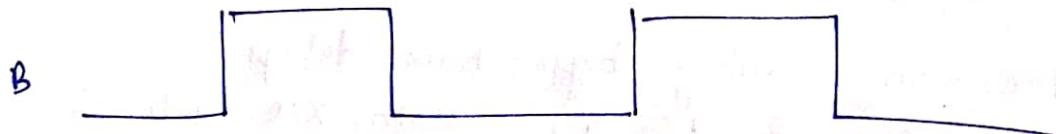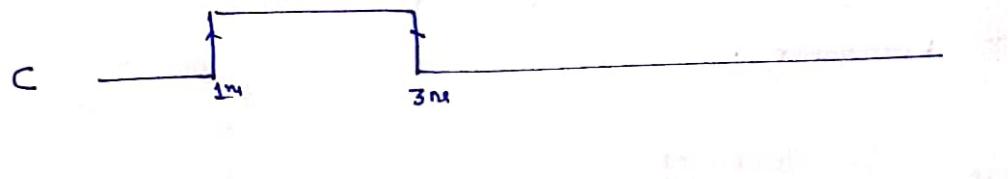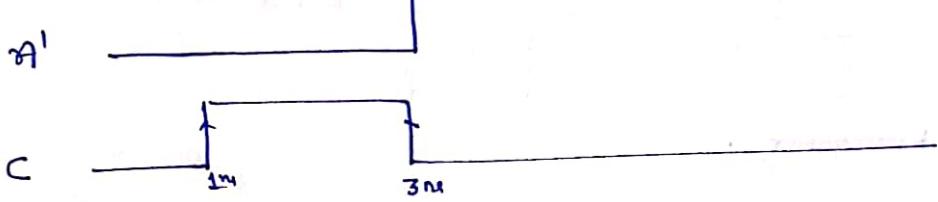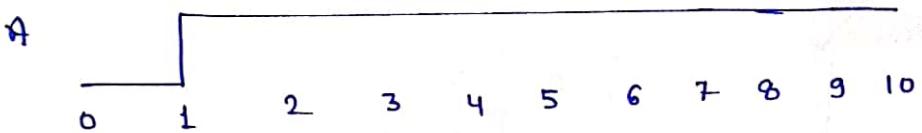

Two positions in o/p

Ques.

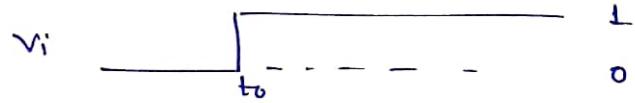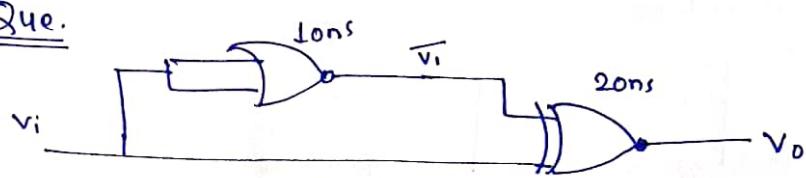

Draw waveform for V_d

note: first make zero delay waveform and then apply delay

Sol


V_i

\bar{V}_i
zero delay

\bar{V}_i
10ns

$V_i \oplus \bar{V}_i$
zero delay

$V_i \oplus \bar{V}_i$
with 20ns
delay

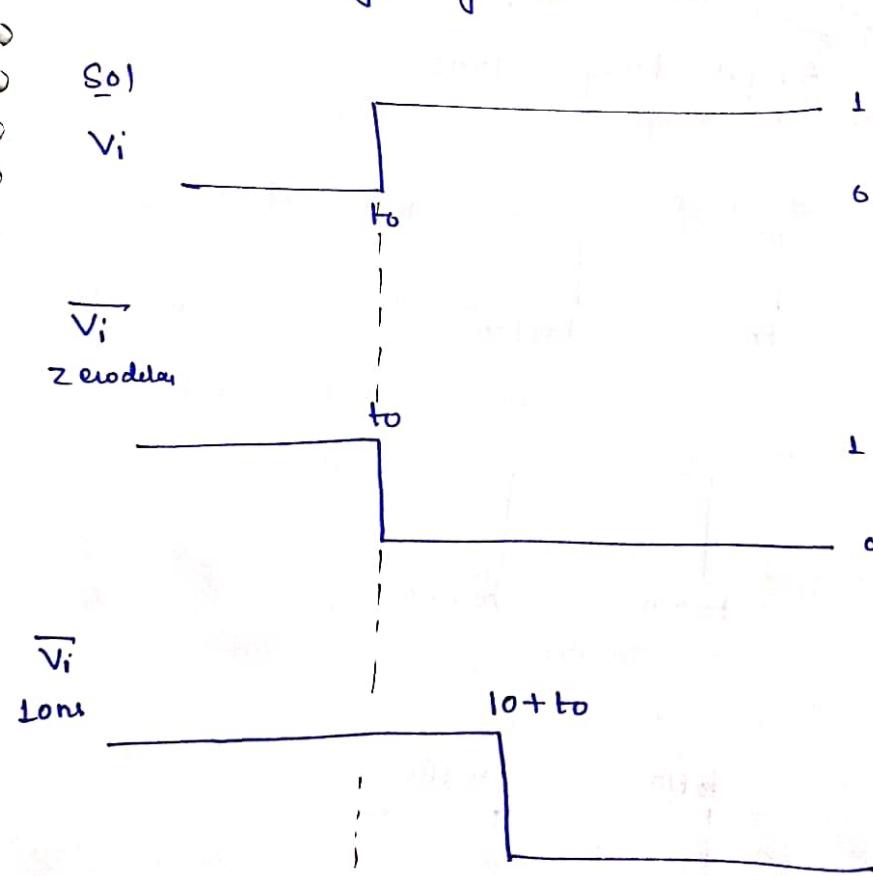



$t_0 + 10$

$t_0 + 10$






$t_0 + 20$

$t_0 + 30$

Ques.

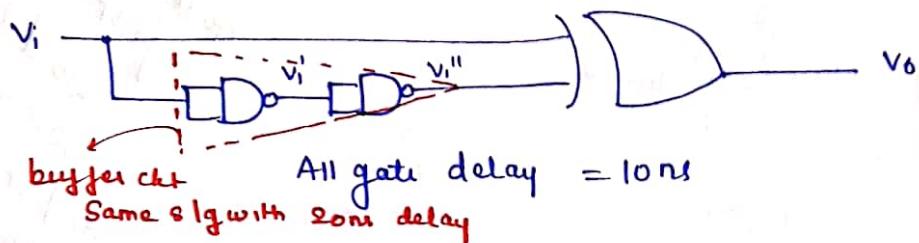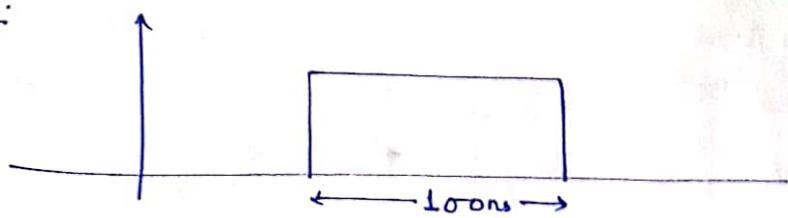

Sol.

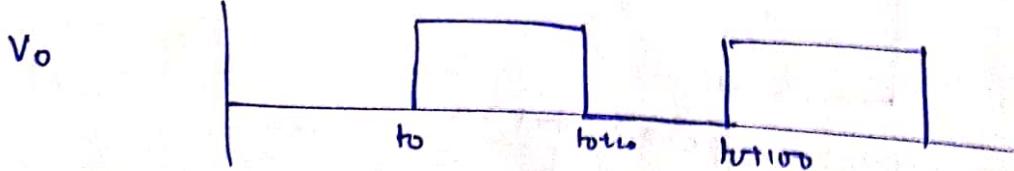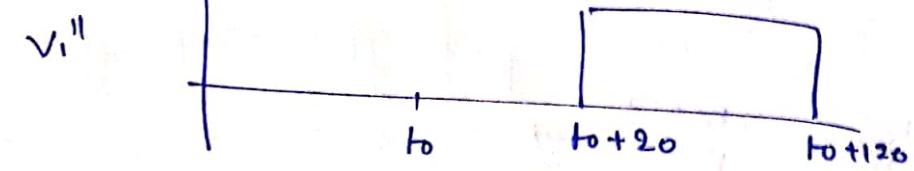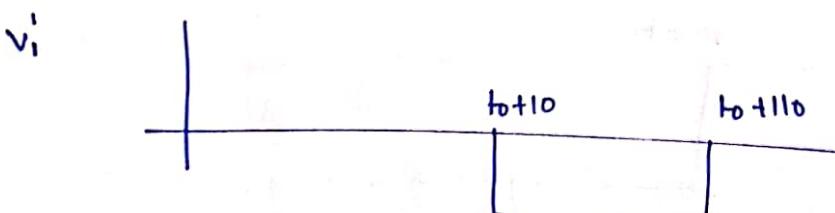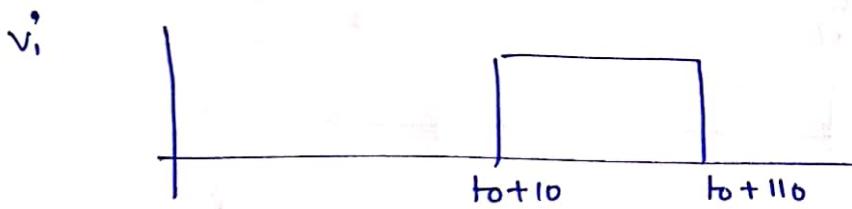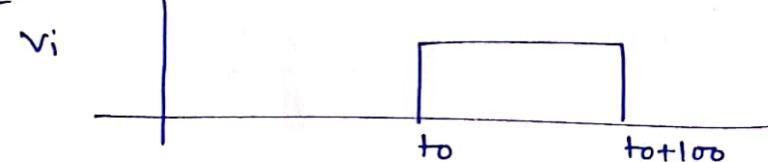

* Implicants, Prime Implicants & Essential Implicants :-

1) Implicants

$$\text{let, } f = \sum m(0, 2, 3, 6, 8, 9, 12, 13, 15)$$

$$i) g_1 = \sum m(0, 3, 8, 12, 15)$$

f is Covering function $g_1 \Rightarrow g_1$ is Subjunction of f i.e g_1 is an Implicant of f .

$$ii) g_2 = \sum m(2, 6, 9, 13, 15)$$

g_2 is Subjunction of f i.e g_2 is an Implicant of f

$$iii) g_3 = \sum m(0, 3, 6, 9, 10^*)$$

f is not Covering function $g_3 \Rightarrow g_3$ is not Subjunction of f
i.e g_3 is not an Implicant of f .

$$iv) g_4 = \sum m(2, 6, 9, 14^*)$$

f is not Covering function $g_4 \Rightarrow g_4$ is not Subjunction of f i.e g_4 is not an Implicant of f .

Ques1. $F(A, B, C, D) = \sum m(1, 5, 7, 8, 10, 12, 13, 15)$

$$h_1 = BD$$

$$h_2 = \bar{A}\bar{C}D$$

$$h_3 = A\bar{B}\bar{C}$$

$$h_4 = A\bar{C}\bar{D}$$

$$h_5 = AB\bar{C}$$

$$h_6 = B\bar{C}D$$

$$h_7 = \bar{A}B\bar{D}$$

$$h_8 = B\bar{C}D$$

$$h_9 = \bar{A}\bar{B}\bar{C}$$

$$\text{Sol: } h_1 = B \odot$$

$$\begin{array}{cccc} A & B & C & D \\ 0 & 1 & 0 & 1 \\ 0 & 1 & 1 & 1 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 1 & 1 \end{array} \rightarrow \begin{array}{c} 5 \\ 7 \\ 13 \\ 15 \end{array}$$

$$h_2 = \bar{A} \bar{C} \odot$$

$$\begin{array}{cccc} A & B & C & D \\ 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 \end{array} \rightarrow \begin{array}{c} 1 \\ 5 \end{array}$$

$$h_3 = A \bar{B} \bar{D}$$

$$\begin{array}{cccc} 1 & 0 & 0 & 0 \\ 1 & 0 & 1 & 0 \end{array} \rightarrow \begin{array}{c} 8 \\ 10 \end{array}$$

$$h_4 = A \bar{C} \bar{D}$$

$$\begin{array}{ccc} A & B & C \\ 1 & 0 & 0 \\ 1 & 1 & 1 \end{array} \begin{array}{c} \bar{D} \\ 0 \\ 0 \end{array} \rightarrow \begin{array}{c} 8 \\ 12 \end{array}$$

$$h_5 = A B \bar{C} \odot$$

$$\begin{array}{cccc} 1 & 1 & 0 & 0 \\ 1 & 1 & 0 & 1 \end{array} \rightarrow \begin{array}{c} 12 \\ 13 \end{array}$$

$$h_6 = A B C \odot$$

$$\begin{array}{cccc} 0 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 \end{array} \rightarrow \begin{array}{c} 5 \\ 13 \end{array}$$

$$h_7 = \bar{A} B \odot$$

$$\begin{array}{cccc} A & B & C & D \\ 0 & 1 & 0 & 1 \\ 0 & 1 & 1 & 1 \end{array} \rightarrow \begin{array}{c} 5 \\ 7 \end{array}$$

$$h_8 = B \bar{C} \bar{D}$$

$$\begin{array}{ccc} A & B & C \\ 0 & 1 & 0 \\ 1 & 1 & 0 \end{array} \begin{array}{c} \bar{D} \\ 0 \\ 0 \end{array} \rightarrow \begin{array}{c} 4 \\ 12 \end{array}$$

If is not Implicant

$$h_9$$

$$\begin{array}{cccc} A & B & C & D \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{array} \rightarrow \begin{array}{c} 0 \\ 1 \end{array}$$

h_9 is not Implicant

Hence only h_8, h_9 are not Implicant of F.

k-map

Implicant :- If group possible?

Yes \rightarrow Implicant

No \rightarrow not prime Implicant

Prime Implicant :- Are best group possible?

Yes \rightarrow Prime Implicant

K map for f

	C_0	$C_0\bar{C}_0$	\bar{C}_0	$C_0\bar{C}_1$	$C_1\bar{C}_0$	C_1
$\bar{A}\bar{B}$	0	1	1	3		2
$\bar{A}B$	4	5	1	7	6	0
$A\bar{B}$	12	13	1	15	1	14
AB	1	1	1	1		1
	8	1	9	14	10	1

Prime Implicants $\rightarrow (5, 7, 13, 15)$

$h_2 (1, 5)$ PI

$h_3 (8, 10)$ PI

$h_4 (8, 12)$ PI

$h_5 (12, 13)$ PI

$h_6 (5, 13)$ Not prime implicant, They can include in Quad

$h_7 (5, 7)$ Not prime implicant

$h_8 (5, 7, 13, 15)$ Prime implicant.

If any term cannot come under Quad they are PI

Essential prime implicants

$h_1 (1, 5)$ EPI due to 1

$h_3 (8, 10)$ EPI due to 10 because 10 has no option of group (8, 10) is compulsory

$h_4 (8, 12)$ NOT EPI (8-10) (12-13) can be possible

$h_5 (12, 13)$ NOT EPI

$h_6 (5, 13)$ NOT EPI

$h_8 (5, 7, 13, 15)$ NOT EPI Quad is not alternative of Quad Quad itself is best group

due to 7 & 15

Note: Implicant \rightarrow any group

Prime Imp. \rightarrow all possible group, can be other option group

EPI \rightarrow no other option for group

Redundant PI \rightarrow group which can't be formed but exist

Que.

AB	CD	00	01	11	10
00	1	0	1	1	1
01	0	1	0	0	0
11	0	1	1	0	0
10	1	0	0	1	1

no. of EPI = 9

Sol (3, 2) (12, 15) (5, 13) (0, 2, 8, 10)

4 essential prime implicants.

Que.

AB	CD	00	01	10	11
00	1	1	0	1	1
01	0	0	0	1	1
10	1	0	0	1	1
11	0	1	0	1	1

no. of essential prime imp.

$$= 4$$

Que. Which are the EPI of following Boolean function

$$f(a, b, c) = a'c + ac' + b'c$$

- a) $a'c$ & ac' b) $a'c$ & $b'c$ c) ac' only d) ac' & bc

Sol $\Sigma m(3, 1, 4, 6, 5)$

a	bc	1	1	1	D
1	1	1	1	1	D
a	1	1	1	1	1
1	1	1	1	1	1
a	1	1	1	1	1

Wrong

a	bc	1	1	c̄a
1	1	1	1	1
a	1	1	1	1
1	1	1	1	1
a	1	1	1	1

Hence opt n

Que. In SOP function


$$f(xyz) = \sum m(2, 3, 4, 5)$$

The prime implicants are

- i) $\bar{x}y, xy$ ii) $\bar{x}y, x\bar{y}\bar{z}, x\bar{y}z$ iii) $\bar{x}y\bar{z}, \bar{x}y\bar{z}xy$


- iv) $\bar{x}y\bar{z}, \bar{x}yz$

- v) $x\bar{y}\bar{z}, x\bar{y}z$

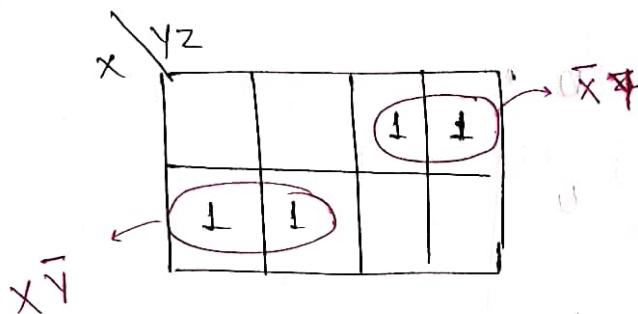

Que. $f(w, x, y, z) = wy + xy + \bar{w}x\bar{y}z + \bar{w}\bar{y}z + xz + \bar{x}\bar{y}z$

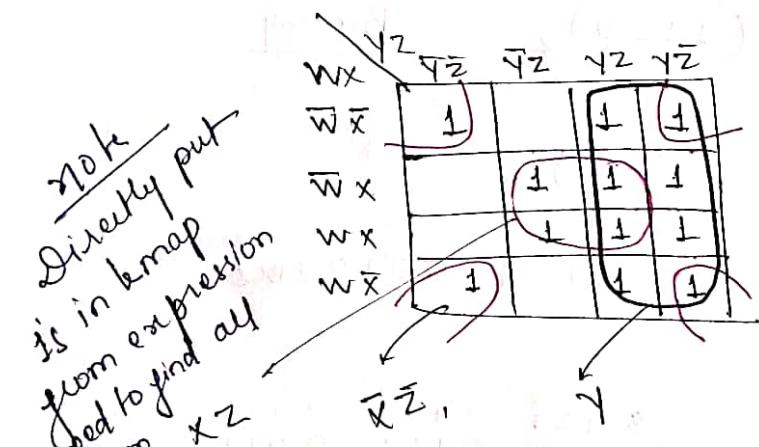which of the following is complete set of EPI?



Hence. $xz, \bar{x}\bar{z}, y$

$wy = wx\bar{y}z$
$1010 \rightarrow 10$
$1011 \rightarrow 11$
$1110 \rightarrow 14$
$1111 \rightarrow 15$

$xy = wx\bar{y}z$
$0110 \rightarrow 6$
$0111 \rightarrow 7$
$1110 \rightarrow 14$
$1111 \rightarrow 15$


$\bar{w}x\bar{y}z \rightarrow 7$

$\bar{w}\bar{x}y$

(Avoid this calcⁿ)

Que $f(x_1, x_2, x_3) = \sum m(1, 3, 6, 7)$

Redundant PI is -

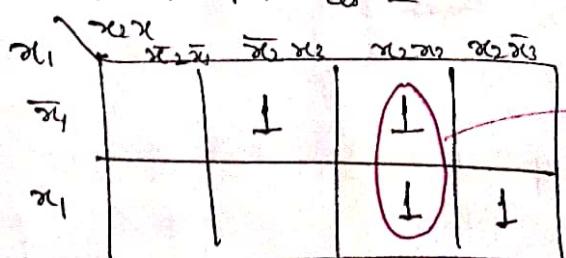

Redundant PI

x_2x_3 i.e.

Pairs which have opt
to form a larger pair

* BCD Codes

Binary Coded decimal :- Every decimal digit is encoded with four binary bit

e.g. $(12)_{10} \xrightarrow{\text{Binary}} (\quad)_2$

$$\begin{array}{r} 12 \\ \hline 2 \\ 6 \\ \hline 2 \\ 3 \\ \hline 2 \\ 1 \\ \hline 2 \end{array}$$


0 1 1 1 1 1 1

$(12)_{10} \longrightarrow (1100)_2 \xrightarrow{\text{Binary}}$

e.g. $(12)_{10} \longrightarrow (\quad)_\text{BCD}$

1 2
0001 0010

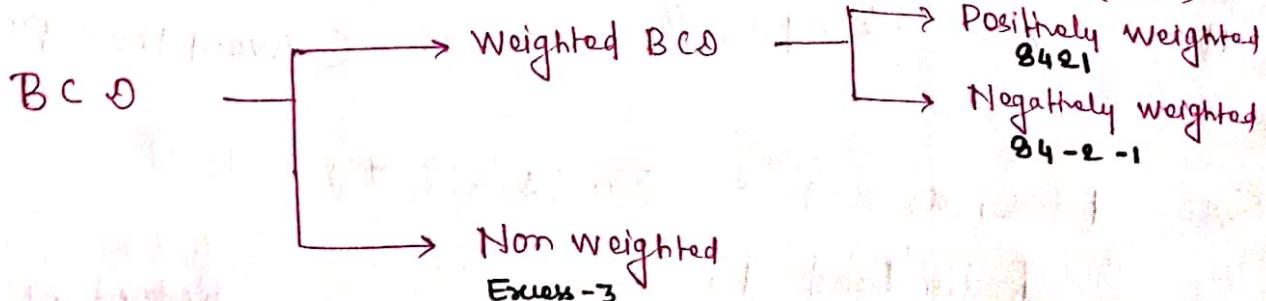e.g. $(243)_{10} \longrightarrow (0010 \quad 0100 \quad 0011)_\text{BCD}$
 $\qquad \qquad \qquad (8421)$



	8 4 2 1	8 4 -2 -1	X S -3
7	0 1 1 1	1 0 0 +	1 0 1 0
5	0 1 0 1	1 0 + +	1 0 0 0

$$(57)_{10} = (0101 \ 0111)_{8421} = (10111001)_{84-2-1}$$

+ (1000 1010)_{XS-3}

Decimal	(Rowed Code 6 unused)	(Rowed 6 unused)	(Rowed 5 unused)	(All 16 codes are used)	
0	0000	0000	0011	0 0 0 0	0000
1	0001	0111	0100	0 0 0 1	0001
2	0010	0110	0101	1 0 0 0	0010
3	0011	0101	0110	0 0 1 1	1001
4	0100	0100	0111	0 1 0 0	1010
5	0101	1011	1000	0 1 0 1	0101
6	0110	1010	1001	0 1 1 0	0110
7	0111	1001	1010	0 1 1 1	1101
8	1000	1000	1011	1 1 1 0	00110
9	1001	1111	1100	1 1 1 1	1111

to a Codeword

Note: Sequential Code : By adding 1, we get next codeword

e.g. BCD & XS-3

Non Sequential Code

e.g. 84-2-1 & BCD

Advantages of Sequential Codes

→ Arithmetic operation are possible in Sq. code

e.g. 8421 BC0 arithmetic

X5-3 Arithmetic

* Self Complementing Code

Number System

$(R-1)$'s
Complement

R's
Complement

eg. Decimal
 $(R=10)$

g's 10's

$$782 \rightarrow \begin{array}{r} 999 \\ - 782 \\ \hline 217 \end{array}$$

Octal
 $(R=8)$

7's 8's

$$\begin{array}{r} 777 \\ - 713 \\ \hline 064 \end{array}$$

Binary
 $(R=2)$

1's 2's

$$\begin{array}{r} 111 \\ - 010 \\ \hline 101 \end{array}$$

$$[8's \text{ comp} = (8-1)'s + 1]$$

9's Complement pair

$$9 \leftrightarrow 0$$

$$8 \leftrightarrow 1$$

$$7 \leftrightarrow 2$$

$$6 \leftrightarrow 3$$


$$5 \leftrightarrow 4$$

eg. BCD, 84-2-1, X5-3 all are having
9's pair

8421 is not Self Complementing

- Self Complementing Code is a Code in which we can obtain Codeword for g's complement of N by from the Code of N by complementing each bit in Code of N
- 2421 is a Self Complementing Code. Any Code which has repeated weight (2 in this case) are Self Complementing.
- Self Complementing property must hold to write Codewords
Hence there are many sequence of 2421 BCD are possible

* Gray Code

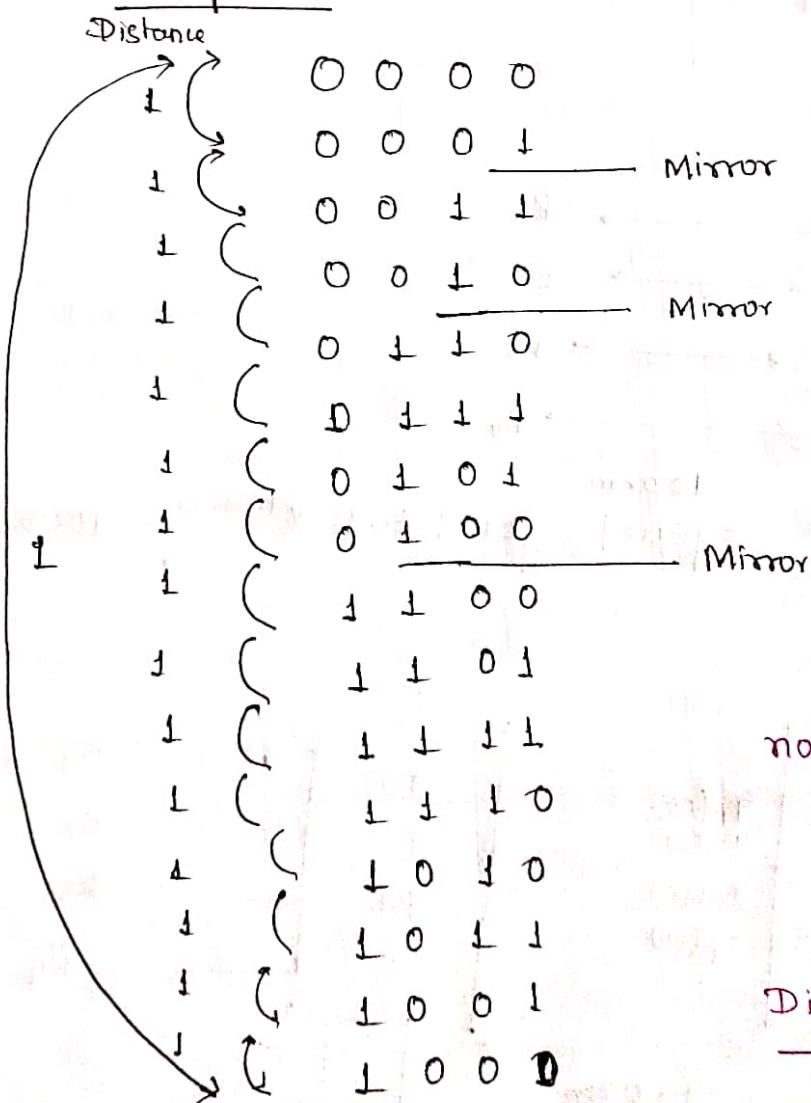

• Gray code is non weighted code.

• Gray code is also called reflective code

• Gray code is not a BCD code because Gray code can be of 2 bit, 3 bit, 4 bit & 8 bit but BCD is only 4 bit.

note:- Gray Code are Unit distance Code

Distance between Code
→ difference in no. of bit

- Gray Code is also called Cyclic Code